

6.45 Given the logic gates shown in Figure 6.96, optimize the following circuit by reducing power consumption without increasing the circuit's delay.

