

1)

ab=00

cd/ef	00	01	11	10
00	0	1	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

ab=10

cd/ef	00	01	11	10
00	32	36	44	40
01	33	37	45	41
11	35	39	47	43
10	34	38	46	42

ab=01

cd/ef	00	01	11	10
00	16	20	28	24
01	17	21	29	25
11	19	23	31	27
10	18	22	30	26

ab=11

cd/ef	00	01	11	10
00	48	52	60	56
01	49	53	61	57
11	51	55	63	59
10	50	54	62	58

$\neg a \neg b \neg c d \neg f, \neg b c d \neg e \neg f, \neg b c d \neg e f, \neg a \neg b \neg c e \neg f, \neg a \neg b d e \neg f, \neg b c d e \neg f, a \neg b \neg d e \neg f, a \neg b \neg c d e f, a b c d e f$

Min SoP = $\neg a \neg b \neg c d \neg f + \neg b c d \neg e \neg f + \neg b c d \neg e f + \neg a \neg b \neg c e \neg f + \neg b c d e \neg f + a \neg b \neg d e \neg f + a \neg b \neg c d e f + a b c d e f$

2,4,6,8,13,14,19,32,40,45,46,63


2	000010	X
4	000100	X
8	001000	X
32	100000	X
6	000110	X
40	101000	X
13	001101	x
14	001110	x
19	001011	
45	101101	x
46	101110	x
63	111111	

2,6	000x10	
4,6	0001x0	
8,40	x01000	
32,40	10x000	
6,14	00x110	
13,45	x01101	
14,46	x01110	


term	19	63	2,6	4,6	8,40	32,40	6,14	13,45	14,46
2			X*						
4				X*					
8					X*				
32						X*			
6				X			X		
40					X	X			
13								X*	
14							X		X
19	X*								
45								X*	
46									X*
63		X*							

Almost every prime implicant is an essential prime implicant. And the one that isn't isn't in the SoP.

 Min SoP= $a!b!c!def + abcdef + !a!b!ce!f + !a!b!cd!f + !bc!d!e!f + a!b!d!e!f + !bcd!ef + !bcde!f$



Q1	Q0	A	N1	N0	X
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	0	0	0

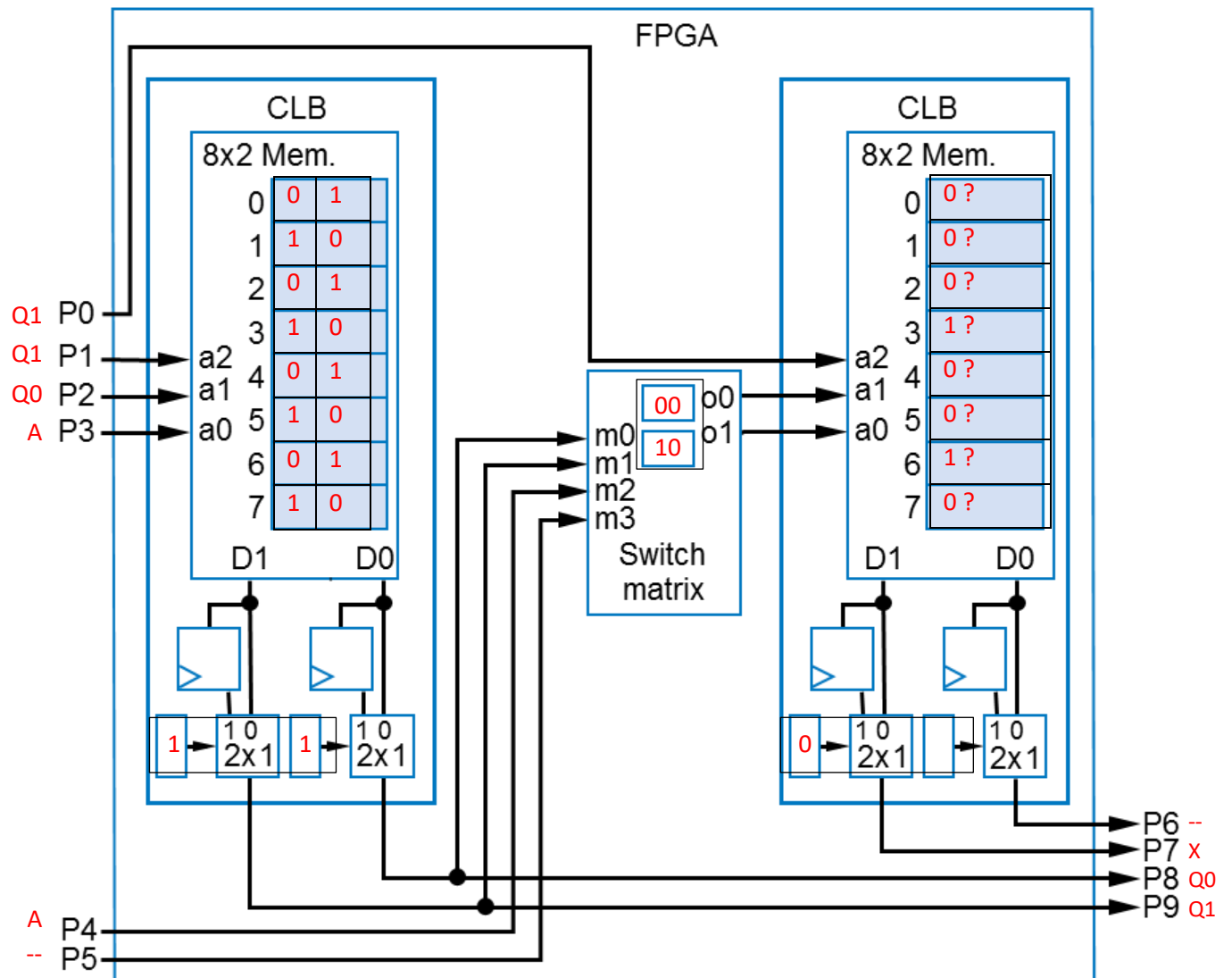

4. .

a. .

- 4-bit: $12 + (2+3+4+5)=26$
- 16-bit: Need to add the logic for P and G to each 4-bit adder. Notice that we already have most of G (all the AND gates) done, so we just need the OR gate for G. So two more gates total. With those two additional that's 28 gates for each of the 4-bit adders. Plus the 14 gates for the CL logic at the next level, that's $28*4+14=126$ gates.
- 64-bit: That's 126 gates for each 16-bit adder. Plus the two to find P and G. Plus the 14 for the CL logic gives us $128*4+14 = 526$.

$$P = P_3P_2P_1P_0$$
$$G = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0$$

b. .

- 4-bit: top is only 2-input gates, so $12 \text{ gates} * 2 = 24$ gate-inputs. The CL logic is 4 inputs in stage 1, 8 in 2, 13 in 3, and 19 in stage 4 = 44 gate inputs. So 68 total inputs.
- 16-bit: Each 4-bit has the 68 inputs plus another 4 for P and 4 for G. So $76*4$. Add in the 44 for the CL logic, you've got 348 inputs.
- 64-bits: Each 16-bit adder has the 348 bits plus another 8 for P and G. Then 44 for the CL logic, you've got $4*(348+8)+44 = 1468$ gate inputs.

c. (reading page 373 gives a fairly good explanation of the logic here).

- 4-bit has 4 gate-delays (1 for P/G, 2 for CL logic, 1 for the XOR to generate s1).
- 16-bit: Adding P and G to the 4-bit adder doesn't add any delay. So just an extra CL logic, which gets us to 6 gate-delays
- 64-bit: Same logic gets us to 8 gate-delays.

d. This problem was defined a bit too poorly to be graded (log base actually matters for what path is critical). Everyone was given full points if an effort was made.

5. .

There was no specific format given for data values, so anything reasonable was taken. The key is the need for self-modifying code.

```
blt  8      1000 2001 // skip increment if mem<101.
add  2000 2000 2002 // increment total
add  2      2    2002 // modify the address to check!
blt  0      2    2003 // keep going if mem[2]<2000.
halt                               // if branch not ta
```

```
2000: 0          //total
2001: 101        //value to compare to
2002: 1          //one
2003: 2000       //if mem[3] isn't this big, keep going.
```