

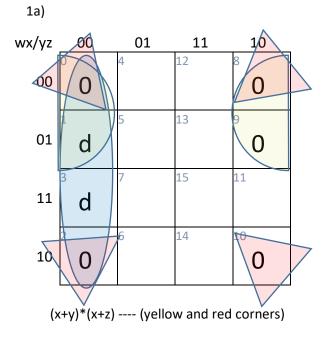
EECS 270, Spring 2023, Homework 5 answers.




1b) That is (abc)+(!a+!b)+a+b = 1.

2)

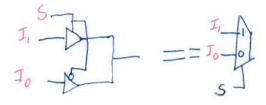

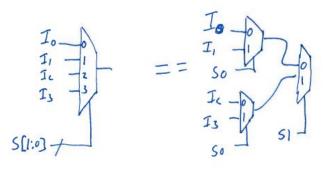

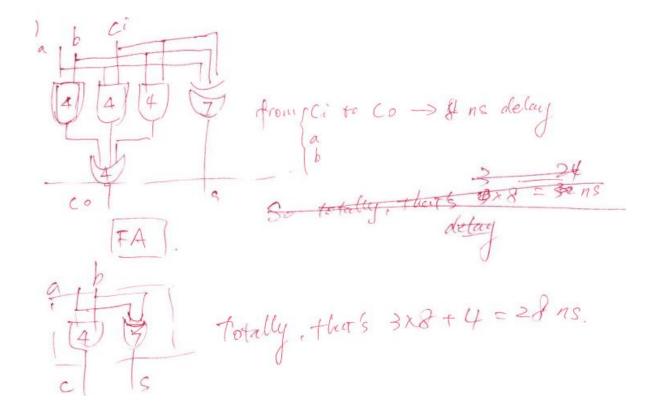

4) Goes from figure B with an XOR to figure c with an AND and then OR and then back to to figure b with an XOR. That's 7+4+4+7=22ns.

5)

State	Next State		
	X=0	X=1	Output (W)
ACF	BE	ACF	0
BE	ACF	G	0
D	BE	ACF	1
G	ACF	D	1

6).

- i. 2¹⁰*2¹⁰/2³=2¹⁷ locations
- ii. 17
- iii. 10 to the decoder, 7 to the MUX

b. .

a.

- i. 2¹⁸
- ii. 18
- iii. 10 to the decoder, 8 to the MUX