

EECS 270 Midterm 1 Exam Closed book portion

Fall 2014

Name: Key unique name: _____

Sign the honor code:

I have neither given nor received aid on this exam nor observed anyone else doing so.

Scores:

| Problem # | Points |
|--------------------------|-------------|
| 1 | /13 |
| 2 | /4 |
| 3 | /6 |
| 4 | /2 |
| <i>Total closed book</i> | <i>/25</i> |
| <i>Total open book</i> | <i>/75</i> |
| Total | /100 |

NOTES:


- 1. This part of the exam is closed everything. No calculators, books, notes, etc.**
- Once you finish this part, turn it in and you'll be given the open book part. You won't be able to come back to this part.
- There are 3 pages total. Count them to be sure you have them all.
- You have about 120 minutes for the exam total. We'd suggest you not spend more than 25 or 30 minutes on this part.

1. Fill in each blank or circle the best answer. [13 points, -2 per wrong or blank answer, min 0]

- a) The 5-bit 2's complement number representation of -7 is 11001.
- b) 110110, when treated as a 6-bit signed-magnitude number, has a decimal representation of -22.
- c) The range of representation for a 7-bit 2's complement number is from -64 to 63.
- d) If a clock has a period of 2ns, it has a frequency of 500 MHz
- e) A sum-of-products representation of $(A+!B)$ is $A + !B$
- f) If you were to represent $A*B*!C$ using canonical sum-of-products, there would be 7 maxterms.
- g) A 2-bit 4 to 1 MUX would require 2 select lines.
- h) That $(A*B) = !(A+!B)$ is an example of the theorem named DeMorgan's law
- i) You are treating the 8-bit numbers $A[7:0]$ and $B[7:0]$ as unsigned numbers. If you set $B[4:0]=A[7:3]$ and $B[7:5]=0$.


B is now equal to A plus / minus / times / modulo / **divided by** 2 / 3 / 4 / **8** / 16 / 32

 2. Draw gates which implement a 4-to-2 encoder. The inputs should be named $A_3, A_2, A_1,$ and A_0 , while the outputs should be named B_1 and B_0 . You may use no more than three 2-input gates (AND, OR, NOR, NAND, XOR or XNOR) and no other logic (including inverters). [4 points]



 3. Complete the following timing diagram for an SR-latch with enable. You may assume that the time scale is such that the gate delay is extremely small and your answer should not reflect those delays. Changes shown to be simultaneous are exactly simultaneous. **[6 points]**

If the value is unknown (or oscillating) at some point, clearly indicate that with hashes (like this)



4. Consider the logic equation: $A = X * (Y + !Y) + (X * !Y)$ Fill in the truth table for this equation. **[2 points, no partial credit]**

| X | Y | A |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

EECS 270 Midterm 1 Exam Open book portion

Fall 2014

Name: Key unique name: _____

Sign the honor code:

I have neither given nor received aid on this exam nor observed anyone else doing so.

Scores:

| Problem # | Points |
|------------------------|------------|
| 1 | /7 |
| 2 | /10 |
| 3 | /12 |
| 4 | /10 |
| 5 | /8 |
| 6 | /12 |
| 7 | /8 |
| 8 | /8 |
| Total open book | /75 |

NOTES:

1. This part of the exam is open books and open notes. You may not use any device capable of communication (cell phones, calculators with wireless, etc.)
2. You have about 120 minutes for the exam total. We'd suggest you not spend more than 25 or 30 minutes on this part.
3. Some questions may be harder than others. Manage your time wisely.


- 1) Design a state transition diagram for a state machine that takes two inputs, A and B and has one output, X. X is to be a 1 if, and only if, A has been the same as B for the last two clock periods. [7 points]

So if

A=000111001

B=100100001

X=001100011

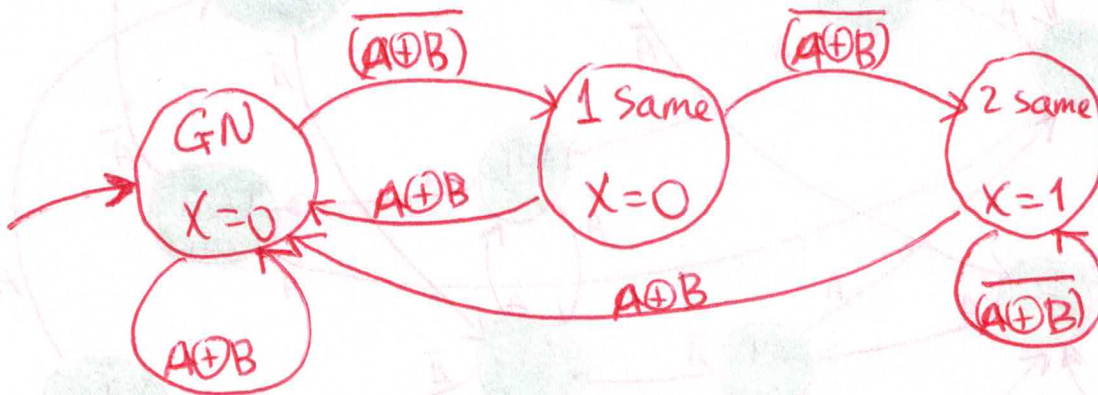



$$A \oplus B = A\bar{B} + \bar{A}B$$

$$\overline{A \oplus B} = \bar{A}\bar{B} + AB$$

- 2) Design a state transition diagram for a state machine that takes one input, A and has one output, X. X should be a 1 if, and only if, the last four values of A have been either 1011, 1001, or 0100. [10 points]

Assume $X=0$, unless shown.

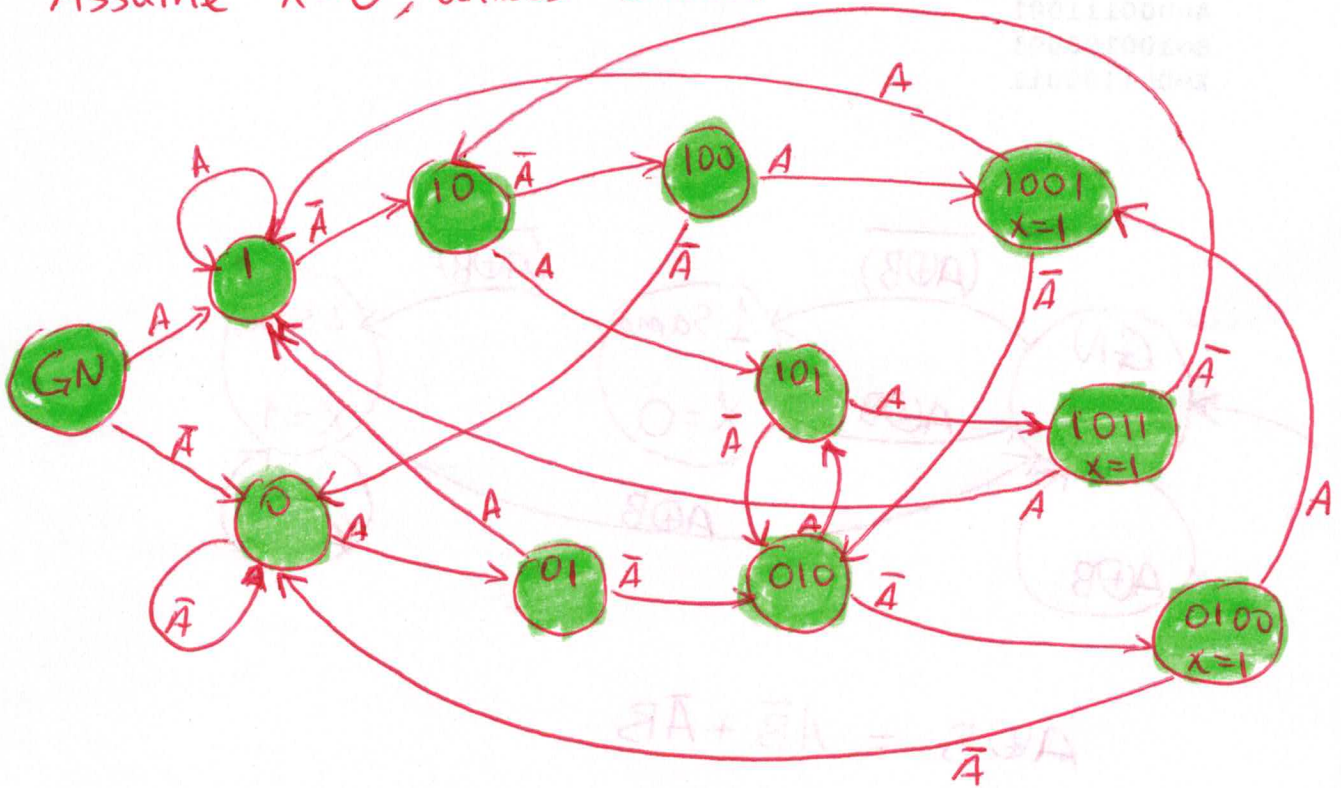

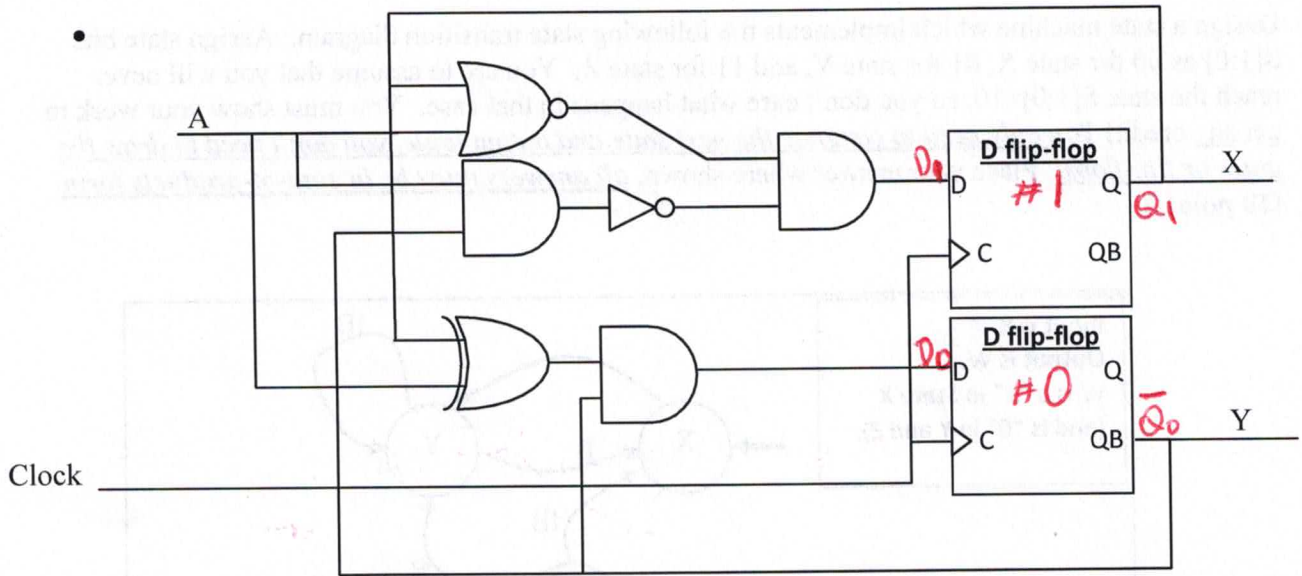


3) Draw the state transition diagram which is implemented by the above circuit. You should assume the initial state is when both flip-flops are "0". You should only include states that can be reached from the initial state. Clearly show your work. [12 points]

$$D_0 = (A \oplus Q_1) \cdot \bar{Q}_0, \quad D_1 = \overline{(A + Q_1)} \cdot A \cdot \bar{Q}_0, \quad X = Q_1, \quad Y = \bar{Q}_0.$$

| Q_1 | Q_0 | A | D_1 | D_0 |
|-------|-------|---|-------|-------|
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 |


$X=0$ and $Y=0$, unless shown

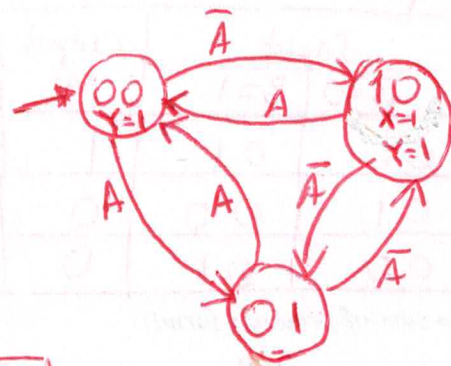

| Current state | Input | | Output | |
|---------------|-------|-----|--------|---|
| | A=0 | A=1 | X | Y |
| 00 | 10 | 01 | 0 | 1 |
| 01 | 10 | 00 | 0 | 0 |
| 10 | 01 | 00 | 1 | 1 |
| 11 | 00 | 00 | 1 | 0 |

Initial State: 00
Reachable States: 10, 01,

 - 4) Design a state machine which implements the following state transition diagram. Assign state bits $S[1:0]$ as 00 for state X, 01 for state Y, and 11 for state Z. You are to assume that you will never reach the state $S[1:0]=10$, so you don't care what happens in that case. You must show your work to get any credit! You only need to compute the next state and output logic, you don't need to draw the gates or flip-flops! Place your answer where shown, all answers must be in sum-of-products form. [10 points]



State assignment.

| State | S_1 | S_0 |
|-------|-------|-------|
| X | 0 | 0 |
| Y | 0 | 1 |
| Z | 1 | 1 |

State/output table.

| Current | Input | | Output W |
|---------|-------|-----|----------|
| | B=0 | B=1 | |
| 00 | 01 | 01 | 1 |
| 01 | 01 | 00 | 0 |
| 11 | 00 | 01 | 0 |

| S_1 | S_0 | B | NS_1 | NS_0 | W |
|-------|-------|---|--------|--------|------|
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | D.C. | D.C. | D.C. |
| 1 | 0 | 1 | D.C. | D.C. | D.C. |
| 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 |

(Be sure all are in sum-of-products form!)

$NS_1 = \underline{0}$


$NS_0 = \bar{S}_1 \bar{S}_0 \bar{B} + \bar{S}_1 \bar{S}_0 B + \bar{S}_1 S_0 \bar{B} + S_1 S_0 B \Leftrightarrow \bar{S}_1 \bar{S}_0 + \bar{S}_1 \bar{B} + S_1 S_0 B$

$W = \underline{\bar{S}_1 \bar{S}_0}$

Treating D.C. as 1's
 $\bar{S}_0 + S_1 B + \bar{S}_1$

 
- 5) Implement a 2-input XOR using only 2-input NAND gates. For full credit, use 5 or fewer NAND gates. Use assume the inputs are labeled A and B while the output is labeled X.
[8 points, half credit for using more than 5 gates]

$$\begin{aligned}
 X &= A \oplus B \\
 &= A\bar{B} + \bar{A}B \quad \text{--- definition of XOR.} \\
 &= \overline{\overline{A\bar{B} + \bar{A}B}} \\
 &= \overline{\overline{A\bar{B}} \cdot \overline{\bar{A}B}} \quad \text{--- involution} \\
 &= \overline{\overline{A}\overline{\bar{B}} \cdot \overline{\bar{A}}\overline{B}} \quad \text{--- De Morgan's}
 \end{aligned}$$



Better Solution. (4 gates)


$$\begin{aligned}
 X &= \overline{\overline{A\bar{B}} \cdot \overline{\bar{A}B}} \quad \text{--- continuing from Above.} \\
 &= \overline{(\overline{A\bar{B}} + \overline{\bar{A}B})} \quad \text{--- Complements + Identity} \\
 &= \overline{A(\bar{A} + \bar{B}) \cdot B(\bar{A} + \bar{B})} \quad \text{--- Distributive} \\
 &= \overline{\overline{A} \cdot \overline{\bar{B}} \cdot \overline{B} \cdot \overline{\bar{A}}} \quad \text{--- De Morgan's}
 \end{aligned}$$

 

| | Min | Max |
|--------|-----|-----|
| OR/AND | 3ns | 6ns |
| NOT | 1ns | 2ns |
| XOR | 3ns | 9ns |

NOR/NAND 2ns 5ns

| DFF: | Min | Max |
|-------------|--------|-----|
| Clock to Q | 2ns | 3ns |
| Set-up time | 7 ns | |
| Hold time | ??? ns | |

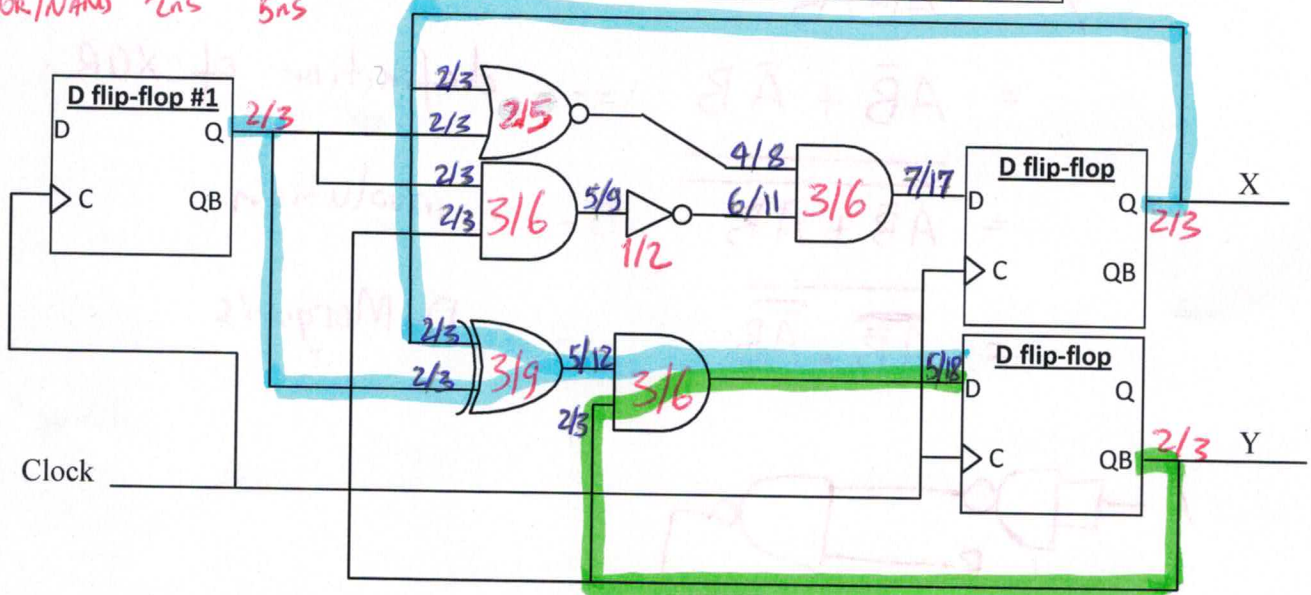

6) Answer the following questions [12 points]

- a. In order for this circuit to work correctly, what range of values that would be acceptable for the hold time requirement of the D flip-flops? Assume the only options range from 1ns to 10ns. Clearly show your work. [6]

Smallest 1ns Largest 5ns

Fastest path (*min-path) is shown in green.

- b. What is the lowest clock period that could be safely used on this circuit? Clearly show your work. [6]

Slowest path shown in blue. (*max-path)

$$\text{Lowest Clock Period} = \text{Delay on slowest path} + \text{Setup Time.}$$

$$= 18\text{ns} + 7\text{ns}$$

$$= 25\text{ns}$$

Note:

$$\text{Delay on slowest path} = \text{clock to Q delay} + \text{combinational logic delay}$$

$$= 3\text{ns} + 15\text{ns}$$

7) Design a circuit which has 5 bits of input ($X[3:0]$ and S), and 5 bits of output ($Y[4:0]$). For this problem, X and Y are both to be considered 2's complement numbers.

- If $S=1$ then Y should be equal to $2X$
- If $S=0$ then Y should be equal to $X/2$ (round down)

Examples:


If $X=0010$ and $S=1$, Y should be 00100 .

If $X=1111$ and $S=0$, Y should be 11111

If $X=1111$ and $S=1$, Y should be 11110

If $X=0011$ and $S=0$, Y should be 00001

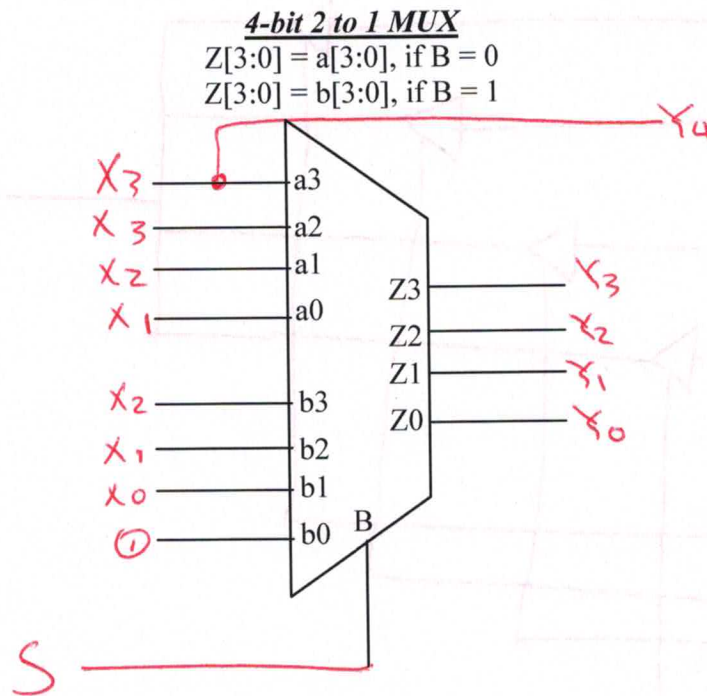You have only one 4-bit 2 to 1 MUX to implement this. You can freely use 1 and 0 as your inputs. Draw your connections using the MUX below. [8 points]



8) Using only tri-state devices, 2-input AND gates, 2-input OR gates, 2 to 4 decoders and inverters, build a 4 to 1 MUX. Use the same labels as the diagram below. Your design must use seven or fewer devices to receive credit. [8 points]

