

## Quiz 3 – EECS 270, Spring '23

Name: \_\_\_\_\_ unique name: \_\_\_\_\_

**Honor code:**

I have not given or received aid on this quiz, nor have I observed anyone else doing so:

Sign here: \_\_\_\_\_

This quiz is graded out of 100 points and is worth about 3% of your class grade. You will have **20** minutes for this quiz. ***Closed everything including calculators!*** To receive partial credit, work must be shown.

---

1. Find the minimum ***product-of-sums***  $\sum_{(a,b,c,d)=(1,4,6,9,11,12,13)+d(0,15)}$  using a K-map. Show your work and clearly circle your answer. **[40]**  
Note: this is Product-of-sums!!!

2. Using a single shift register (given below), a decoder (any size), inverters (as many as needed), and up to four 2-input gates of any type, build a device which takes a single-bit input  $X$  and has an output  $Y$  go high if the last 3 values have been 001 or the last two values have been 11. On this shift register, on the rising edge  $Y[0]$  gets the Shift in value,  $Y[1]$  gets the  $Y[0]$  value, etc.

