

Quiz 4 EECS 270 Spring 2023.

Name: _____ uname: _____

Honor code:


I have not given or received aid on this quiz, nor have I observed anyone else doing so:

Sign here: _____

This quiz is graded out of 100 points and is worth about 4% of your class grade. You will have 20 minutes for this quiz. ***Closed everything including calculators!*** To receive partial credit, work must be shown.

1. Transistor to truth table [35 points, -6 per wrong or blank entry, minimum 0]

A	B	C	OUT
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

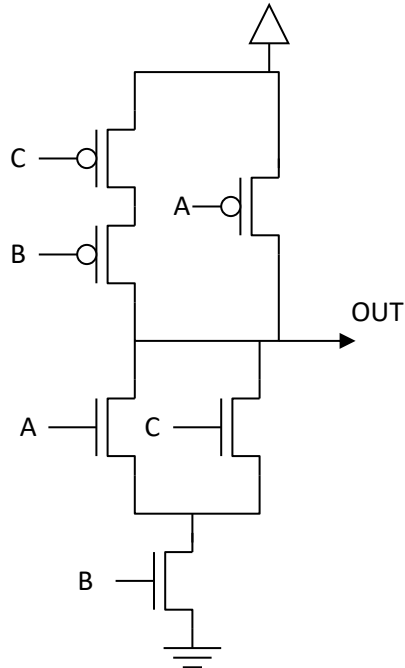

Fill in the above truth table with either "1", "0", "Hi-Z" or "Smoke" (the last if OUT is connected to both Vcc and Ground).

Quiz 4 EECS 270 Spring 2023.

2. Consider the following state table. Minimize the number of states. Give your answer as a state diagram. A is the initial state. [35 points]

State	Next State		Output (W)
	X=0	X=1	
A	A	B	0
B	A	B	1
C	E	A	1
D	D	B	0
E	C	D	1

3. Say we wish to design a memory with that where each location has 2 bits of data using the figure to the right.

[30 points]

- a. How many addresses would you have? _____

- b. There are 5 blanks in the figure. Fill them each in with values that would complete our design. Let address bits be a bus named "A" and the output be a bus named D.

