

## Quiz 4 – EECS 270, Spring '07

Name: KEY unique name: KEY

**Honor code:**

I have not given or received aid on this quiz, nor have I observed anyone else doing so:


Sign here: \_\_\_\_\_

This quiz is graded out of 100 points and is worth about 4% of your class grade. You will have 25 minutes for this quiz. **Closed everything including calculators!** To receive partial credit, work must be shown.


1. Transistor problem. [30]

A	B	C	OUT
0	0	0	<u>1</u>
0	0	1	<u>1</u>
0	1	0	<u>1</u>
0	1	1	<u>0</u>
1	0	0	<u>1</u>
1	0	1	<u>0</u>
1	1	0	<u>1</u>
1	1	1	<u>0</u>

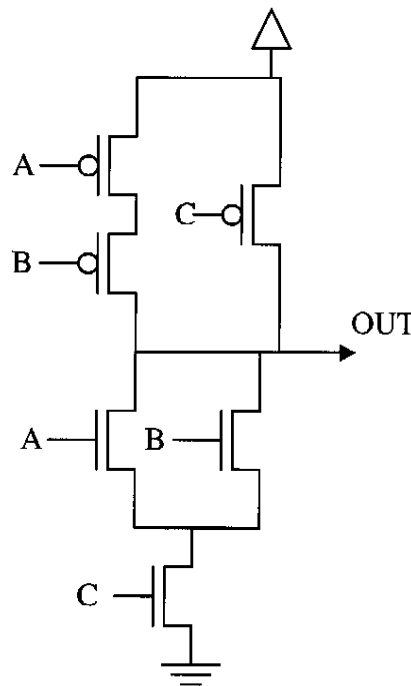
Fill in the above truth table with either "1", "0", "Hi-Z" or "Smoke" (the last if OUT is connected to both Vcc and Ground).



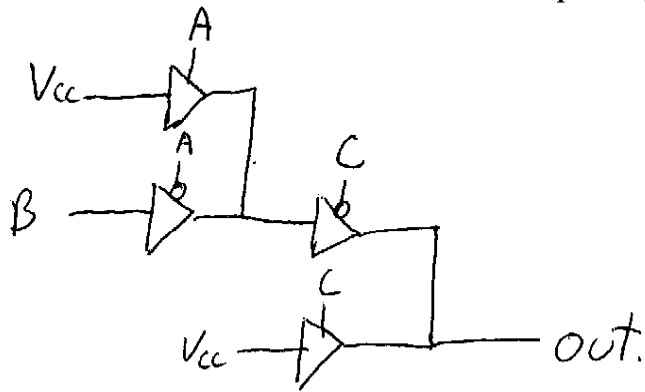2. Using only tri-state drivers and inverters, design a 3-input OR gate. You can freely use "GND" and "Vcc" as needed. For full points your design should use 8 or less devices. [35]




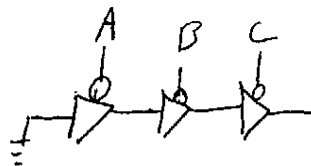Note: A common error was to try to "push" HiZ through a device



If  $\bar{C} = B$ , the output is unknown!

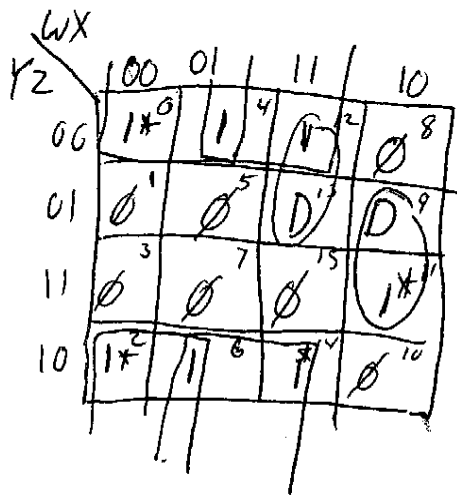3. Using a K-map, find the minimal sum-of-products of  $\Sigma_{(w,x,y,z)} (0,2,4,6,11,12,14) + d(9,13)$ . Place a star (\*) next to each *distinguished 1* in your K-map. [35]



~~$\bar{w}\bar{x}\bar{y}\bar{z}$~~

$$\bar{w}\bar{z} + x\bar{z} + w\bar{x}z$$