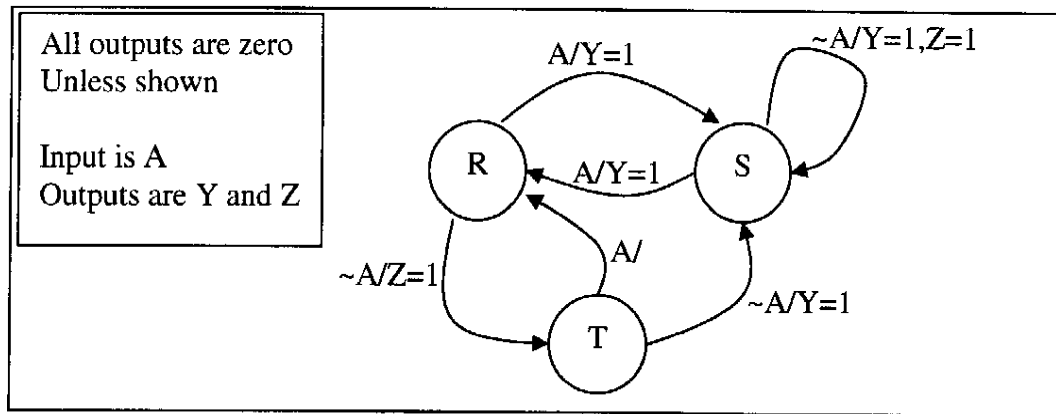



Quiz 5 – Spring 2007 – EECS 270


Name: _____ uname: _____

This quiz is graded out of 100 points. Please remember you can drop your lowest quiz score. You will have 25 minutes for the quiz. It is closed book and closed notes. Show your work and ***circle your answer!***



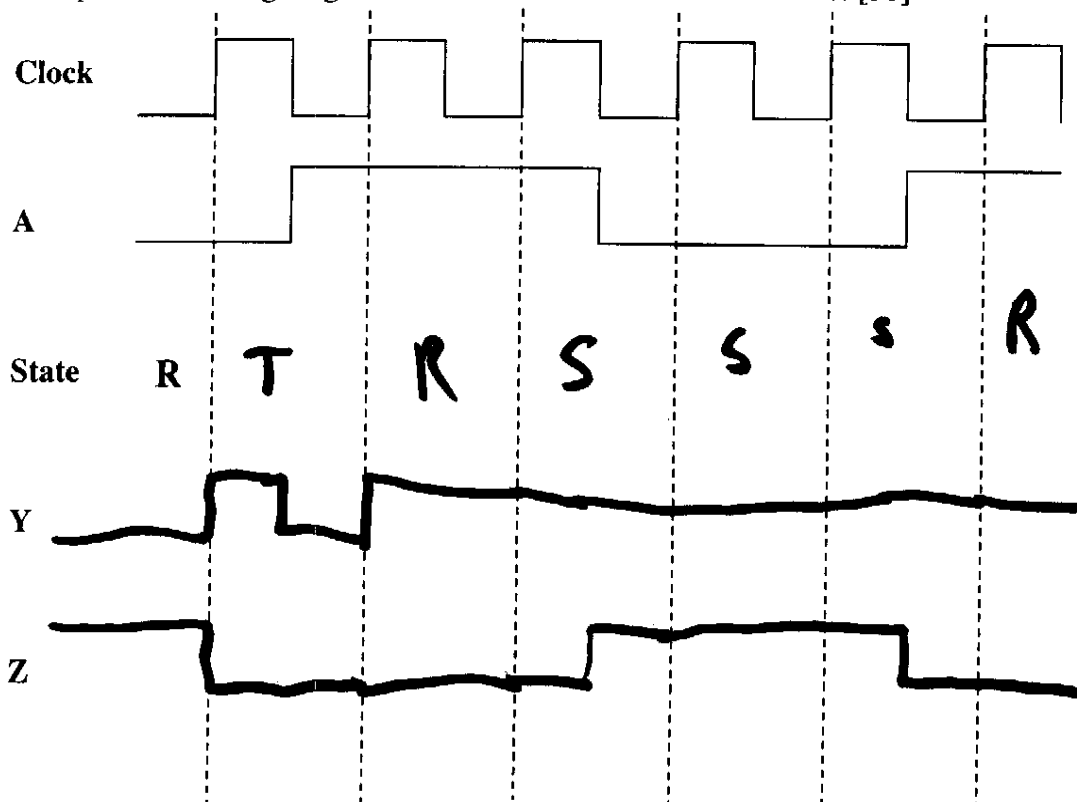1. Complete the timing diagram for the state machine shown above: [50]



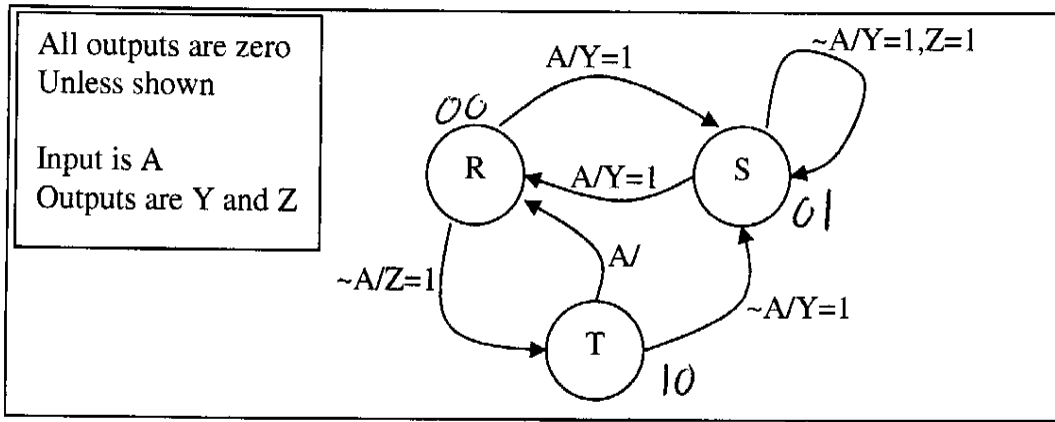

2. For this problem, assign state bits $S[1:0]$ as 00 for state R, 01 for state S, and 10 for state T. Using a K-map, find the *minimal sum-of-products* for next state ($NS[1:0]$) and the outputs (Y and Z). You must show your work to get any credit! [50]

A	S_0	S_1	NS_1	NS_0	Y	Z
0	0	0	1	0	0	1
0	0	1	0	1	1	1
0	1	0	0	1	1	0
0	1	1	D.C.	D.C.	D.C.	D.C.
1	0	0	0	1	1	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	D.C.	D.C.	D.C.	D.C.

NS₁

S_0	S_1	00	01	11	10
0	0	1	0	0	0
1	0	X	X	0	

NS₀

S_0	S_1	00	01	11	10
0	0	0	1	0	1
1	0	1	X	X	0

Y

S_0	S_1	00	01	11	10
0	0	0	1	1	1
1	0	X	X	1	

Z

S_0	S_1	00	01	11	10
0	0	1	0	0	0
1	0	X	X	0	

$\bar{A}S_1$

$$NS_1 = \bar{A} \bar{S}_0 \bar{S}_1$$

$$NS_0 = \bar{A} S_0 + \bar{A} S_1 + A \bar{S}_1 \bar{S}_0$$

$$Y = S_0 + \bar{A} S_1 + A \bar{S}_1$$

$$Z = \bar{A} \bar{S}_1$$