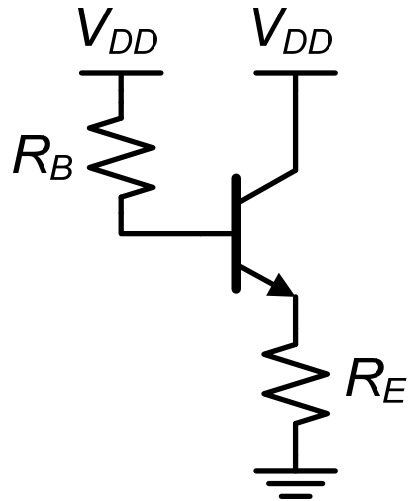


NPN Large Signal (Assume FAR)



$$V_{DD} = 10V$$

$$\beta = 100$$

$$V_A = \text{infinity}$$

$$R_B = 1k$$

$$R_E = 1k$$

$$V_{BEon} = 0.7V \leftarrow$$

$$V_{CEsat} = 0.5V \leftarrow$$

Solve for IC

1. Substitute large-signal FAR model
2. Solve for IC
3. Check assumption

$$V_E \approx 9.2V$$

$$V_{LE} = V_{DD} - V_E$$

$$= 0.8V$$

Large-Sig model


$$I_E = I_B + I_C = \frac{I_C}{\beta} + I_C = \frac{\beta + 1}{\beta} I_C$$

$$V_E = I_E R_E = \frac{\beta + 1}{\beta} I_C R_E$$


$$V_B = V_E + 0.7V$$

$$\frac{V_{DD} - V_B}{R_B} = I_B = \frac{I_C}{\beta} = \frac{V_{DD} - \frac{\beta + 1}{\beta} I_C R_E - 0.7}{R_B}$$
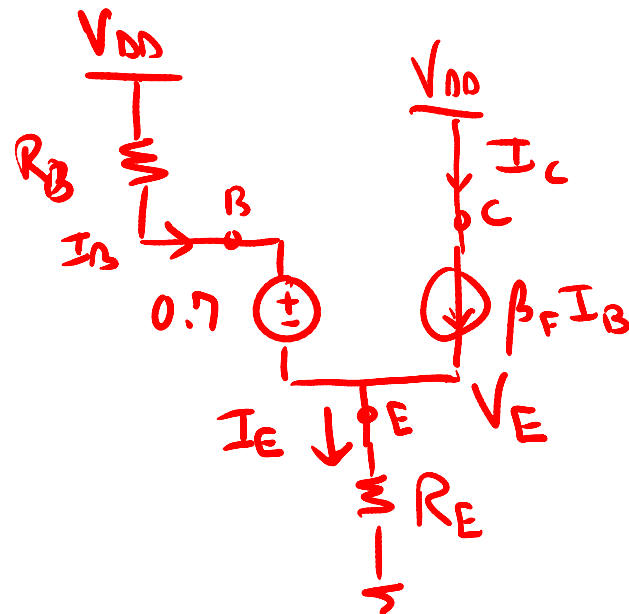
$$I_C = \frac{V_{DD} - 0.7}{\frac{R_B}{\beta} + R_E \frac{\beta + 1}{\beta}} = \frac{9.3}{10 + 1000 \cdot \frac{101}{100}} \approx 9.2mA$$




NPN Large Signal (Assume SAT)

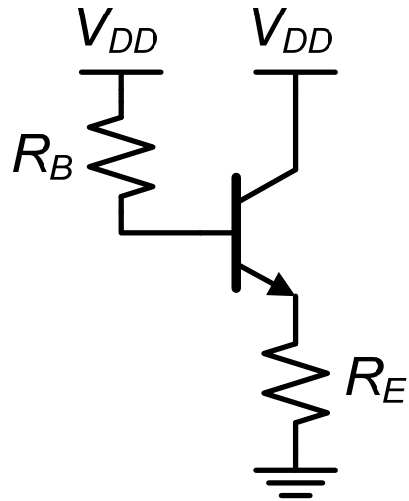

$V_{DD} = 10V$
 $\beta = 100$
 $V_A = \text{infinity}$
 $R_B = 1k$
 $R_E = 1k$
 $V_{BE(on)} = 0.7V$
 $V_{CE(sat)} = 0.5V$

Solve for I_C

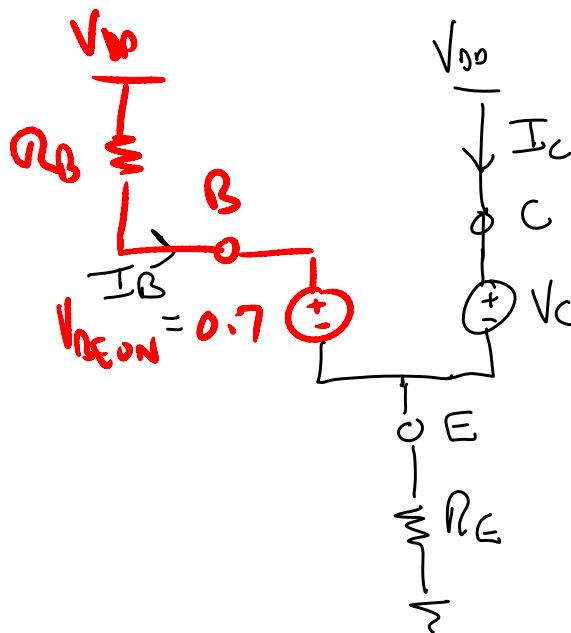1. Substitute large-signal SAT model
2. Solve for I_C
3. Check assumption



$$V_E = V_{DD} - V_{CE(sat)} = 9.5V$$

$$V_B = V_E + V_{BE(on)} = 10.2V$$


$$I_B = \frac{V_{DD} - V_B}{R_B} = \frac{-0.2}{R_B} = -200 \mu A$$

$$I_E = I_B + I_C = \frac{I_C}{\beta} + I_C = \frac{\beta + 1}{\beta} I_C$$

$$I_E = \frac{V_E}{R_E} = 9.5 \text{ mA}$$

$$I_C = I_E - I_B$$

PNP Large Signal (1)

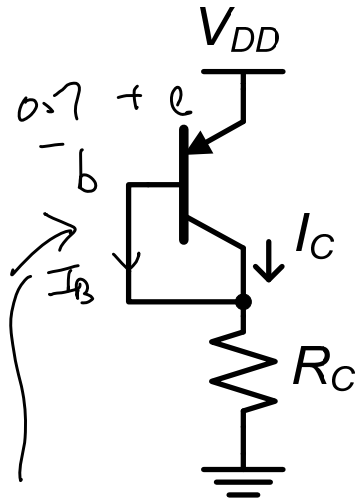


$V_{DD} = 10V$
 $\beta = 100$
 $V_A = \text{infinity}$
 $R_C = 1k$
 $V_{BEon} = -0.7V$
 $V_{CEsat} = -0.5V$

Solve for I_C

1. Choose region of operation
2. Substitute model
3. Solve for I_C
4. Check assumption

"Diode Connected"

Assume FAR

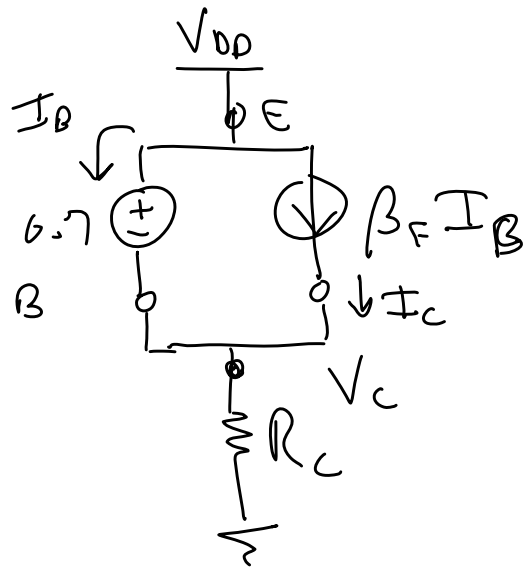

$$V_C = (-I_B + \beta_F I_B) R_C = \left(\frac{I_C}{\beta_F} + I_C \right) R_C = \frac{\beta_F + 1}{\beta_F} I_C R_C$$

$$V_C = V_{DD} - 0.7 = \frac{\beta_F + 1}{\beta_F} I_C R_C$$

$$I_C = \frac{V_{DD} - 0.7}{\frac{\beta + 1}{\beta} R_C}$$

$$\star = \frac{9.3}{1.01 \cdot 1k} \approx 9.2mA$$


$$V_{CE} = ? = -0.7$$

$$|V_{CE}| > |V_{CE(sat)}| \quad \text{FAR} \checkmark$$

PNP Large Signal (2)

Find expression for I_C

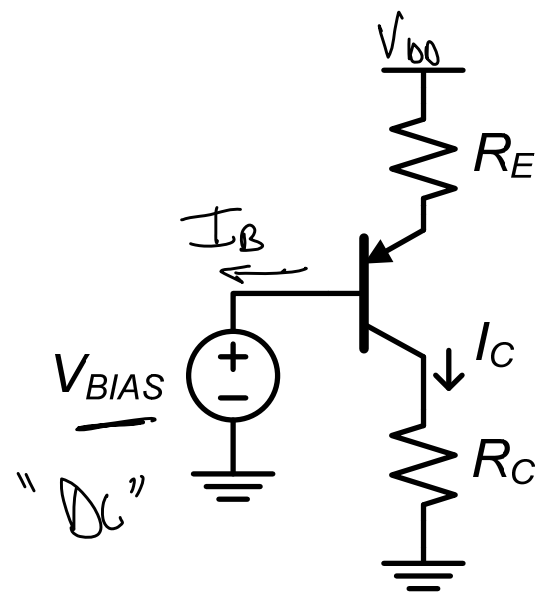
1. Choose region of operation
2. Substitute model
3. Find expression for I_C



$V_{BIAS} \ll V_{DD}$ PNP = ON FAR/ SAT ?

Assume FAR

L.S. Model: V_{DD} R_E I_E

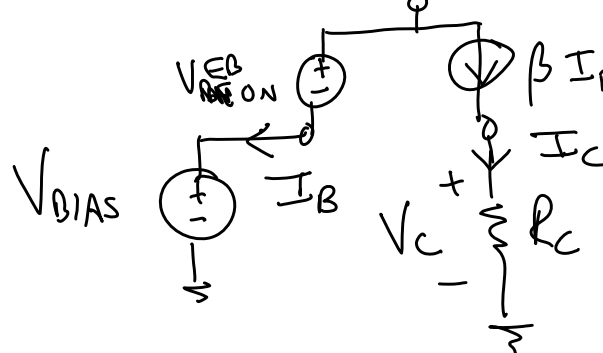

$$I_E = I_B + \beta I_B \left(1 + \frac{V_{EC}}{V_A}\right)$$


$$I_E = \frac{I_C}{\beta \left(1 + \frac{V_{EC}}{V_A}\right)} + I_C$$

$$V_{EC} = V_E - V_C = (V_{BIAS} + V_{EB(on)}) - I_C R_C$$

$$\frac{V_{DD} - V_{BIAS} - V_{EB(on)}}{R_E} = \frac{I_C}{\beta \left[1 + \frac{(V_{BIAS} + V_{EB(on)}) - I_C R_C}{V_A}\right]} + I_C$$


Solve for $I_C \dots$

NMOS DC Model

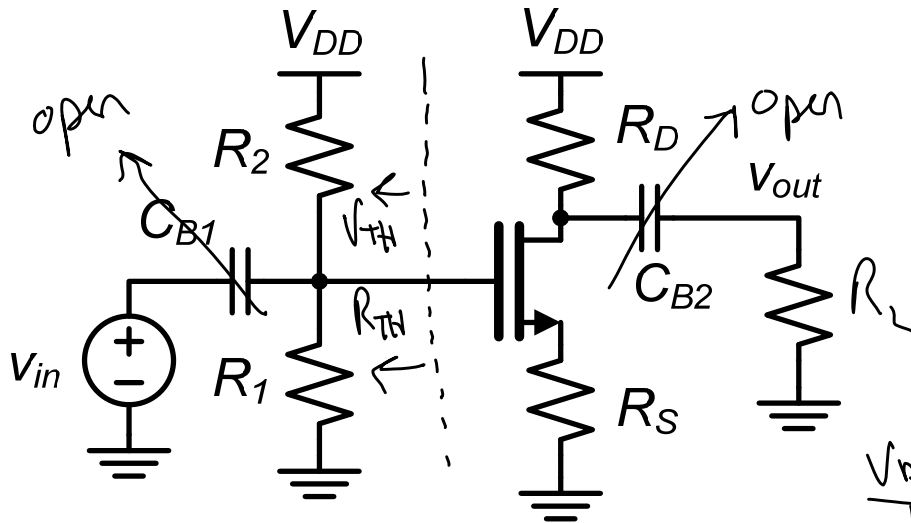

Find expression for I_D

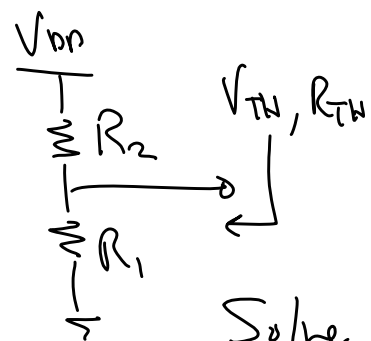1. Choose region of operation
2. Substitute model
3. Find expression for I_D



$$V_{TH} = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Solve for I_D

$$I_S = I_D$$


$$V_S = I_D R_S$$

$$V_D = V_{DD} - I_D R_D \quad V_G = V_{TH}$$

$$C_{B1} = C_{B1G}$$

② DC $C_{B1G} \Rightarrow$ open

Choose Sat.

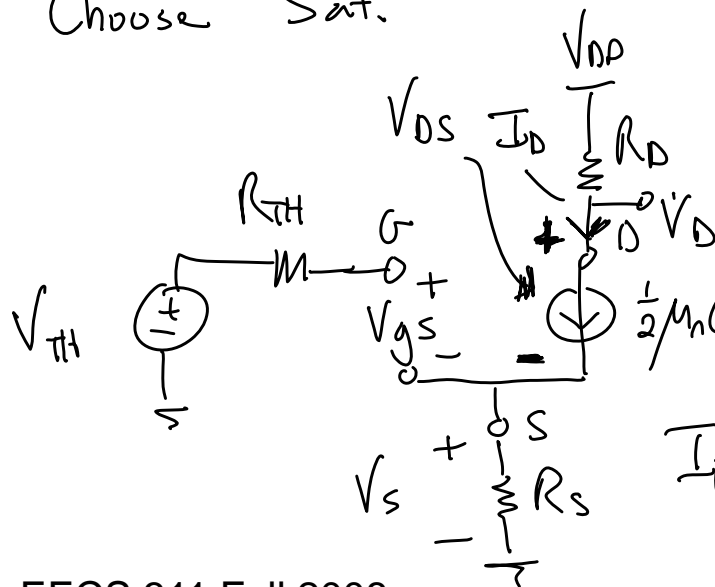


$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds}) = I_D$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[(V_{TH} - I_D R_S) - V_{TH} \right]^2 \left[1 + \lambda (V_{DD} - I_D R_D - I_D R_S) \right]$$


Solve for $I_D \dots$

NPN Small Signal Rout

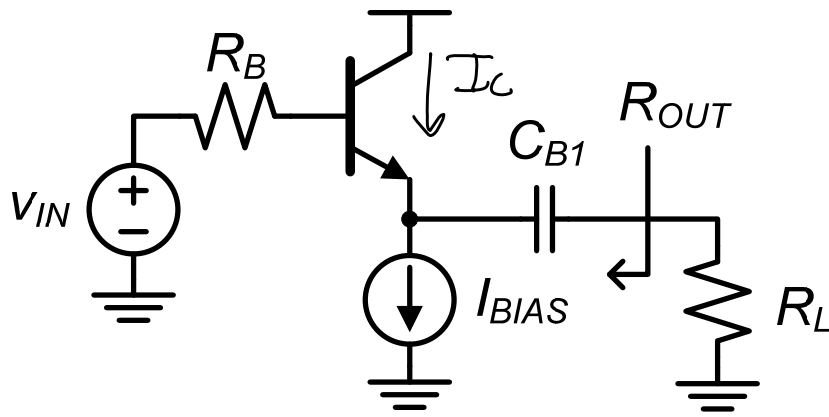


Neglect r_o in BJT model

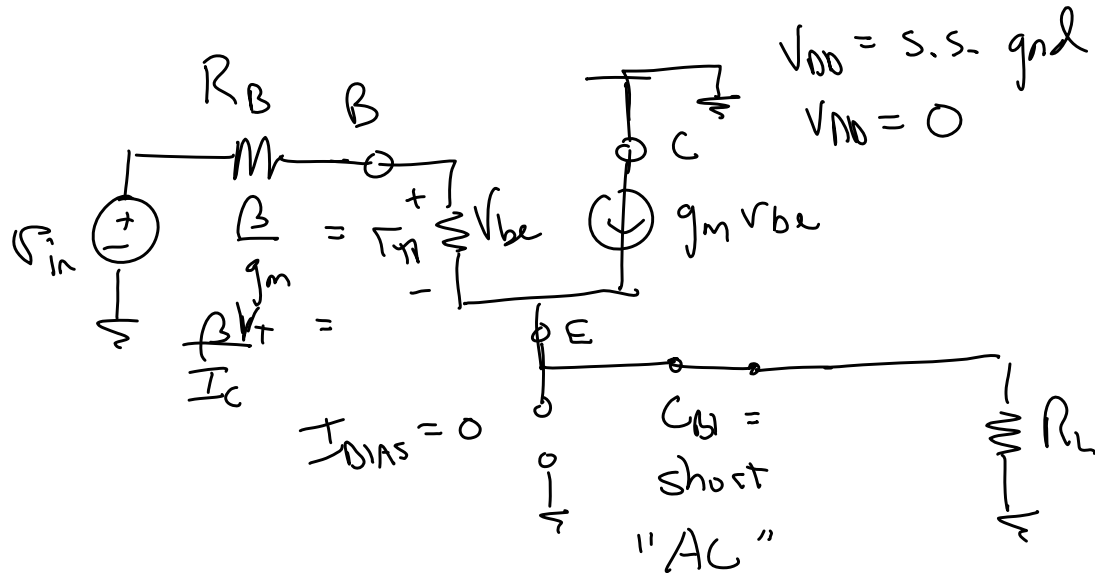1. Find small signal AC model
2. Apply test source to measure Rout
3. $R_{out} = v_t / i_t$



Find R_{out}

Zero ~~dep.~~ indep. sources (v_{in})

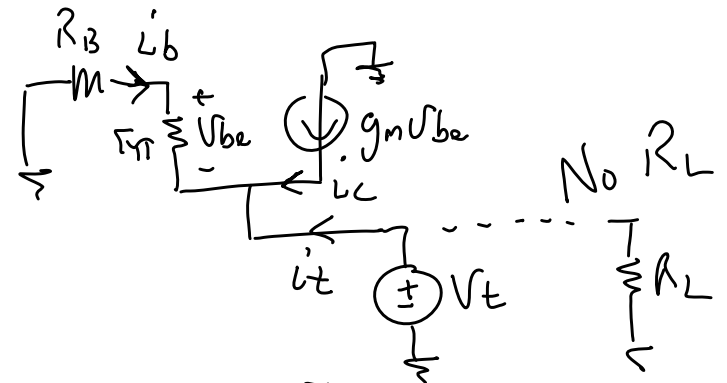


$$v_{be} = -v_t \frac{r_{\pi}}{r_{\pi} + R_B} \quad i_c = g_m \left(-v_t \frac{r_{\pi}}{r_{\pi} + R_B} \right)$$

$$i_b = -\frac{v_t}{r_{\pi} + R_B}$$

$$i_t = -i_b - i_c = +v_t \frac{r_{\pi}}{r_{\pi} + R_B} + v_t \frac{g_m r_{\pi}}{r_{\pi} + R_B}$$

$$R_{out} = \frac{v_t}{i_t} = \frac{r_{\pi} + R_B}{1 + g_m r_{\pi}} = \frac{r_{\pi} + R_B}{1 + \beta_F} = \frac{r_{\pi}}{1 + \beta_F} + \frac{R_B}{1 + \beta_F} \approx \frac{1}{g_m} + \frac{R_B}{\beta}$$

OCTC to Find f_L

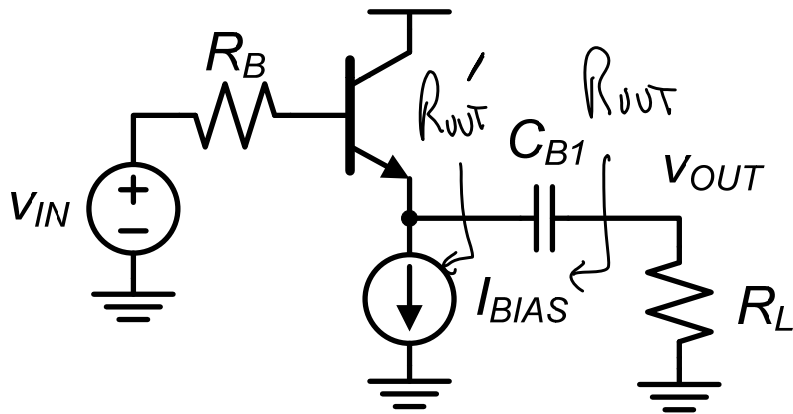

Neglect r_o in BJT model


1. Find small signal low-freq model
2. Apply OCTC

$$R_{out}' = \frac{1}{g_m} + \frac{R_B}{\beta} = R_{out}$$

OCTC

Find R_{B1} for C_{B1}


→ replace C_{B1} w/ V_t

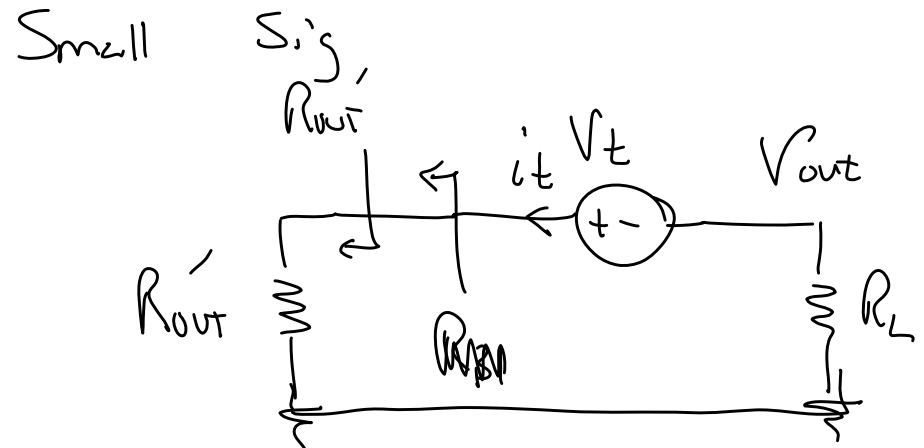

$$R_{D1} = \frac{1}{g_m} + R_L \approx R_{out}'$$



NPN Design Example (1)

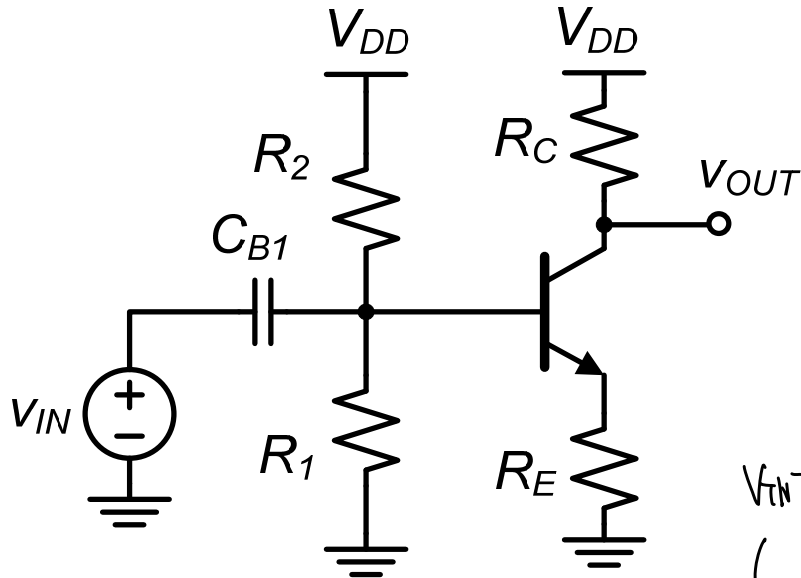Find relationship between Power, DC bias stability, and gain



① DC Bias

Assume FAR,
 $C_{B1} = \text{open}$

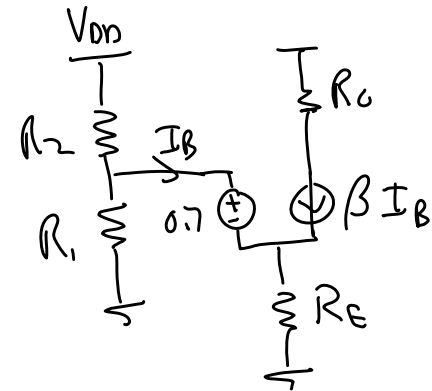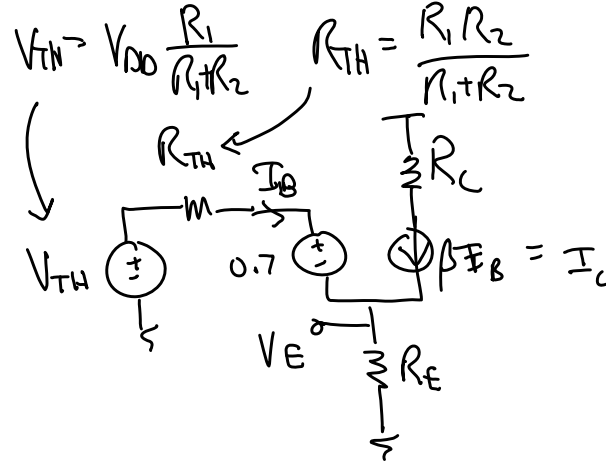

$$V_E = (I_B + I_C) R_E = \frac{\beta + 1}{\beta} I_C R_E$$

$$I_B = \frac{I_C}{\beta} = \frac{V_{TH} - 0.7 - V_E}{R_{TH}}$$


$$= \frac{V_{TH} - 0.7 - \frac{\beta + 1}{\beta} I_C R_E}{R_{TH}}$$

$$I_C = \frac{V_{TH} - 0.7}{\frac{R_{TH}}{\beta} + \frac{\beta + 1}{\beta} R_E} \approx \frac{V_{TH} - 0.7}{\frac{R_{TH}}{\beta} + R_E}$$

$$\Rightarrow \frac{R_{TH}}{\beta} \ll R_E \Rightarrow I_C \text{ indep of } \beta$$

But, small R_{TH} = high power


② Power

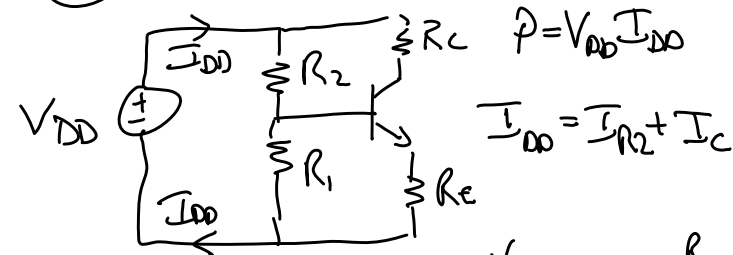

Find I_{R2} :


$$I_{R2} = \frac{V_{DD}}{R_1 + R_2} + I_B \frac{R_1}{R_1 + R_2}$$
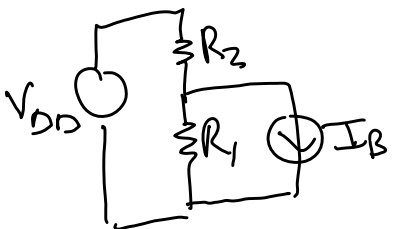
$$= \frac{V_{DD}}{R_1 + R_2} + \frac{I_C}{\beta} \frac{R_1}{R_1 + R_2}$$




$$P = \frac{V_{DD}^2}{R_1 + R_2} + V_{DD} I_C \left[1 + \frac{1}{\beta} \frac{R_1}{R_1 + R_2} \right]$$

NPN Design Example (2)

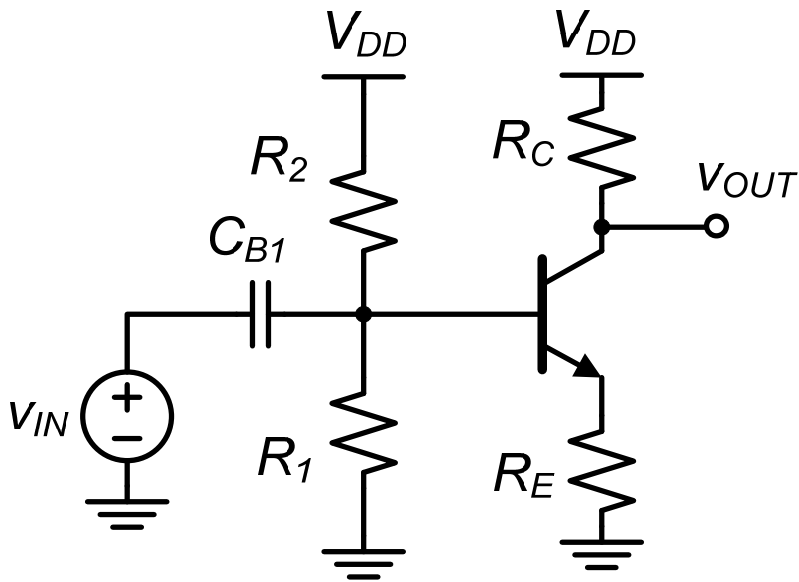

SS. AC model! $C_{B1} = \text{short}$

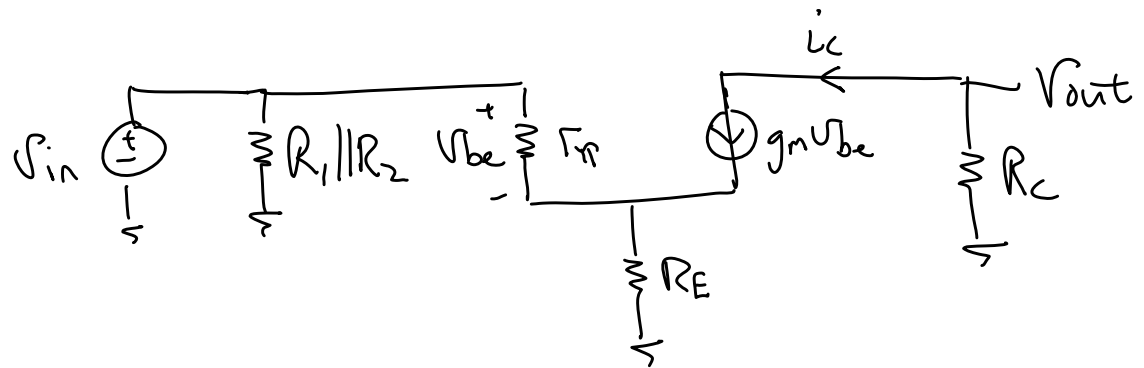

$$V_e = i_c R_E = \left(\frac{V_{be}}{r_{\pi}} + g_m V_{be} \right) R_E \quad V_{be} = V_{in} - V_e$$

$$V_{be} = V_{in} - V_{be} R_E \left(\frac{1}{r_{\pi}} + g_m \right) \quad V_{be} = \frac{V_{in}}{1 + R_E \left(\frac{1}{r_{\pi}} + g_m \right)}$$

$$i_c = g_m V_{be} = V_{in} \frac{g_m}{1 + \underbrace{g_m R_E + \frac{R_E}{r_{\pi}}}}_{\frac{R_E g_m}{\beta}} \approx V_{in} \frac{g_m}{1 + g_m R_E}$$

$$V_{out} = -i_c R_C = V_{in} \frac{g_m R_C}{1 + g_m R_E}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_m R_C}{1 + g_m R_E} \approx - \frac{V_{RC}/V_T}{1 + V_{RE}/V_T} \quad \text{For } I_C \approx I_E$$

Gain independent of power! 9