

University of Michigan
EECS 311: Electronic Circuits
Fall 2008

Quiz 2

11/3/2008

NAME: _____

Honor Code:


I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code.

Signature _____


Problem	Points	Score	Initials
1	26		
2	20		
3	30		
4	24		
	Total		

Problem 1 (26 Points): Potpourri – this problem has four unrelated parts.

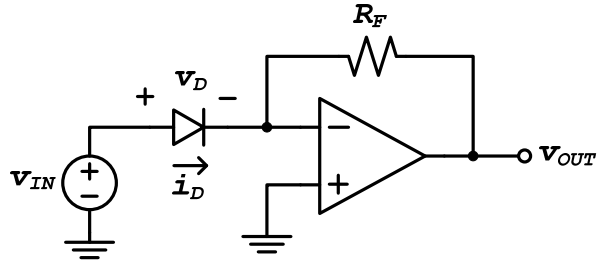- a) Find the expression for gain $A_v = v_{OUT}/v_{IN}$ of the circuit below. Use the exact model for the diode, $i_D = I_S(e^{v_D/V_T} - 1)$. Assume the opamp is ideal.




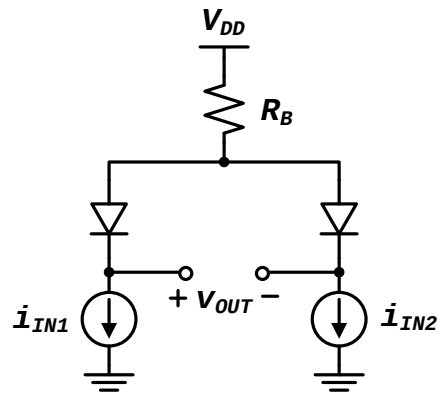- b) Find an expression for the voltage v_{OUT} for the circuit below assuming $i_{IN1} > 0$ and $i_{IN2} > 0$. Use the exact model for the diodes, $i_D = I_S(e^{v_D/V_T} - 1)$, assuming the two diodes are identical (same values for I_S and same temperature).




Initials: _____

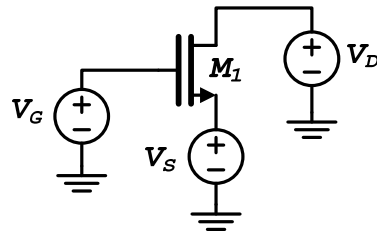- c) Identify the region of operation of M_1 in the circuit below when $V_G = 2\text{ V}$, $V_D = 3\text{ V}$, and $V_S = -1\text{ V}$. Assume $V_{TN} = 1\text{ V}$ and ignore the body-effect on threshold voltage.




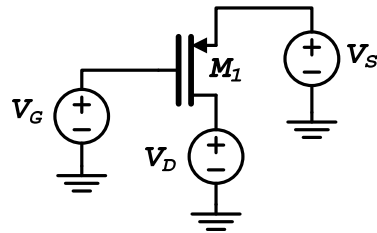- d) Identify the region of operation of M_1 in the circuit below when $V_G = 3\text{ V}$, $V_D = 5\text{ V}$, and $V_S = 5\text{ V}$. Assume $V_{TP} = -1\text{ V}$ and ignore the body-effect on threshold voltage.



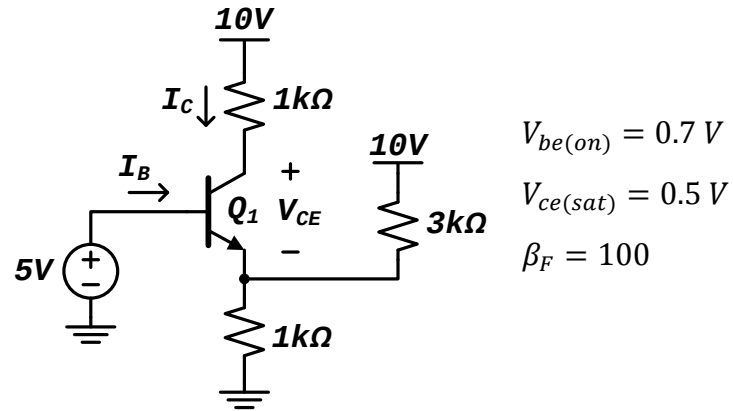Problem 2 (20 Points):

Use the following circuit and ignore base-width modulation for all parts.




- a) Substitute the simplified large-signal model for the BJT in the forward-active region using the constant-voltage source model for the base-emitter junction diode. Solve for the values of I_C and V_{CE} .

Initials: _____

- b) Substitute the simplified large-signal model for the BJT in the saturation region using the constant-voltage source models for the base-emitter and collector-emitter voltages. Solve for the values of I_B and I_C .

c) Given your answers to parts a) and b), is Q_1 in the forward-active or saturation region.

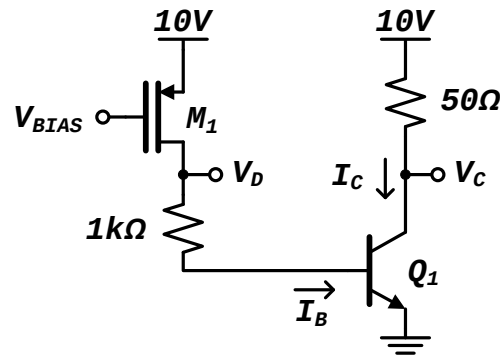Problem 3 (30 Points): Use the circuit shown below to answer all of the following parts. Use the constant-voltage source model for the base-emitter junction diode of Q_1 . Ignore channel-length modulation, body effect, and base-width modulation for all parts.



$$\mu_p C_{ox} \frac{W}{L} = 500 \mu A/V^2$$

$$V_{tp} = -1.0 V$$

$$V_{be(on)} = 0.7 V$$

$$V_{ce(sat)} = 0.5 V$$


$$\beta_F = 100$$

- a) Assuming Q_1 is kept in the forward-active region, find the numerical value of I_B required to support $I_C = 1 mA$.


b) Assuming M_1 is kept in saturation, find the numerical value of V_{BIAS} required to support I_B from part a).

c) Find the maximum value of I_C allowed while keeping Q_1 in the forward-active region.

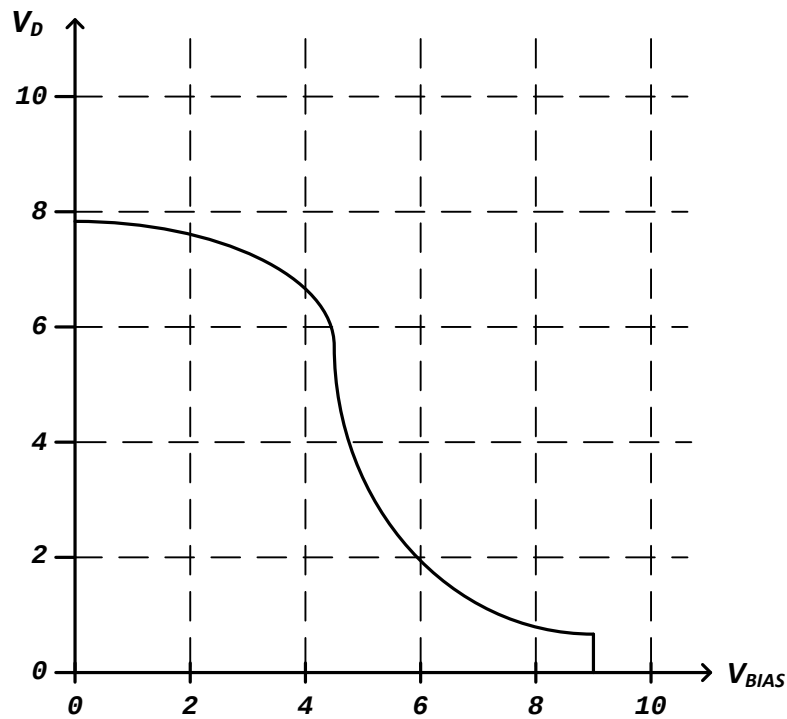
- d) As V_{BIAS} is swept from 0 to 10 V, the drain voltage V_D follows the graph shown below. Label the regions on the graphs where M_1 is in *cutoff*, *linear*, and *saturation*, specifically showing the values of V_{BIAS} at the boundaries between regions.



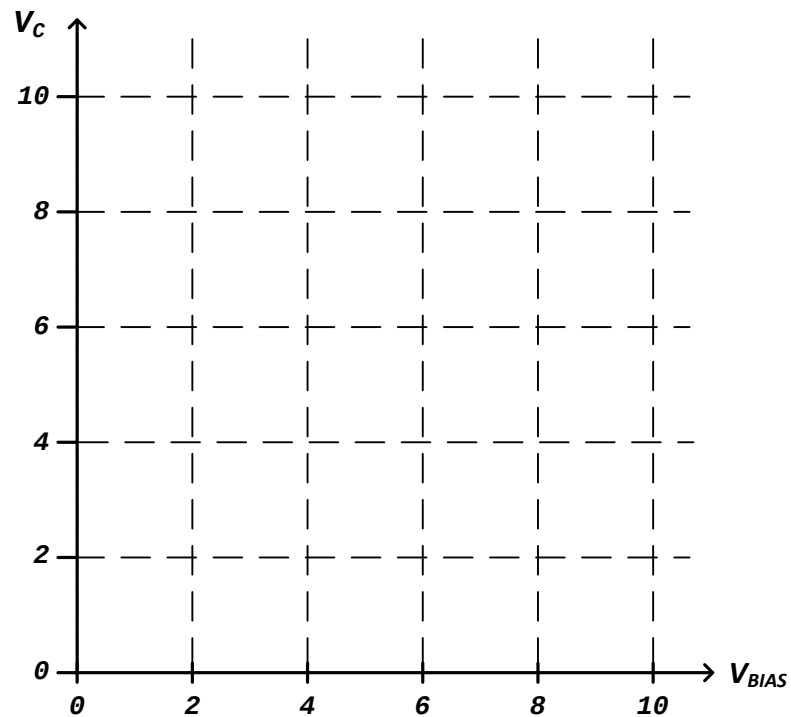
- e) Sketch the voltage at node V_C as V_{BIAS} is swept from 0 to 10 V. Use the graph from part d), giving you V_D as V_{BIAS} is swept over the same range, to generate your sketch. Label the regions on the graph where Q_1 is in *off*, *forward-active*, and *saturation*.



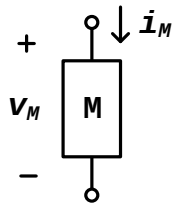Problem 4 (24 Points): A non-linear two-terminal device M has the following I-V relationship, given in an expression and also plotted. Use this device to answer the following questions about small-signal analysis.




$$i_M = 0.01 \cdot v_M^2 \text{ A}$$

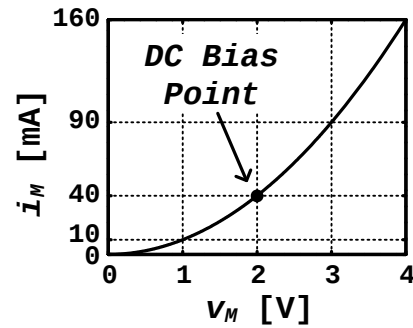

- a) Derive an expression for the small-signal conductance i_m/v_m , linearized around a DC operating point defined by variables I_M and V_M .


- b) Complete the small-signal model by drawing the circuit element in the box that should be used to model the device in small-signal. Evaluate the value of this element at the bias current of $I_M = 40 \text{ mA}$ as shown in the graph above.

Small-Signal Model

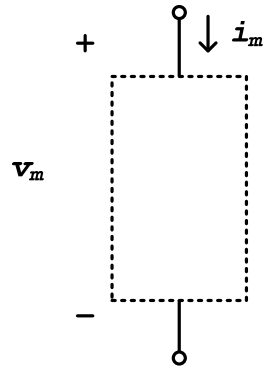

Initials: _____

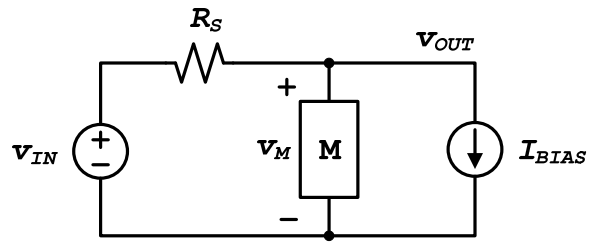- c) The device is used in the following circuit. Draw the complete small-signal circuit, substituting the model for the device found in part b). Assume I_{BIAS} is a DC bias current.



(Space for additional work)