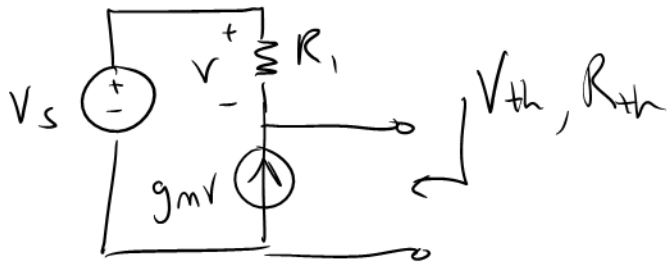


Problem Set 1 Solutions

Pl.1 a) J+B 1.24




Open ckt V_{th} KCL @ output

$$g_m v + \frac{v}{R} = 0 \quad \text{only solution } v = 0$$

$$\boxed{V_{th} = V_s}$$

R_{th} with $V_s = 0$


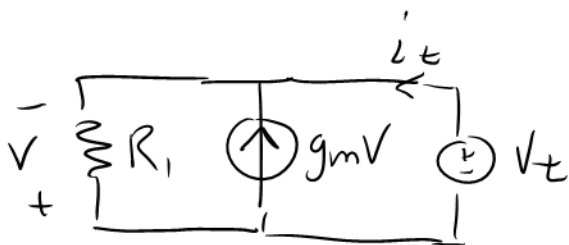


$$v = -V_t$$


$$i_t = \frac{V_t}{R} + g_m V_t$$

$$\boxed{R_{th} = R \parallel \frac{1}{g_m}}$$

b) J+B 1.25

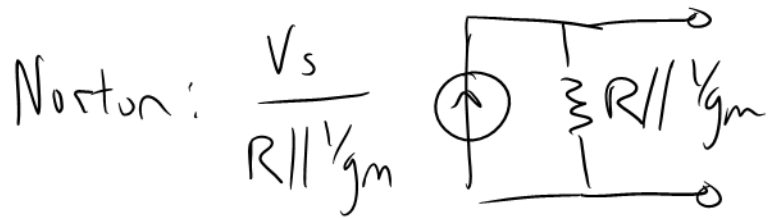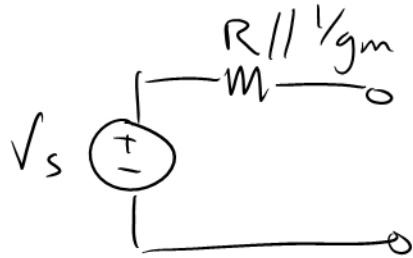


c) J+B 1.26 a)

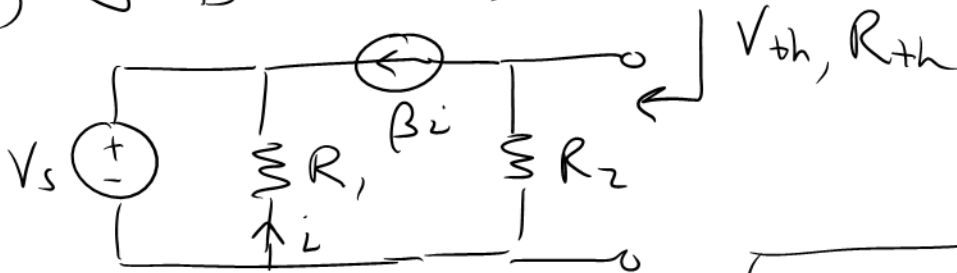

$$i = -\frac{V_s}{R_1} \quad V_{th} = -\beta i \cdot R_2 = V_s \beta \frac{R_2}{R_1}$$

R_{th} w/ $V_s = 0$

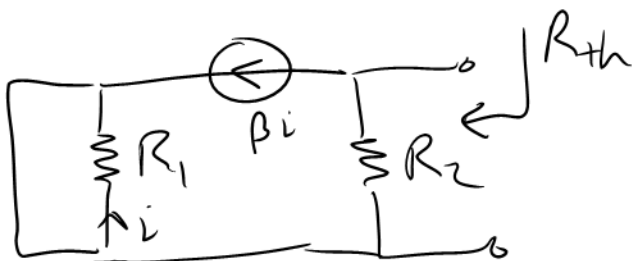

$$V_{R_2} = 0 \Rightarrow i = 0$$

$$R_{th} = R_2$$

$\beta + 1$ 1.26 b)




V_{th}

$$V_{oc} = -\beta i R_2$$

$$i = -i_s - \beta i \Rightarrow i = -\frac{i_s}{1+\beta}$$

$$V_{oc} = V_{th} = i_s \frac{\beta}{1+\beta} R_2$$

R_{th} w/ $i_s = 0$

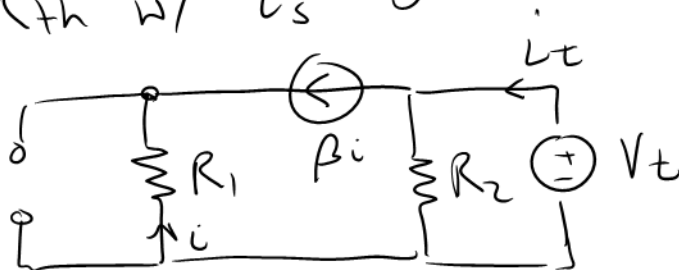


$$KCL: i + \beta i = 0 \quad i = 0$$

$$i_t = \frac{V_t}{R_2} + \cancel{\beta i} = \frac{V_t}{R_2}$$

$$R_{th} = R_2$$


d) J+B: 1.29

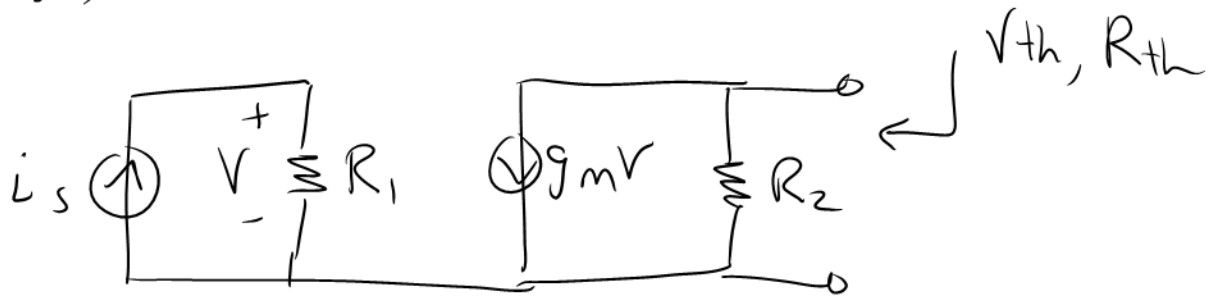

$$V = I_s R_1, \quad V_{oc} = -g_m V R_2$$

$$\boxed{V_{th} = -g_m I_s R_1 R_2}$$

$R_{th}, I_s = 0$

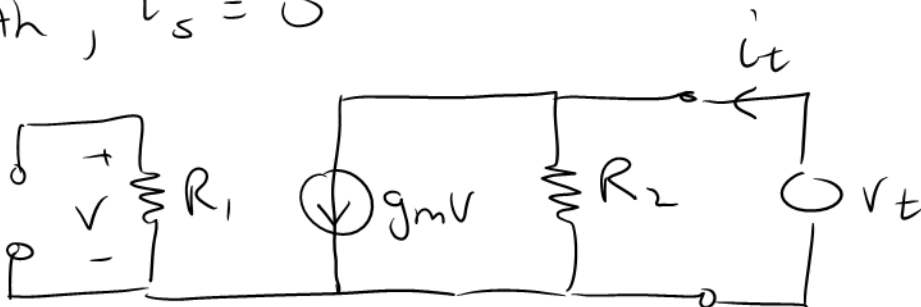


$$V = 0, \quad g_m V = 0$$

$$I_t = \cancel{g_m V} + \frac{V_t}{R_2} = \frac{V_t}{R_2}$$


$$\boxed{R_{th} = R_2}$$

P1.2

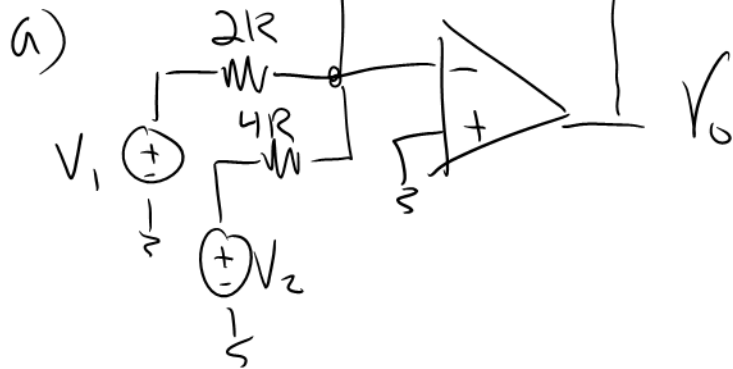

Superposition:

Solve for $V_0 = f(V_1) |_{V_2=0}$

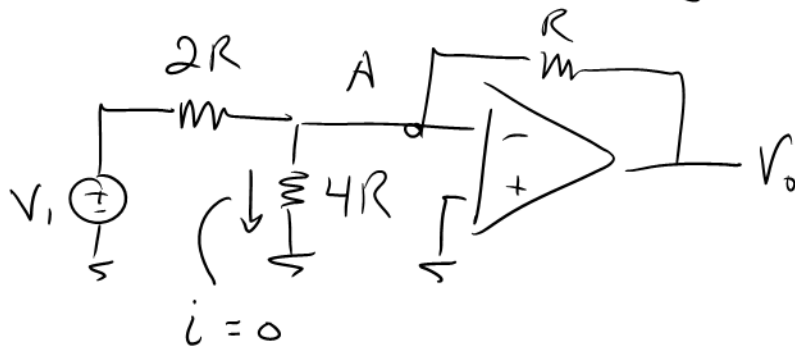


KCL @ A

$$\frac{V_1 - 0}{2R} + 0 + \frac{V_0 - 0}{R} = 0$$

$$V_0 = -V_1 \frac{R}{2R} = -\frac{1}{2} V_1$$

Solve for $V_0 = f(V_2) |_{V_1=0}$

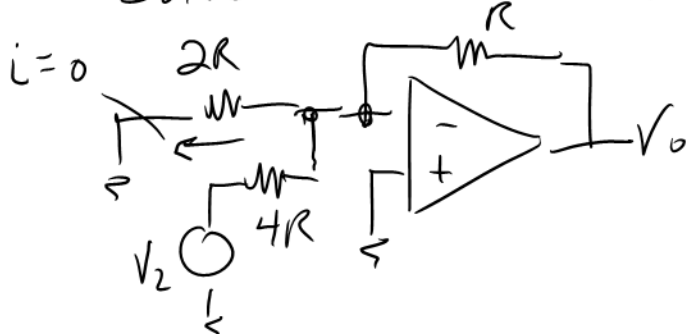

$$\frac{V_2 - 0}{4R} + \frac{V_0 - 0}{R} = 0$$

$$V_0 = -\frac{1}{4} V_2$$

Pl.2 a) (cont)

Putting together:


$$V_o = -\left(\frac{1}{2}V_1 + \frac{1}{4}V_2\right)$$

b)

V_1	V_2	V_o
0	0	0
0	V_{ref}	$-\frac{1}{4}V_{ref}$
V_{ref}	0	$-\frac{1}{2}V_{ref}$
V_{ref}	V_{ref}	$-\frac{3}{4}V_{ref}$


This implements a 2-bit digital-to-analog converter (DAC)

P1.3

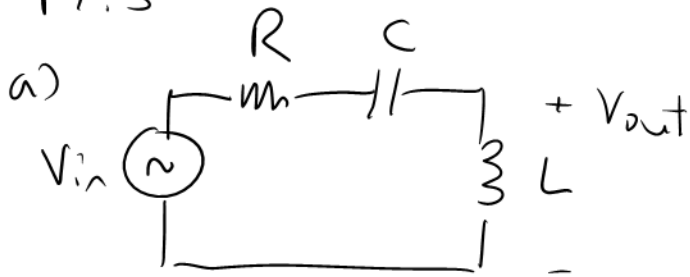

Voltage divider
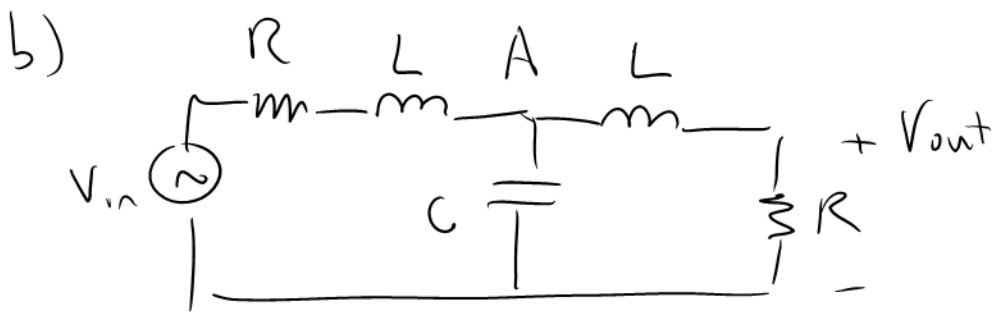
$$V_{out} = V_{in} \cdot \frac{sL}{R + \frac{1}{sC} + sL} = \boxed{\frac{s^2 LC}{1 + sRC + s^2 LC}}$$



① Find V_A

$$V_A = V_{in} \frac{(R + sL) \parallel \frac{1}{sC}}{R + sL + \underbrace{(R + sL) \parallel \frac{1}{sC}}_{\frac{R + sL}{1 + sC(R + sL)}}}$$

$$V_A = V_{in} \frac{\cancel{(R + sL)}}{(\cancel{R + sL})(1 + sC(R + sL)) + \cancel{(R + sL)}} = V_{in} \frac{1}{2 + sC(R + sL)}$$


② Find $V_{out} = f(V_A)$

$$V_{out} = V_A \frac{R}{R + sL}$$

③ Substitute V_A

$$V_{out} = V_{in} \frac{1}{2 + sC(R + sL)} \cdot \frac{R}{R + sL}$$
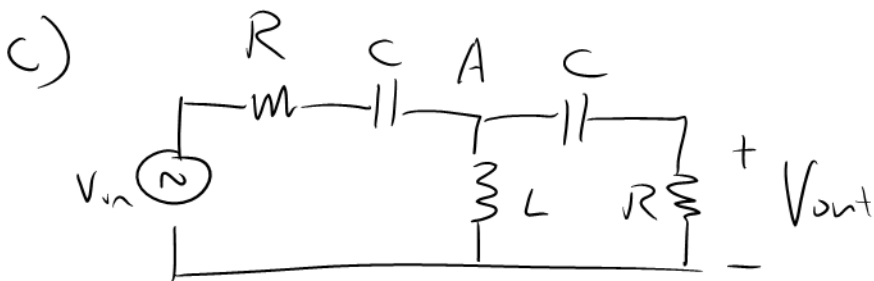
$$A_v = \frac{1}{2} \frac{1}{\left(1 + \frac{sRC}{2} + \frac{s^2 LC}{2}\right) \left(1 + sL/R\right)}$$



Find V_A :

$$V_A = V_{in} \frac{sL \parallel (R + 1/sC)}{(R + 1/sC) + \underbrace{sL \parallel (R + 1/sC)}} = \frac{sL(R + 1/sC)}{sL + R + 1/sC}$$

$$V_A = V_{in} \frac{SL(R + Y_{SC})}{(R + Y_{SC})(sL + R + Y_{SC}) + SL(R + Y_{SC})}$$


$$= V_{in} \frac{sL}{R + 2sL + 1/sC} = \frac{s^2LC}{1 + sRC + 2s^2LC}$$

Find V_{out} :

$$V_{out} = V_A \frac{R}{R + Y_{SC}} = \frac{sRC}{1 + sRC}$$

Substituting:
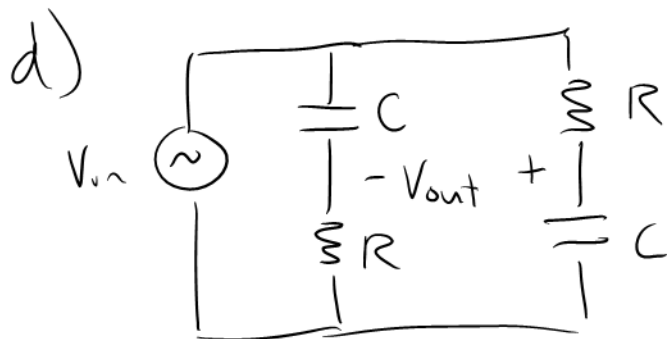
$$\frac{V_{out}}{V_{in}} = \frac{s^3RLC^2}{(1 + sRC + 2s^2LC)(1 + sRC)}$$





$$V_{out} = V_{in} \frac{1/sC}{R + 1/sC} - V_{in} \frac{R}{R + 1/sC}$$



$$A_v = \frac{1 - sRC}{1 + sRC}$$

P1.4

a) $A_v = \frac{1}{1 + s/10^3}$

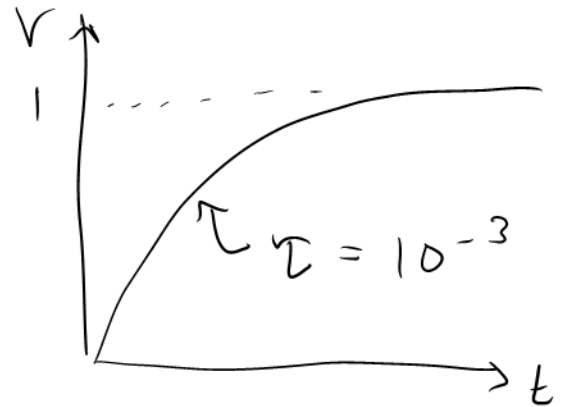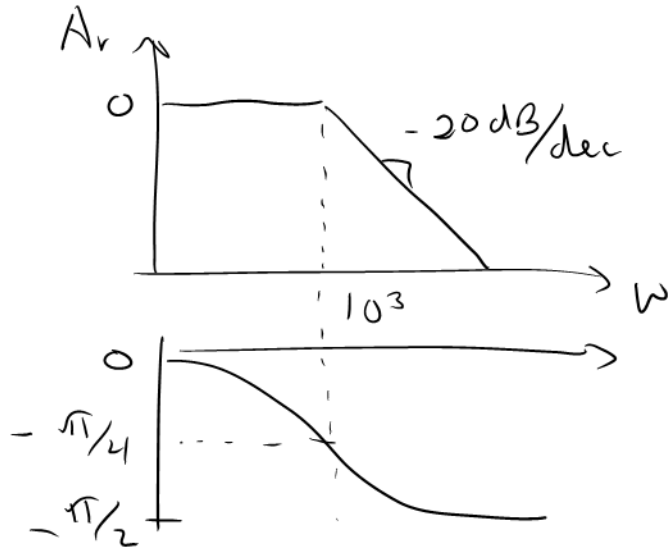

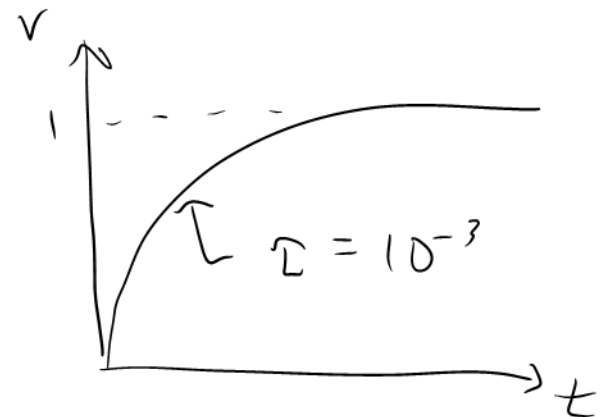
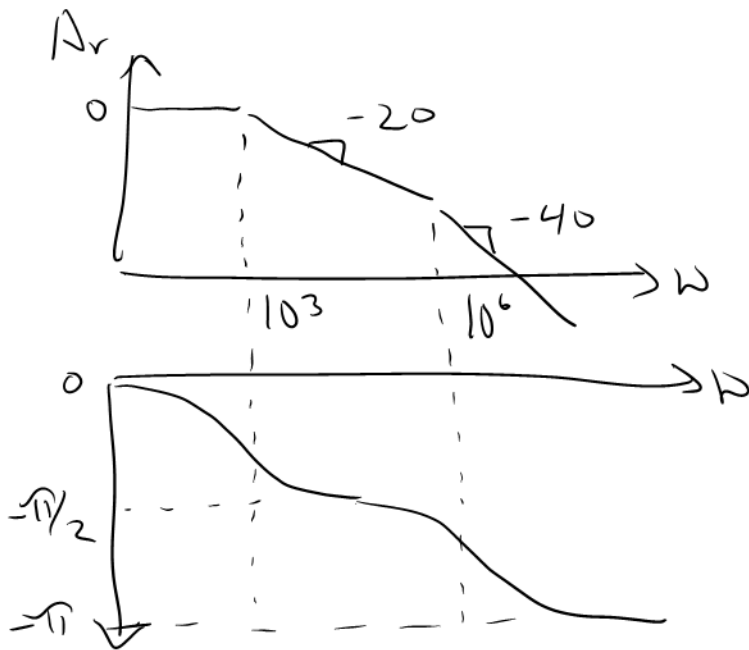
b) $A_v = \frac{1}{(1 + \frac{s}{10^3})(1 + \frac{s}{10^6})}$



Second time constant
is $10^{-6} \rightarrow$ much
faster than 10^{-3}
Approx as 1st order

$$c) A_v = \frac{s/10^3}{1 + (s/10^3)^2}$$

$$Q = \infty$$

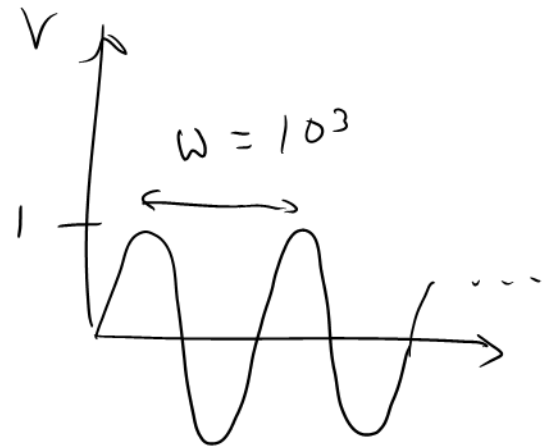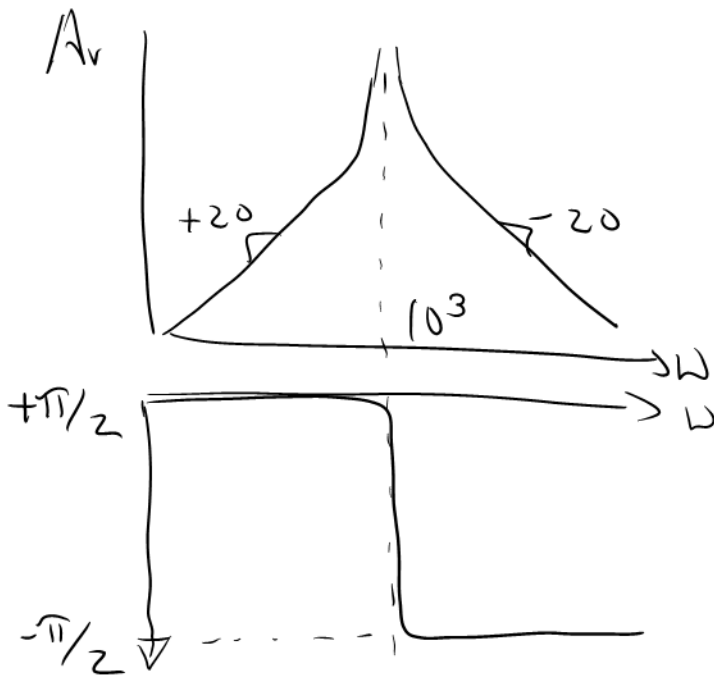

$$d) A_v = \frac{1}{1 + \frac{s}{10^4} + (\frac{s}{10^3})^2}$$

$$Q = 10$$

