

P2.1

$$11.38) A_v = -6 \text{ V/V}$$

$$a) Z_{in} = 20 \text{ k}\Omega$$

$$Z_{out} = 0 \Omega$$

$$b) A_v = 1 + \frac{R_F}{R_i} = 1 + 8 = 9 \text{ V/V}$$


$$Z_{in} = 75 \text{ k}\Omega$$

$$Z_{out} = 0$$

$$c) A_v = 0 \text{ V/V}$$

$$Z_{in} = 160 \text{ k}\Omega$$

$$Z_{out} = 0 \Omega$$

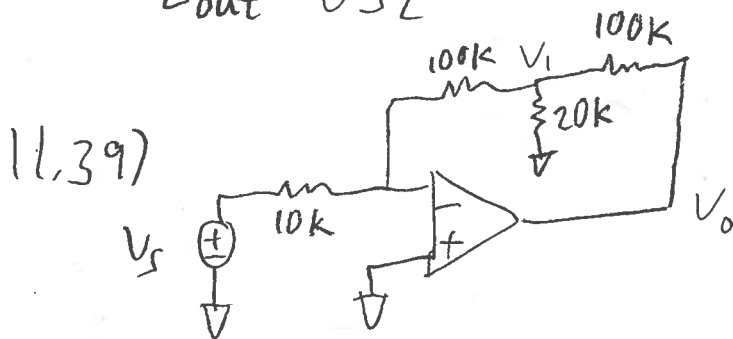

$$Z_{in} = 10 \text{ k}\Omega$$

$$Z_{out} = 0 \Omega$$

$$\frac{V_s}{10\text{k}} = \frac{-V_1}{100\text{k}}$$

$$\frac{-V_1}{100\text{k}} = \frac{V_1}{20\text{k}} + \frac{V_1 - V_o}{100\text{k}}$$


$$\Rightarrow \frac{V_1}{50\text{k}} + \frac{V_1}{20\text{k}} = \frac{V_o}{100\text{k}} \Rightarrow \frac{7V_1}{100\text{k}} = \frac{V_o}{100\text{k}}$$

$$7V_1 = V_o$$

$$\therefore 10 V_s = -\frac{V_o}{7}$$

$$\frac{V_o}{V_s} = (-70 \text{ V/V})$$

P2.2

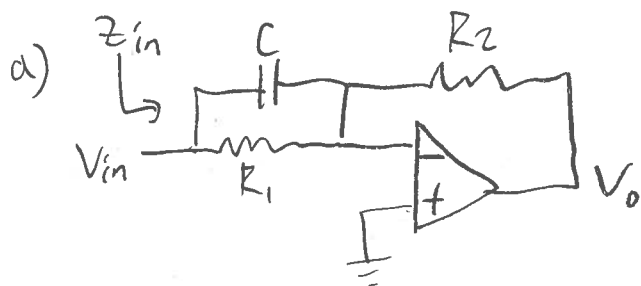

$$Z_{in} = R_1 \parallel \frac{1}{sC} = \frac{R_1}{1 + sR_1C}$$

$$\frac{V_o}{V_{in}} = -\frac{Z_f}{Z_i} = -\frac{R_2}{R_1 \parallel \frac{1}{sC}} = -\frac{R_2}{\frac{R_1}{1 + sR_1C}} = -\frac{R_2}{R_1} (1 + sR_1C)$$

b)

$$\frac{V_o}{V_{in}} = -\frac{Z_f}{Z_i} = -\frac{1/sC}{R} = -\frac{1}{sRC} \quad Z_{in} = R$$

c)

$$\frac{V_o}{V_{in}} = 1 \quad Z_{in} = \infty$$

d)


$$V_- = \frac{R_1}{R_1 + R_2} V_o = V_+ = V_{in}$$

$$\frac{V_o}{V_{in}} = 1 + \frac{R_2}{R_1}$$

$$Z_{in}: V_o = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

$$i_{test} = \frac{V_{test} - \left(1 + \frac{R_2}{R_1}\right) V_{test}}{R_L}$$

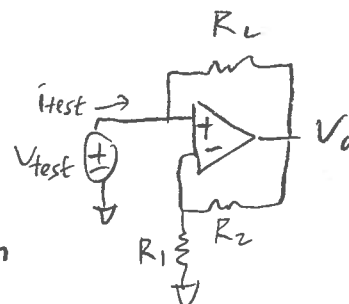
$$= V_{test} \left(-\frac{R_2}{R_1 R_L}\right)$$



$$Z_{in} = -\frac{R_1 R_L}{R_2}$$

↑
 < 0 only possible w/
 active elements such
 as an op-amp.

P2.3

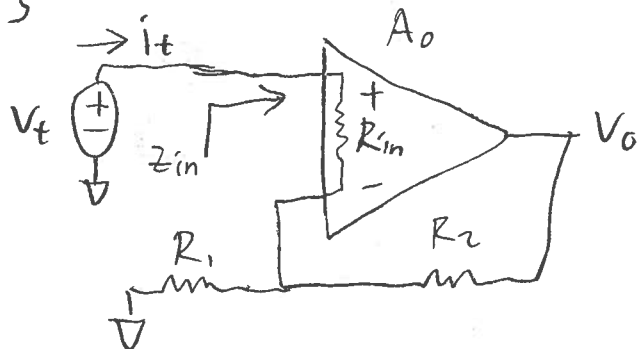

$$\begin{aligned} V_o &= A_o (V_+ - V_-) \\ i_t + \frac{V_o - V_-}{R_2} &= \frac{V_-}{R_1} \quad (2) \\ i_t R_{in} &= V_+ - V_- \\ V_o &= A_o i_t R_{in} \quad (1) \\ V_+ &= V_t \\ V_- &= V_t - i_t R_{in} \quad (3) \end{aligned}$$

① & ③ into ②:

$$i_t + \frac{A_o i_t R_{in} - (V_t - i_t R_{in})}{R_2} = \frac{V_t - i_t R_{in}}{R_1}$$

$$i_t \left(1 + \frac{A_o R_{in}}{R_2} + \frac{R_{in}}{R_2} + \frac{R_{in}}{R_1} \right) = V_t \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$i_t \frac{R_1 R_2 + A_o R_1 R_{in} + R_1 R_{in} + R_2 R_{in}}{R_1 R_2} = V_t \frac{R_1 + R_2}{R_1 R_2}$$


$$Z_{in} = \frac{R_1 R_2 + R_1 R_{in} + R_2 R_{in} + A_o R_1 R_{in}}{R_1 + R_2}$$

assuming $R_{in} \gg R_1, R_2$

$$Z_{in} \approx \frac{R_{in} (R_1 + R_2 + A_o R_1)}{R_1 + R_2} \approx R_{in} \left(1 + \frac{A_o R_1}{R_1 + R_2} \right)$$
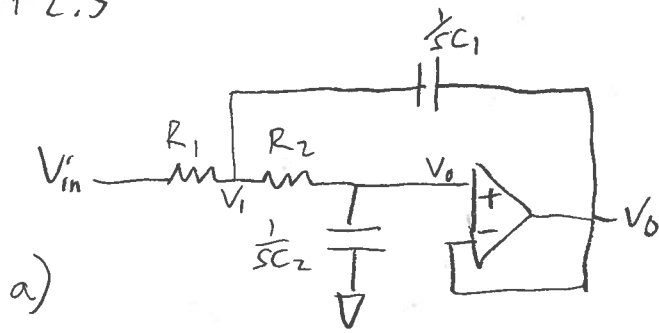
#2.5

$$\frac{V_{in} - V_1}{R_1} + sC_1(V_0 - V_1) = \frac{V_1 - V_0}{R_2} \quad (1)$$



$$\frac{V_1 - V_0}{R_2} = sC_2 V_0$$

$$V_1 = V_0(sR_2C_2 + 1) \quad (2)$$


plug (2) into (1):

$$\frac{V_{in} - V_0(1 + sR_2C_2)}{R_1} + sC_1V_0(-sR_2C_2) = \frac{V_0 sR_2C_2}{R_2}$$

$$V_{in} - V_0(1 + sR_2C_2) = V_0(sR_1C_2 + s^2R_1R_2C_1C_2)$$

$$V_{in} = V_0(sC_2(R_1 + R_2) + s^2R_1R_2C_1C_2 + 1)$$
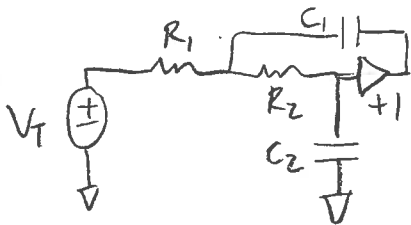
$$\frac{V_0}{V_{in}} = \frac{1}{s^2R_1R_2C_1C_2 + sC_2(R_1 + R_2) + 1}$$



$$\Rightarrow Z_{in} = R_1 + \frac{1}{sC_2} \left(\frac{1 + sR_2C_2}{1 + sR_2C_1} \right)$$


b)

$$A_v = \frac{1}{\left(\frac{s}{\omega_n}\right)^2 + \frac{s}{\omega_n} \frac{C_2(R_1 + R_2)}{\sqrt{R_1R_2C_1C_2}} + 1}$$

$$d = \frac{C_2(R_1 + R_2)}{\sqrt{R_1R_2C_1C_2}}$$

P2,4

a)

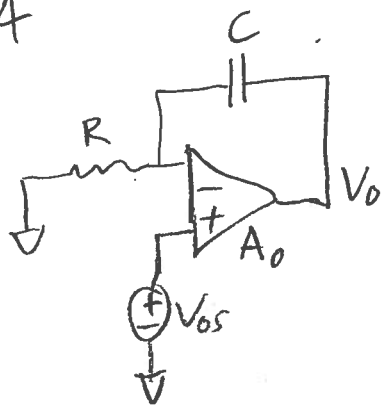

$$V_0 = A_0(V_{os} - V_-) \Rightarrow V_- = V_{os} - \frac{V_0}{A_0}$$

$$\frac{V_0 - V_-}{\frac{1}{sC}} = \frac{V_-}{R} \Rightarrow V_- \left(\frac{1}{R} + sC \right) = sC V_0$$

$$\left(V_{os} - \frac{V_0}{A_0} \right) \left(\frac{1+sRC}{R} \right) = sC V_0$$

$$V_{os} - \frac{V_0}{A_0} = \frac{sRC}{1+sRC} V_0$$

$$V_{os} = V_0 \left(\frac{sRC}{1+sRC} + \frac{1}{A_0} \right) = V_0 \left(\frac{sRCA_0 + 1 + sRC}{A_0(1+sRC)} \right)$$

$$\frac{V_0}{V_{os}} = \frac{A_0(1+sRC)}{1+sRC + sRCA_0} = \frac{A_0(1+sRC)}{1+sRC(1+A_0)}$$

b) at DC, $\frac{V_0}{V_{os}} = \frac{A_0}{1} = A_0$

$\therefore$ s.s. $V_0 = A_0 V_{os}$