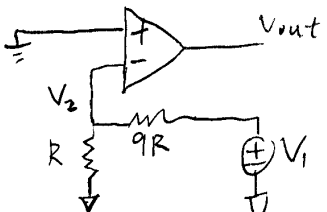


# EECS 311 - fall 08 - HW3 sol'ns

P3.1  $A(s) = \frac{10^6}{1+s}$  for all parts

a)   $B(s) = \frac{V_2}{V_1} = \frac{1}{10}$   
 $\beta(s) = 10$   
 $\frac{V_{out}}{V_{in}} = \frac{A(s)}{1 + A(s)\beta(s)} = \frac{\frac{10^6}{1+s}}{1 + \frac{10^6}{1+s} \cdot 10} = \frac{10^6}{s + (10^5 + 1)}$

b)  $B(s) = \frac{R + \frac{1}{sC}}{10R + \frac{1}{sC}} = \frac{1 + sRC}{1 + 10sRC}$

$\frac{V_{out}}{V_{in}} = \frac{\frac{10^6}{1+s}}{1 + \frac{10^6}{1+s} \cdot \frac{1 + sRC}{1 + 10sRC}} = \frac{10^6}{1+s} \cdot \frac{1 + sRC}{1 + 10sRC}$



c)  $B(s) = \frac{R}{R + (9R // \frac{1}{sC})} = \frac{R}{R + \frac{9R/sC}{9R + 1/sC}} = \frac{1}{1 + \frac{9}{1 + 9sRC}} = \frac{1 + 9sRC}{10 + 9sRC}$

$\frac{V_{out}}{V_{in}} = \frac{\frac{10^6}{1+s}}{1 + \frac{10^6}{1+s} \cdot \frac{1 + 9sRC}{10 + 9sRC}} = \frac{10^6}{1+s} \cdot \frac{1 + 9sRC}{10 + 9sRC}$

d)  $\beta(s) = \frac{R}{sL + \frac{1}{sC} + R} = \frac{sRC}{s^2LC + sRC + 1}$

$\frac{V_{out}}{V_{in}} = \frac{\frac{10^6}{1+s}}{1 + \frac{10^6}{1+s} \cdot \frac{sRC}{s^2LC + sRC + 1}} = \frac{10^6}{1+s} \cdot \frac{sRC}{s^2LC + sRC + 1}$



(over for plots)

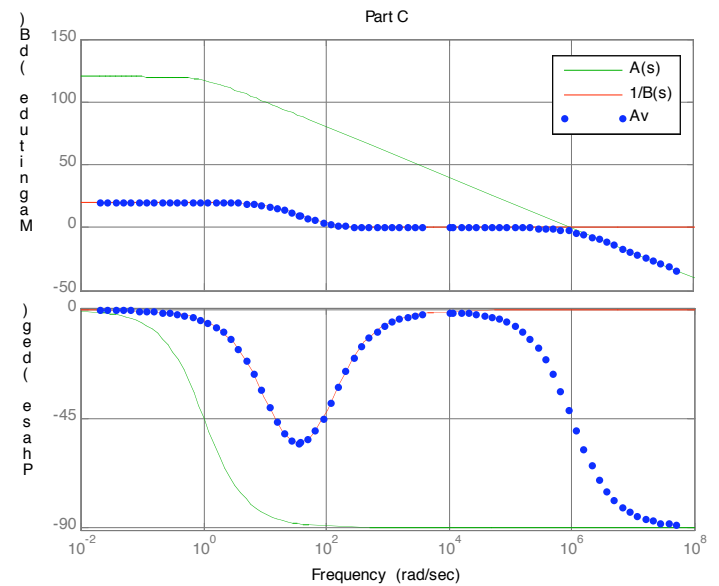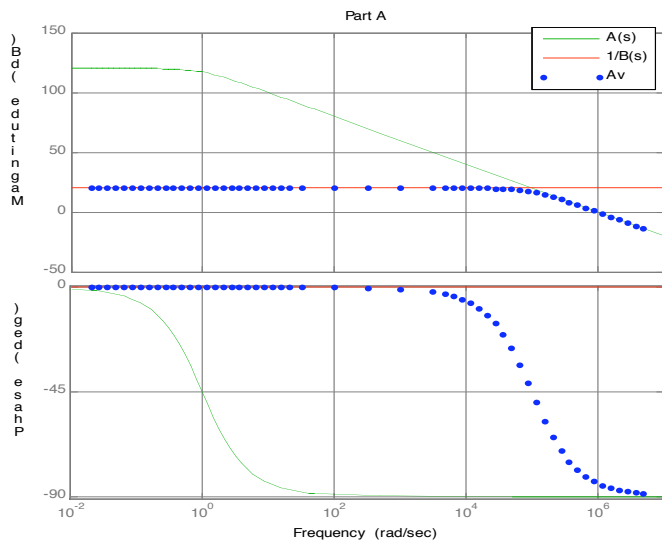

%%% Example Matlab Code for P3.1

```
close all; clear;
s=tf('s');
% Amplifier A(s)
A_s = 1e6/(1+s);
% This is an example Beta B(s),
% substitute for other B(s)
B_s = 0.1*s/s;
% Vout/Vin = A(s)/(1+B(s)*A(s))
vout_vin = A_s/(1+B_s*A_s);
% Plot A(s), 1/B(s), and Vout/Vin
figure;
bode(A_s, 'g:', 1/B_s, 'r-', vout_vin, 'b. ');
title('Part A');
legend('A(s)', '1/B(s)', 'Av');
grid on;
```

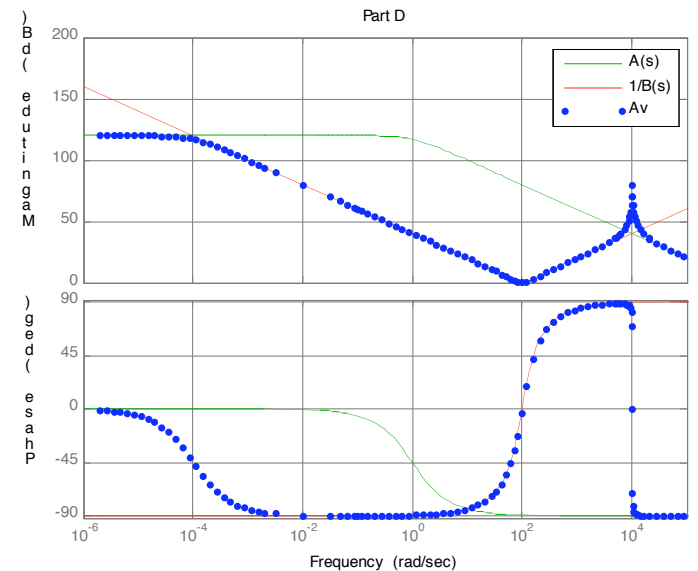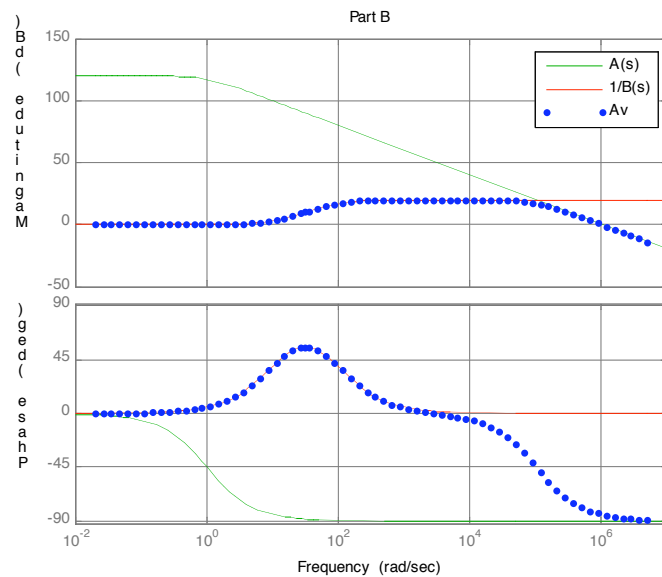$B_s = (1+0.09*s)/(10+0.09*s);$   
(Is the only difference)



$B_s = (1+0.01*s)/(1+0.1*s);$   
(Is the only difference)

$B_s = (0.01*s)/((0.0001*s^2) + (0.01*s) + 1);$   
(Is the only difference)

P3.2  $H(s) = \frac{K |P_1| |P_2|}{(s - P_1)(s - P_2)}$

a)  $P_1 = -100$ ,  $P_2 = -10,000$ ,  $(K=2)$

$$H(s) = \frac{2 \times 10^6}{(s+100)(s+10^4)} = \frac{2 \times 10^6}{s^2 + 10100s + 10^6} = \frac{2}{\left(\frac{s}{1000}\right)^2 + \underbrace{\frac{10100}{1000}}_d \frac{s}{1000} + 1}$$

$\uparrow$   $\omega_n$        $\downarrow$   $d$

$d = 10.1$        $\omega_n = 1000 \frac{\text{rad}}{\text{s}}$

group IV formulas:

$$\gamma_{\min} = \frac{d^2 - 4(1-K)}{4} \approx 26.5 \text{ pick } \gamma = 26.5$$

$$K_{\min} = \frac{4(1+\gamma) - d^2}{4} \approx 2 \text{ satisfied.}$$

assuming we picked  $\gamma$ , use group IV formulas:

$$d = \frac{1}{T_1} + T_1(1 + \gamma - K)$$

$$10.1 = \frac{1}{T_1} + T_1(1 + 26.5 - 2) \Rightarrow T_1 \approx 0.196078 \text{ or } 0.2$$

$\approx 5.1$

group II formulas:

$$d = \frac{(1 + \gamma - K)}{T_2} + T_2 \Rightarrow T_2 = 5.1 \text{ or } 5$$

group I formulas:


$$d = \frac{(1-K)}{T_2} + T_2(1+P) \Rightarrow P = 1.06$$

$$\therefore T_1 = R_1 C_1 \omega_n = 0.2 \Rightarrow R_1 C_1 = 2 \times 10^{-4}$$

$$T_2 = R_2 C_2 \omega_n = 5 \Rightarrow R_2 C_2 = 5 \times 10^{-3}$$

$$\gamma = C_2 / C_1 = 26.5$$

$$P = R_1 / R_2 = 1.06$$

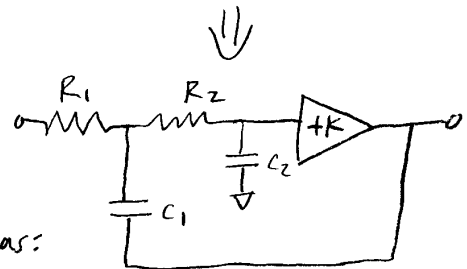

$$T_1, T_2 = 1$$

pick

$T_1 = 0.2$   
 $T_2 = 5$

pick  
 $C_1 = 1 \text{ nF}$

solve  $\Rightarrow$

$$C_2 \approx 26.5 \text{ nF}$$

$$R_1 \approx 200 \text{ k}\Omega$$

$$R_2 \approx 188.6 \text{ k}\Omega$$

3,2  
b)

$$H(s) = \frac{K|P_1||P_2|}{(s-P_1)(s-P_2)}$$

$$P_1 = -\frac{1000}{\sqrt{2}} + j\frac{1000}{\sqrt{2}} \quad P_2 = -\frac{1000}{\sqrt{2}} - j\frac{1000}{\sqrt{2}} \quad K=1$$

$$\Downarrow \quad |P_1| = 1000 = |P_2|$$

$$H(s) = \frac{10^6}{\left[s + \left(\frac{1000}{\sqrt{2}} - j\frac{1000}{\sqrt{2}}\right)\right] \left[s + \left(\frac{1000}{\sqrt{2}} + j\frac{1000}{\sqrt{2}}\right)\right]} = \frac{10^6}{s^2 + 1000\sqrt{2}s + \left(\frac{10^6}{2} + \frac{10^6}{2}\right)}$$

$$= \frac{1}{\left(\frac{s}{1000}\right)^2 + \sqrt{2}\left(\frac{s}{1000}\right) + 1} \Rightarrow \left( \begin{array}{l} \omega_n = 1000 \\ d = \sqrt{2} \end{array} \right) \quad (K=1)$$

group IV formulas:

$$\gamma_{\min} = \frac{d^2 - 4(1-K)}{4} = \frac{1}{2}$$

$$K_{\min} = \frac{4(1+\gamma) - d^2}{4} \leq K=1 \Rightarrow \gamma \leq \frac{1}{2}$$

$\therefore$  we must use  $\gamma = \frac{1}{2}$

$$d = \frac{1}{T_1} + T_1(1+\gamma-K) \Rightarrow T_1 \approx 1.41421356237 = \sqrt{2} = T_1$$

$$T_2 = \frac{1}{T_1} = \frac{1}{\sqrt{2}} = T_2$$

using group III formulas:

$$d = \frac{(1+\rho)}{T_1} + T_1(1-K) \Rightarrow \rho = 1$$

$$\therefore R_1 C_1 = \frac{\sqrt{2}}{1000}$$

$$R_2 C_2 = \frac{1}{1000\sqrt{2}}$$

$$R_1/R_2 = 1$$


$$C_2/C_1 = \frac{1}{2}$$

pick  $C_1 = 1\text{ nF} \Rightarrow$  solve

$\Downarrow$


$$C_1 = 1\text{ nF} \quad C_2 = 0.5\text{ nF}$$

$$R_1 = R_2 = 1.41\text{ M}\Omega$$

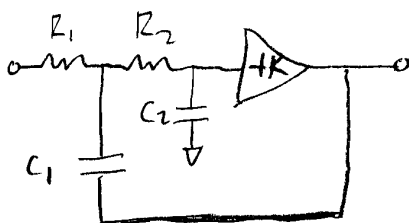

P3.3

3.78)

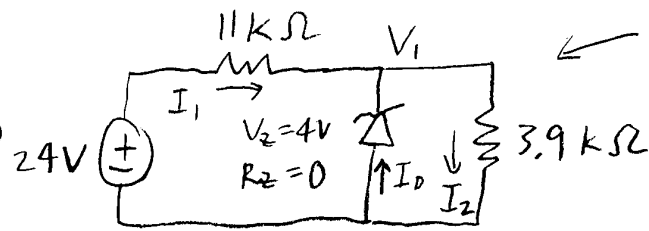

← this is a basic shunt regulator!


$$\text{w/o the zener, } V_1 = \frac{3.9}{14.9} 24 = 6.28 \text{ V} > V_z$$

$$\therefore \text{w/ the zener, } V_1 = 4 \text{ V}$$

$$I_1 = I_z - I_D \Rightarrow \frac{24 - 4}{11 \text{ k}} = \frac{4}{3.9 \text{ k}} - I_D$$

$$I_D \approx -792 \mu\text{A}$$

$$V_D = -4 \text{ V}$$

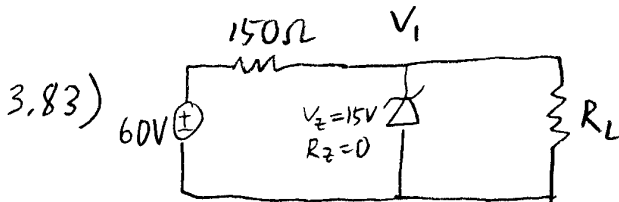

a)  $R_L = 100$

$$\text{w/o zener, } V_1 = \frac{100}{250} 60 = 24 \text{ V} > V_z$$

$$\therefore \text{w/ zener, } V_1 = V_z = 15 \text{ V}$$

$$I_D = \frac{60 - 15}{150} - \frac{15}{100} = 0.15 \text{ A}$$


$$P_{\text{diode}} = V_D I_D = 15 (0.15) = 2.25 \text{ W}$$

b)  $R_L = \infty$  then the diode clamps  $V_1 = 15 \text{ V}$

$$I_D = \frac{60 - V_1}{150} = 0.3 \text{ A}$$


$$P_{\text{diode}} = 15 (0.3) = 4.5 \text{ W}$$

P3.4  
3.91

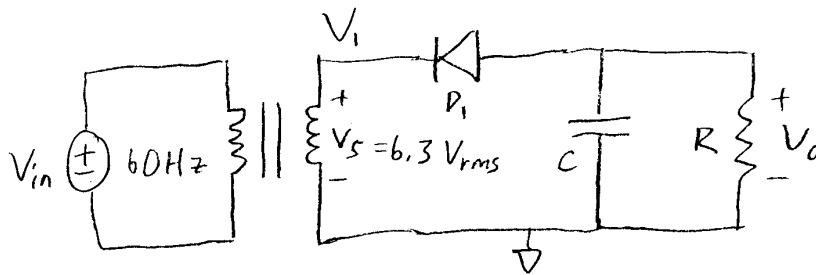

a)

a plot of  $V_1$  would look like:

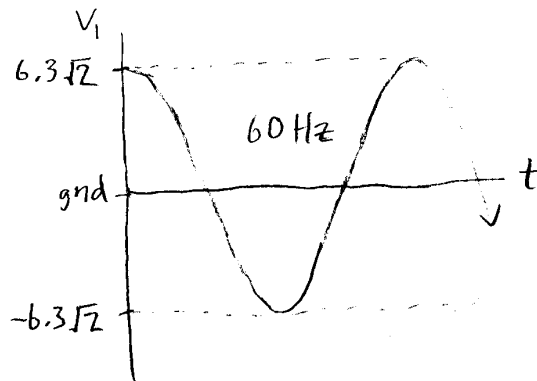

assuming  $C$  is discharged,  $D_1$  is off for  $V_1 > 0$ , and begins to conduct when  $V_1 < -V_{D,on} = -1$  as  $V_1 \downarrow$  to  $-6.3\sqrt{2}$  V,  $V_0$  tracks  $V_1$  through  $D_1$  where  $V_0 = V_1(t) + V_D$   
 $\therefore V_0 \rightarrow -6.3\sqrt{2} + 1$  as  $V_1 \rightarrow -6.3\sqrt{2}$

assuming  $R$  is big and  $V_0$  is restored before  $C$  can lose too much charge every  $\frac{1}{2}$  cycle,

$$V_{0,dc} = -6.3\sqrt{2} + 1 \approx \boxed{-7.91 \text{ V}}$$

b)  $R = 0.5 \Omega$ , find  $C_{min}$  for which  $V_{out,ripple} \leq 0.25 \text{ V}$

$$V_r = (V_p - V_{on}) \left[ 1 - e^{-\frac{T - \Delta T}{RC}} \right]$$

$$\Delta T \approx \frac{1}{\omega} \sqrt{\frac{2T}{RC} \frac{(V_p - V_{on})}{V_p}}$$

$$\approx \frac{6.45314 \times 10^{-4}}{\sqrt{C}}$$

or

$$0.25 = (6.3\sqrt{2} - 1) \left[ 1 - e^{-\frac{\frac{1}{60} - \Delta T}{0.5C}} \right]$$



$$C_{min} \approx \boxed{1.0 \text{ F}} \Rightarrow \Delta T \ll T \checkmark$$

$T - \Delta T \approx 1.602 \times 10^{-2} \ll RC \checkmark$

$V_p = 6.3\sqrt{2}$   
 $V_{on} = 1$   
 $R = 0.2$   
 $T = \frac{1}{f} = \frac{1}{60}$

$\Delta T \text{ also } \approx \frac{1}{\omega} \sqrt{\frac{2V_r}{V_p}}$   
 for  $\Delta T \ll T$   
 &  $RC \gg T - \Delta T$

P3,5  
11.91

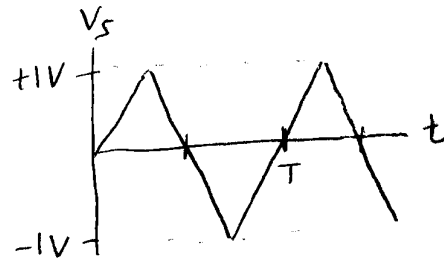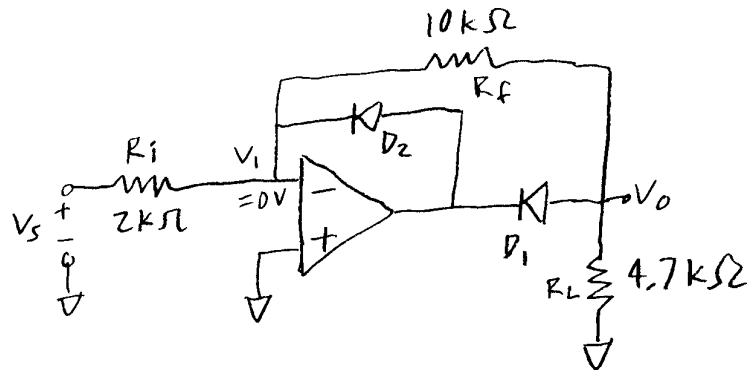

for  $V_s > 0 \Rightarrow D_2$  off &  $D_1$  on  
 $\frac{V_1 - V_s}{R_i} = \frac{V_o - V_1}{R_f} \Rightarrow \frac{V_o}{V_s} = -\frac{R_f}{R_i}$   
 for  $V_s < 0 \Rightarrow D_1$  off &  $D_2$  on  
 $V_o = 0$

