

**University of Michigan**  
**EECS 311: Electronic Circuits**  
**Fall 2008**

PROBLEM SET 5


Issued 10/15/2008  
Due in Lecture 10/22/2008

J&B refers to the course text: "Microelectronic Circuit Design (3rd Edition)," by Richard Jaeger and Travis Blalock.

**P5.0** Fill out the anonymous, midterm evaluation online by following these steps below. This is completely anonymous (even though you've logged in through CTools), and very valuable to me for making changes to the class *while you're still taking it*.

- a) Go to <https://ctools.umich.edu/portal>
- b) Enter your username and password and click on "Login" button.
- c) Click on "Teaching Questionnaires" in the left navigation menu under My Workspace.
- d) Click on a link under "Current evaluations to take".

**P5.1** For the circuit shown in Figure 1, derive expressions for  $I_C$  and  $I_E$  in terms of  $\beta_F$ , and find the value of  $V_{BE}$  given  $I_B = 10\mu A$  and the reverse saturation current of the B-E junction diode is  $I_S = 10^{-17}$ . Ignore base-width modulation.

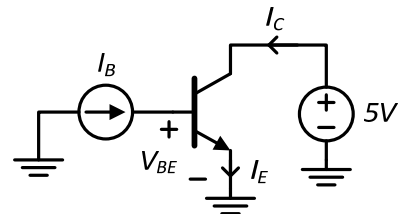


**Figure 1.**

**P5.2** The current gain of a BJT from the emitter to the collector is given by  $I_C/I_E \equiv \alpha_F$  when in the forward-active region, where  $\alpha_F = \beta_F/(1 + \beta_F)$ . Use this to answer the following parts. Ignore base-width modulation.

- a) Derive the above expression for  $\alpha_F$ . Use the circuit shown in Figure 1.
- b) Derive an expression for  $I_B/I_E$  in terms of only  $\alpha_F$ .
- c) We often approximate that  $I_E \approx I_C$ . Given that up to a 5% error is acceptable, we can use the approximation of  $I_E \approx I_C$  by placing the following condition on  $\alpha_F$ :  $\alpha_F > 0.95$ . What is the minimum value of  $\beta_F$  allowed that satisfies this condition? What is the minimum value of  $\beta_F$  if only a 1% error is acceptable?

**P5.3** J&B Problem 5.2. Ignore base-width modulation. You are asked to find  $I_S$  in this problem. In J&B,  $I_S$  is defined for collector current as follows:  $I_C = I_S e^{V_{BE}/V_T}$ . Base current is therefore  $I_B = (I_S/\beta_F) \cdot e^{V_{BE}/V_T}$ .

**P5.4** Find the values of base and collector currents  $I_B$  and  $I_C$  for the circuit shown in Figure 2, given that  $\alpha_F = 0.995$ . Ignore base-width modulation.

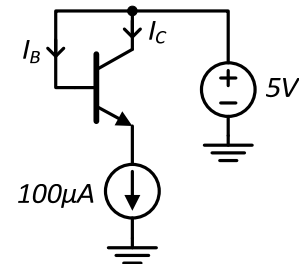

**Figure 2.**

**P5.5** J&B Problem 5.72.

**P5.6** J&B Problem 5.82. In J&B, “Q-point” refers to the quiescent, or DC bias point. Assume  $\beta_R = 1$ . Ignore base-width modulation.

**P5.7** J&B Problem 5.85. In J&B, “Q-point” refers to the quiescent, or DC bias point. Assume  $V_{BE,on} = 0.7V$ . Ignore base-width modulation.

**P5.8** J&B Problem 5.87, part (a) only. Assume  $V_{BE,on} = 0.7V$ . Ignore base-width modulation.