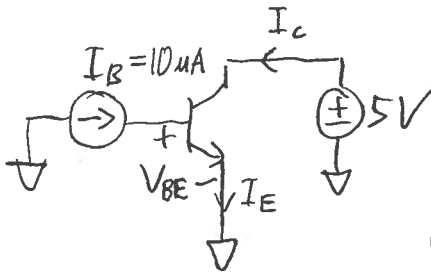


EECS 311 - fall 2008 - HW#5 sol'ns

P5.1



BE $I_s = 10^{-17}$
ignore V_A

$V_{CE} > V_{BE} = V_{BE,on}$ For, Act.

$$I_C = I_B \beta_F \approx I_s e^{V_{BE}/V_T}$$

$$I_E = I_B + I_C = (1 + \beta_F) I_B$$

$$I_B = I_s e^{V_{BE}/V_T}$$

$$\frac{V_{BE}}{V_T} = \ln\left(\frac{I_B}{I_s}\right) \Rightarrow V_{BE} = V_T \ln\left(\frac{I_B}{I_s}\right) \approx 0.718 \text{ V}$$

$\uparrow$
0.026 @ room T

P5.2

$$a) \alpha_F = \frac{I_C}{I_E} = \frac{\beta_F I_B}{(1 + \beta_F) I_B} = \frac{\beta_F}{1 + \beta_F}$$

$$b) \alpha_F = \frac{\beta_F}{1 + \beta_F} \Rightarrow \beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

$$\frac{I_B}{I_E} = \frac{1}{1 + \beta_F} = \frac{1}{1 + \frac{\alpha_F}{1 - \alpha_F}} = 1 - \alpha_F$$

c) 5% tolerance:

$$\alpha_F > 0.95$$

$$\begin{aligned} \beta_F &> \frac{\alpha_F}{1 - \alpha_F} \\ &> \frac{0.95}{1 - 0.95} \\ &> 19 \end{aligned}$$


1% tolerance:

$$\alpha_F > 0.99$$

$$\begin{aligned} \beta_F &> \frac{0.99}{1 - 0.99} \\ &> 99 \end{aligned}$$

P5.3

a)

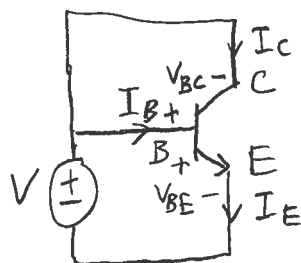

b) $V = 0.640 \text{ V}$ find I_S, β_F, β_R ($\alpha_R = 0.5$)

$$I_C = 275 \mu\text{A}$$

$$I_B = 4 \mu\text{A}$$

$$V_{BE} > 0$$

$$V_{BC} = 0 \text{ (not on)}$$

$$V_{CE} = V_{BE}$$

$$\left. \begin{array}{l} V_{BE} > 0 \\ V_{BC} = 0 \text{ (not on)} \\ V_{CE} = V_{BE} \end{array} \right\} \text{for, act, } I_C = I_S e^{V_{BE}/V_T}$$

$$275 \times 10^{-6} = I_S e^{0.64/0.026}$$

$$I_S \approx 5.61 \times 10^{-15} \text{ A}$$

$$\beta_F = \frac{I_C}{I_B} = 68.75 \text{ A/A}$$

$$\beta_R = \frac{\alpha_R}{1 - \alpha_R} = \frac{0.5}{1 - 0.5} = 1$$

P5.4

$$I_B + I_C = I_E = 10^{-4}$$

$$I_B (1 + \beta_F) = 10^{-4}$$

$$I_B = \frac{1}{10^4 (1 + 199)} = 0.5 \mu\text{A}$$

$$I_C = \beta_F I_B = 99.5 \mu\text{A}$$

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.995}{1 - 0.995} = 199$$

BJT is diode connected

↳ for, act, mode

P5.5 | npn, for. act., $I_B = 3 \mu A$, $V_{CE} = 5V \rightarrow I_C = 240 \mu A$

5.72
J&B)

find β_{FO} & V_A

$V_{CE} = 10V \rightarrow I_C = 265 \mu A$

$$\beta_F = \beta_{FO} \left(1 + \frac{V_{CE}}{V_A}\right) = \frac{I_C}{I_B}$$


$$\textcircled{1} \quad \frac{240}{3} = \beta_{FO} \left(1 + \frac{5}{V_A}\right) \quad \left. \begin{array}{l} \\ \end{array} \right\} \beta_{FO} = \frac{215}{3} \approx \textcircled{71.7 \text{ A/A}}$$

$$\textcircled{2} \quad \frac{265}{3} = \beta_{FO} \left(1 + \frac{10}{V_A}\right) \quad \left. \begin{array}{l} \\ \end{array} \right\} V_A = \textcircled{43 \text{ V}}$$

P5.6 | $\beta_R = 1$, $\beta_F = 50$, $V_{BE} = 0.7V$

5.82
J&B)

a)

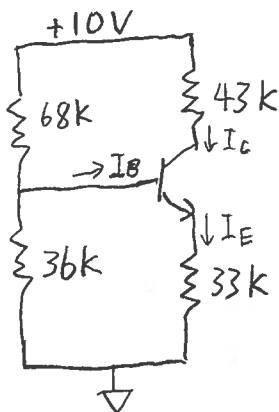

$$\frac{10 - V_B}{68000} - \frac{V_B}{36000} = I_B$$

$$V_E = I_E (33000) = (1 + \beta_F) I_B 33000 = 51(33000) I_B$$

$$V_B - V_E = 0.7$$

$$10 - V_C = 43000 I_C = 43000(50) I_B$$

4 eq. 4 unknown:

$$\textcircled{I_B \approx 1.618 \mu A} \Rightarrow I_C = \beta_F I_B \approx \textcircled{80.9 \mu A}$$

$$\text{for. act. } \left\{ \begin{array}{l} V_B \approx 3.4234 \text{ V} \\ V_E \approx 2.7234 \text{ V} \\ V_C \approx 6.5208 \text{ V} \end{array} \right\} \textcircled{V_{CE} \approx 3.797 \text{ V}}$$

$$\text{b) } \frac{5(10 - V_B)}{68000} - \frac{5V_B}{36000} = I_B$$

$$V_E = 51 \left(\frac{33000}{5} \right) I_B$$

$$V_B - V_E = 0.7$$

$$10 - V_C = \frac{43000}{5} (50) I_B$$

$$\textcircled{I_B \approx 8.091 \mu A} \Rightarrow I_C \approx 404.6 \mu A$$

$$V_B \approx 3.4234 \text{ V}$$

$$V_E \approx 2.7234 \text{ V}$$

$$V_C \approx 6.5208 \text{ V}$$

for. act. mode ✓

$$\textcircled{V_{CE} \approx 3.797 \text{ V}}$$

(over)

c) $V_{EB} = 0.7$

$$\frac{10 - V_B}{36000} - \frac{V_B}{68000} = -I_B$$

$$10 - V_E = 33000(51) I_B$$

$$V_C = 43000(50) I_B$$

$$I_B \approx 1.618 \mu A \Rightarrow I_C \approx 80.9 \mu A$$

$$V_B \approx 6.5766 V$$

$$V_E \approx 7.2766 V$$

$$V_C \approx 3.4792 V$$

for. act. mode ✓

$$V_{EC} \approx 3.797 V$$

d) $V_{EB} = 0.7$

$$\frac{5(10 - V_B)}{36000} - \frac{5V_B}{68000} = -I_B$$

$$10 - V_E = \frac{33000}{5}(51) I_B$$

$$V_C = \frac{43000}{5}(50) I_B$$

$$I_B \approx 8.091 \mu A \Rightarrow I_C \approx 404.6 \mu A$$

$$V_B \approx 6.5766 V$$

$$V_E \approx 7.2766 V$$


$$V_C \approx 3.4792 V$$

for. act. mode

$$V_{EC} \approx 3.797 V$$

P5.7

5.85)
J & B)

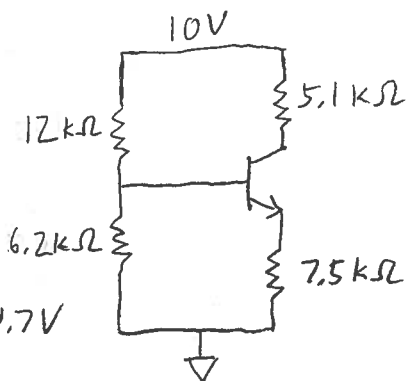

$$V_{BE,on} = 0.7V$$

$$\beta_F = 100$$

same approach as before...

$$I_B \approx 3.554 \mu A \Rightarrow I_C \approx 355.4 \mu A$$

$$V_B \approx 3.392 V$$

$$V_E \approx 2.692 V$$


$$V_C \approx 8.188 V$$

for. act. mode ✓

$$V_{CE} \approx 5.496 V$$

P5.8

5.87)
J & B)

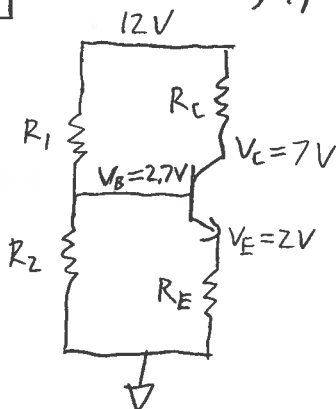

4-res design, npn, $I_C = 1mA$, $V_{CE} = 5V$, $V_E = 2V \rightarrow V_{CC} = 12V$

$$R_C = \frac{12 - 7}{10^{-3}} \approx 5k\Omega$$

$$R_E = \frac{2}{I_B + I_C} = \frac{2}{10^{-3}(1 + \frac{1}{100})} \approx 1.980k\Omega$$

$$I_B = \frac{I_C}{\beta_F} = 10\mu A = \frac{12 - 2.7}{R_1} - \frac{2.7}{R_2} \Rightarrow R_1 = \frac{9.3 \times 10^5 R_2}{R_2 + 2.7 \times 10^5}$$

pick $R_2 = 50k\Omega$

$$R_1 \approx 145.3k\Omega$$

these values ensure I_B doesn't suck all the current from the V_B bias network