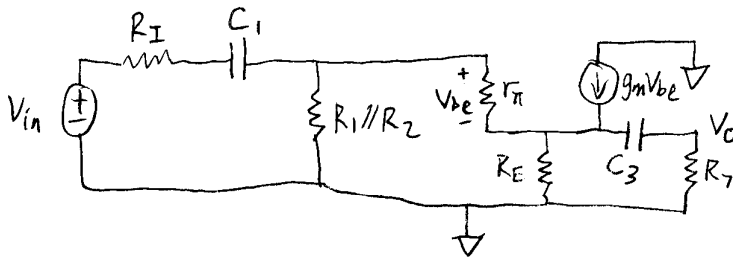


EECS 311 - HW#7 solutions (fall 2008)

1) a) low freq:



$$C_1 = 4.7 \mu\text{F}$$

$$C_3 = 10 \mu\text{F}$$

$$R_1 = 100 \text{ k}\Omega$$


$$R_2 = 300 \text{ k}\Omega$$

$$R_E = 13 \text{ k}\Omega$$

$$R_I = 2 \text{ k}\Omega$$

$$R_7 = 100 \text{ k}\Omega$$

midband:

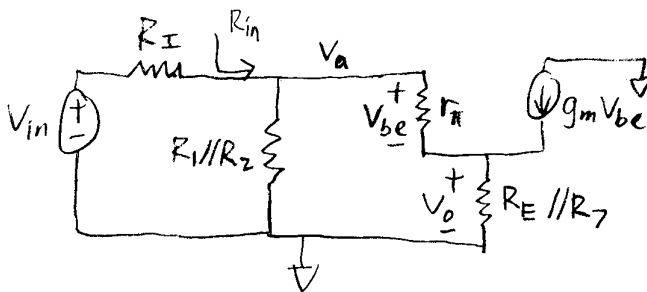

$$g_m = \frac{I_C}{V_T}$$

$$\beta_o = g_m r_{\pi} = 100$$

ignore r_o
 V_A not given } $r_o \approx \frac{V_A}{I_C}$

$$I_C = 0.25 \text{ mA}$$

$$V_{CC} = 12 \text{ V}$$

b) SCTC:

$$C_1: R_{1,eq} = R_I + \overbrace{[R_1 // R_2 // (r_{\pi} + (1 + g_m r_{\pi}) R_E)]}^{R_{in}}$$

$$C_3: R_{3,eq} \approx R_7 + (R_E // \frac{1}{g_m})$$

$$f_L = \left(\frac{1}{R_{1,eq} C_1} + \frac{1}{R_{3,eq} C_3} \right) \frac{1}{2\pi} \approx \boxed{0.623 \text{ Hz}}$$

MATLAB

attached

$$A_v = \frac{R_{in}}{R_I + R_{in}} \frac{(1 + \beta_o)(R_E // R_7)}{r_{\pi} + (1 + \beta_o)(R_E // R_7)} \approx \boxed{0.964 \text{ V/V}}$$

$$V_a = V_{be} + V_o$$


$$= i_b r_{\pi} + (1 + \beta_o) i_b (R_E // R_7) \Rightarrow i_b = \frac{V_a}{r_{\pi} + (1 + \beta_o)(R_E // R_7)}$$

$$V_a \left(1 - \frac{r_{\pi}}{r_{\pi} + (1 + \beta_o)(R_E // R_7)} \right) = V_o$$

$$2) \omega_L = \frac{1}{R_{1eq} C_1} + \frac{1}{R_{3eq} C_3} = 2\pi f_L = 20\pi$$

$$C_3 = \frac{\left(20\pi - \frac{1}{R_{1eq} C_1}\right)^{-1}}{R_{3eq}} \approx \boxed{0.167 \mu F}$$

MATLAB attached

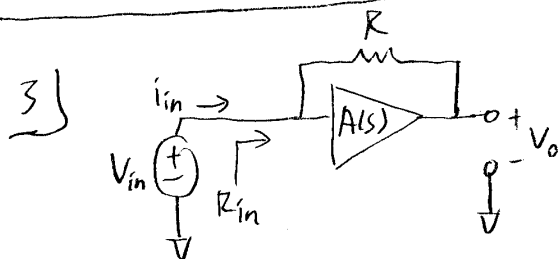


$$R_{in} = \frac{V_{in}}{i_{in}} = \frac{R}{1-A(s)}$$

$$i_{in} = \frac{V_{in} - V_{out}}{R} = \frac{V_{in}(1-A(s))}{R}$$

4) midband: ignore r_o

(DC bias in MATLAB attached)

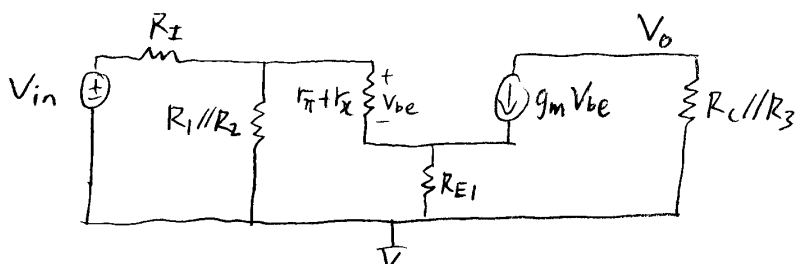

$$R_I = 250$$

$$R_1 = 10K$$

$$R_2 = 30K$$

$$r_x = 350$$

$$R_{E1} = 200$$

$$R_C = 4.3K$$

$$R_3 = 47K$$

$$C_1 = 5\mu$$

$$C_2 = 1\mu$$

$$C_3 = 4.7\mu$$

$$\beta_0 = 100$$

$$f_T = 200MHz$$

$$C_u = 1pF$$

$$a) A_{mid} \approx \frac{R_1 // R_2 // (r_{\pi} + r_x + (1 + \beta_0) R_{E1})}{R_I + R_1 // R_2 // (r_{\pi} + r_x + (1 + \beta_0) R_{E1})} \left[- \frac{g_m (R_C // R_3)}{1 + g_m R_{E1}} \right] \approx \boxed{-17.6 \%}$$

$$b) R_{1,eq} = R_I + [R_1 // R_2 // (r_{\pi} + r_x + (1 + \beta_0) R_{E1})]$$

MATLAB attached

$$R_{2,eq} = R_3 + [R_C]$$

$$R_{3,eq} = R_{E1} + \frac{1}{g_m}$$

$$f_L = \frac{1}{2\pi} \left(\frac{1}{R_{1,eq} C_1} + \frac{1}{R_{2,eq} C_2} + \frac{1}{R_{3,eq} C_3} \right) \approx \boxed{166 Hz}$$

$$4] c) f_T = \frac{g_m}{C_\pi + C_\mu} \Rightarrow C_\pi = \frac{g_m}{f_T} - C_\mu$$

$$R_{\pi,eq} = \left[\frac{1}{r_\pi} + \frac{1+g_m R_{E1}}{R_S + R_{E1}} \right]^{-1}$$


$$R' = R_I // R_1 // R_2 // (r_\pi + r_x + (1+\beta_o)R_{E1})$$

$$R'' = R_C // R_3$$

$$G_m = \frac{g_m}{1+g_m R_{E1}}$$

$$R_{u,eq} = R' + R''(1+G_m R')$$
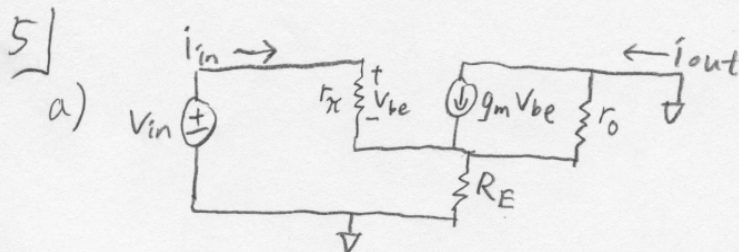
$$f_H = \frac{1}{2\pi} \left(\frac{1}{R_{\pi,eq} C_\pi + R_{u,eq} C_\mu} \right) \approx \boxed{8.55 \text{ MHz}}$$



$$\text{KCL: } i_{in} + g_m V_{be} = \frac{V_{in} - V_{be}}{R_E // r_o} \quad V_{be} = i_{in} r_\pi$$


$$i_{in} \left(1 + g_m r_\pi + \frac{r_\pi}{R_E // r_o} \right) = \frac{V_{in}}{R_E // r_o}$$

$$R_{in} = \frac{V_{in}}{i_{in}} = \boxed{r_\pi + \underbrace{(1+g_m r_\pi)}_{\beta_o} (R_E // r_o)}$$

$$\begin{aligned} i_{out} &= g_m V_{be} - \frac{(V_{in} - V_{be})}{r_o} \\ V_{be} &= i_{in} r_\pi = \frac{r_\pi V_{in}}{r_\pi + (1+\beta_o)(R_E // r_o)} = \frac{r_\pi V_{in}}{R_{in}} \\ i_{out} &= V_{in} \left(\frac{\beta_o}{R_{in}} - \frac{1}{r_o} + \frac{r_\pi}{R_{in} r_o} \right) \end{aligned}$$

$$G_m = \frac{i_{out}}{V_{in}} = \frac{\beta_o r_o - R_{in} + r_\pi}{r_o R_{in}} = \boxed{\frac{\beta_o r_o - (1+\beta_o)(R_E // r_o)}{r_o (r_\pi + (1+\beta_o)(R_E // r_o))}} \approx \frac{g_m}{1+g_m R_E}$$

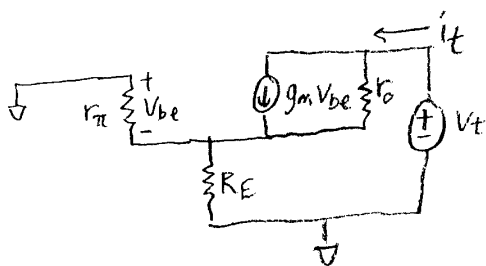↑
assumes $r_\pi \gg R_E$
 $r_o \gg r_\pi$
 $\beta_o \gg 1$



$$i_t = \frac{-V_{be}}{r_{\pi} \parallel R_E} = g_m V_{be} + \frac{V_t + V_{be}}{r_o}$$

$$\Downarrow \quad V_{be} = -i_t (r_{\pi} \parallel R_E) \Rightarrow i_t = -g_m (r_{\pi} \parallel R_E) i_t + \frac{V_t - i_t (r_{\pi} \parallel R_E)}{r_o}$$

$$i_t \left(1 + g_m (r_{\pi} \parallel R_E) + \frac{r_{\pi} \parallel R_E}{r_o} \right) = \frac{V_t}{r_o}$$

$$R_{out} = \frac{V_t}{i_t} = \boxed{r_o [1 + g_m (r_{\pi} \parallel R_E)] + (r_{\pi} \parallel R_E)} \approx r_o (1 + g_m R_E)$$

assumes
 $r_o \gg r_{\pi} \gg R_E$

$$\begin{aligned} b) R_{in} &= r_{\pi} + (1 + g_m r_{\pi}) (R_E \parallel r_o) \\ &\approx r_{\pi} + (1 + g_m r_{\pi}) R_E \quad (r_o \gg R_E) \\ &\approx r_{\pi} + g_m r_{\pi} R_E \quad (\beta_o = g_m r_{\pi} \gg 1) \\ &\approx r_{\pi} (1 + g_m R_E) \end{aligned}$$

$$\begin{aligned} G_m &= \frac{\beta_o r_o - (1 + \beta_o) (R_E \parallel r_o)}{r_o (r_{\pi} + (1 + \beta_o) (R_E \parallel r_o))} \\ &\approx \frac{\beta_o r_o - \beta_o R_E}{r_o (r_{\pi} + \beta_o R_E)} \quad (r_o \gg R_E, \beta_o \gg 1) \\ &\approx \frac{\beta_o (r_o - R_E)}{r_o (r_{\pi} + \beta_o R_E)} \approx \frac{\beta_o r_o}{r_o (r_{\pi} + \beta_o R_E)} \quad (r_o \gg R_E) \\ &\approx \frac{g_m r_{\pi}}{r_{\pi} + g_m r_{\pi} R_E} \approx \frac{g_m}{1 + g_m R_E} \end{aligned}$$


conditions used: $r_o \gg R_E$ & $\beta_o = g_m r_{\pi} \gg 1$

$$\begin{aligned}
 c) R_{out} &= r_o [1 + g_m (r_\pi \parallel R_E)] + (r_\pi \parallel R_E) \\
 &\approx r_o [1 + g_m R_E] + R_E \quad (r_\pi \gg R_E) \star \\
 &\approx r_o (1 + g_m R_E) \quad (r_o \gg R_E)
 \end{aligned}$$

6) a) $A_v = \frac{V_A}{V_{in}} \cdot \frac{V_{out}}{V_A} = \frac{R_{in}}{R_B + R_{in}} \cdot (-g_m R_{out})$ r_o ignored for all of #6

$$\approx \frac{-r_\pi (1 + g_m R_E)}{R_B + r_\pi (1 + g_m R_E)} \cdot \frac{g_m R_C}{1 + g_m R_E} = \boxed{-g_m R_C \frac{r_\pi}{R_B + r_\pi}} \quad R_E = 0$$


↑ use this

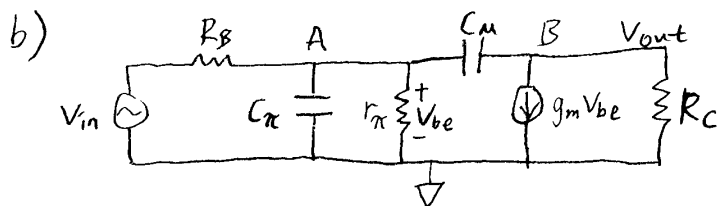

$$\begin{aligned}
 C_A &= C_\pi + C_\mu (1 - A_v) \\
 C_B &= C_\mu (1 - A_v^{-1})
 \end{aligned}
 \left. \vphantom{\begin{aligned} C_A &= C_\pi + C_\mu (1 - A_v) \\ C_B &= C_\mu (1 - A_v^{-1}) \end{aligned}} \right\} A_v \text{ from part a}$$

$$\begin{aligned}
 c) R_{A,eq} &= R_B \parallel r_\pi \\
 R_{B,eq} &= R_C \\
 f_H &= \frac{1}{2\pi} \left(\frac{1}{R_{A,eq} C_A + R_{B,eq} C_B} \right)
 \end{aligned}$$
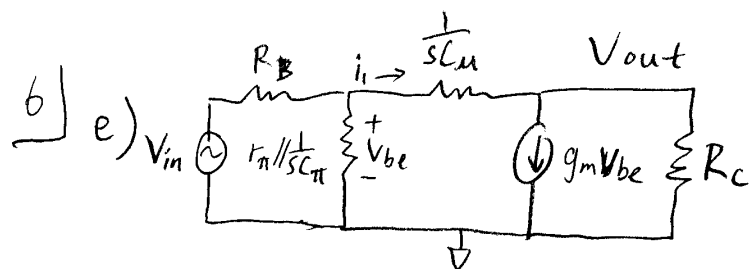
$$\begin{aligned}
 d) A_v &\approx -1,389 \text{ V/V} \\
 f_H &\approx 75,0 \text{ kHz} \\
 &(\text{plot \& code attached})
 \end{aligned}$$



$$\begin{aligned}
 \text{KCL} \quad i_1 &= g_m V_{be} + \frac{V_{out}}{R_C} \\
 \text{KCL} \quad \frac{V_{in} - V_{be}}{R_B} &= i_1 + \frac{V_{be}}{r_{\pi} // \frac{1}{sC_{\pi}}}
 \end{aligned}
 \left. \vphantom{\begin{aligned} \text{KCL} \quad i_1 &= g_m V_{be} + \frac{V_{out}}{R_C} \\ \text{KCL} \quad \frac{V_{in} - V_{be}}{R_B} &= i_1 + \frac{V_{be}}{r_{\pi} // \frac{1}{sC_{\pi}}} \end{aligned}} \right\} \begin{aligned} \frac{V_{in}}{R_B} &= g_m V_{be} + \frac{V_{out}}{R_C} + \frac{V_{be}}{r_{\pi} // \frac{1}{sC_{\pi}}} + \frac{V_{be}}{R_B} \\ &= V_{be} \left(g_m + \frac{1}{r_{\pi} // \frac{1}{sC_{\pi}}} + \frac{1}{R_B} \right) + \frac{V_{out}}{R_C} \end{aligned} \quad (1)$$

$$\Omega\text{'s Law} \quad V_{be} - \frac{i_1}{sC_u} = V_{out}$$

$$V_{be} = V_{out} + \frac{g_m}{sC_u} V_{be} + \frac{V_{out}}{sR_C C_u}$$

$$V_{be} \left(1 - \frac{g_m}{sC_u} \right) = V_{out} \left(1 + \frac{1}{sR_C C_u} \right)$$

$$\parallel$$

$$\frac{sC_u - g_m}{sC_u}$$

$$V_{be} = V_{out} \left(\frac{sR_C C_u + 1}{sR_C C_u} \right) \frac{sC_u}{sC_u - g_m}$$

$$= V_{out} \frac{(sR_C C_u + 1)}{R_C (sC_u - g_m)} \quad (2)$$

plug (2) into (1):

$$\frac{V_{in}}{R_B} = V_{out} \left[\frac{sR_C C_u + 1}{R_C (sC_u - g_m)} \left(g_m + \frac{1}{r_{\pi} // \frac{1}{sC_{\pi}}} + \frac{1}{R_B} \right) + \frac{1}{R_C} \right]$$

$$\frac{V_{out}}{V_{in}} = \left\{ R_B \left[\right] \right\}^{-1}$$

f) plots attached, the gain matches up to $\sim 10 \text{ kHz}$,
 " phase " " " $\sim 1 \text{ kHz}$

```

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #1
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

R1 = 100e3;
R2 = 300e3;
Ri = 2e3;
Re = 13e3;
R7 = 100e3;
Bf = 100; % current gain, A/A
Af = Bf/(Bf+1);
Vt = 0.026; % thermal voltage @ room temp.
Ic = 0.25e-3;

gm = Ic/Vt;
rpi = Bf/gm;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Midband gain
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Rin = (1/R1 + 1/R2 + 1/(rpi+(1+Bf)*Re))^-1;
RL = (1/Re + 1/R7)^-1;
Gain = (Rin/(Ri+Rin))*((1+Bf)*RL/(rpi+(1+Bf)*RL))

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% SCTC - fL
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C1 = 4.7e-6;
C3 = 10e-6;
Re_eq1 = Ri+Rin;
Re_eq3 = R7 + (1/Re + gm)^-1;

FL = (1/(Re_eq1*C1) + 1/(Re_eq3*C3))/(2*pi) %Hz

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #2
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C3 = ((20*pi - (1/(Re_eq1*C1)))^-1)/Re_eq3

clc;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #4
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Vcc = 12;
R1 = 10e3;
R2 = 30e3;
Ri = 250;
rx = 350;
Re1 = 200;
Re2 = 1100;
Rc = 4.3e3;
R3 = 47e3;
Vbeon = 0.7;

```

```

Bf = 100; % current gain, A/A
Af = Bf/(Bf+1);
Vt = 0.026; % thermal voltage @ room temp.

% DC bias

Vb = R1*Vcc/(R1+R2)
Ve = Vb-Vbeon
Ie = Ve/(Re1+Re2);
Ic = Af*Ie
Vc = Vcc - (Ic*Rc) % check for FAR mode

gm = Ic/Vt;
rpi = Bf/gm;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Midband gain
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Rin = (1/R1 + 1/R2 + 1/(rpi+rx+(1+Bf)*Re1))^-1;
Rout = (1/Rc + 1/R3)^-1;
Gain = -(gm/(1+gm*Re1))*(Rout) * (Rin/(Ri+Rin))

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% SCTC - fL
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C1 = 5e-6;
C2 = 1e-6;
C3 = 4.7e-6;
Re_eq1 = Ri+Rin;
Re_eq2 = R3+Rc;
Re_eq3 = Re1 + (1/gm);

FL = (1/(Re_eq1*C1) + 1/(Re_eq2*C2) + 1/(Re_eq3*C3))/(2*pi) %Hz

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% OCTC - fH
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Cu = 1e-12;
ft = 200e6;
Cpi = (gm/ft) - Cu

GS=1/Ri+1/R1+1/R2;
Rs=1/GS;
Rpi_eq = 1/(1/rpi+(1+gm*Re1)/(Rs+Re1))

Rin = 1/(1/Ri + 1/R1 + 1/R2 + 1/(rpi+rx+(1+Bf)*Re1));
Rout = 1/(1/Rc + 1/R3);
GM = gm/(1+gm*Re1);
Ru_eq = Rin + Rout*(1+GM*Rin);

FH = 1/(2*pi*(Rpi_eq*Cpi + Ru_eq*Cv))


```



```

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #6
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

```

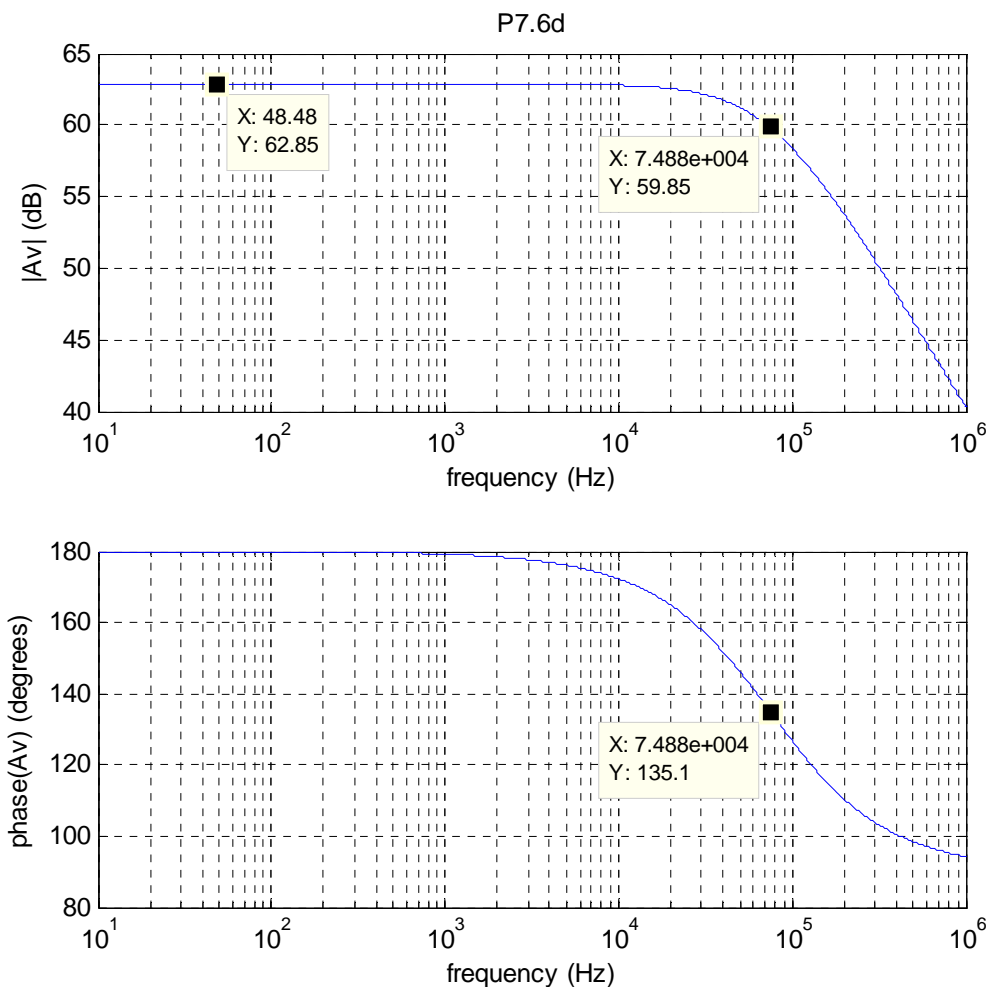

```

Rb = 1e3;
Rc = 50e3;
Bf = 100;
Cu = 2e-12;
Cje = 0; %no depletion cap, just consider diffusion cap for B-E junction
Ic = 1e-3;
Tf = 500e-12;
Vt = 0.026;

gm = Ic/Vt;
rpi = Bf/gm;
Cpi = gm*Tf;

Av = -gm*Rc*(rpi/(Rb+rpi));
CA = Cpi + Cu*(1-Av);
CB = Cu*(1-(1/Av));
RAeq = (1/Rb + 1/rpi)^-1;
RBeq = Rc;

fH = (1/(RAeq*CA + RBeq*CB))/(2*pi)

f = logspace(1,6,10000);

```

```



Gain = Av./(1+(j*f./fH));
subplot(2,1,1);
semilogx(f,20*log10(abs(Gain)));
grid on
xlabel('frequency (Hz)');
ylabel('|Av| (dB)');
title('P7.6d');
subplot(2,1,2);
semilogx(f,angle(Gain)*180/pi);
grid on
xlabel('frequency (Hz)');
ylabel('phase(Av) (degrees)');

```

```

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #6e
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

```

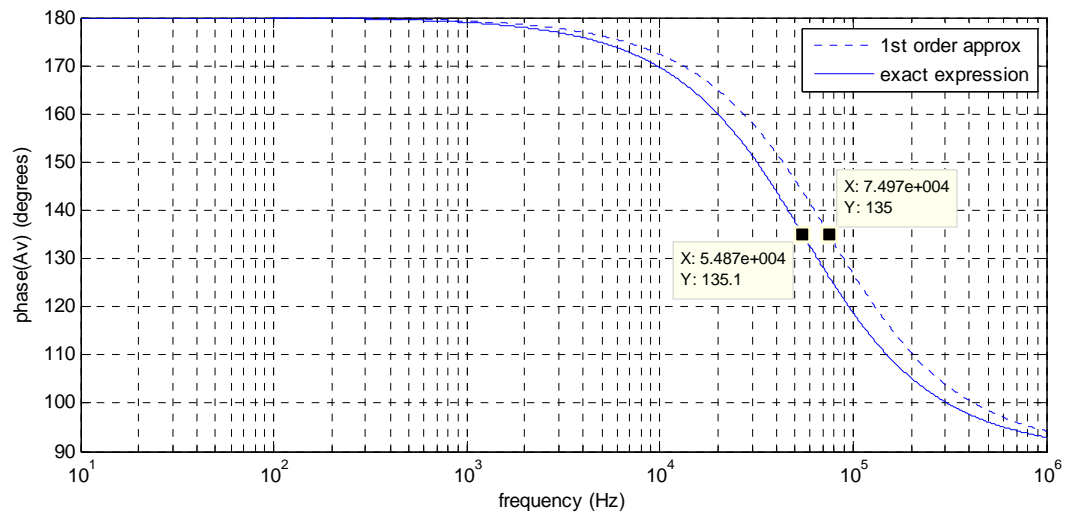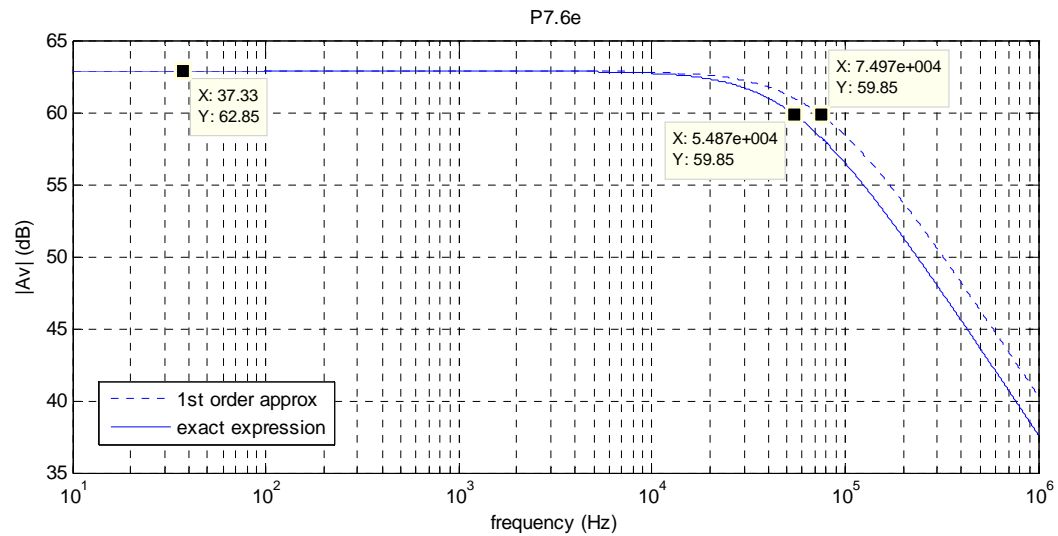

```

Gain_e = 1./ (Rb.*(((1+j*2*pi.*f.*Rc*Cu)./(Rc.*(j*2*pi.*f.*Cu-
gm))).*(gm+((1/rpi)+j*2*pi.*f.*Cpi)+(1/Rb)))+(1/Rc)));
subplot(2,1,1);
semilogx(f,20*log10(abs(Gain)),':');
hold on
semilogx(f,20*log10(abs(Gain_e)));
hold off
grid on
xlabel('frequency (Hz)');
ylabel('|Av| (dB)');
title('P7.6e');
legend('1st order approx','exact expression');
subplot(2,1,2);
semilogx(f,angle(Gain)*180/pi,':');
hold on
semilogx(f,angle(Gain_e)*180/pi);
hold off
grid on
xlabel('frequency (Hz)');
ylabel('phase(Av) (degrees)');
legend('1st order approx','exact expression');

```