
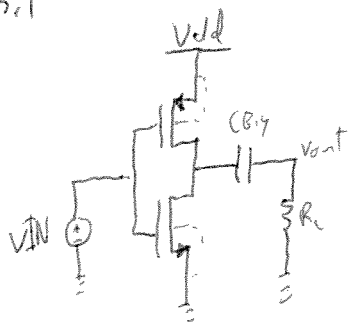


R3.1

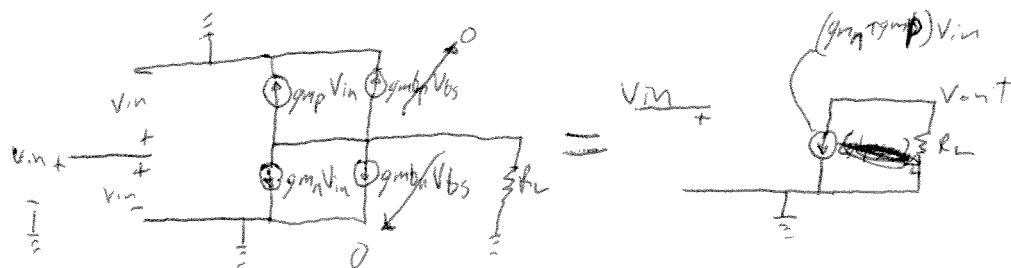

Small signal model




$$G_m = g_{m_n} + g_{m_p}$$

$$A_v = -(g_{m_n} + g_{m_p}) R_L$$

$$R_{in} = \infty \quad R_{out} = R_L$$

R3.2

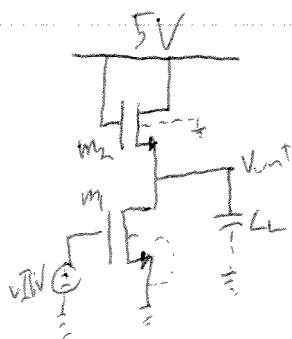

Looking into the source of $m_2 \rightarrow R = \frac{1}{g_{m_2} + g_{mb_2}} = R_{out}$

$$R_{in} = \infty \quad G_m = g_{m_1} \quad A_v = -\frac{g_{m_1}}{g_{m_2} + g_{mb_2}} = \frac{-g_{m_1}}{g_{m_2}(1+\eta)} \approx \frac{-\sqrt{w_1/L_1}}{\sqrt{w_2/L_2}(1+\eta)}$$

~~scribble~~

$$V_{IN} = v_{int} + V_{gs1} \quad I_{D1} = I_{D2} = \frac{1}{2} K_n' \frac{w_1}{L_1} (V_{gs1} - V_{tn})^2 = 8 \mu A$$

$$V_{s2} = V_{dd} - \left(\sqrt{\frac{I_{D2} \cdot 2}{K_n' w_2/L_2}} + V_{tn} \right) = 2V$$

$$V_{gs2} = V_{dd} - V_{s2} = 3V$$

$$V_{ds1} = V_{s2} \quad V_{ds2} = V_{dd} - V_{s2} = 3V$$

$$V_{ds1} > V_{gs1} - V_{tn} \quad \checkmark$$

$$V_{ds2} > V_{gs2} - V_{tn} \quad \checkmark$$

$$g_{m1} = \frac{2I_{D1}}{(V_{gs1} - V_{tn})} = 16 \mu A/V$$

$$g_{m2} = \frac{2I_{D2}}{(V_{gs2} - V_{tn})} = 8 \mu A/V$$


$$G_m = 16 \mu A/V$$

$$R_{out} = 113.64 \text{ k}\Omega$$

$$R_{in} = \infty$$

$$A_v = -1.8152$$

R3.3

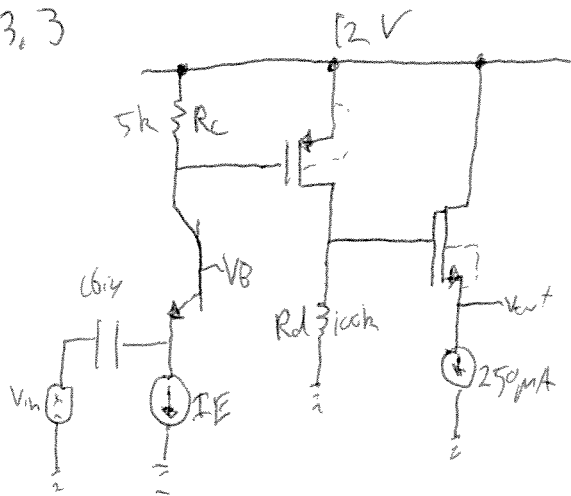

a) stage 1 = C-B
 stage 2 = C-S
 stage 3 = C-D

b) $R_{in} = 50 \text{ ohms} = \frac{1}{g_{m1}}$

$$g_{m1} = \frac{1}{50} = \frac{I_C}{V_T} \quad I_C \approx I_E$$

$$I_E = \frac{V_T}{50} = 500 \mu A$$

c) stage 1
 $V_B = \text{arbitrary}$ $r_{pi} = \frac{\beta}{g_{m1}} = 7.55 \text{ k}\Omega$

$$V_C = V_{DD} - I_C R_C \approx 9.51 \text{ kV}$$

stage 2

$$V_{g2} = V_C$$

$$V_{gs2} = V_{g2} - V_{DD} = -2.4834 \text{ V}$$

$$I_{d2} = \frac{1}{2} K_p (V_{gs2} - V_{tp})^2 = 44.01 \mu A$$

$$V_{d2} \approx I_{d2} R_d = 4.4 \text{ V}$$

$$V_{ds2} = V_{d2} - V_{DD} = -7.5988 \text{ V}$$

$$|V_{ds2}| > |V_{gs2} - V_{tp}| \checkmark$$

$$g_{m2} = \frac{2I_{d2}}{|V_{gs2} - V_{tp}|} = 59.3 \mu S$$

stage 3

$$V_{g3} \approx V_{d2}$$

$$V_{gs3} = \sqrt{\frac{2(250 \mu A)}{K_n}} + V_{tn} = 3.887 \text{ V}$$


$$V_{s3} = V_{g3} - V_{gs3} \approx 0.5145 \text{ V}$$

$$V_{ds3} = V_{DD} - V_{s3} = 11.4855 \text{ V}$$

$$V_{ds3} > V_{gs3} - V_{tn} \checkmark$$

$$g_{m3} = \frac{2I_{d3}}{V_{gs3} - V_{tn}} = 173.2 \mu S$$

d)

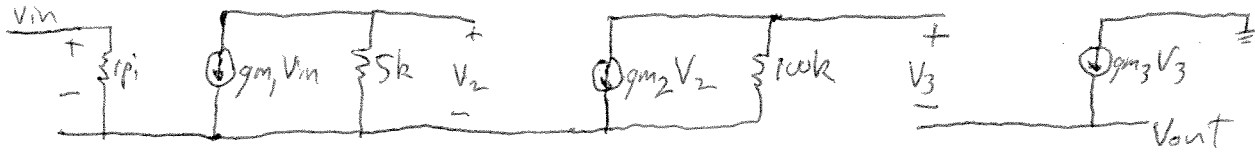


e) $R_{in} = 50 \text{ ohms}$

$$R_{out} = \frac{1}{g_{m3}} = 5.774 \text{ k}\Omega$$

$$A_v = (C-B)(C-D)(C-E) \approx (g_{m1} R_c)(-g_{m2} R_d)(1) = -589.45$$

R3.4

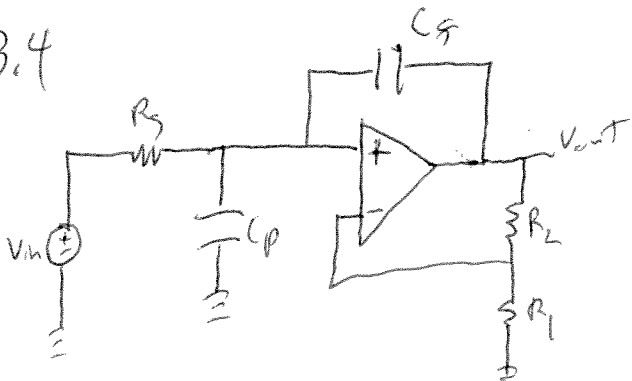

Non-inverting op-amp


$$A_v = 1 + \frac{R_2}{R_1}$$

$$C_{in} = C_p + C_f(1 - A_v) = 0$$

$$C_{in} = C_p + C_f(-R_2/R_1) = 0$$

$$C_p = C_f \frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = \frac{C_p}{C_f}$$

R3.5

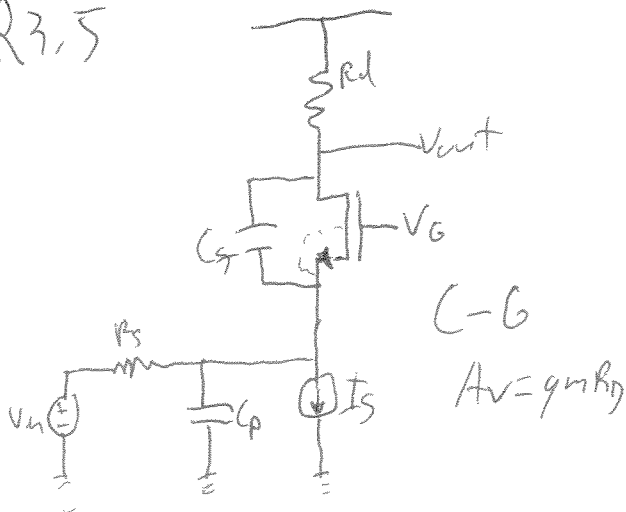


$$C_p = -C_f(1 - g_m R_D)$$

~~$$\frac{C_p + C_f}{C_f} = g_m R_D$$~~


trick question

$I_{in} \neq 0$, Miller multiplication can't be used

R3.6

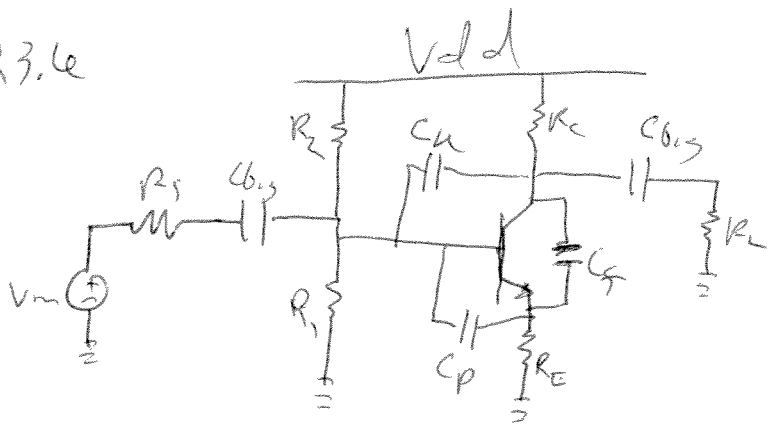

Small signal

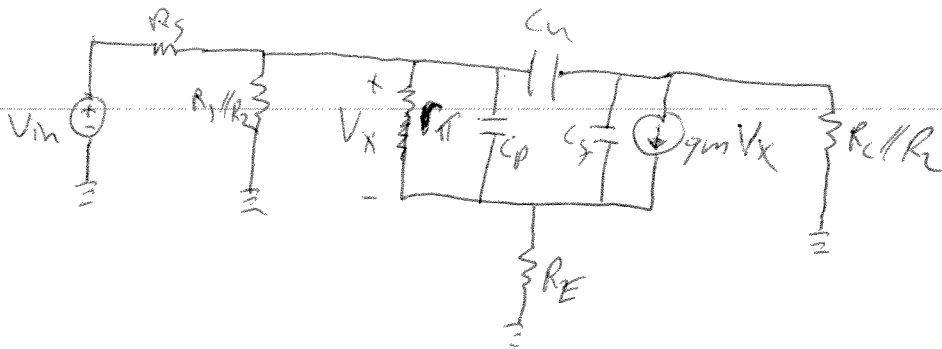

$$R_{uo} = R_1 // R_2 // R_5 // (r_{\pi} (1 + g_m R_E)) + R_C // R_L + \left(\frac{g_m}{1 + g_m R_E} \right) (R_C // R_L) (R_1 // R_2 // R_5 // (r_{\pi} (1 + g_m R_E)))$$

$$R_{po} = r_{\pi} // \left[\frac{R_1 // R_2 // R_5 + R_E}{1 + g_m R_E} \right]$$

$$R_{so} = \frac{R_C // R_L (R_E + r_{\pi} + R_5 // (R_1 // R_2)) + R_E (r_{\pi} + R_5 // (R_1 // R_2))}{R_E + r_{\pi} + R_5 // (R_1 // R_2) + g_m R_E r_{\pi}}$$

$$f_{3dB} \approx \frac{1}{2\pi [C_{u1} R_{uo} + C_p R_{po} + C_s R_{so}]}$$