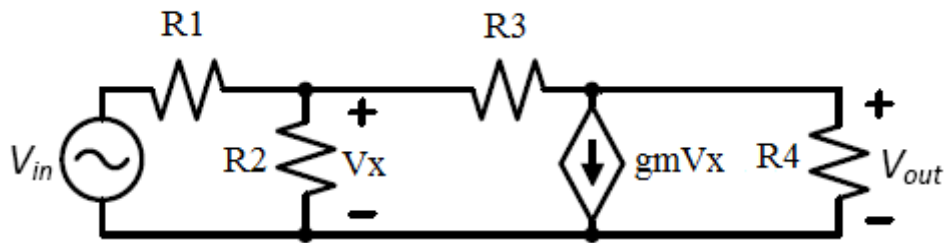


University of Michigan
EECS 311: Electronic Circuits
Fall 2009
Review for Quiz #1

R1.1 Derive the Thevenin equivalent voltage and resistance seen by V_{out} in the circuit below.




R1.2 Sketch the asymptotic Bode plot (magnitude and phase) for the following transfer function.


$$H(s) = \frac{1000(s + 10)}{(s + 100)(s^2 + 2s + 1)}$$

R1.3 Use the follow S&K topology to design a bandpass filter with the following specifications:

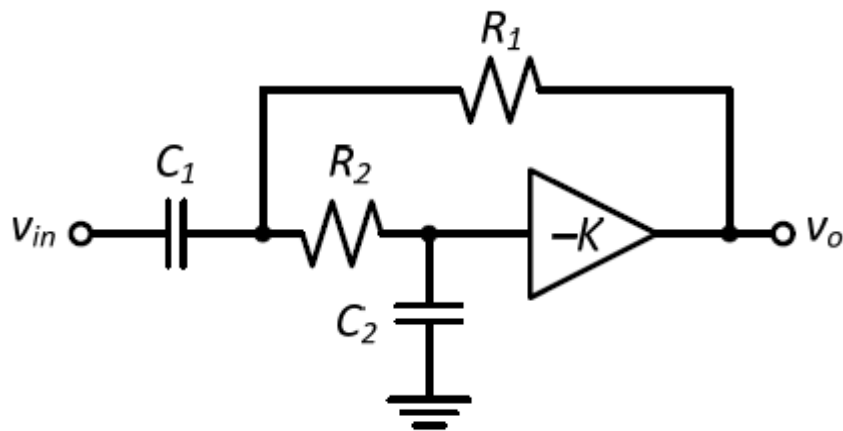$h = -20$
 $\omega_n = 100\text{kHz}$
 $d = 1/7$




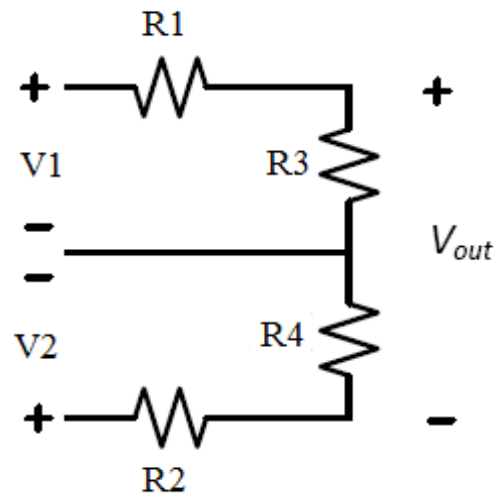R1.4 Derive the CMRR of the following circuit.



R1.5 Given a first order step response, with a rise time $t_r = 100\text{ns}$ and a final value of 1, will a system intended to produce this output be able to, when its slew rate is $20\text{ V}/\mu\text{s}$? What value of τ will put the step response just at the Slew Rate?

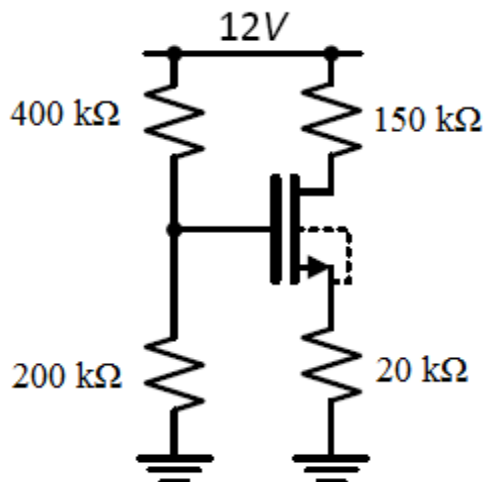R1.6 Find I_d through the transistor below. $V_{tn} = 1\text{V}$, $\lambda = 0$, $K_n = 60\mu\text{A}/\text{V}^2$



R1.7 Using the Constant voltage drop model with $V_{on} = 0.6\text{ V}$, sketch a plot of V_{out} vs. time when $V_{in} = A \sin(\omega_0 t)$.

