
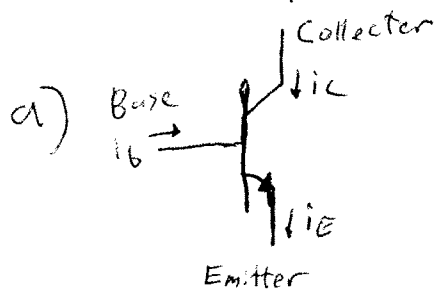


R2.1





NPN

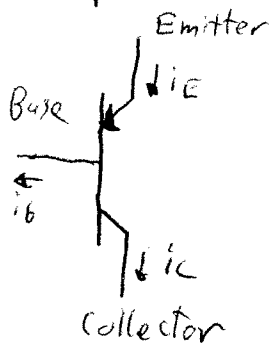



PNP









b)

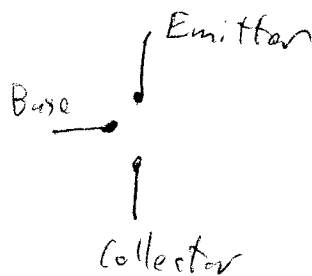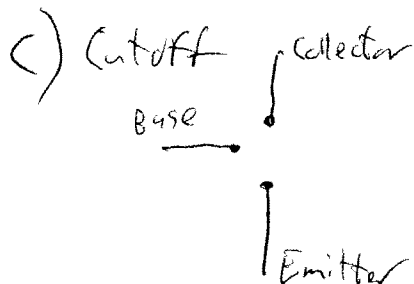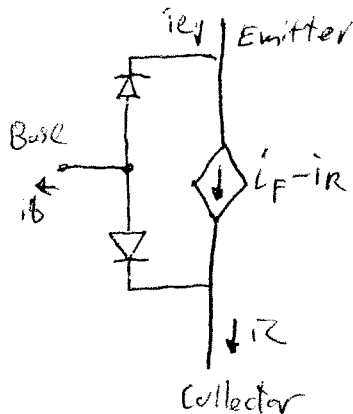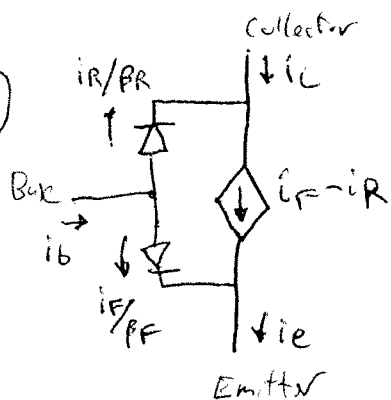


SAT

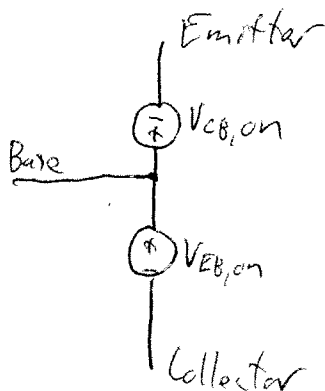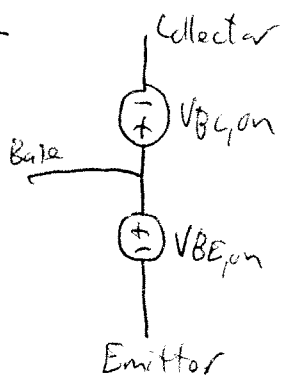

FAR

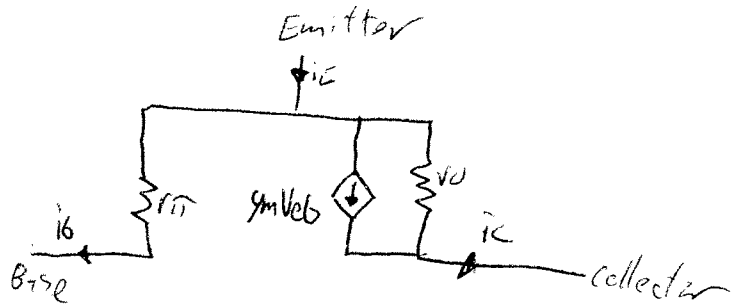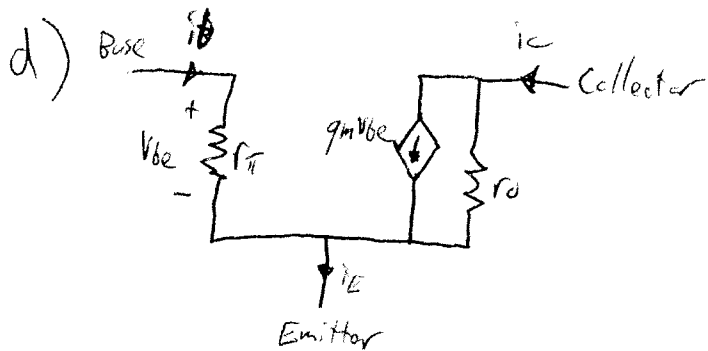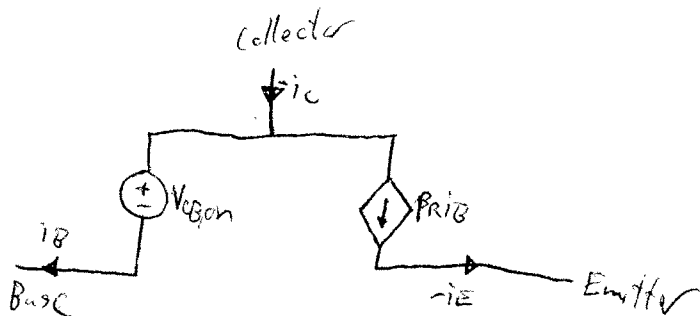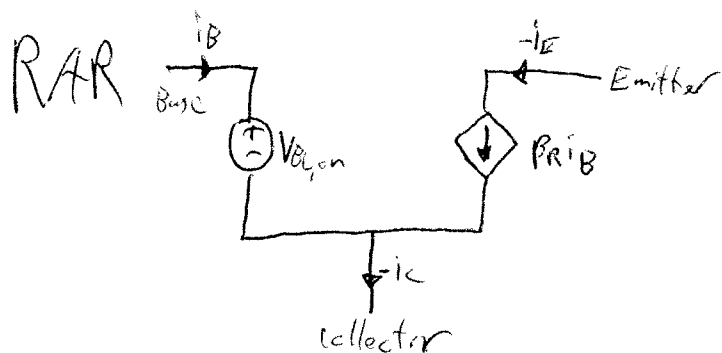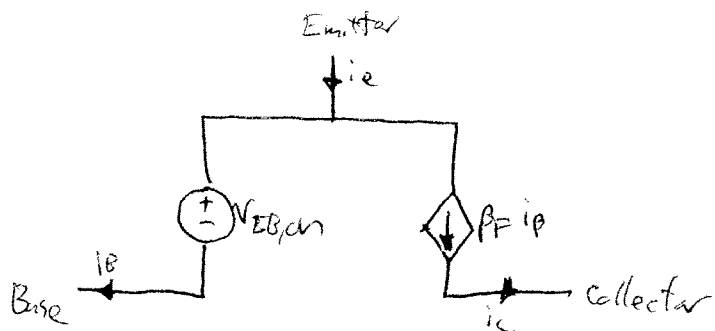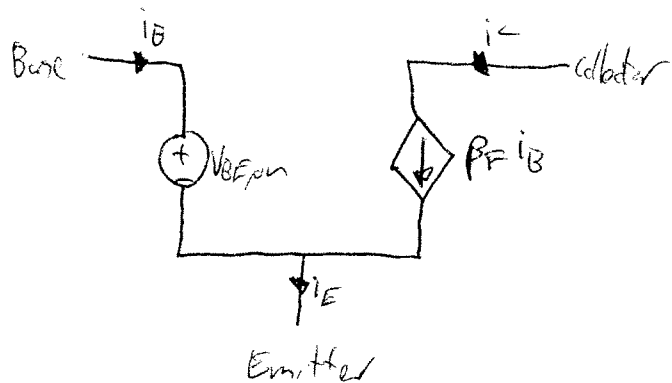

R2.2

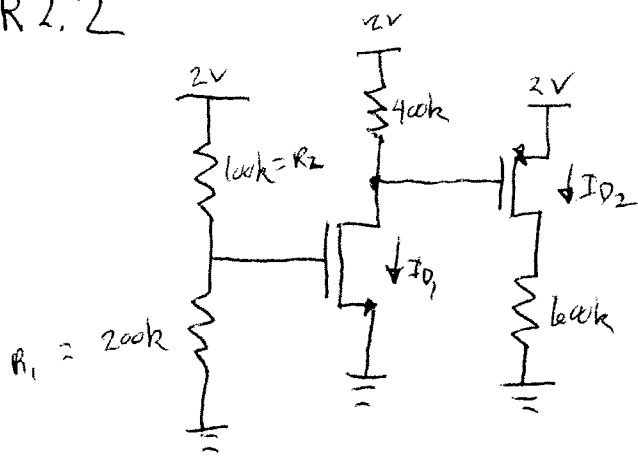

$$V_{TN} = 1V$$

$$V_{TP} = -1V$$

$$K_n = 60 \mu A/V^2$$

$$K_p = 40 \mu A/V^2$$

Assume
SAT for
Both

$$I_{D1} = \frac{V_{DD} - V_{D1}}{400k} = \frac{1}{2} K_n (V_{GS1} - V_{TN})^2$$

$$V_{GS1} = V_{DD} \frac{R_1}{R_1 + R_2}$$

$$I_{D2} = \frac{V_{D2}}{600k} = \frac{1}{2} K_p (V_{GS2} - V_{TP})^2$$

$$V_{GS2} = V_{D1} - V_{DD}$$

$$V_{D1} = 0.6667V = V_{DS1}$$

$$V_{GS1} = 1.333V$$

$$V_{D2} = 1.333V \rightarrow V_{DS2} = V_{D2} - V_{DD} = -0.6667V$$

$$V_{GS2} = -1.333V$$


$$V_{DS1} \geq V_{GS1} - V_{TN} \quad \checkmark$$

$$V_{DS2} \leq V_{GS2} - V_{TP} \quad \checkmark$$

$$I_{D1} = 3.333 \mu A$$

$$I_{D2} = 2.222 \mu A$$

R2.3

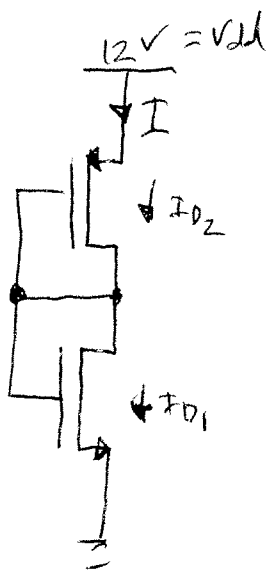

$$V_{TN} = 1V$$

$$V_{TP} = -1V$$

$$K_n = 60 \mu A/V^2$$

$$K_p = 40 \mu A/V^2$$

Both Gates connected to Drains $\rightarrow$ Both always in SAT

$$I_{D1} = I_{D2} = I$$

$$K_n (V_{gs1} - V_{TN})^2 = K_p (V_{gs2} - V_{TP})^2$$

$$\downarrow$$


$$V_{gs2} = V_{gs1} - V_{DD}$$

$$V_{gs1} = \frac{K_n \cdot V_{TN} \pm \sqrt{K_n K_p} (V_{DD} - V_{TN} + V_{TP}) - K_p (V_{DD} + V_{TP})}{K_n - K_p}$$

$$= \boxed{5.4949V} \text{ or } -43.4949V$$

$$I = \frac{1}{2} K_n (V_{gs1} - V_{TN})^2 = \boxed{606.12 \mu A}$$

R2.4

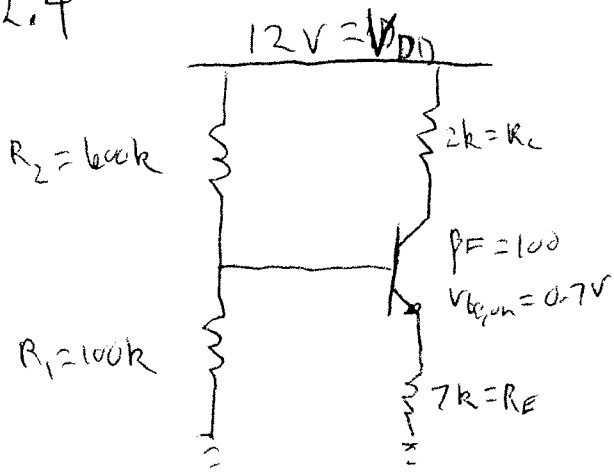

$\beta_F \uparrow 10\%$

$$\% \text{ Error } I_C = \left| \frac{I_{C, \text{change}} - I_{C, \text{nom}}}{I_{C, \text{nom}}} \right| = \frac{\Delta I_C}{I_{C, \text{nom}}}$$

1st way

$$\text{KVL} \rightarrow I_C = \beta_F \frac{V_{DD} \frac{R_1}{R_1 + R_2} - V_{BE,on}}{R_1 || R_2 + (\beta_F + 1) R_E}$$

$\beta_F = 100 \rightarrow I_C = 127.95 \mu A$

$\beta_F = 110 \rightarrow I_C = 129.37 \mu A$

$\% \text{ Error } I_C = 1.0747\%$

$R_E = 0$

$\beta_F = 100 \rightarrow I_C = 1.183 \text{ mA}$

$\beta_F = 110 \rightarrow I_C = 1.302 \text{ mA}$

$\% \text{ Error } I_C = 10.1\%$



2nd way

$$\frac{\partial I_C / \partial \beta_F}{I_{C, \text{nom}}} = \frac{\Delta I_C / \Delta \beta_F}{I_{C, \text{nom}}} \approx \frac{1}{\beta_F} \left(1 - \frac{I_C R_E}{I_B R_1 || R_2 + I_C R_E} \right) \approx \frac{\% \text{ Error } I_C}{\% \text{ Error } \beta_F} \cdot \frac{1}{\beta_F}$$

$R_E = 7k \rightarrow \% \text{ Error } I_C \approx 1.0813\%$

$R_E = 0 \rightarrow \% \text{ Error } I_C \approx \% \text{ Error } \beta_F \approx 10\%$

R 2.5

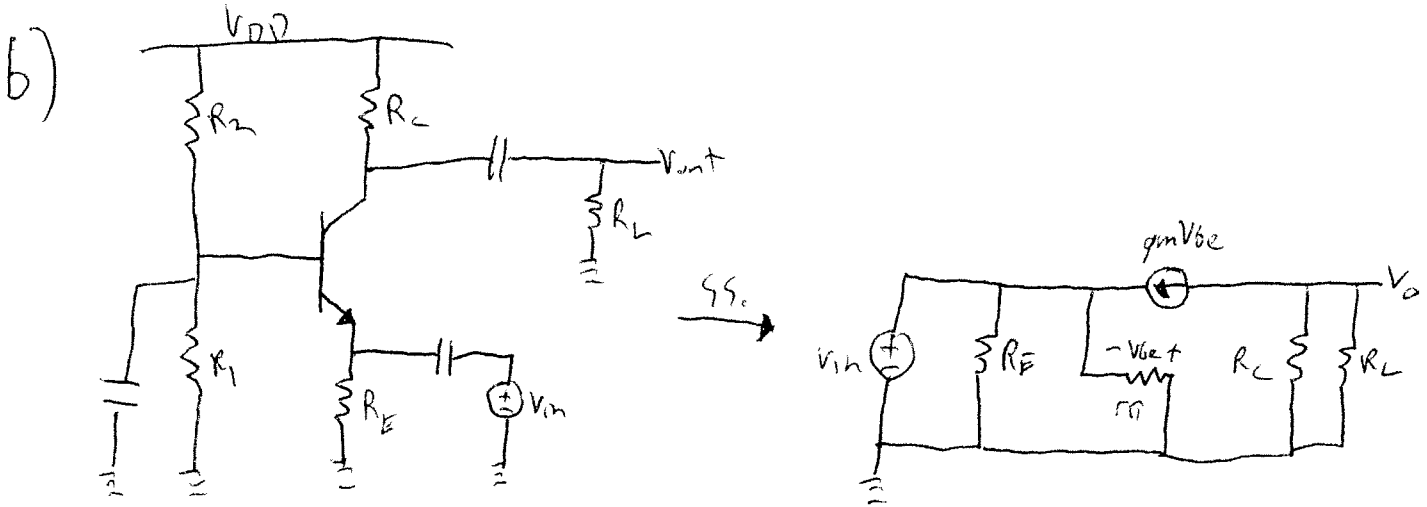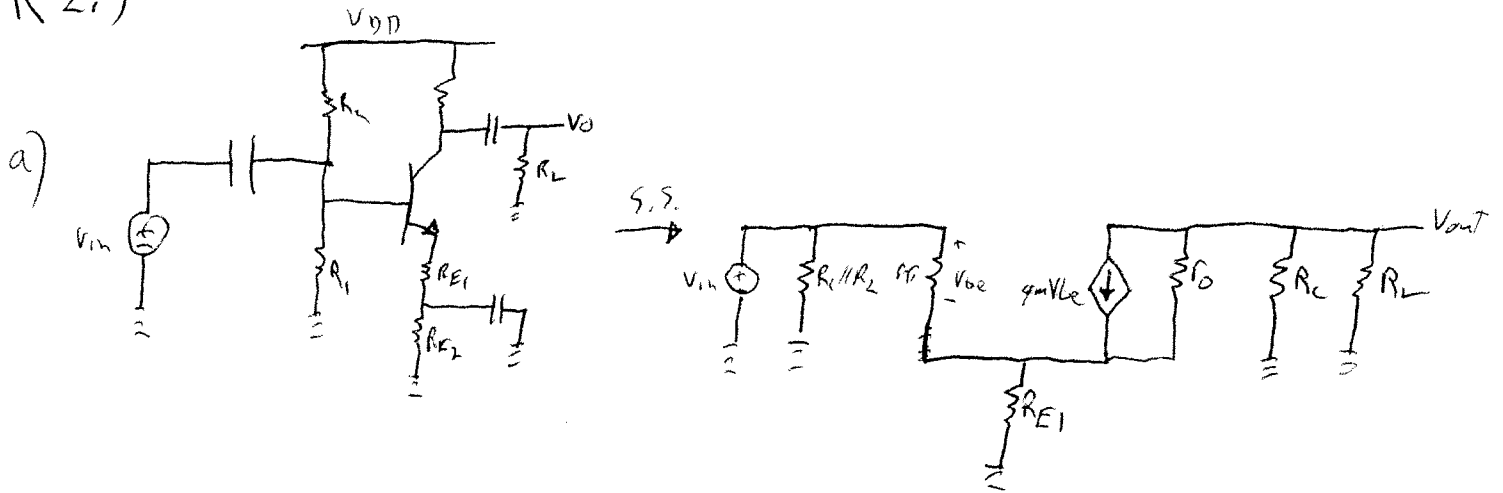

R 2.6

$$V_o \approx -g_m V_{be} \cdot R_C // R_L$$

$$= g_m V_{in} R_C // R_L$$

$$\frac{V_o}{v_{in}} = +g_m R_C // R_L$$