

## SK Design Example

- Design a 2<sup>nd</sup> order highpass filter with:

$$d = \sqrt{2}$$

$$\omega_n = 10^3 \text{ rad} / \text{s}$$

- The generic transfer function of a highpass 2<sup>nd</sup> order filter is:

$$H(s) = \frac{K(s/\omega_n)^2}{1 + d(s/\omega_n) + (s/\omega_n)^2}$$

- This filter has a passband gain of K


- Next we go through **4 design decisions** you have to make, and calculations for parameters that result from those decisions

EECS 311 Fall 2009

1

## SK Design Example

- Use circuit #3 from the SK paper

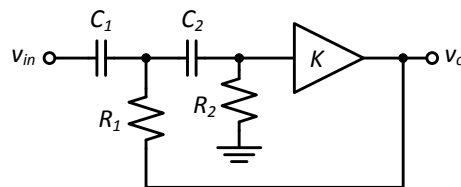

- ❖ **Decision 1:** Choose that we want to specify  $\gamma$  and  $T_1$ , then solve for  $\rho$  and  $T_2$

- This implies we're using Formula Group 1 in SK paper

EECS 311 Fall 2009

2

## SK Design Example

- ❖ **Decision 2:** Choose  $C_1$  equals  $C_2$

$$C_1 = C_2$$

$$\gamma = \frac{C_2}{C_1} = 1$$

- **Next step:** find minimum allowed amp gain:  $K_{min}$ 
  - Equation from Formula Group 1 is SK

$$K_{min} = \frac{4(1+\gamma) - d^2}{4(1+\gamma)} = \frac{4(1+1) - 2}{4(1+1)} = \frac{3}{4}$$

- ❖ **Decision 3:** Choose value for  $K$  greater or equal to  $K_{min}$

$$K \geq K_{min}$$

$$K = 1$$

EECS 311 Fall 2009

3

## SK Design Example

- **Next step:** Solve for the value of  $T_1$ 
  - From the SK paper, Formula Group 1

$$d = \frac{1-K}{T_1} + T_1(1+\gamma)$$

- We already have  $K = 1$ ,  $\gamma = 1$ , and  $d = \text{sqrt}(2)$   
Plugging in...

$$d = \frac{1-1}{T_1} + T_1(1+1) = \sqrt{2}$$

$$T_1 = \frac{\sqrt{2}}{2} = \frac{1}{\sqrt{2}} \approx 0.7$$

- **Next step:** Solve for the value for  $T_2$

$$T_2 = \frac{1}{T_1} = \sqrt{2} \approx 1.4$$

EECS 311 Fall 2009

4

## SK Design Example

- Summary so far...

$$\gamma = 1 \quad T_1 \approx 0.7$$

$$K = 1 \quad T_2 \approx 1.4$$

- Next step: Choose actual component values

- We'll need to know  $\omega_n$  to un-normalize

- $\omega_n$  was given with the filter specifications (slide 1)

$$\omega_n = 10^3 \text{ rad} / \text{s}$$

## SK Design Example

❖ **Decision 4:** Choose a value for  $C_1$ , then  $C_2 = C_1$  since  $\gamma = 1$

$$C_1' = C_2' = 1 \mu\text{F}$$

- Next step: solve for rest of the component values

- Starting with  $T_1$

$$T_1 = R_1' C_1' \omega_n = 0.7 \quad R_1' = \frac{0.7}{1 \mu\text{F} \cdot 10^3} = 700 \Omega$$

- Next,  $T_2$

$$T_2 = R_2' C_2' \omega_n = 1.4 \quad R_2' = 1.4 \text{ k}\Omega$$

## SK Design Example

- Final circuit

