

**University of Michigan**  
**EECS 311: Electronic Circuits**  
**Fall 2009**

LAB 2 – NON-IDEAL OPAMPS

Issued 10/5/2008  
Pre-Lab Completed 10/12/2008  
Lab Due in Lecture 10/21/2008

## Introduction

In this lab you will characterize an LM741 operational amplifier from Fairchild Semiconductor, with emphasis on the following non-ideal properties of opamps: finite gain, bandwidth, offset voltage, and slew rate. A datasheet for this opamp may be found at:


LM741 Datasheet: <http://www.eecs.umich.edu/courses/eecs311/f09/labs/lm741.pdf>

To adequately prepare you for this lab, a custom model of a non-ideal opamp has been developed in Cadence that you will characterize through simulations by using the same experiments that will be used in lab to characterize the LM741. The model of the opamp in Cadence is not meant to match the performance of the LM741, but it has similar limitations (finite gain, bandwidth, offset voltage, and slew rate).

Complete all pre-lab exercises before attempting the in-lab exercises. Use the Pre-Lab Report Template and In-Lab Report Template at the end of this assignment to record data and answer questions. Have the GSI sign off on the specified exercises on the check-off sheet at the end of this assignment. Hand in the check-off sheet, both report templates, and the requested plots at the beginning of lecture on the due date.

## Pre-Lab Exercises

Complete all of the following exercises before attempting the in-lab exercises. Use Cadence to simulate circuits where requested, using the *lab1\_opamp* component in the *EECS311Lib* library for all problems. Refer to the online Cadence tutorial to setup your Cadence environment and for basic information on using Cadence.

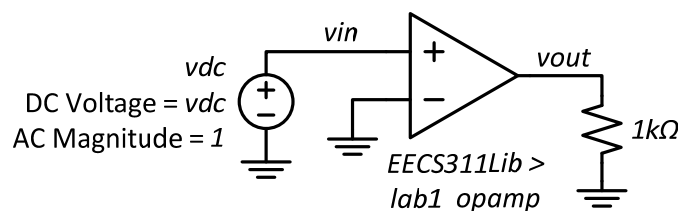


**Figure 1. Cadence schematic for exercises P2.1-3.**

- P2.1** Review the online Cadence tutorial at the following site and refer to this tutorial for guidance in completing any of the following problems. In Cadence, create a library called *lab2*. Within your *lab2* library, create a new schematic cell view called *prelab* and build the schematic shown in Figure 1. Make sure you *Check and Save* your schematic.

<http://www.eecs.umich.edu/courses/eecs311/f09/tutorials>

- P2.2** Launch Analog Environment and perform a DC sweep of the variable  $vdc$  (DC input voltage in Figure 1) from  $-5mV$  to  $+5mV$  in 10k steps. Plot the output voltage as a function of the swept input voltage. Determine the DC offset voltage and the DC open-loop gain of the amplifier  $A_0$  from the simulated response.
- P2.3** In Analog Environment, set the  $vdc$  variable to the offset voltage value found in P2.2 that results in  $V_{out} = 0$ . Then perform an AC analysis from  $1Hz$  to  $1GHz$  with an AC magnitude of  $v_{in} = 1V$ . Plot the open-loop transfer function  $H(s) = 20\log(v_{out}/v_{in})$  and find the open-loop DC gain and 3dB bandwidth of the amplifier.

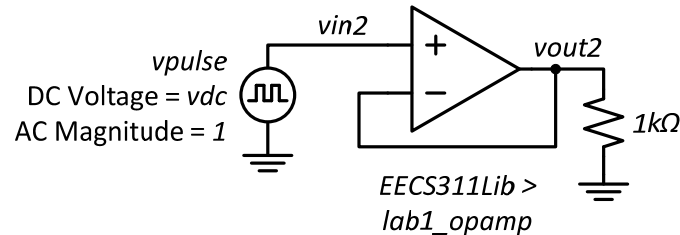

**Figure 2. Circuit for exercises P2.4 and P2.5.**

- P2.4** On the same schematic, without altering the circuit used for P2.2 and P2.3, add a second opamp configured for unity-gain as shown in Figure 2. Use different net names to label the wires – Cadence treats separate wires with the same net name as shorted together. Using Analog Environment, perform an AC analysis from  $1Hz$  to  $1GHz$  with an AC magnitude of  $v_{in} = 1V$ . Plot the transfer function  $H(s) = 20\log(v_{out2}/v_{in2})$  and find the closed-loop DC gain and 3dB bandwidth of the amplifier. Plot the open-loop amplifier and unity-gain amplifier transfer functions on the same graph. At approximately what frequency and gain do the asymptotes of the plots join?
- P2.5** Perform a transient analysis for  $40\mu s$  of the unity gain amplifier, check the *conservative* option in the transient analysis window. Use the  $vpulse$  source in the *analogLib* library for a square wave input source. Give the  $vpulse$  a period of  $20\mu s$ , pulse width of  $10\mu s$ ,  $1ps$  rise/fall time, and Voltage 1 & 2 values of  $\pm 1mV$ . Plot the output voltage and measure the time constant of the step response. Increase the values of Voltage 1 & 2 to  $\pm 10V$  and re-simulate the transient response. Determine the region in which the output of the amplifier is slew rate limited, and measure the slew rate.

Note: slew rate is defined as the maximum rate of change of the output voltage ( $dv_{out}/dt$ ) of the opamp. An opamp cannot change its output voltage faster than the slew rate limit.

## In-Lab Exercises

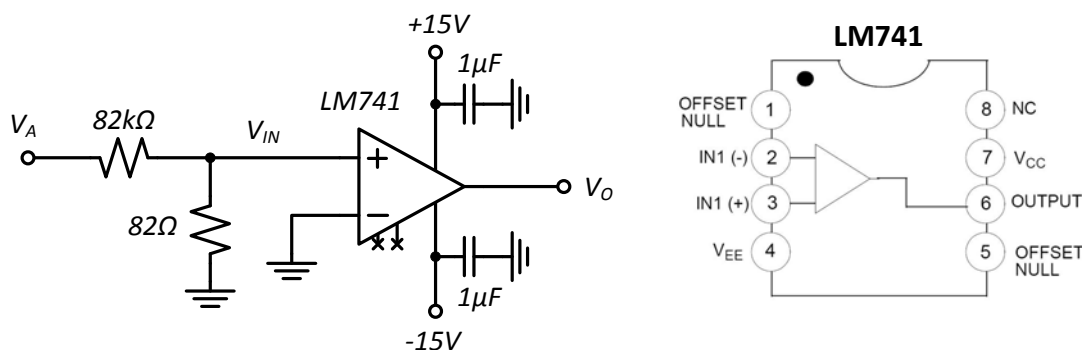


Figure 3. Circuit for exercises L2.1 and pinout of LM741.

**L2.1** This part of the lab will use the HP4155 Semiconductor Parameter Analyzer to measure the open-loop characteristics of a 741 opamp. Construct the circuit shown in Figure 3.

Before inserting the 82kΩ and 82Ω resistors on the board, record the measured values of the two resistors. Use these measurements to accurately compute the ratio of  $V_A$  to  $V_{IN}$ .

Connect your circuit to the HP4155 using the connections below by using the wires on the HP4155:

Circuit Net	HP4155 Connection
$V_a$	VSU1 (Voltage Source 1)
Ground	GND
$V_o$	VMU1 (Voltage Monitor 1)

Load and execute the program *P741* on the HP4155, which performs a DC sweep of the voltage  $V_a$  from -10V to +10V while recording the output voltage. Refer to the online HP4155 tutorial for instructions on how to load a program:

<http://www.eecs.umich.edu/courses/eecs311/f09/tutorials/hp4155.html>

Measure the offset voltage  $V_{off}$  and open-loop DC gain  $A_0$  of the amplifier the same way you did in P2.2. Make sure you take into account the scaling factor of the resistive divider in your circuit when calculating  $V_{off}$  and  $A_0$ . You may need to modify the settings in the HP4155 to reduce the step size of the input voltage to accurately capture the output voltage swing.

Important: You must take into account the scaling factor of the resistive divider in your circuit when calculating  $V_{off}$  and  $A_0$ . The HP4155 will report values relative to the swept voltage  $V_A$ , not  $V_{IN}$ .

**L2.2** Using the same opamp you used in L2.1, build a unity gain buffer on your proto-board following the schematic in Figure 4. Connect the input voltage  $V_{IN}$  to ground and measure the output voltage at  $V_O$  with a multimeter set to the mV scale. This will be equal to the offset voltage.

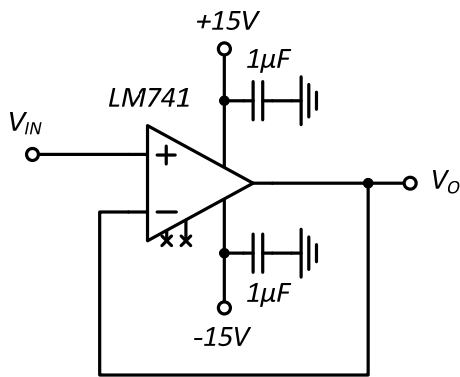


Figure 4. Circuit for exercises L2.2-6.


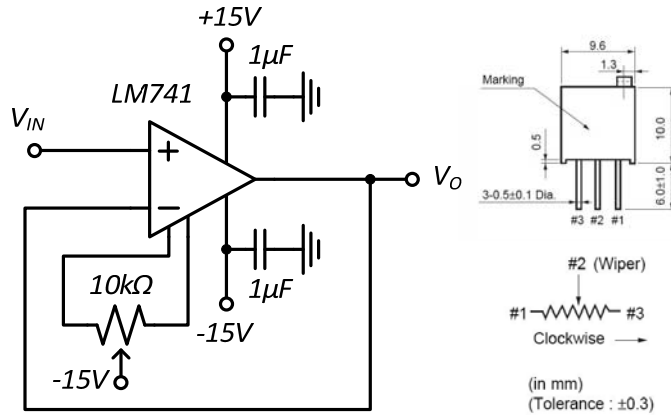


Figure 5. Circuit for exercise L2.2 with offset null.

- L2.3** Connect a  $10k\Omega$  potentiometer across the offset null pins of the LM741 (pins 1 and 5), with the wiper connected to  $-15V$  as shown in Figure 5. Connect the input of the amplifier to ground. While measuring the output voltage with a multimeter set to the mV scale, tune the potentiometer until you see 0V. This nulls out the offset voltage of the amplifier. Then remove the potentiometer and measure the values of resistances between the #1 and #3 pins and the wiper (#2). Keep the potentiometer out for the remainder of the experiments. Show your offset compensated amplifier to the GSI and be prepared to answer questions.
- L2.4** Connect the input of the unity-gain amplifier (Figure 4) to the function generator configured as a square wave, 10Vppk, and high-Z mode. Identify the region of the output signal over which the opamp is slew-rate limited. Measure the slew rate for both a positive slope and negative slope.
- L2.5** Configure the function generator as a sine wave in high-Z mode. Choose an input amplitude small enough that you will not be slew rate limited. The maximum  $dV_o/dt$  of a sine wave is  $\omega \cdot V_{oppk}/2$ . Using both channels on the oscilloscope, simultaneously measure the input and output voltages. Record the input and output amplitudes from 1kHz to 10MHz in logarithmic steps of 3 points per decade. Additionally measure the 3dB frequency and approximate the phase shift from input to output at that frequency.
- L2.6** Configure the function generator as a square wave in high-Z mode. Choose an input amplitude to keep the output step response from being slew-rate limited. Measure the 10%-90% rise-time of the output waveform. Show your step response to the GSI and be prepared to answer questions.
- L2.7** Using the same opamp as in the previous exercises, reconnect the amplifier in an inverting configuration with a gain of -10 using the schematic shown in Figure 6. Determine appropriate values for  $R_1$  and  $R_2$ , and measure their values before inserting them into the circuit. Choose the input amplitude for the function generator so that the output is not slew-rate limited. Record the input and output amplitudes from 1kHz to 10MHz in logarithmic steps of 3 points per decade. Additionally, measure the 3dB frequency and approximate the phase shift from input to output at that frequency. Show your amplifier and results to the GSI and be prepared to answer questions.

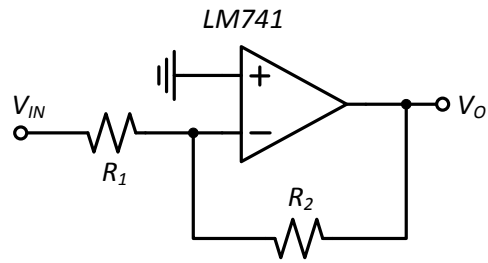

**Figure 6. Circuit for exercises L2.7. Decoupling capacitors and offset compensation are not shown.**



**University of Michigan**  
**EECS 311: Electronic Circuits**  
**Fall 2008**

LAB 1 – PRE-LAB REPORT TEMPLATE

NAME: \_\_\_\_\_

LAB SECTION: \_\_\_\_\_

**Pre-Lab Exercises**

P2.2 DC Offset Voltage = \_\_\_\_\_

DC Open-Loop Gain = \_\_\_\_\_

Attach a plot of the DC sweep.

P2.3 DC Open-Loop Gain = \_\_\_\_\_

3dB Frequency = \_\_\_\_\_

Calculate the gain-bandwidth product = \_\_\_\_\_

P2.4 Frequency at which asymptotes join = \_\_\_\_\_

Compare this frequency to the gain-bandwidth product from P1.3.

Attach one plot containing the AC sweep results from both amplifiers.

P2.5 Time constant of unity-gain amplifier = \_\_\_\_\_

Slew rate = \_\_\_\_\_



**University of Michigan**  
**EECS 311: Electronic Circuits**  
**Fall 2009**

**LAB 2 – CHECK-OFF SHEET**

NAME: \_\_\_\_\_

LAB SECTION: \_\_\_\_\_

Have the GSI check you off on the following exercises after you have completed them. Be prepared to answer questions about your circuit or the results.

**Exercise ..... Date Completed**

P2.x Prelab Report Template..... \_\_\_\_\_

L2.3 Offset compensated circuit..... \_\_\_\_\_

L2.6 Step response..... \_\_\_\_\_

L2.7 Frequency response..... \_\_\_\_\_



**University of Michigan**  
**EECS 311: Electronic Circuits**  
**Fall 2009**

LAB 2 – REPORT TEMPLATE

NAME: \_\_\_\_\_

LAB SECTION: \_\_\_\_\_

Use the following lab report template to record your measurements. Use the space provided to answer questions.

**Lab Report Template**

L2.1  $R_1 =$  \_\_\_\_\_

$R_2 =$  \_\_\_\_\_

DC Offset Voltage = \_\_\_\_\_

DC Open-Loop Gain = \_\_\_\_\_

L2.2 DC Offset Voltage of Unity-Gain Amplifier = \_\_\_\_\_

Compare the measurements of offset voltage and open-loop gain from L2.1 and L2.2 with the value specified in the Fairchild LM741 datasheet available on the EECS 311 website.

L2.3 Output Offset Voltage after Nulling = \_\_\_\_\_

Potentiometer Resistances:  $R_{1-to-wiper} =$  \_\_\_\_\_

$R_{2-to-wiper} =$  \_\_\_\_\_

L2.4 Slew Rate Pos Slope = \_\_\_\_\_ Slew Rate Neg Slope = \_\_\_\_\_

Compare the measured slew rate with the value specified in the Fairchild LM741 datasheet available on the EECS 311 website.

L2.5 Record values in the table below.

L2.6 Step Response Output Amplitude = \_\_\_\_\_

10%-90% Rise-Time = \_\_\_\_\_

Compare the measured rise time with the value specified in the Fairchild LM741 datasheet available on the EECS 311 website.

Assuming the step response is first-order, calculate the value of the 3dB frequency.

$\omega_{3dB} = 1/\tau =$  \_\_\_\_\_

L2.7 Record values in the table below. Then answer the following questions.

Using a graphing tool such as Matlab or Excel, calculate the transfer function in dB and plot the two frequency responses on a single graph. Use a log-scale for the frequency axis. Label the two curves and the axes. Attach this plot.

Calculate the gain-bandwidth products for the two configurations.

L2.5 = \_\_\_\_\_, L2.7 = \_\_\_\_\_

Should gain-bandwidth all be equal assuming a first-order opamp? Are they? Explain.

Compare the unity-gain 3dB frequency from L2.5 with the results from L2.6.

What should the phase of a first-order amplifier be at the 3dB frequency? \_\_\_\_\_

What do the measurements of phase tell you about the assumption of a first-order amplifier in each configuration?

	L2.5	L2.7
$R_1$		
$R_2$		
1kHz ( $V_{IN} / V_O$ )	/	/
2kHz ( $V_{IN} / V_O$ )	/	/
5kHz ( $V_{IN} / V_O$ )	/	/
10kHz ( $V_{IN} / V_O$ )	/	/
20kHz ( $V_{IN} / V_O$ )	/	/
50kHz ( $V_{IN} / V_O$ )	/	/
100kHz ( $V_{IN} / V_O$ )	/	/
200kHz ( $V_{IN} / V_O$ )	/	/
500kHz ( $V_{IN} / V_O$ )	/	/
1MHz ( $V_{IN} / V_O$ )	/	/
2MHz ( $V_{IN} / V_O$ )	/	/
5MHz ( $V_{IN} / V_O$ )	/	/
10MHz ( $V_{IN} / V_O$ )	/	/
3dB Frequency		
Phase Shift		