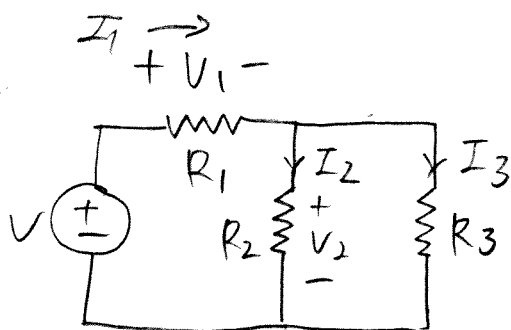


EECS 311 PS1 Solution

P1.1
1.20




$$V = 10V$$

$$R_1 = 22k\Omega$$

$$R_2 = 47k\Omega$$

$$R_3 = 180k\Omega$$

P.1
 V_1, V_2, I_2, I_3

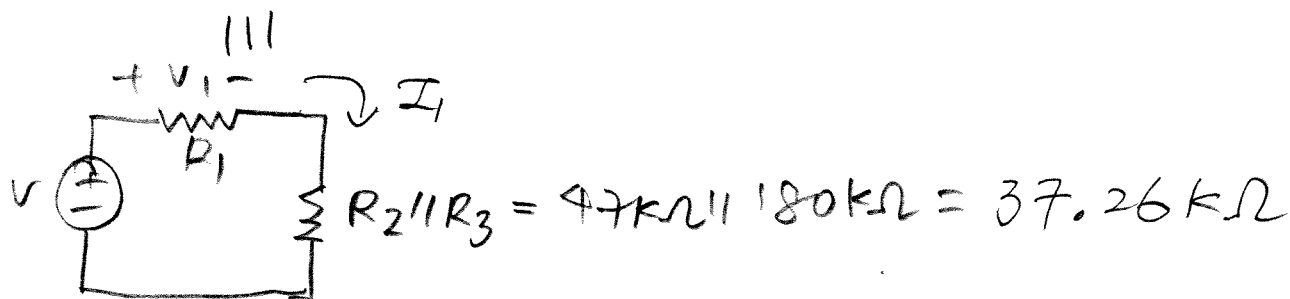

$$I_1 = \frac{V}{R_1 + (R_2 || R_3)} = \frac{10}{22k + 37.26k} = 0.168mA$$


$$\therefore V_1 = I_1 R_1 = 0.168mA \times 22k = \boxed{3.69V} \#$$

$$V_2 = V - V_1 = 10 - 3.69 = \boxed{6.31V} \#$$

$$I_2 = \frac{V_2}{R_2} = \frac{6.31}{47k} = \boxed{0.134mA} \#$$

$$I_3 = \frac{V_2}{R_3} = \frac{6.31}{180k} = \boxed{0.035mA} \#$$

1.22

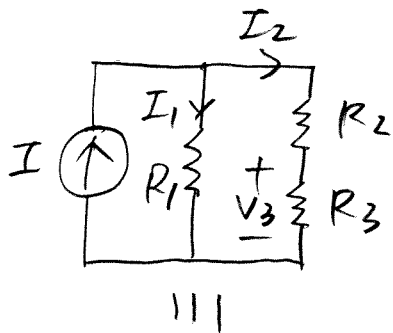


$$I = 5 \text{ mA}$$

$$R_1 = 2.4 \text{ k}\Omega$$

$$R_2 = 5.6 \text{ k}\Omega$$

$$R_3 = 3.6 \text{ k}\Omega$$

I_1, I_2, V_3 ?

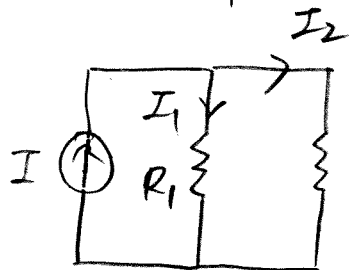


$$R_{eq} = R_2 + R_3 = 9.2 \text{ k}\Omega$$

$$I_1 = I \times \frac{R_{eq}}{R_1 + R_{eq}} = 5 \text{ mA} \times \frac{9.2 \text{ k}}{2.4 \text{ k} + 9.2 \text{ k}} = \boxed{3.97 \text{ mA}}$$

$$I_2 = I \times \frac{R_1}{R_1 + R_{eq}} = 5 \text{ mA} \times \frac{2.4 \text{ k}}{2.4 \text{ k} + 9.2 \text{ k}} = \boxed{1.03 \text{ mA}}$$

$$V_3 = I_2 R_3 = 1.03 \text{ mA} \times 3.6 \text{ k} = \boxed{3.71 \text{ V}} \#$$

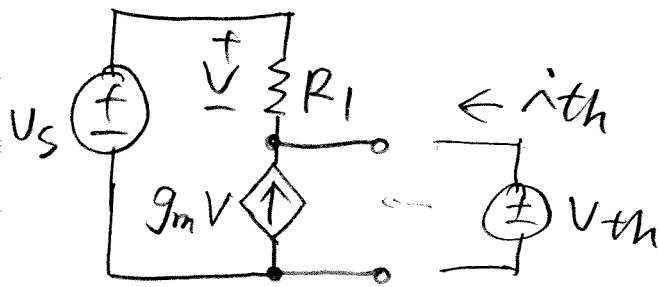1.24
✓


① find open circuit voltage :

$$g_m V + \frac{V}{R} = 0 \Rightarrow \text{only } V = 0 \text{ will satisfy}$$

$$\therefore \boxed{V_{th} = V_s}$$

② find short circuit current

$$i_{th} = -g_m V - \frac{V}{R_1}$$

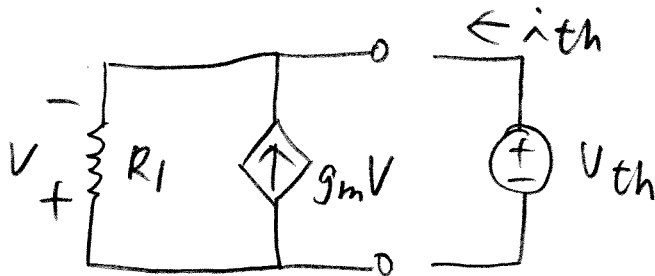

$$\because V = -V_{th} \Rightarrow \boxed{i_{th} = g_m V_{th} + \frac{V_{th}}{R_1}}$$

$$R_{th} = \frac{V_{th}}{i_{th}} = \frac{1}{g_m + \frac{1}{R_1}} = \boxed{R_1 \parallel \frac{1}{g_m}}$$

$$= 50K \parallel \frac{1}{0.002} = \boxed{495 \Omega}$$


$$= 40$$

$$= 41 \ll \frac{1}{0.025} \quad P.4$$

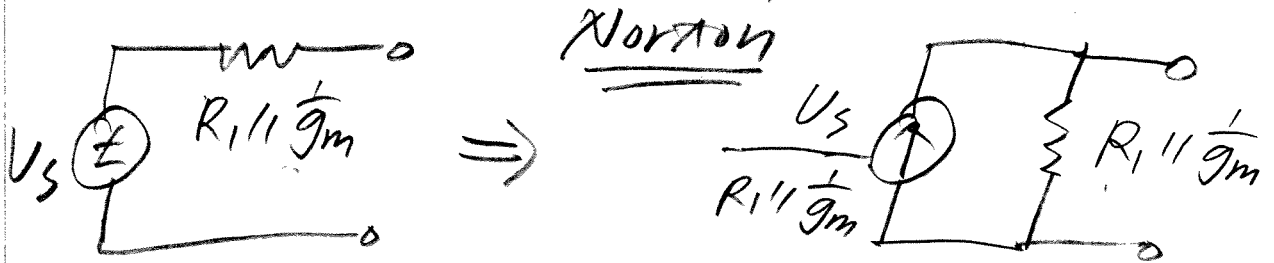
1.25



From 1.24,
We know that $V_{th} = V_s$, $R_{th} = R_1 \parallel \frac{1}{g_m}$




1.26(a)

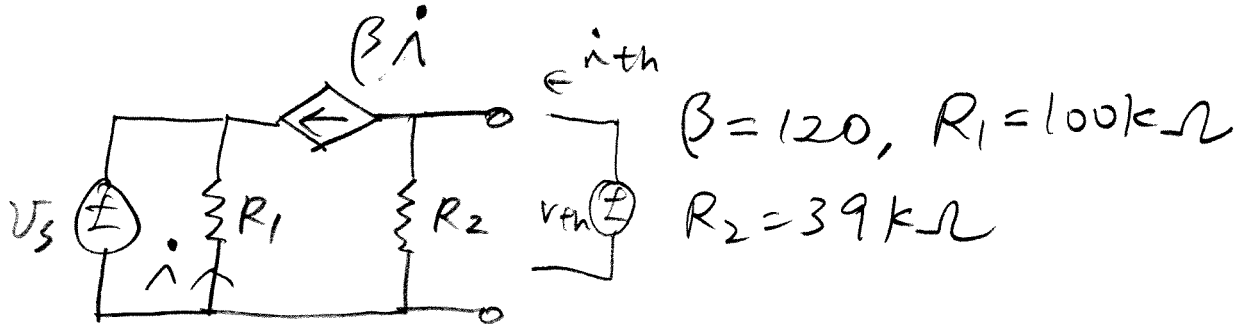

① find open circuit voltage:

$$i = \frac{-V_s}{R_1}, \quad V_{th} = -\beta i \cdot R_2 = V_s \beta \frac{R_2}{R_1}$$


② find short short current:

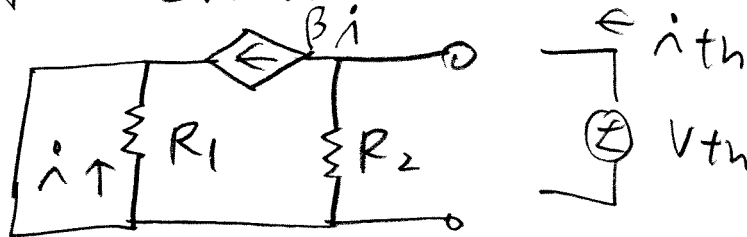


Current won't flow into $R_1 \Rightarrow i = 0$

$$\therefore R_{th} = R_2 = 39 \text{ k}\Omega$$

Thevenin equivalent

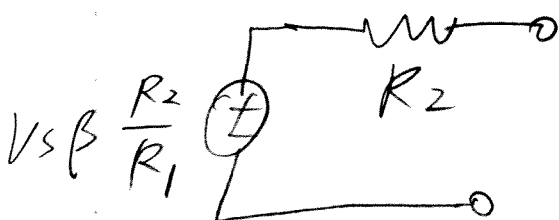

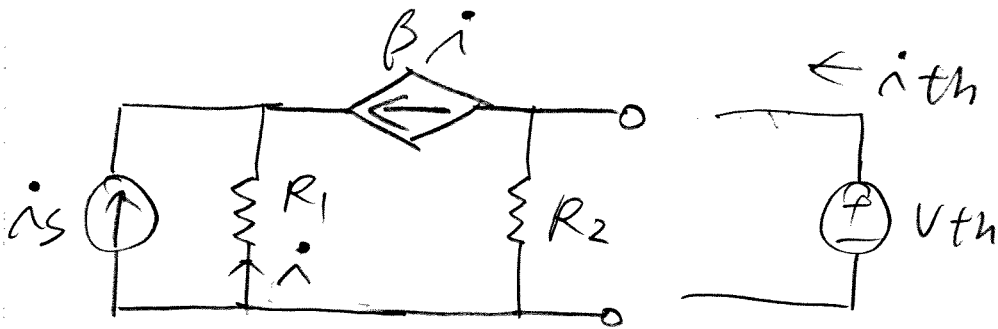1.26(b)
✓


① open circuit voltage :

$$V_{th} = -\beta i R_2$$

$$i = -i_s - \beta i \Rightarrow i = \frac{-i_s}{1+\beta}$$

$$V_{th} = i_s \frac{\beta}{1+\beta} R_2$$

② Short circuit current :

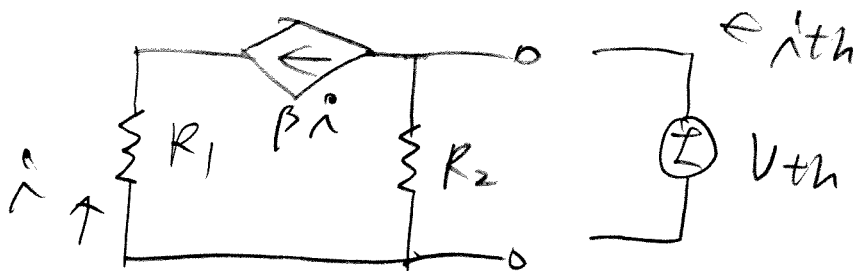


$$\text{KCL: } i + \beta i = 0 \Rightarrow i = 0$$

$$i_{th} = \frac{V_{th}}{R_2} + \cancel{\beta i} = \frac{V_{th}}{R_2}$$

$$R_{th} = \frac{V_{th}}{i_{th}} = R_2 = 39 \text{ k}\Omega$$



Theremin equivalent circuit

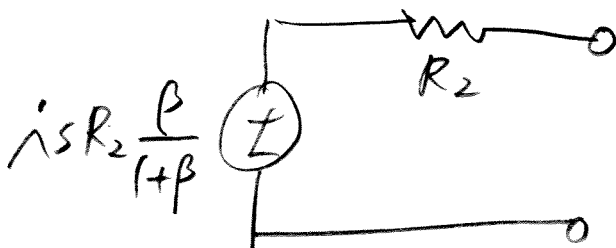

1.27
✓

P.6


from 1.26 (a)

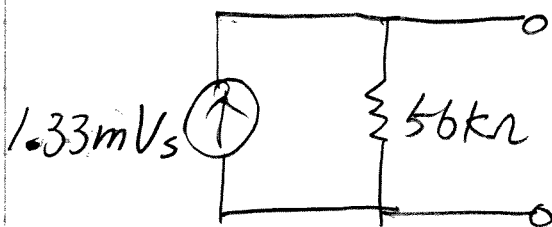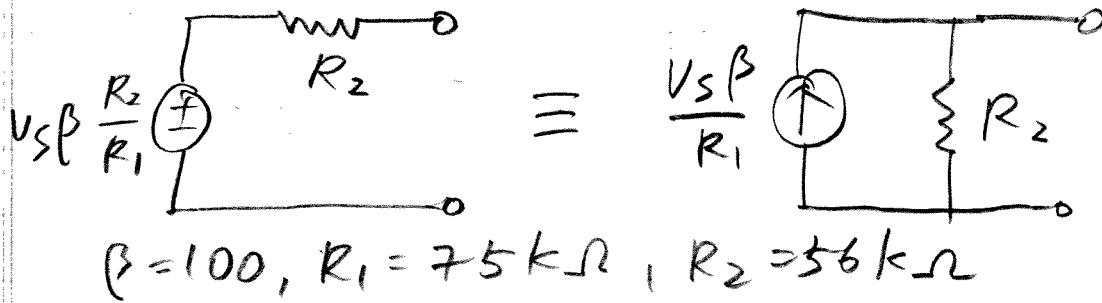

Norton equivalent

P1.2
10.37

✓

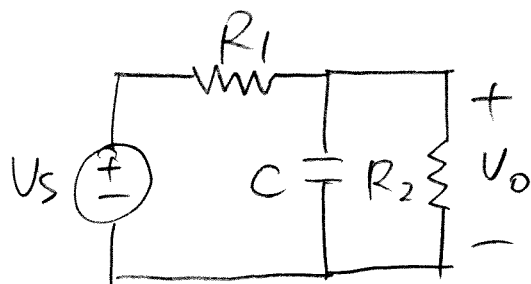

$$\frac{V_O}{V_S} = \frac{R_2}{R_1 + R_2} \left(\frac{1}{1 + \frac{s}{\omega_H}} \right)$$

$$R_1 = 1 \text{ k}\Omega, R_2 = 1.5 \text{ k}\Omega, C = 0.01 \mu\text{F}$$


$$A_V(s) = \frac{\frac{R_2}{R_1 + R_2}}{1 + \frac{s}{\omega_H}}$$

$$A_0 = \frac{R_2}{R_1 + R_2} = \frac{1.5}{1 + 1.5} = \boxed{0.6} = -4.4 \text{ dB}$$

$$f_H = \frac{1}{2\pi} \frac{1}{(R_1 \parallel R_2)C} = \frac{1}{2\pi} \times \frac{1}{(1 \text{ k}\Omega \parallel 1.5 \text{ k}\Omega) \times 0.01 \mu\text{F}} = \boxed{26.52 \text{ kHz}}$$

10.40

✓

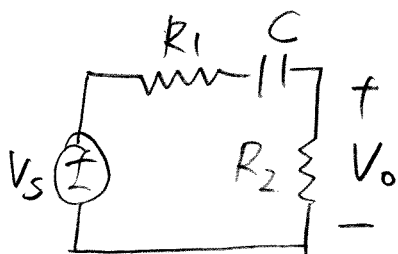

$$\frac{V_O}{V_S} = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{s}{s + \omega_L} \right)$$

$$R_1 = 8.2 \text{ k}\Omega, R_2 = 20 \text{ k}\Omega, C = 0.01 \mu\text{F}$$

$$A_V(s) = \frac{\frac{R_2}{R_1 + R_2}}{1 + \frac{\omega_L}{s}}$$

$$A_0 = \frac{R_2}{R_1 + R_2} = \frac{20}{8.2 + 20} = \boxed{0.71} \approx -3 \text{ dB}$$

$$f_H = \frac{1}{2\pi} \times \frac{1}{(R_1 + R_2)C} = \frac{1}{2\pi} \times \frac{1}{28.2 \text{ k}\Omega \times 0.01 \mu\text{F}} = \boxed{564 \text{ Hz}} \#$$

P.7

10.43



$$A_v(s) = \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)}$$

$$= \frac{1000}{(1 + \frac{20\pi}{s})(1 + \frac{s}{2\pi \times 10^4})}$$

$$A_0 = 1000 = \boxed{60 \text{ dB}} \#$$

$$f_H = \frac{2\pi \times 10^4}{2\pi} = \boxed{10 \text{ kHz}} \#$$

$$f_L = \frac{20\pi}{2\pi} = \boxed{10 \text{ Hz}} \#$$

$$BW = f_H - f_L = 10 \text{ k} - 10 = \boxed{9.99 \text{ kHz}} \#$$

Band-pass amplifier #

10.44



$$A_v(s) = \frac{10^4 s}{s + 200\pi} = \frac{10^4}{1 + \frac{200\pi}{s}}$$

$$A_0 = 10^4 = \boxed{80 \text{ dB}} \#$$

$$f_H = \boxed{\infty} \#$$

$$f_L = \frac{200\pi}{2\pi} = \boxed{100 \text{ Hz}} \#$$

$$BW = f_H - f_L = \boxed{\infty} \#$$

high-pass amplifier #

10.45
✓

$$A_v(s) = \frac{2\pi \times 10^6}{s + 200\pi} = \frac{10^4}{1 + \frac{s}{200\pi}}$$

$$A_0 = 10^4 = \boxed{80 \text{ dB}} \quad \#$$

$$f_H = \frac{200\pi}{2\pi} = \boxed{100 \text{ Hz}} \quad \#$$

$$f_L = \boxed{0 \text{ Hz}} \quad \#$$

$$BW = f_H - f_L = \boxed{100 \text{ Hz}} \quad \#$$

Low-pass amplifier #

10.46
✓

$$A_v(s) = \frac{-10^7 s}{s^2 + 10^5 s + 10^{14}}$$

It's in the form of narrow band pass amplifier.

$$A_v(s) = A_0 \frac{s \frac{\omega_0}{Q}}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}, \quad \boxed{A_0 = -100} \quad \#$$

$$\omega_0^2 = 10^{14} \Rightarrow f_0 = \frac{1}{2\pi} \sqrt{10^{14}} = 1.59 \times 10^6 \text{ Hz}$$

$$\frac{\omega_0}{Q} = 10^5 \Rightarrow Q = 10^2 = \boxed{100} \quad \#$$

$$BW = \frac{f_0}{Q} = \frac{1.59 \times 10^6}{100} = \boxed{1.59 \times 10^4 \text{ Hz}} \quad \#$$

$$f_H = f_0 + \frac{BW}{2} = 1.59 \times 10^6 + 0.795 \times 10^4 = \boxed{1597950 \text{ Hz}}$$

$$f_L = f_0 - \frac{BW}{2} = 1.59 \times 10^6 - 0.795 \times 10^4 = \boxed{1582050 \text{ Hz}}$$

10.47

$$A_v(s) = -20 \frac{s^2 + 10^{12}}{s^2 + 10^4 s + 10^{12}}$$

✓ It's in the form of band-rejection amplifiers #

$$A_v(s) = A_0 \frac{s^2 + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0^2 = 10^{12} \Rightarrow f_0 = \frac{1}{2\pi} \sqrt{10^{12}} = 159155 \text{ Hz}$$

$$\frac{\omega_0}{Q} = 10^4 \Rightarrow Q = 10^2 = 100$$

$$BW = \frac{f_0}{Q} = \frac{159155}{100} = \boxed{1591.55 \text{ Hz}} \#$$

$$f_H = f_0 + \frac{BW}{2} = 159155 + \frac{1591.55}{2} = \boxed{159951 \text{ Hz}} \#$$

$$f_L = f_0 - \frac{BW}{2} = 159155 - \frac{1591.55}{2} = \boxed{158359 \text{ Hz}} \#$$

10.48

$$A_v(s) = \frac{4\pi^2 \times 10^{14} s^2}{(s+20\pi)(s+50\pi)(s+2\pi \times 10^5)(s+2\pi \times 10^6)}$$

$$= \frac{1000}{\left(1 + \frac{20\pi}{s}\right) \left(1 + \frac{50\pi}{s}\right) \left(1 + \frac{s}{2\pi \times 10^5}\right) \left(1 + \frac{s}{2\pi \times 10^6}\right)}$$

$$A_0 = 1000 = \boxed{60 \text{ dB}} \#$$

The midband gain is always defined as the region of highest gain, and the cutoff frequencies are defined in terms of the midband gain.

$$|A_v(j\omega_L)| = \frac{A_0}{f_2} = |A_v(j\omega_H)|$$

$$f_{L1} = \frac{20\pi}{2\pi} = 10 \text{ Hz}$$

$$f_{H1} = 10^5 \text{ Hz} \#$$

$$f_{L2} = \frac{50\pi}{2\pi} = 25 \text{ Hz}$$

$$f_{H2} = 10^6 \text{ Hz}$$

$$f_H = 10^6 \text{ Hz}$$

check the freq in the above equation $\Rightarrow f_L = 25 \text{ Hz}$

P1.3
10.43

P.11

$$V_{in}(s) = 1 \angle 0^\circ, \omega = 2000\pi$$

$$A_v(s) = \frac{1000}{(1 + j\frac{\omega}{5})(1 + \frac{s}{2\pi \times 10^4})}$$

$$|A_v(j2000\pi)| = \frac{1000}{\sqrt{(\frac{1000}{1000})^2 + (\frac{9}{100})^2}} = 707.107$$

$$\angle A_v(j2000\pi) = \angle(1000^\circ - \tan^{-1} \frac{\frac{9}{100}}{\frac{1000}{1000}}) = -5.137^\circ$$

Phasor form

$$A_v(s) = \frac{1000}{\sqrt{2}} \angle -5.137^\circ$$

$$V_{out}(t) = A_v(s) \times V_{in}(t)$$

$$= (\frac{1000}{\sqrt{2}} \angle -5.137^\circ) \times (1 \angle 0^\circ)$$

$$= \frac{1000}{\sqrt{2}} \angle -5.137^\circ$$

$$\Rightarrow V_{out}(t) = 707.107 \cos(2\pi \times 1000t - 5.137^\circ)$$

$$|V_{out}| = 20 \log(707.107) = 57 \text{ dB}$$

#

10.44

p.12

$$V_{in}(t) = 1 \angle 0^\circ, \quad \omega = 2000\pi$$

$$A_v(s) = \frac{10^4}{1 + \frac{200\pi}{s}}$$

$$A_v(j2000\pi) = \frac{10^4}{1 + \frac{1}{j10}}$$

$$|A_v(j2000\pi)| = \frac{10^4}{\sqrt{1 + \frac{1}{100}}} = 9950.37$$

$$\angle A_v(j2000\pi) = \angle 10^4 - \tan^{-1} \frac{1}{10} = +5.71$$

$$\text{Phasor form: } A_v(s) = 9950.37 \angle 5.71$$

$$V_{out}(t) = A_v(s) \times V_{in}(t)$$

$$= (9950.37 \angle 5.71) \times (1 \angle 0^\circ)$$

$$= 9950.37 \angle 5.71$$

$$\Rightarrow V_{out}(t) = 9950.37 \cos(2\pi \times 1000t + 5.71^\circ)$$

$$|V_{out}| = 20 \log 9950.37 = 80 \text{ dB}$$

#

P13

10.45

✓

$$V_{in}(t) = 1 \angle 0^\circ, \quad W = 2000\pi$$

$$A_v(s) = \frac{10^4}{1 + \frac{s}{2000\pi}}$$

$$A_v(j2000\pi) = \frac{10^4}{1 + j10}$$

$$|A_v(j2000\pi)| = \frac{10^4}{\sqrt{1 + 10^2}} = 995.04$$

$$\angle A_v(j2000\pi) = \angle 10^4 - \tan^{-1} \frac{100}{1} = -89.43^\circ$$

Phasor form: $A_v(s) = 995.04 \angle -89.43^\circ$

$$V_{out}(t) = A_v(s) \times V_{in}(t)$$

$$= (995.04 \angle -89.43^\circ) \times 1 \angle 0^\circ$$

$$= 995.04 \angle -89.43^\circ$$

$$\Rightarrow V_{out}(t) = 995.04 \cos(2\pi \times 1000t - 89.43^\circ)$$

*

$$|V_{out}| = 20 \log(995.04) = 60 \text{ dB}$$

10.46

$$V_{in}(t) = 1 \angle 0^\circ, \quad \omega = 2000\pi$$

✓

$$A_v(s) = - \frac{10^7 s}{s^2 + 10^5 s + 10^{14}} = - \frac{10^7}{s + 10^5 + \frac{10^{14}}{s}}$$

$$A_v(j2000\pi) = \frac{-10^7}{j2000\pi + 10^5 + \frac{10^{14}}{j2000\pi}} = \frac{-10^7}{10^5 - j1.59 \times 10^6}$$

$$|A_v(j2000\pi)| = \frac{10^7}{\sqrt{(10^5)^2 + (1.59 \times 10^6)^2}} = 0.00063$$

$$\angle A_v(j2000\pi) = \angle -10^7 - \tan^{-1} \frac{1.59 \times 10^6}{10^5}$$

$$= -90^\circ$$

phasor form $A_v(s) = 0.00063 \angle -90^\circ$

$$V_{out}(t) = A_v(s) \times V_{in}(t)$$

$$= (0.00063 \angle -90^\circ) \times (1 \angle 0^\circ)$$

$$= 0.00063 \angle -90^\circ$$

$$\Rightarrow \boxed{V_{out}(t) = 0.00063 \cos(2\pi \times 1000 t - 90^\circ)} \quad \#$$

$$|V_{out}| = 20 \log 0.00063 = -64 \text{ dB}$$

P1.4
10.43

✓

p.15

$$A_V(s) = \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)}$$

Initial Value Theorem:

$$\begin{aligned} \lim_{t \rightarrow 0^+} A_V(t) &= \lim_{s \rightarrow \infty} s \times \frac{1}{s} A_V(s) \\ &= \lim_{s \rightarrow \infty} \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)} \\ &= \lim_{s \rightarrow \infty} \frac{10^3}{(s + 20\pi) \left(\frac{1}{2\pi \times 10^7} + \frac{1}{s \times 10^3} \right)} \\ &= \boxed{\cancel{1000}} \# \lim_{s \rightarrow \infty} = 0 \end{aligned}$$

($\infty \times \frac{1}{\infty} = 1$)

Final Value Theorem:

$$\begin{aligned} \lim_{t \rightarrow \infty} A_V(t) &= \lim_{s \rightarrow 0} s \times \frac{1}{s} A_V(s) \\ &= \lim_{s \rightarrow 0} \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)} \\ &= \lim_{s \rightarrow 0} \frac{10^3}{(s + 20\pi) \left(\frac{1}{2\pi \times 10^4} + \frac{1}{s} \right)} \\ &= \frac{10^3}{20\pi \times \infty} \\ &= \boxed{0} \# \end{aligned}$$

10.44

$$A_v(s) = \frac{10^4 s}{s + 200\pi}$$

✓

Initial Value Theorem:

$$\begin{aligned} \lim_{t \rightarrow 0^+} A_v(t) &= \lim_{s \rightarrow \infty} s \times \frac{1}{s} A_v(s) \\ &= \lim_{s \rightarrow \infty} \frac{10^4 s}{s + 200\pi} = \lim_{s \rightarrow \infty} \frac{10^4}{1 + \frac{200\pi}{s}} \\ &= \boxed{10^4} \# \end{aligned}$$

Final value Theorem:

$$\begin{aligned} \lim_{t \rightarrow \infty} A_v(t) &= \lim_{s \rightarrow 0} s \times \frac{1}{s} A_v(s) \\ &= \lim_{s \rightarrow 0} \frac{10^4 s}{s + 200\pi} = \lim_{s \rightarrow 0} \frac{10^4}{1 + \frac{200\pi}{s}} \rightarrow \infty \\ &= \boxed{0} \# \end{aligned}$$

10.45

✓

$$A_v(s) = \frac{2\pi \times 10^6}{s + 200\pi}$$

Initial value Theorem:

$$\begin{aligned} \lim_{t \rightarrow 0^+} A_v(t) &= \lim_{s \rightarrow \infty} s \times \frac{1}{s} A_v(s) = \lim_{s \rightarrow \infty} \frac{2\pi \times 10^6}{s + 200\pi} \rightarrow 0 \\ &= \boxed{0} \# \end{aligned}$$

Final value Theorem:

$$\lim_{t \rightarrow \infty} A_v(t) = \lim_{s \rightarrow 0} \frac{2\pi \times 10^6}{s + 200\pi} = \frac{10^4}{\frac{s}{200\pi} + 1} = \boxed{10^4} \#$$

10.46

✓

P.17

$$A_v(s) = - \frac{10^7 s}{s^2 + 10^5 s + 10^{10}}$$

Initial value Theorem:

$$\begin{aligned} \lim_{t \rightarrow 0^+} A_v(t) &= \lim_{s \rightarrow \infty} s \times \frac{1}{s} A_v(s) \\ &= \lim_{s \rightarrow \infty} \frac{-10^7 s}{s^2 + 10^5 s + 10^{10}} \\ &= \lim_{s \rightarrow \infty} \frac{-1}{\frac{s}{10^7} + \frac{1}{10^2} + \frac{10^7}{s}} \\ &= \boxed{-1} \# \end{aligned}$$


Final value Theorem:

$$\begin{aligned} \lim_{t \rightarrow \infty} A_v(t) &= \lim_{s \rightarrow 0} s \times \frac{1}{s} A_v(s) \\ &= \lim_{s \rightarrow 0} \frac{-10^7 s}{s^2 + 10^5 s + 10^{10}} \\ &= \lim_{s \rightarrow 0} \frac{-1}{\frac{s}{10^7} + \frac{1}{10^2} + \frac{10^7}{s}} \rightarrow \infty \\ &= \boxed{0} \# \end{aligned}$$

P1.5

P1.18


a)

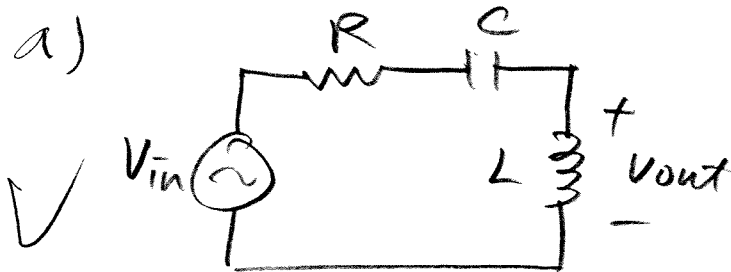

Using voltage divider

$$\frac{V_{out}}{V_{in}} = \frac{sL}{R + \frac{1}{sC} + sL} = \frac{s^2 L C}{1 + sRC + s^2 L C}$$

b)

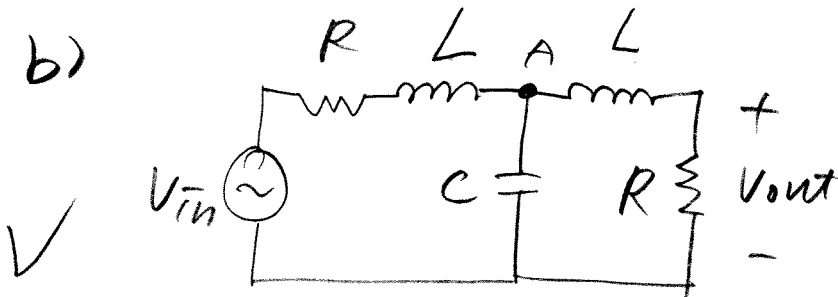

① Find V_A

$$V_A = V_{in} \times \frac{(R + sL) \parallel \frac{1}{sC}}{R + sL + [(R + sL) \parallel \frac{1}{sC}]}$$

$$\frac{R + sL}{1 + sC(R + sL)}$$

$$V_A = V_{in} \frac{(R + sL)}{(R + sL)(1 + sC(R + sL)) + (R + sL)} \cdot \frac{1}{1}$$

$$= V_{in} \frac{1}{2 + sC(R + sL)}$$

② Find $V_{out} = f(V_A)$

$$V_{out} = V_A \times \frac{R}{R + sL}$$


③ Substitute V_A

$$V_{out} = V_{in} \times \frac{1}{2 + sC(R + sL)} \times \frac{R}{R + sL}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{R}{(2 + sC(R + sL))(R + sL)}} \quad \#$$

c)

✓

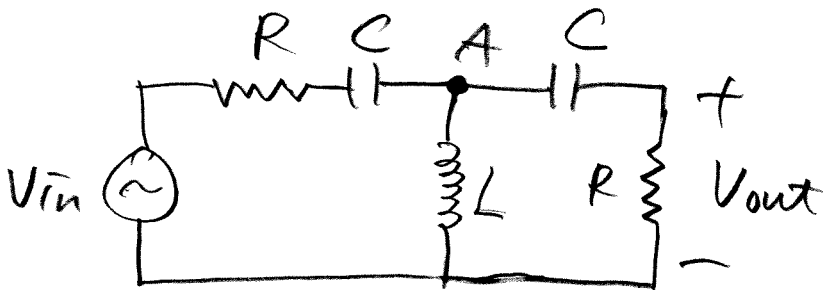

① Find V_A

$$V_A = V_{in} \times \frac{sL \parallel (R + \frac{1}{sC})}{(R + \frac{1}{sC}) + (sL \parallel (R + \frac{1}{sC}))}$$

$$\frac{sL(R + \frac{1}{sC})}{sL + R + \frac{1}{sC}}$$

$$V_A = V_{in} \times \frac{sL(R + \frac{1}{sC})}{(R + \frac{1}{sC})(sL + R + \frac{1}{sC}) + sL(R + \frac{1}{sC})}$$

$$= V_{in} \times \frac{sL}{(sL + R + \frac{1}{sC}) + sL} = V_{in} \frac{s^2 L C}{1 + sRC + 2s^2 L C}$$


② Find V_{out}

$$V_{out} = V_A \times \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{1 + sRC} V_A$$

③ Substitute V_A

$$\frac{V_{out}}{V_{in}} = \frac{sRC}{1 + sRC} \times \frac{s^2 L C}{1 + sRC + 2s^2 L C} = \frac{s^3 R L C^2}{(1 + sRC + 2s^2 L C)(1 + sRC)}$$

d)

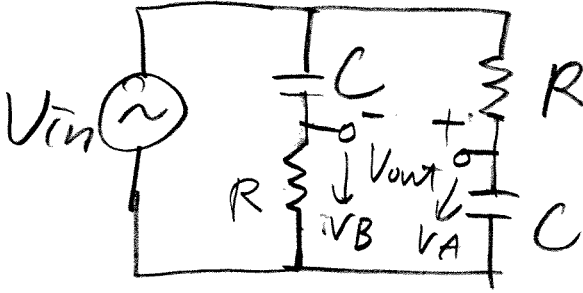

$$V_{out} = V_A - V_B$$

$$= V_{in} \times \frac{\frac{1}{sC}}{\frac{1}{sC} + R} - V_{in} \times \frac{R}{R + \frac{1}{sC}}$$

$$= V_{in} \times \left(\frac{1}{1 + R s C} - \frac{R s C}{R s C + 1} \right)$$



$$\boxed{\frac{V_{out}}{V_{in}} = \frac{1 - R s C}{1 + R s C}} \quad \#$$

P1.6

a)

✓

$$A_v = \frac{1}{1 + \frac{s}{10^3}}$$

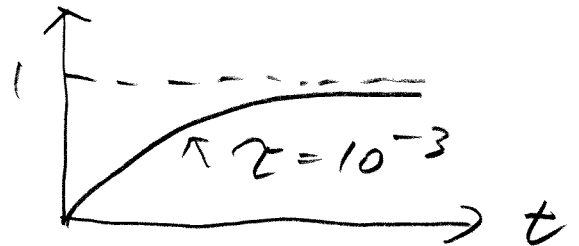
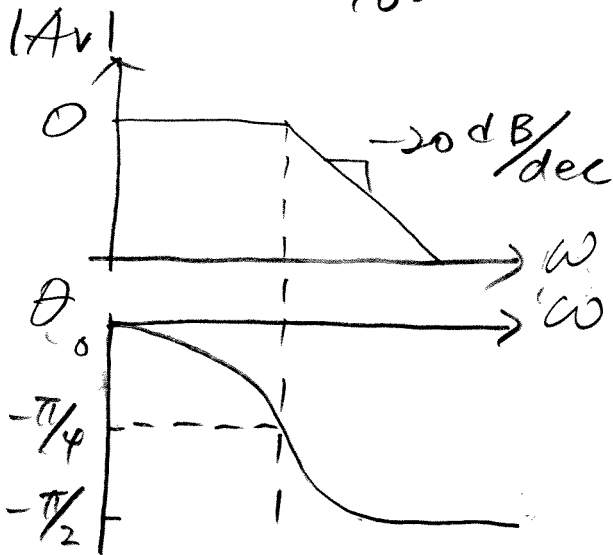


P. 21



b)

✓

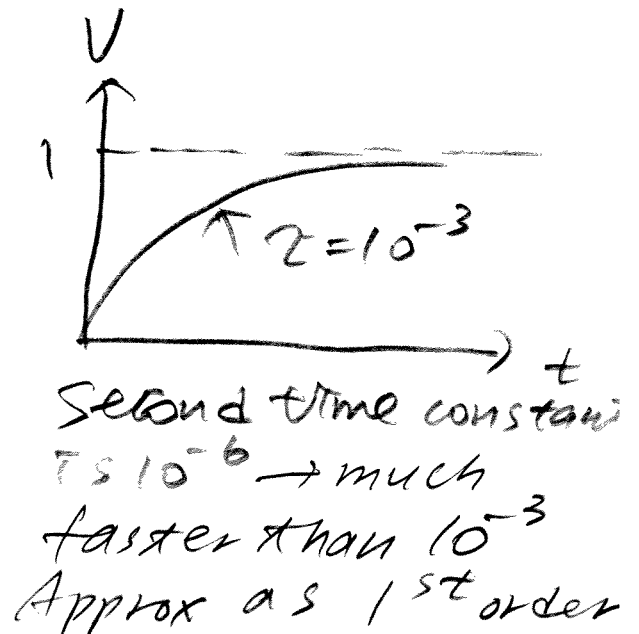
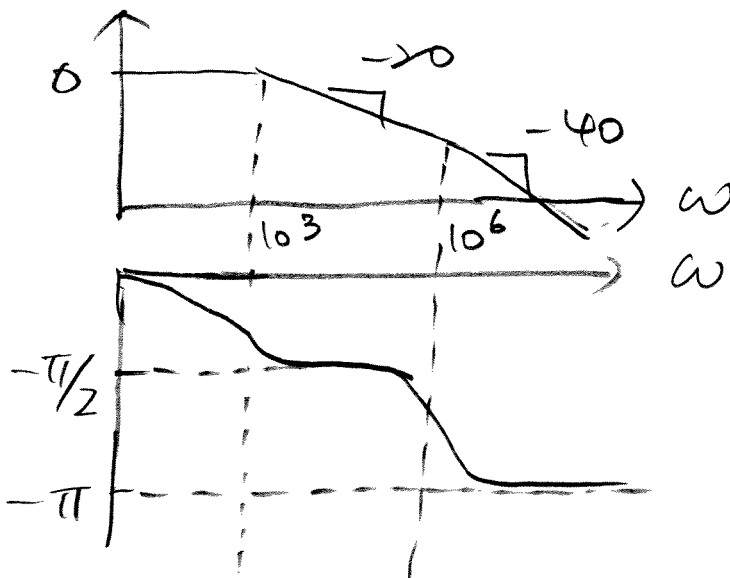
$$A_v = \frac{1}{(1 + \frac{s}{10^3})(1 + \frac{s}{10^6})}$$



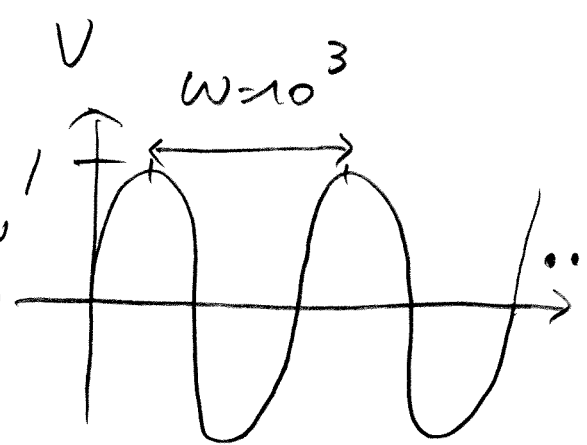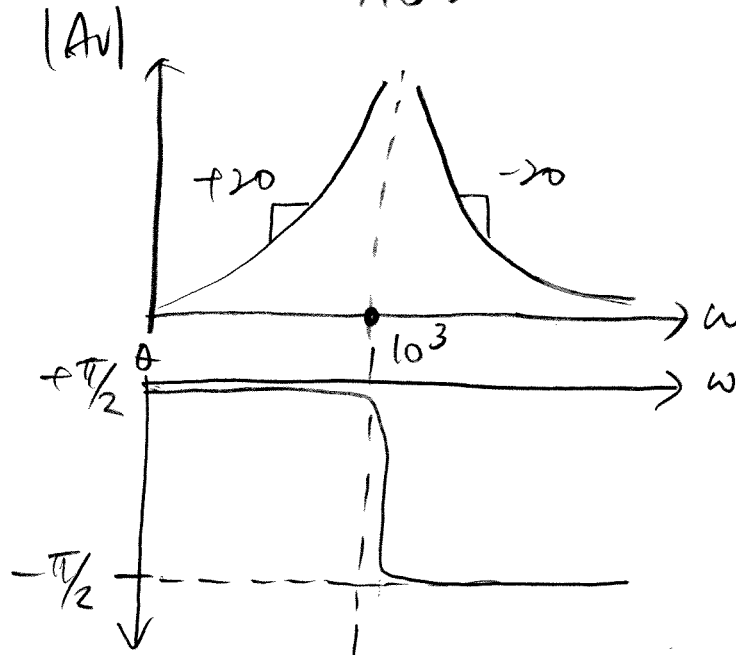c) $A_v = \frac{s/10^3}{1 + (s/10^3)^2}$, $Q = \infty$



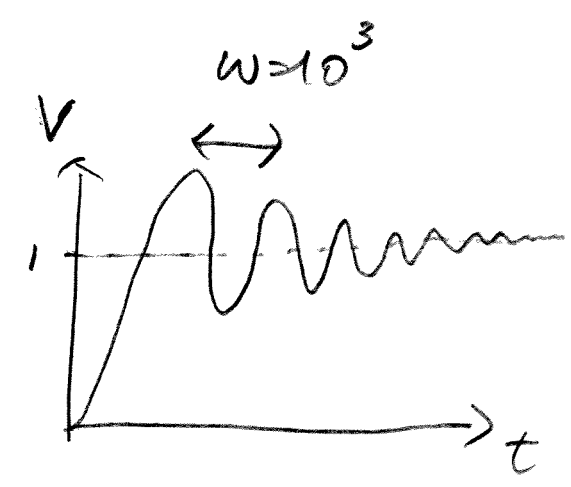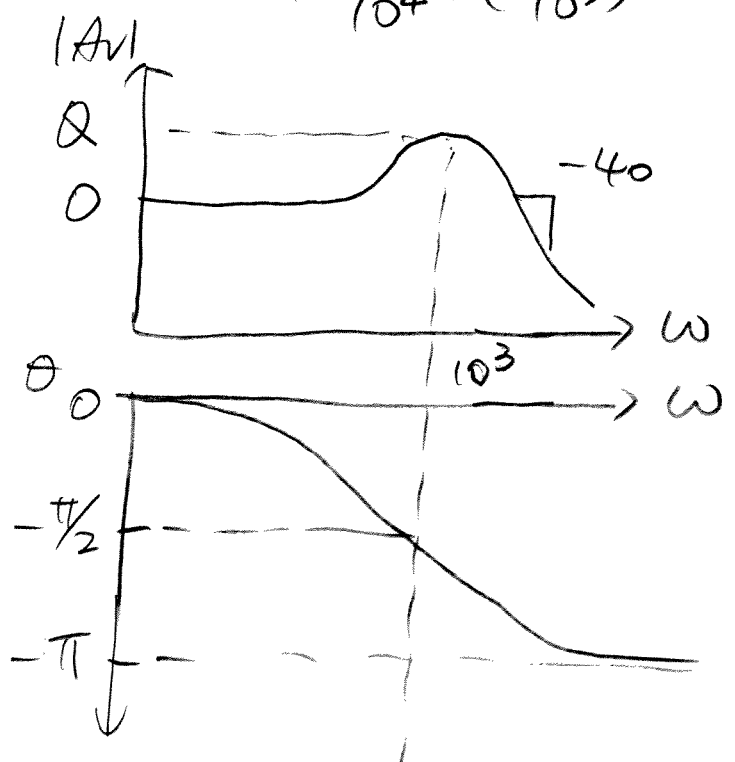
d) $A_v = \frac{1}{1 + \frac{s}{10^4} + (\frac{s}{10^3})^2}$, $Q = 10$



P1.7
a) 11.37

✓

17.13

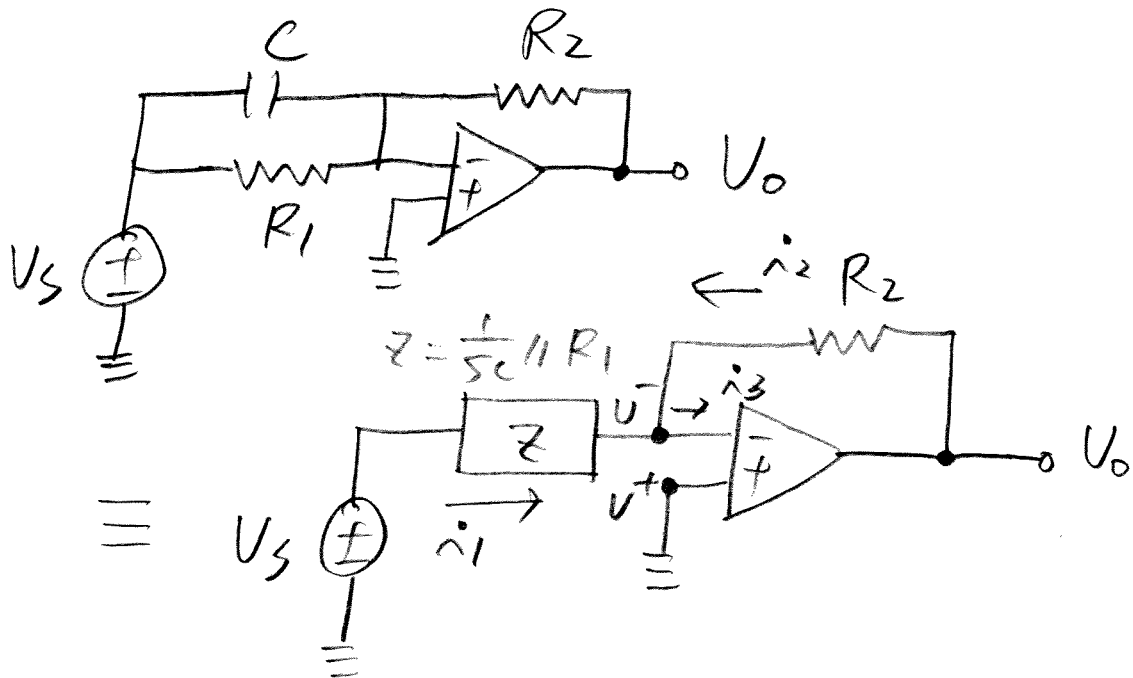

$$\dot{i}_1 + \dot{i}_2 = \dot{i}_3$$

∵ ideal opamps

$$\dot{i}_3 = 0, \quad V^- = V^+ = 0$$

$$\Rightarrow \dot{i}_1 = \frac{V_s}{\frac{1}{sC} \parallel R_1}$$

$$\dot{i}_2 = \frac{V_o}{R_2}$$

$$\therefore \dot{i}_1 + \dot{i}_2 = 0 \Rightarrow \dot{i}_1 = -\dot{i}_2$$


$$\therefore \frac{V_s}{\frac{1}{sC} \parallel R_1} = -\frac{V_o}{R_2}$$

$$\Rightarrow \frac{V_o(s)}{V_s(s)} = -\frac{R_2}{\frac{1}{sC} \parallel R_1} = \frac{-R_2}{\frac{\frac{R_1}{sC}}{\frac{1}{sC} + R_1}}$$

$$= -\frac{R_2}{\frac{R_1}{1 + R_1 sC}}$$

$$= \left[-\frac{R_2}{R_1} (1 + R_1 sC) \right]_{\#}$$

b) 11.39 find voltage gain only

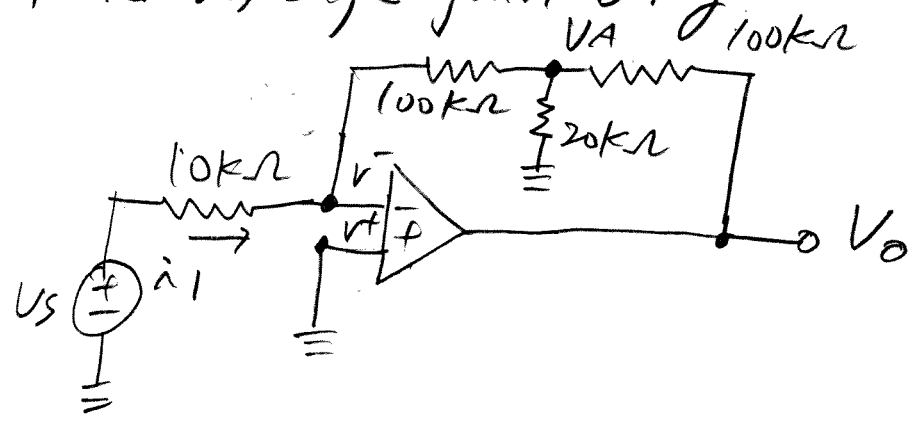

(∵ ideal opamps ∴ $V^- = V^+ = 0$)

$$i_1 = \frac{V_s}{10k}, \quad V_A = V^- - 100k i_1 = -10 V_s$$

KCL @ V_A :

$$\frac{V_A}{20k} + \frac{(V_A - V_o)}{100k} + \frac{V_A}{100k} = 0$$

$$\Rightarrow \frac{-10 V_s}{20k} + \frac{(-10 V_s - V_o)}{100k} - \frac{10 V_s}{100k} = 0$$

$$\Rightarrow \frac{-V_s}{2k} - \frac{V_s}{10k} - \frac{V_o}{100k} - \frac{V_s}{10k} = 0$$


$$\Rightarrow \frac{V_o}{100k} = -\left(\frac{1}{2k} + \frac{1}{10k} + \frac{1}{10k}\right) V_s$$

$$\Rightarrow V_o = -\left(\frac{5+2}{10k}\right) \times 100k \times V_s$$

$$\Rightarrow \boxed{\frac{V_o}{V_s} = -70} \quad \#$$

c) 11.42(a)

✓

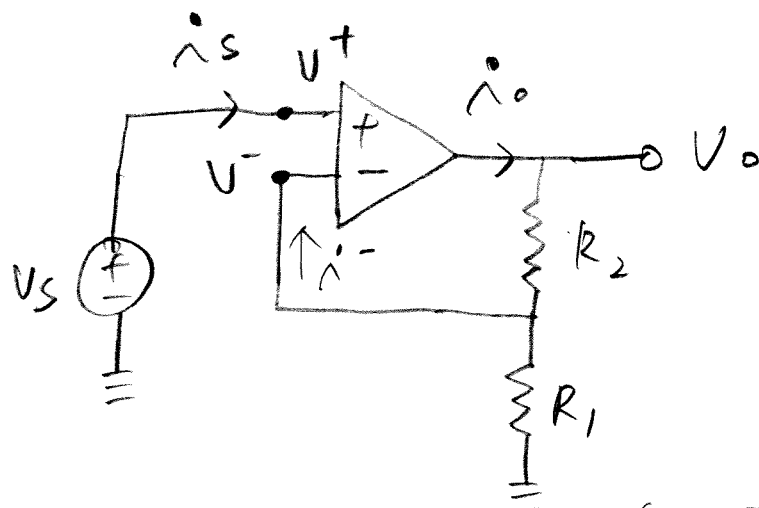


For ideal opamps: $V^+ = V^- = V_s$, $i^- = 0$

$$V_s = \frac{R_1}{R_1 + R_2} V_o$$

$$\Rightarrow \boxed{\frac{V_o}{V_s} = \frac{R_1 + R_2}{R_1}} \#$$

11.42(b)

✓

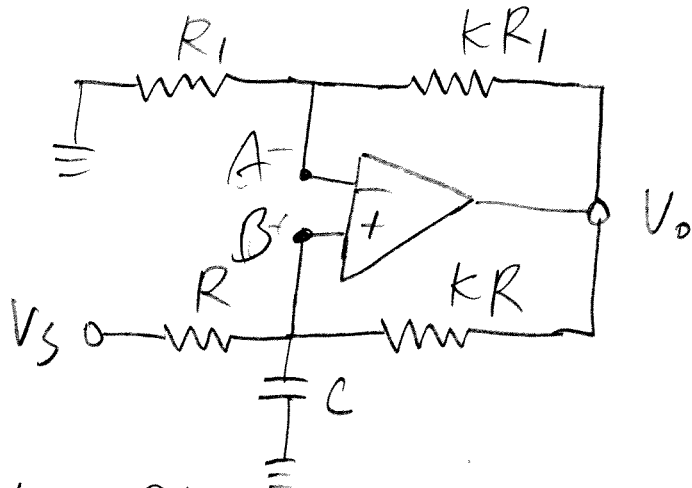

$$V_A = V_o \frac{R_1}{R_1 + kR_1}$$

$$= V_o \frac{1}{1+k} = V_B$$

KCL @ B

$$\frac{V_B - V_s}{R} + \frac{V_B - V_o}{kR} + \frac{V_B}{sC} = 0$$


$$\left(\frac{1}{R} + \frac{1}{kR} + sC\right) V_B - \frac{V_o}{kR} = \frac{V_s}{R}$$

$$\left[\left(\frac{k+1+sCkR}{kR}\right)\left(\frac{1}{1+k}\right) - \frac{1}{kR}\right] V_o = \frac{V_s}{R}$$

$$\Rightarrow \frac{\cancel{k+1} + sC\cancel{kR} - 1 - \cancel{k}}{\cancel{k}(1+k)} V_o = \frac{V_s}{R} \Rightarrow \boxed{\frac{V_o}{V_s} = \frac{1+k}{sCkR}} \#$$

2) 11.45(a)

✓

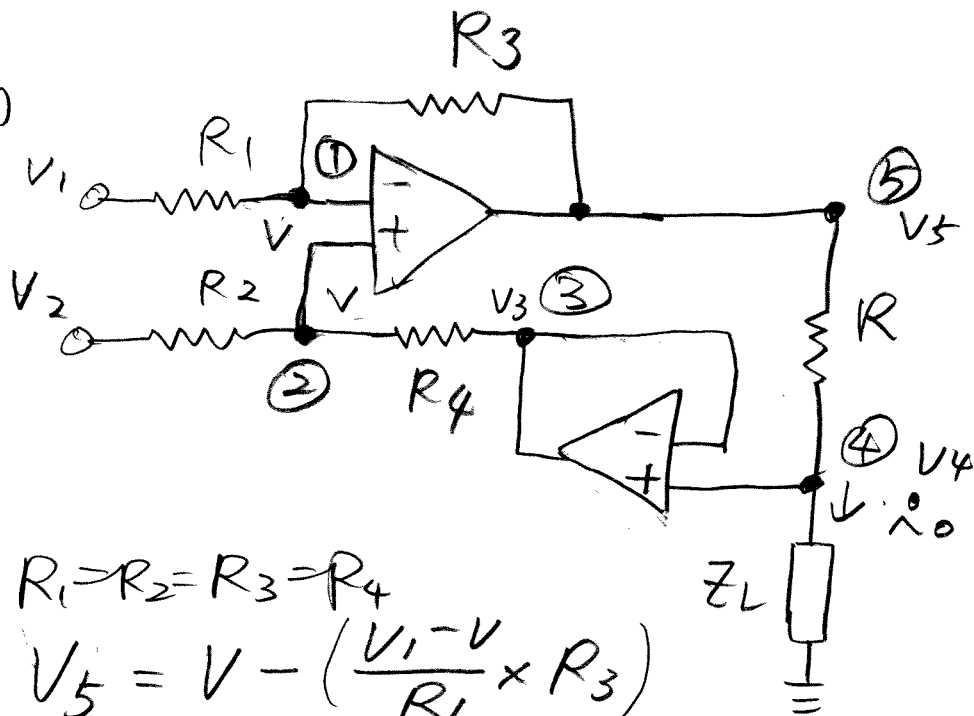

$$R_1 = R_2 = R_3 = R_4$$

$$V_5 = V - \left(\frac{V_1 - V}{R_1} \times R_3 \right)$$

$$= \left(1 + \frac{R_3}{R_1} \right) V - \frac{R_3}{R_1} V_1 = 2V - V_1$$


$$V_3 = V_4 = V - \left(\frac{V_2 - V}{R_2} \times R_4 \right)$$

$$= \left(1 + \frac{R_4}{R_2} \right) V - \frac{R_4}{R_2} V_2 = 2V - V_2$$

$$i_o = \frac{V_5 - V_4}{R} = \frac{2V - V_1 - 2V + V_2}{R} = \frac{V_2 - V_1}{R}$$

$$\Rightarrow \boxed{i_o = \frac{V_2 - V_1}{R}} \quad \#$$

e) 11.49
V

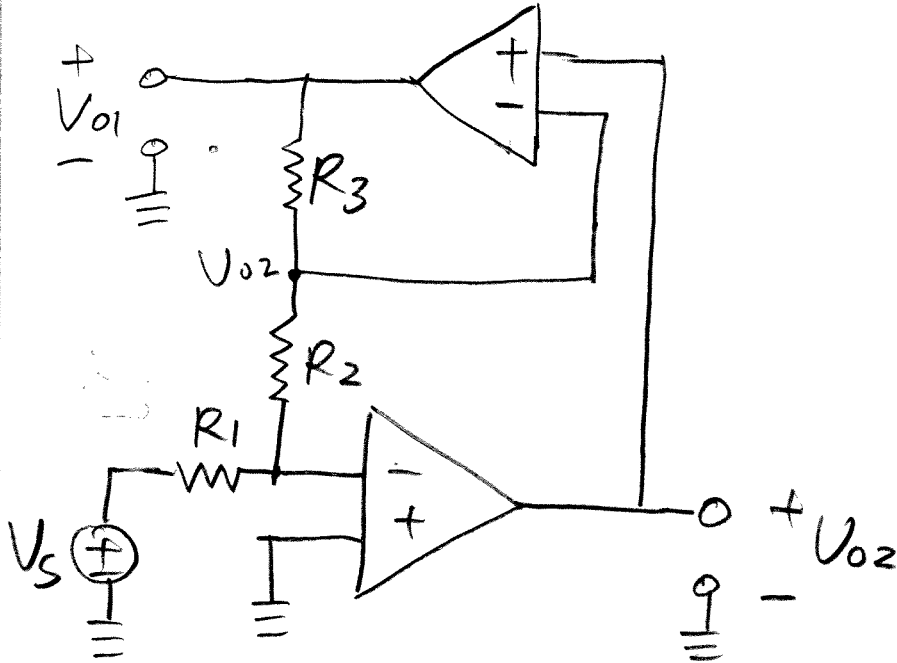

$$\frac{V_S}{R_1} = \frac{-V_{02}}{R_2} = \frac{V_{02} - V_{01}}{R_3}$$

$$\Rightarrow \boxed{V_{02} = -\frac{R_2}{R_1} V_S}$$

$$\frac{V_S}{R_1} = \frac{-\frac{R_2}{R_1} V_S - V_{01}}{R_3}$$

$$\Rightarrow V_S = \frac{-R_2 V_S - R_1 V_{01}}{R_3}$$

$$\Rightarrow -(R_2 + R_3) V_S = -R_1 V_{01}$$

$$\Rightarrow \boxed{V_{01} = -\frac{R_2 + R_3}{R_1} V_S}$$

#