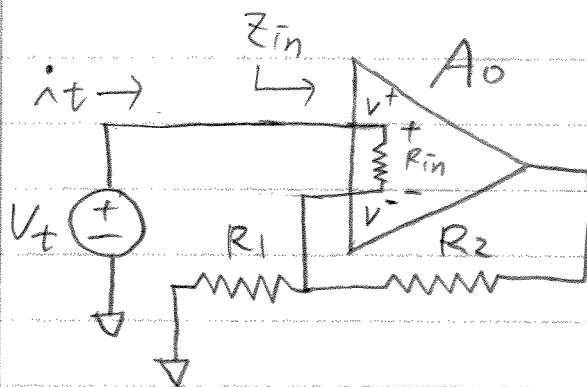


P3.1

EECS 311 PS3 Solution.

P. 1



$$V_o = A_o(V^+ - V^-)$$

$$V_t = V^+ \quad \text{--- ①}$$

$$V^- = V^+ - i_t R_{in} \quad \text{--- ②}$$

$$i_t + \frac{V_o - V^-}{R_2} = \frac{V^-}{R_1} \quad \text{--- ③}$$

plug ①, ② into ③

$$i_t + \frac{i_t R_{in} A_o - (V_t - i_t R_{in})}{R_2} = \frac{V_t - i_t R_{in}}{R_1}$$

$$i_t \left(1 + \frac{A_o R_{in}}{R_2} + \frac{R_{in}}{R_2} + \frac{R_{in}}{R_1} \right) = V_t \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$i_t \left(\frac{R_1 R_2 + A_o R_1 R_{in} + R_1 R_{in} + R_2 R_{in}}{R_1 R_2} \right) = V_t \frac{R_1 + R_2}{R_1 R_2}$$

$$\Rightarrow R_{in} = \frac{R_1 R_2 + R_1 R_{in} + R_2 R_{in} + A_o R_1 R_{in}}{R_1 + R_2} \quad (R_{in} \gg R_1, R_2)$$

$$\Rightarrow R_{in} \approx \frac{R_{in} (R_1 + R_2 + A_o R_1)}{R_1 + R_2}$$


$$\approx \boxed{R_{in} \left(1 + \frac{A_o R_1}{R_1 + R_2} \right)}$$

#

P.2

P3.2

a)

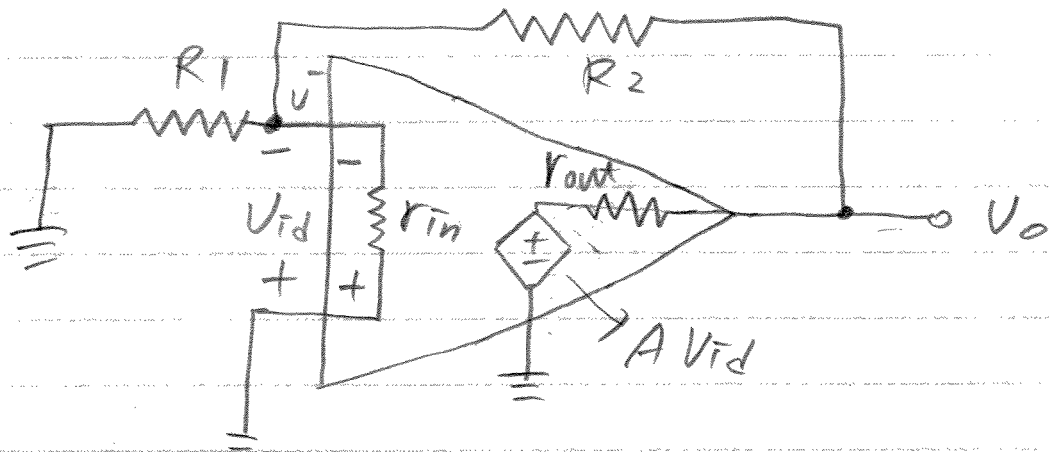

$$R_1 = 5.6 \text{ k}\Omega, R_2 = 47 \text{ k}\Omega, A = 100 \text{ dB} = 10^5$$

$$r_{in} = 400 \text{ k}\Omega, r_{out} = 200 \Omega, \beta = \frac{R_1}{R_1 + R_2} = 0.106$$

$$\Rightarrow R_{in} = R_1 + \left(r_{in} \parallel \frac{R_2}{1+A} \right)$$

$$= 5.6 \text{ k} + \left(400 \text{ k} \parallel \frac{47 \text{ k}}{1+10^5} \right)$$

$$\approx \boxed{5.6 \text{ k}\Omega} \#$$

$$\frac{V_o - 0}{R_2} = \frac{0 - V_x}{R_1} \Rightarrow \frac{V_o}{R_2} = -\frac{V_x}{R_1}$$

$$\Rightarrow A_v = \frac{V_o}{V_x} = -\frac{R_2}{R_1} = -\frac{47}{5.6} = \boxed{-8.39} \#$$

$$\Rightarrow R_{out} = \frac{R_o}{1+A\beta} = \frac{200}{1+10^5 \times 0.106} = \boxed{18.86 \text{ m}\Omega} \#$$

Appendix A3

Effect of resistor tolerance on CMRR of one amplifier differential circuit

In Figure A3.1 the amplifier is assumed ideal, resistors have tolerance $100 \times$ per cent per cent and worst case CMRR is considered. An input common mode signal e_{cm} gives rise to an output signal

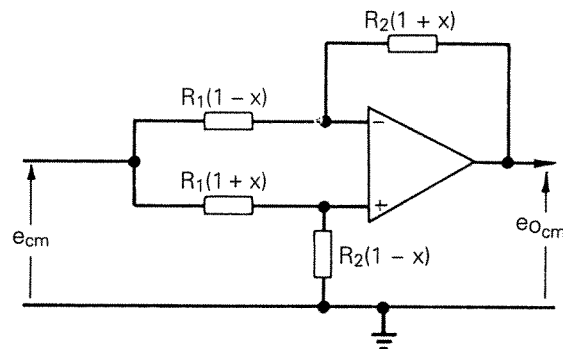


Figure A3.1 CMRR due to resistor tolerance with worst case distribution

$$\begin{aligned}
 e_{o_{cm}} &= e_{cm} \left[\frac{R_2(1-x)}{R_2(1-x) + R_1(1+x)} \frac{R_1(1-x) + R_2(1+x)}{R_1(1-x)} \right. \\
 &\quad \left. - \frac{R_2(1+x)}{R_1(1-x)} \right] \\
 &= e_{cm} \frac{R_2}{R_1} \left[\frac{R_1(1-x) + R_2(1+x)}{R_2(1-x) + R_1(1+x)} - \frac{1+x}{1-x} \right] \\
 &= e_{cm} \frac{R_2}{R_1} \frac{R_1 4x}{R_2(1-x)^2 + R_1(1+x^2)} \\
 &\cong e_{cm} \frac{R_2}{R_1} \frac{4x R_1}{R_2 + R_1}
 \end{aligned}$$

Thus common mode gain

$$\frac{e_{o_{cm}}}{e_{cm}} = \frac{R_2}{R_1} \frac{4x R_1}{R_2 + R_1}$$

$$\text{and CMRR} = \frac{\text{differential gain}}{\text{common mode gain}} \cong \frac{\frac{R_2}{R_1}}{\frac{R_2}{R_1} \frac{4x R_1}{R_2 + R_1}}$$

$$\text{CMRR} \cong \frac{1 + \frac{R_2}{R_1}}{4x} \quad (\text{A3.1})$$

A3.1 CMRR of one amplifier differential circuit due to non-infinite CMRR of operational amplifier

Common mode signal applied to op-amp

$$= e_{cm} \frac{R_2}{R_1 + R_2} \quad (\text{see Figure A3.2})$$

Non-infinite CMRR of an op-amp is represented by an equivalent input error signal $e_{\epsilon_{cm}}$ applied directly to the input terminal of the op-amp

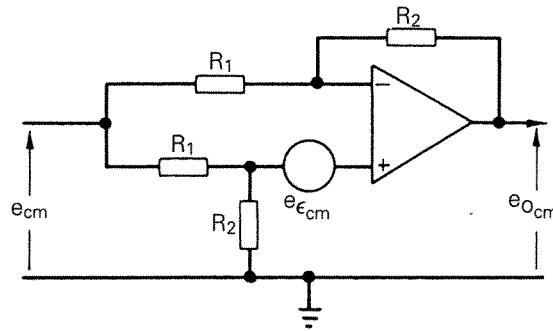


Figure A3.2 CMRR of circuit due to non-infinite CMRR of amplifier

$$e_{\epsilon_{cm}} = \frac{e_{cm} \frac{R_2}{R_1 + R_2}}{\text{CMRR}_{(A)}}$$


$e_{\epsilon_{cm}}$ gives an output signal

$$e_{o_{cm}} = e_{\epsilon_{cm}} \left(1 + \frac{R_2}{R_1} \right)$$

Worst case consideration

P.3

P3.3

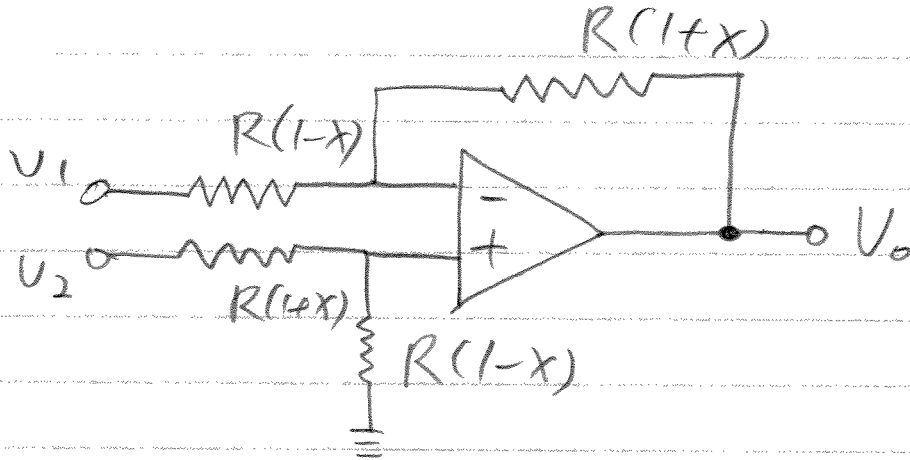

$$x = 0.05\%$$


CMRR (due to resistor tolerance)

$$= \frac{1 + \frac{R_2}{R_1}}{4x} = \frac{1 + 1}{4 \times 0.05\%} = 1000 = 60 \text{ dB}$$

#

P3.4

P.4

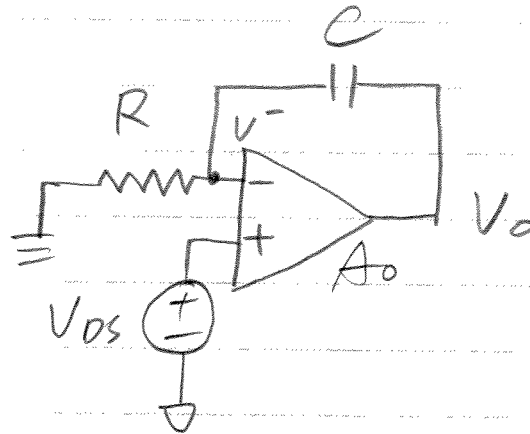

a)

$$V_O = A_O (V_{Os} - V^-)$$

$$\Rightarrow V^- = V_{Os} - \frac{V_O}{A_O}$$

$$\frac{V_O - V^-}{\frac{1}{sC}} = \frac{V^-}{R}$$

Substitue V^-

$$\Rightarrow V^- \left(\frac{1}{R} + sC \right) = sC V_O$$

$$\Rightarrow \left(V_{Os} - \frac{V_O}{A_O} \right) \left(\frac{1}{R} + sC \right) = sC V_O$$

$$\Rightarrow V_{Os} - \frac{V_O}{A_O} = \frac{sRC V_O}{1 + sRC}$$

$$\Rightarrow V_{Os} = V_O \left(\frac{sRC}{1 + sRC} + \frac{1}{A_O} \right) = V_O \left(\frac{sRC A_O + 1 + sRC}{A_O (1 + sRC)} \right)$$

$$\Rightarrow \frac{V_O}{V_{Os}} = \frac{A_O (1 + sRC)}{1 + sRC + sRC A_O} = \boxed{\frac{A_O (1 + sRC)}{1 + sRC (1 + A_O)}} \quad \#$$

b) at DC,

$$\frac{V_O}{V_{Os}} = \frac{A_O}{1} = A_O$$

$$\boxed{V_O = A_O V_{Os}} \quad \#$$

P3.5

P.5

Both inverting and noninverting amplifiers will have the same output resistance.

$$Z_{out} \approx \frac{R_o}{1 + A\beta}$$

$$A(s) = \frac{A_o}{1 + \frac{s}{\omega_B}}$$

Where ω_B = open loop bandwidth of the op amp.

$$Z_{out} = \frac{R_o}{1 + \frac{A_o\beta}{1 + \frac{s}{\omega_B}}} = \boxed{\frac{R_o(s + \omega_B)}{s + \omega_B(1 + A_o\beta)}}$$

#