

EECS 311 PS4 Solution

P.1

P4.1

$$f_M \leq \frac{SR}{2\pi V_{AS}}$$

$$\leq \frac{10 \frac{V}{\mu s}}{2\pi \times 10V}$$

$$\leq 159.16 \text{ kHz}$$

$$f_M = 159.16 \text{ kHz} \quad \#$$

P4.2

$$SR = \frac{\Delta V}{\Delta t} = \frac{20V}{2\mu s} = 10 \frac{V}{\mu s} \quad \#$$

P4.3

3.21

$$I_D = I_S (e^{\frac{V_D}{nV_T}} - 1)$$

pick the value from the graph

$$V_{D1} = 0.6V \Rightarrow I_{D1} = 10^{-4}A$$

$$V_{D2} = 0.2V \Rightarrow I_{D2} = 10^{-9}A$$

$$\frac{I_{D1}}{I_{D2}} = \frac{e^{\frac{V_{D1}}{nV_T}} - 1}{e^{\frac{V_{D2}}{nV_T}} - 1} \Rightarrow \frac{10^{-4}}{10^{-9}} = \frac{e^{\frac{0.6}{n(25m)}} - 1}{e^{\frac{0.2}{n(25m)}} - 1}$$

$$\Rightarrow n = 1.39 \quad \#$$

$$10^{-4} = I_S \times (e^{\frac{0.6}{1.39 \times 25m}} - 1)$$

$$\Rightarrow I_S = 3.17 \times 10^{-12} A$$

#

$$3.22 \quad I_s = 10^{-18} \text{ A}, n = 1.05$$

$$a) \quad I_D = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$70 \mu = 10^{-18} \left(e^{\frac{V_D}{1.05 \times 25 \text{ m}}} - 1 \right)$$

$$\Rightarrow \boxed{V_D = 0.836 \text{ V}} \#$$

$$b) \quad 5 \mu = 10^{-18} \left(e^{\frac{V_D}{1.05 \times 25 \text{ m}}} - 1 \right)$$

$$\Rightarrow \boxed{V_D = 0.767 \text{ V}} \#$$

$$c) \quad I_D = 10^{-18} \times (e^0 - 1) = \boxed{0 \text{ A}} \#$$

$$d) \quad I_D = 10^{-18} \times \left(e^{\frac{-0.075}{1.05 \times 25 \text{ m}}} - 1 \right)$$

$$= \boxed{-9.43 \times 10^{-19} \text{ A}} \#$$

$$e) \quad I_D = 10^{-18} \times \left(e^{\frac{-5}{1.05 \times 25 \text{ m}}} - 1 \right)$$


$$= \boxed{-1 \times 10^{-18} \text{ A}} \#$$

3.24 $I_s = 10^{-17} \text{ A}, n = 1$

a) $V_D = 0.675 \text{ V}$
 $I_D = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$
 $= 10^{-17} \left(e^{\frac{0.675}{1 \times 25 \text{ m}}} - 1 \right)$
 $= \boxed{5.32 \mu\text{A}} \#$

b) $5.32 \mu\text{A} \times 3 = 10^{-17} \times \left(e^{\frac{V_D}{1 \times 25 \text{ m}}} - 1 \right)$
 $\boxed{V_D = 0.7 \text{ V}} \#$

3.66

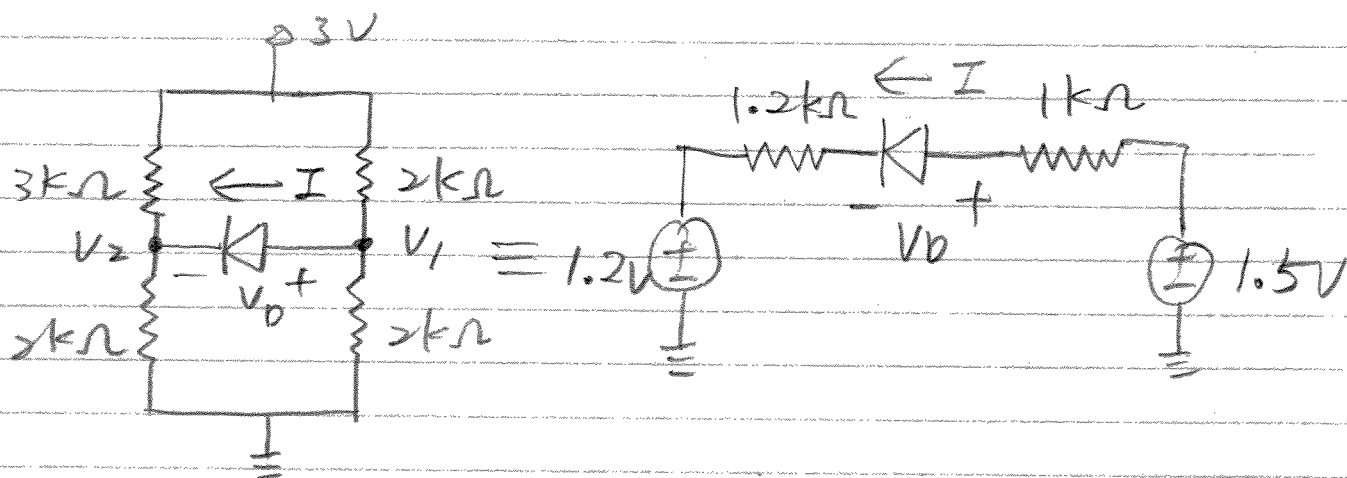

a) Ideal diode model (no voltage drop)


$V_D = 0$
 $I_D = \frac{1.5 - 1.2}{(1.2 + 1) \text{ k}} = 0.13 \text{ mA}$ #

b) constant voltage drop ($V_{on} = 0.6V$)

$$V_D = 0.6V$$

$$I_D = \frac{1.5 - 0.6 - 1.2}{(1.2 + 1)k} = -0.13mA$$

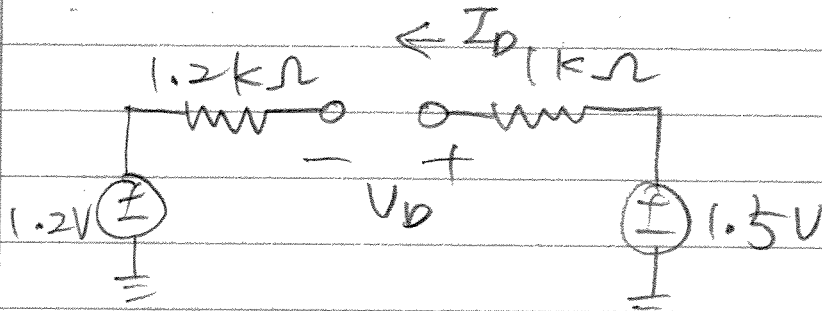The current is negative which violates the convention diode model when the diode is on. $\Rightarrow$ Diode is off




$$\therefore \boxed{I_D = 0A, V_D = 1.5 - 1.2 = 0.3V} \quad \#$$

c) The second model is more realistic. The voltage across the diode for b) is not sufficient to turn on the diode, so the resulting current will be really small.


3.69

p. 5

a)

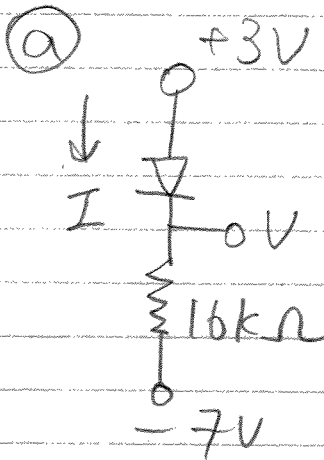

(b)

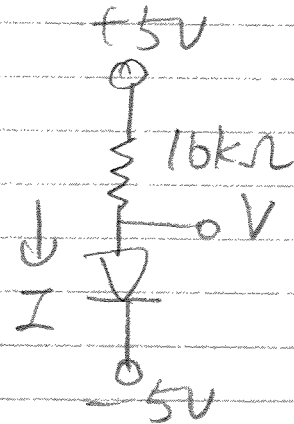

$$V = 3V$$

$$I = \frac{3 + 7}{16k} = 0.625mA$$


#

$$V = -5V$$

$$I = \frac{5 + 5}{16k} = 0.625mA$$

#

(c)

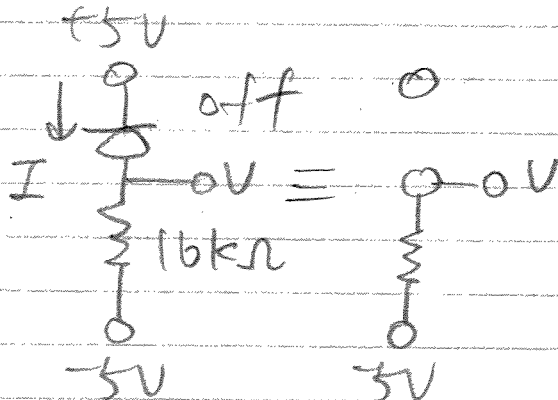


$$I = 0A$$

$$V = -5V$$

#

(d)

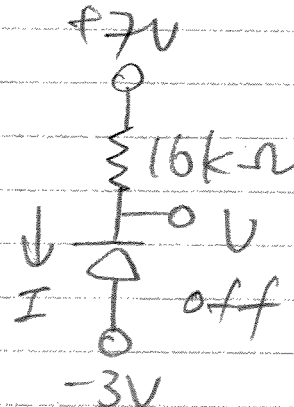

$$I = 0A$$


$$V = 7V$$

#

3.69

P. 6


b)

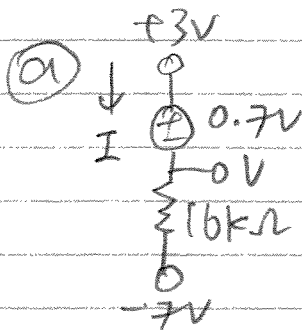

$$V = 2.2V$$

$$I = \frac{2.2 + 7}{16k} = 0.575mA$$


(b)

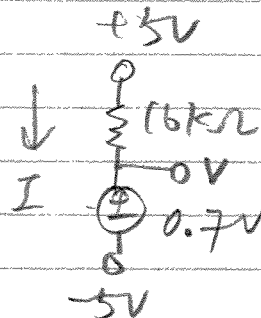

$$V = -5 + 0.7 = -4.3V$$

$$I = \frac{5 + 4.3}{16k} = 0.58mA$$


(c)

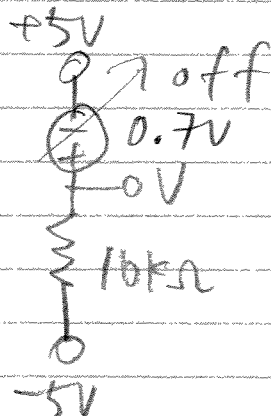

$$V = -5V$$

$$I = 0A$$

(d)

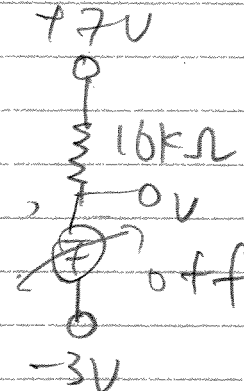


$$V = 7V$$

$$I = 0A$$

3.71

a)

①

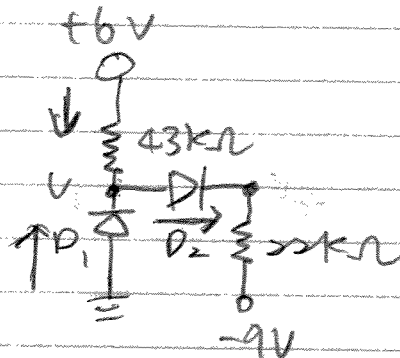Assume D_1 off, D_2 on $D_2: V_2 = 0, I_2 = \frac{15}{65k} = 0.23mA$ $\Rightarrow V_1 = -3.89V$ (D_1 should be on)Assume D_1 on, D_2 on $D_2: I_2 = \frac{0+9}{22k} = 0.409mA$ $V_2 = 0$ $D_1: V_1 = 0$

$$I_1 = \frac{6 - (-9 + 22 \times 0.409)}{43k} - 0.409$$

$$= -0.269mA$$

$$D_1: V_1 = 0$$


$$I_1 = 0.269mA$$

$$D_2: V_2 = 0$$

$$I_2 = 0.409mA$$

#

②

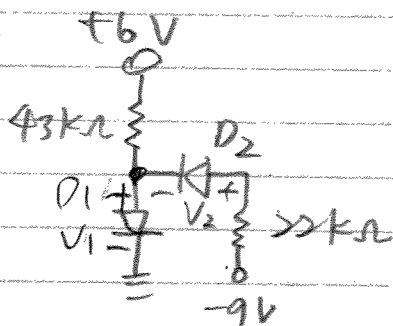Assume D_2 off, D_1 on $\checkmark D_1: V_1 = 0, I_1 = \frac{6}{43k} = 0.139mA$ Assume D_1 off, D_2 on (x)


$$D_1: V_1 = 0$$

$$I_1 = 0.139mA$$

$$D_2: V_2 = -9V$$

$$I_2 = 0A$$

#

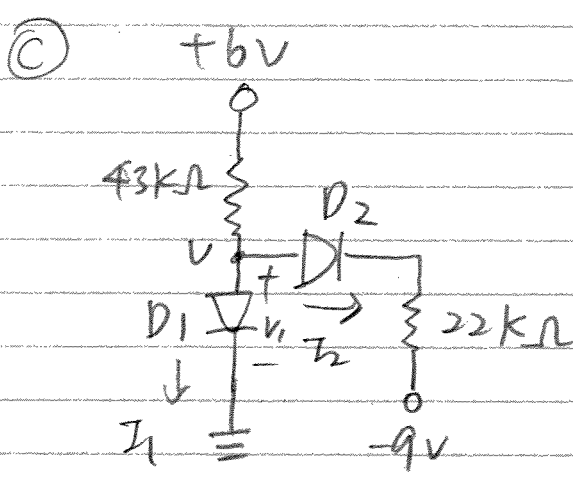


Assume D_1, D_2 are on
 $D_2: V_2 = 0$
 $I_2 = \frac{9}{22k} = 0.409 \text{ mA}$
 $D_1: V_1 = 0$
 $I_1 = \frac{6 - (-9 + 22k \times 0.409 \text{ mA})}{43k} - 0.409 \text{ mA}$
 $= -0.269 \text{ (mA)}$

$\Rightarrow D_1$ is off.
 Assume D_1 is off, D_2 is on
 $D_2: I_2 = \frac{6+9}{65k} = 0.23 \text{ mA}$

$D_1:$
 $V_1 = 6 - 43k \times 0.23 \text{ mA} = -3.89 \text{ V}$
 $I_1 = 0 \text{ A}$

$D_2:$
 $V_2 = 0 \text{ V}$
 $I_2 = 0.23 \text{ mA}$

#

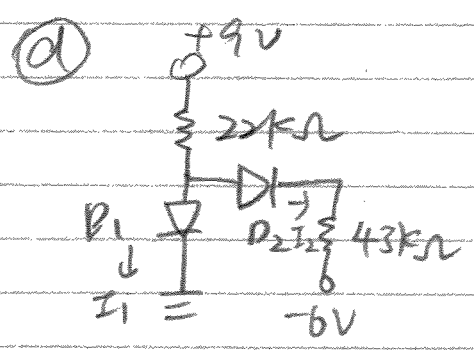

Assume all on
 $D_2: V_2 = 0$
 $I_2 = \frac{0+6}{43k} = 0.139 \text{ mA}$
 $D_1: V_1 = 0$
 $I_1 = \frac{9 - (-6 + 43k \times 0.139)}{22k} - 0.139 \text{ mA} = 0.27 \text{ mA}$


$D_1: V_1 = 0$
 $I_1 = 0.41 \text{ mA}$

$D_2: V_2 = 0$
 $I_2 = 0.27 \text{ mA}$

#

3.71

b)

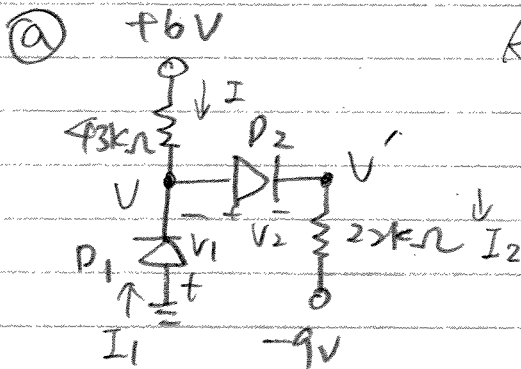

$$V_{on} = 0.75V$$

Assume D_1 on, D_2 on

$$V = -0.75V, I_1 = \frac{6 + 0.75}{43k} = 0.157mA$$


$$V' = -1.4V, I_2 = 0.345mA$$

$$D_1: V_1 = 0.75V$$

$$I_1 = 0.345 - 0.157 = 0.188mA$$

$$D_2: V_2 = 0.75V$$

$$I_2 = 0.345mA$$

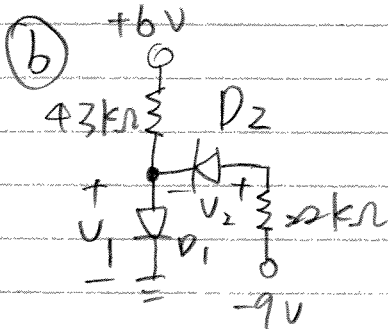Assume D_1 on, D_2 off


$$V_1 = 0.75V, I_1 = 0.122mA$$

$$D_1: V_1 = 0.75V$$

$$I_1 = 0.122mA$$

$$D_2: V_2 = -9.75V$$

$$I_2 = 0A$$

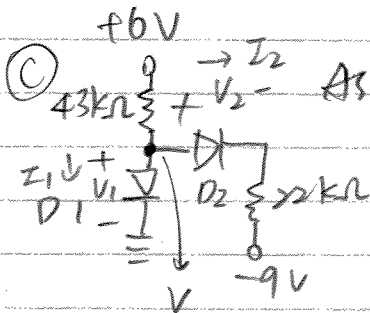Assume D_1 is off, D_2 is on

$$I_2 = \frac{(6 - 0.75 + 9)}{65k} = 0.219mA$$

$$V = 6 - 43k \times (0.219)m = -3.417V$$

Assumption was correct.


$$D_1: V_1 = -3.42V$$

$$I_1 = 0A$$

$$D_2: V_2 = 0.75V$$

$$I_2 = 0.219mA$$

P.10

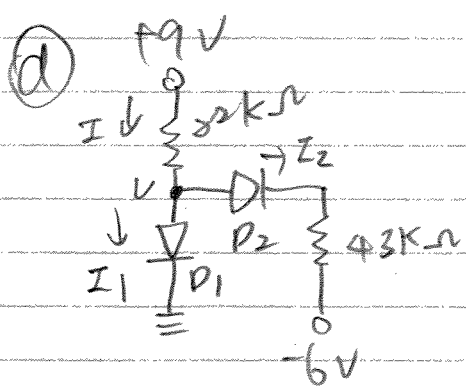


Assume D_1, D_2 are on
 $V = 0.75V$, $I = \frac{9 - 0.75}{22K} = 0.375mA$
 $I_2 = \frac{6}{43K} = 0.14mA$

$D_1: V_1 = 0.75V$ $I_1 = 0.235mA$ $D_2: V_2 = 0.75V$ $I_2 = 0.14mA$




#

3.98

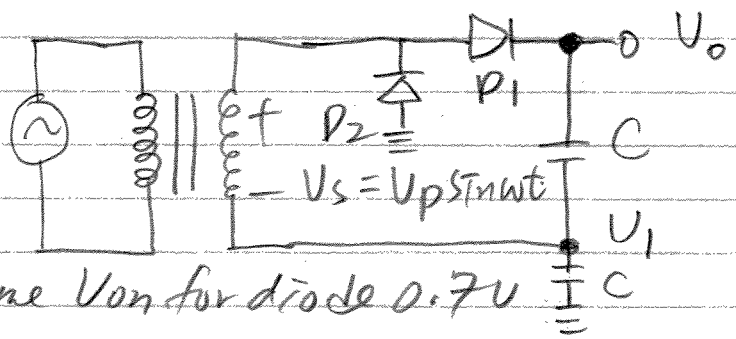

$V_p = 17$
 $V_c = 17 \sin wt$

Assume V_{on} for diode $0.7V$

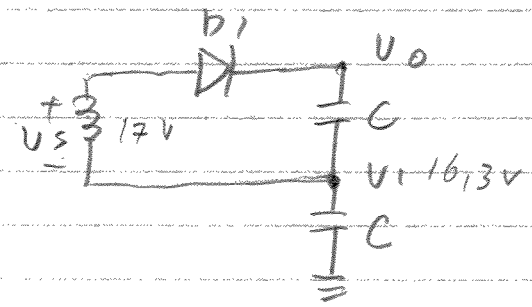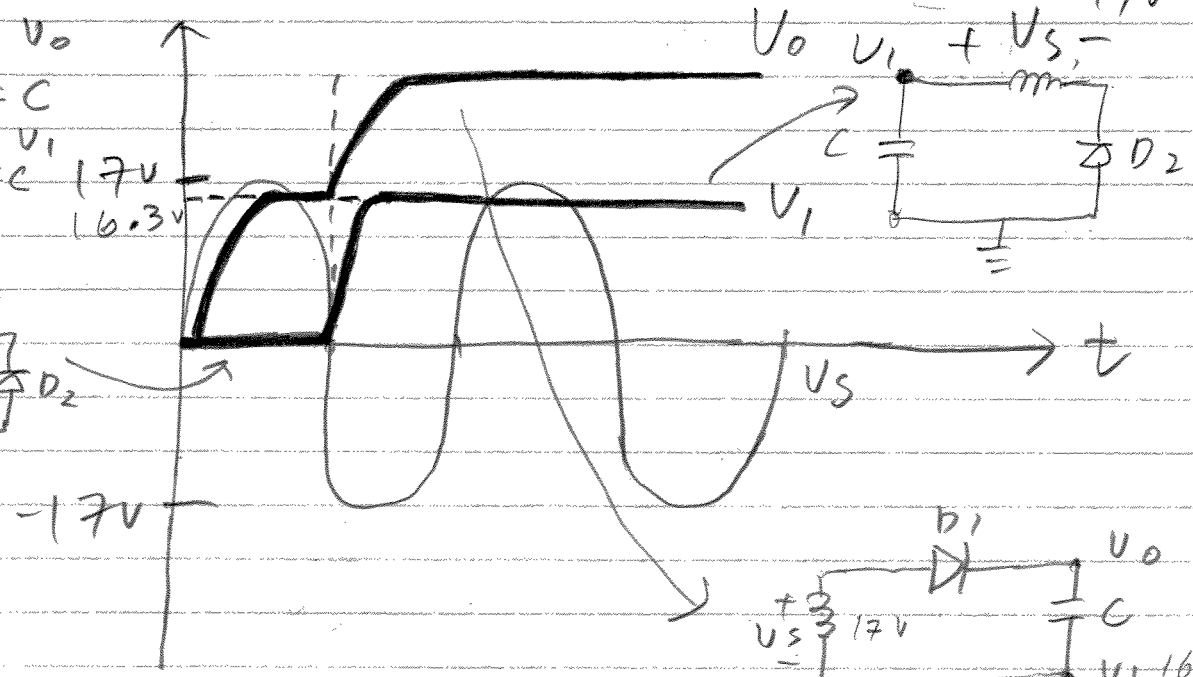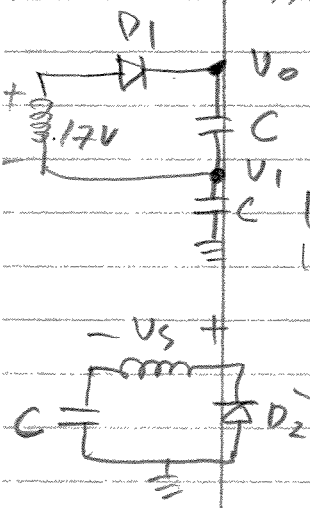

$$V_{DC} = 16.3 + 16.3$$

$$= \boxed{32.6V} \quad \#$$

$$3.119 \quad I_c = 1 - 10^{-15} [\exp(40V_c) - 1] \text{ A}$$

$$P = V_c I_c$$

$$= V_c \{1 - 10^{-15} [\exp(40V_c) - 1]\}$$

$P_{\max}$ occurs when $\frac{dP}{dV_c} = 0$

$$\frac{dP}{dV_c} = \{1 - 10^{-15} [\exp(40V_c) - 1]\}$$

$$+ V_c \times \{-10^{-15} [\exp(40V_c) - 1]\} \times 40 = 0$$





Solving V_c

$$\Rightarrow \boxed{\begin{array}{l} V_{oc} = 0.78 \text{ V} \\ I_{sc} = 0.96 \text{ A} \\ P_{\max} = 0.75 \text{ W} \end{array}}$$

#


11.91

p. 12

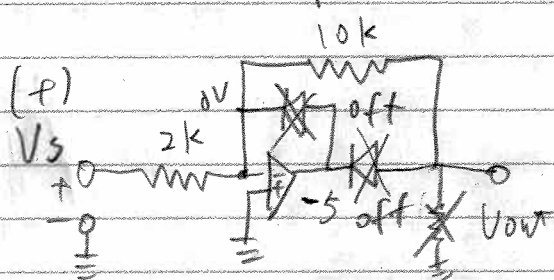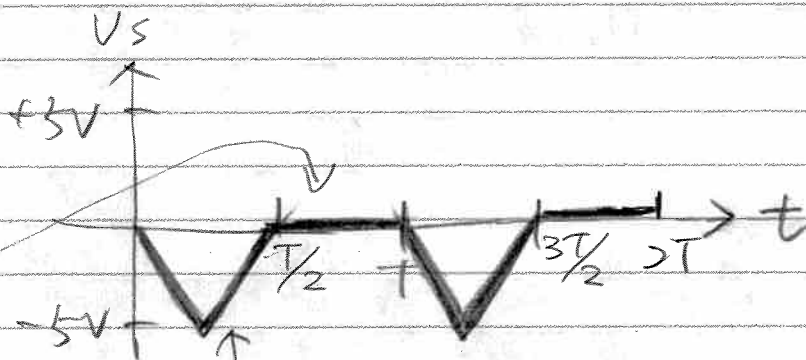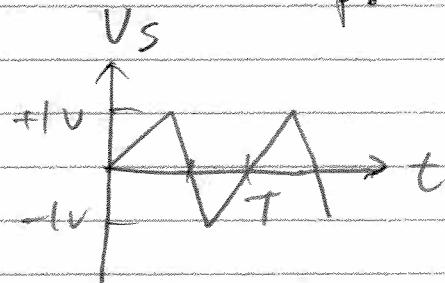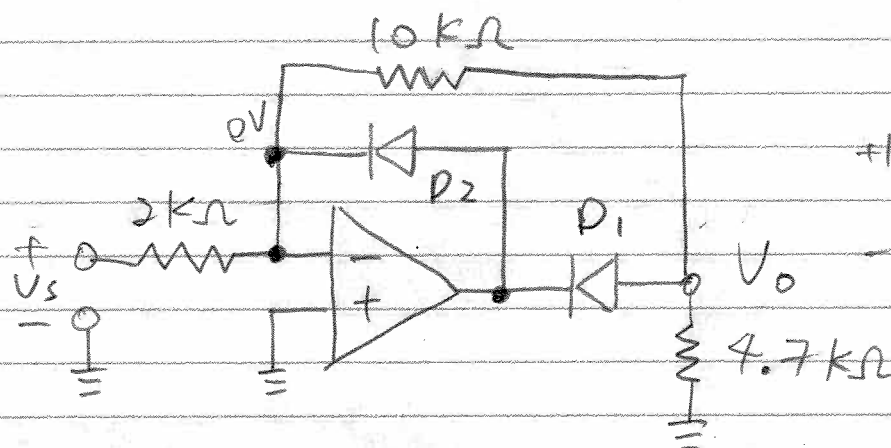

$$\frac{V_s}{2k} = \frac{-V_{out}}{10k}$$

$$\Rightarrow V_{out} = -5V_s$$

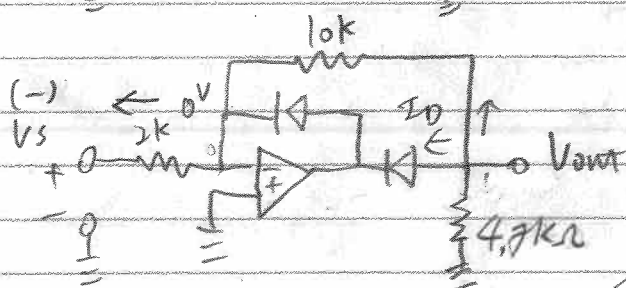

assumed diodes are on ($V_{out} = 1$)

$$I_D + \frac{1}{10k} + \frac{1}{4.7k} \neq 0$$

$\therefore$ diodes are off


assume diodes are off

$$\frac{V_{out}}{4.7k} + \frac{V_{out}}{10k} = 0$$

$$V_{out} = 0$$

P4.4

P.13

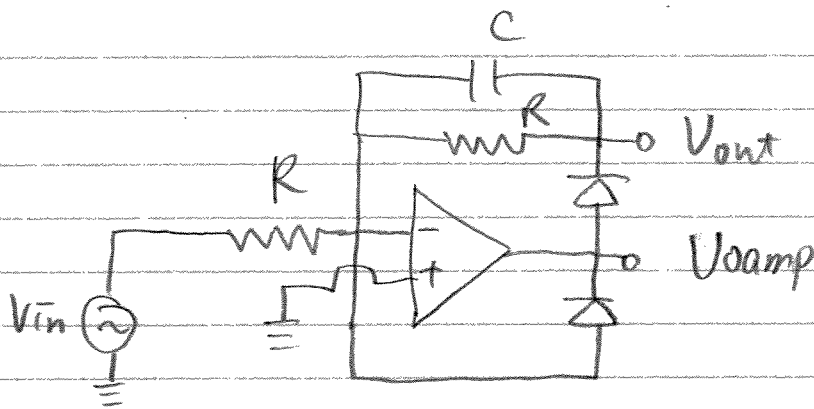

$$V_{in} = 0.5 \cos \omega t$$

$$V_{on} = 0.6 \text{ V}$$

