

EECS 311 PS5 Solution

P.1

P5.1

(a) For $V_{GS} = 0V$,
 $\Rightarrow$ cutoff region, $I_D = 0$ #

(b) For $V_{GS} = 1V$,
 $\Rightarrow$ cutoff region, $I_D = 0$ #

(c) For $V_{GS} = 2V$, $V_{DS} = 0.1V$
 $\Rightarrow V_{GS} - V_t > V_{DS} \Rightarrow$ triode region

$$I_D = K_n' \frac{W}{L} \left(V_{GS} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$= \left(250 \frac{\mu A}{V^2} \right) \left(\frac{10}{1} \right) \left(2 - 1 - \frac{0.1}{2} \right) (0.1) = 237.5 \mu A$$
 #

(d) For $V_{GS} = 3V$, $V_{DS} = 0.1V$
 $\Rightarrow V_{GS} - V_t = 2V > V_{DS} \Rightarrow$ triode region


$$I_D = K_n' \frac{W}{L} \left(V_{GS} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$= \left(250 \frac{\mu A}{V^2} \right) \left(\frac{10}{1} \right) \left(3 - 1 - \frac{0.1}{2} \right) (0.1)$$

$$= 987.5 \mu A$$
 #

(e) $K_n = K_n' \frac{W}{L} = 250 \frac{\mu A}{V^2} \times 10 = 2.5 \frac{mA}{V^2}$ #

P5.2
(a)

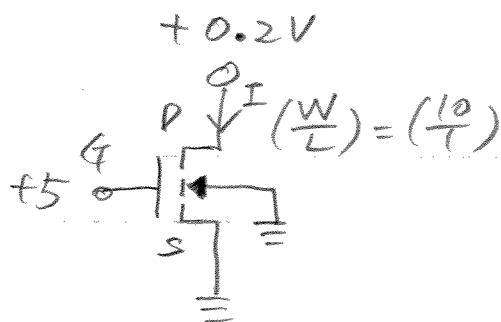

$$V_{GS} = V_G - V_S = 5V$$

$$V_{DS} = V_D - V_S = 0.2V$$

$$V_{GS} - V_{th} > V_{DS}$$


$$\Rightarrow \text{Triode region}$$

$$I = K_n' \frac{W}{L} \left(V_{GS} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$= \left(100 \frac{\mu A}{V^2} \right) \left(\frac{10}{1} \right) \left(5 - 0.7 - \frac{0.2}{2} \right) 0.2$$

$$= \boxed{840 \mu A} \#$$

(b)

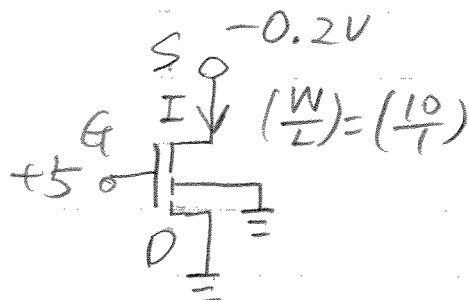

$$V_{GS} = V_G - V_S = 5.2V$$

$$V_{DS} = V_D - V_S = 0.2V$$

$$V_{GS} - V_{th} > V_{DS}$$

$$I = -K_n' \frac{W}{L} \left(V_{GS} - V_{th} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$= - \left(100 \frac{\mu A}{V^2} \right) \left(\frac{10}{1} \right) \left(5.2 - 0.7 - \frac{0.2}{2} \right) 0.2$$

$$= \boxed{-880 \mu A} \#$$

P5.3

(a)

$$\begin{aligned} R_{on} &= \frac{1}{k_n' \frac{W}{L} (V_{GS} - V_{th})} \\ &= \frac{1}{100 \times 10^{-6} \times \left(\frac{100}{1}\right) \times (5 - 0.65)} \\ &\approx \boxed{23 \Omega} \# \end{aligned}$$

(b)

$$\begin{aligned} R_{on} &= \frac{1}{k_n' \frac{W}{L} (V_{GS} - V_{th})} \\ &= \frac{1}{100 \times 10^{-6} \times \left(\frac{100}{1}\right) \times (3.3 - 0.5)} \\ &\approx \boxed{35.7 \Omega} \# \end{aligned}$$

P5.4 NMOS, $k_n = 250 \mu A/V^2$, $V_{tn} = 1V$


(a) $V_{GS} = 5V$, $V_{DS} = 6V$
 $V_{DS} > V_{GS} - V_{tn} \Rightarrow$ Saturation region #

(b) $V_{GS} = 0V$, $V_{DS} = 6V$
 $V_{GS} < V_{tn} \Rightarrow$ cutoff region #

(c) $V_{GS} = 2V$, $V_{DS} = 2V$
 $V_{GS} - V_{tn} = 1 < V_{DS} = 2V \Rightarrow$ Saturation region #

(d) $V_{GS} = 1.5V$, $V_{DS} = 0.5V$
 $V_{GS} - V_{tn} = 0.5 = V_{DS}$
 $\Rightarrow$ Boundary between triode and saturation region #

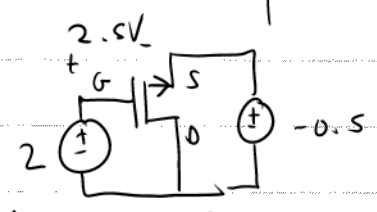
(e) $V_{GS} = 2V$, $V_{DS} = -0.5V$ Drain & Source flip
 ~~$V_{GS} - V_{tn} = 2 - 1 = 1 > V_{DS}$~~
 $\Rightarrow$ triode region #



(f) $V_{GS} = 3V$, $V_{DS} = -6V$
 ~~$V_{GS} - V_{tn} = 2 > V_{DS} = -6V$~~
 $\Rightarrow$ triode region #


$V_{GS} = 2.5V$
 $V_{DS} = 0.5V$ Linear

$V_{DS} < 0$ D & S terminals flip

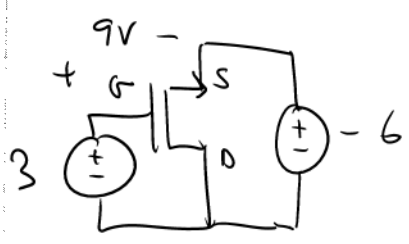

$V_{GS} = 3V > V_{tn}$
 $V_{DS} = 6V < V_{GS} - V_{tn}$
Linear

P5.5

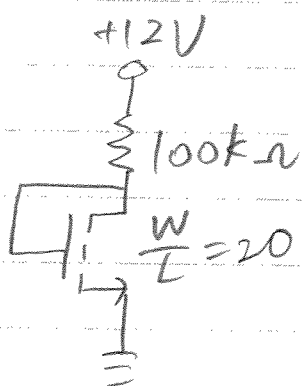

(a) $\lambda = 0, \frac{W}{L} = 20.$

The transistor is in saturation region since its gate and drain are connected together.

$$I_D = \frac{12 - V_{GS}}{100k} = \frac{1}{2} \times 100 \frac{\mu A}{V^2} \times 20 \times (V_{GS} - 0.75)$$

$$\Rightarrow V_{GS} = 0.4V \text{ or } 1.08V$$

(V_{GS} should be greater than V_{th})

$$I_D = \frac{12 - 1.08}{100k} = \boxed{109.2 \mu A} \#$$

(b) $\lambda = 0.02 V^{-1}$

$$I_D = \frac{12 - V_{GS}}{100k} = \frac{1}{2} \times 100 \frac{\mu A}{V^2} \times 20 (V_{GS} - 0.75)^2 (1 + 0.02 V_{GS})$$

$$\Rightarrow V_{GS} = 0.41V \text{ or } 1.07V$$

$$I_D = \frac{12 - 1.07}{100k} = \boxed{109.3 \mu A} \#$$

P5.6 NMOS, $\frac{W}{L} = 8$, $V_{T0} = 1V$, $2\Phi_F = 0.6V$,
 $k = 0.7\sqrt{V}$, $V_{SB} = 3V$, $V_{GS} = 2.5V$, $V_{DS} = 5V$

(a)

$$V_{TN} = 1 + 0.7(\sqrt{3+0.6} - \sqrt{0.6}) = 1.79V$$

$$V_{GS} - V_{TN} = 2.5 - 1.79 = 0.71 < V_{DS} = 5V$$

$\Rightarrow$ Saturation region

$$I_D = 100\mu \times \frac{1}{2} \times 8 \times (0.71)^2$$

$$= \boxed{201.64\mu A} \#$$

(b)

$V_{DS} = 0.5V \Rightarrow$ Triode region.

$$I_D = 100\mu \times 8 \times \left(0.71 - \frac{0.5}{2}\right) \times 0.5$$

$$= \boxed{184\mu A} \#$$

P5.7 $V_{BS} = 0V$, $W/L = 20$, PMOS, $V_{tp} = -0.75V$

(a) $V_{GS} = -1.1V$, $V_{DS} = -0.2V$
 $V_{SG} - |V_{tp}| = 1.1 - 0.75 = 0.35V$
 $V_{SD} = 0.2V$
 $V_{SD} < V_{SG} - |V_{tp}| \Rightarrow$ triode region

$$I_D = 40\mu \times 20 \times \left(0.35 - \frac{0.2}{2}\right) 0.2$$
$$= \boxed{40\mu A} \quad \#$$

(b) $V_{GS} = -1.3V$, $V_{DS} = -0.2V$
 $V_{SG} - |V_{tp}| = 1.3 - 0.75 = 0.55V$, $V_{SD} = 0.2V$
 $V_{SD} < V_{SG} - |V_{tp}| \Rightarrow$ triode region

$$I_D = 40\mu \times 20 \times \left(0.55 - \frac{0.2}{2}\right) 0.2 = \boxed{72\mu A} \quad \#$$

(c) $V_{BS} = 1V$, $V_{GS} = -1.1V$, $V_{DS} = -0.2V$
 $V_{tp} = -0.75 - 0.5(\sqrt{1+0.6} - \sqrt{0.6})$
 $= -0.995V$

$$V_{SG} - |V_{tp}| = 1.1 - 0.995 = 0.105V$$
$$V_{SD} = 0.2V, V_{SD} > V_{SG} - |V_{tp}|$$

$\Rightarrow$ saturation region

$$I_D = \frac{1}{2} \times 40\mu \times 20 \times (0.105)^2$$
$$= \boxed{4.41\mu A} \quad \#$$

P.8

(d)

$$V_{BS} = 1V,$$

$$V_{SG} - |V_{tp}| = 1.3 - 0.995 = 0.3V$$

$$V_{SD} = 0.2V$$


⇒ Triode region

$$I_D = 40\mu \times \left(0.3 - \frac{0.2}{2}\right) \times 0.2 \times 20$$

$$= \boxed{32\mu A} \quad \#$$


P5.8

(a)

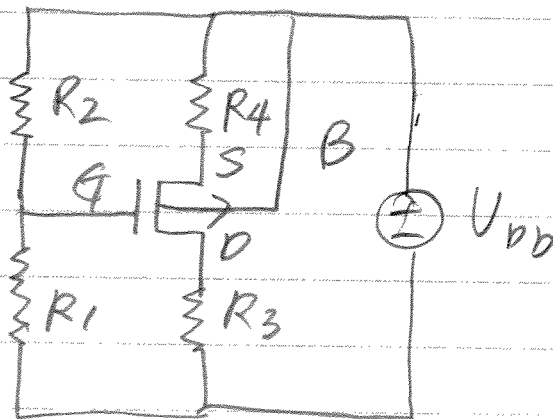

$$V_{DD} = 10V$$


(b)

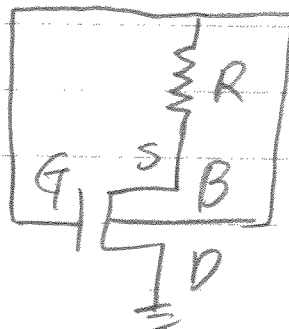

$$+18V$$

P5.9

P.9

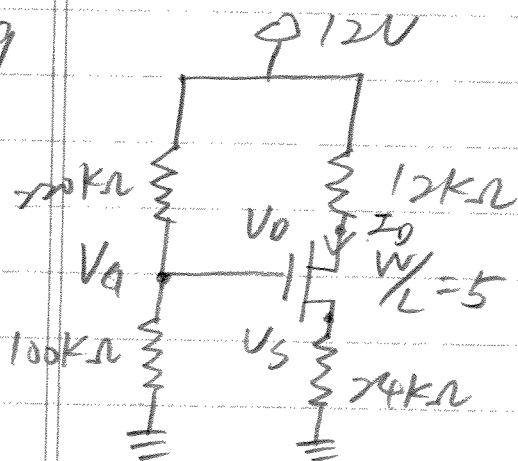

$$V_{th} = 1V, \lambda = 0, \\ \mu_n C_{ox} = K_n' = 100 \mu A/V^2$$

$$V_G = 12 \times \frac{100}{100 + 200} = 3.75V$$

$$V_D = 12 - I_D \times 12k$$

$$V_S = 24k \times I_D$$

$$I_D = \frac{1}{2} \times 100\mu \times 5 \times (3.75 - 24k \cdot I_D - 1)^2$$

$$\Rightarrow I_D = 90 \mu A \text{ or } 146 \mu A$$

$$\textcircled{1} I_D < 90 \mu A$$

$$V_{GS} = 3.75 - 2.16 = 1.59V$$

$$V_{DS} = 10.92 - 2.16 = 8.76V$$

$$V_{DS} > V_{GS} - V_t \Rightarrow \text{Saturation region.}$$


$$\textcircled{2} I_D = 146 \mu A$$

$$V_{GS} = 3.75 - 3.5 = 0.25V$$

$$V_{GS} < V_t \Rightarrow \text{Cutoff region.}$$

$$\Rightarrow \boxed{I_D = 90 \mu A} \#$$

P5.10

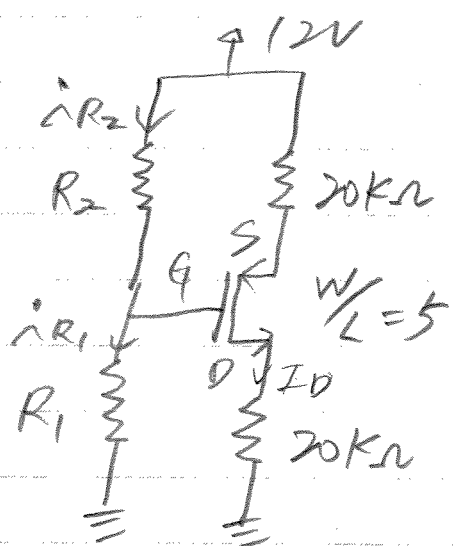PMOS, $I_D = 100\mu A$ $I_{R1} = I_{R2} = 10\mu A$ $V_{TP} = -1V, \lambda = 0, \mu_n C_{ox} = 40\mu A/V$

$$100\mu = \frac{1}{2} \times 40\mu \times 5 \times \left\{ \left[(12 - 20k \cdot 100\mu) - V_G \right] - 1 \right\}$$

$$V_G = I_{R1} \times R_1 = 10\mu \cdot R_1$$

$$\rightarrow V_G = 8V \text{ or } 10V$$

$$\textcircled{1} V_G = 8V$$

$$V_S = 12 - 20k \times 100\mu = 10V$$

$$V_{SG} = 2V > |V_{TP}|$$

$$V_{SG} - |V_{TP}| = 1 < V_{SD} = 8V$$

Saturation region

$$\textcircled{2} V_G = 10V$$

$$V_S = 10V \Rightarrow V_{SG} = 0V < |V_{TP}|$$

Cutoff region

$$\therefore \boxed{V_G = 8V}$$

$$\Rightarrow \frac{R_1}{R_1 + R_2} \times 12 = 8$$

$$\frac{12}{R_1 + R_2} = 10\mu$$

$$\Rightarrow \begin{cases} R_1 = 0.8M\Omega \\ R_2 = 0.4M\Omega \end{cases}$$

#