

EECS 413 PS6 Solution

P.1

P6.1

$$I_C = \beta_F I_B = 200 \times 10 \mu = \boxed{2 \text{ mA}} \#$$

$$I_E = (\beta_F + 1) I_B = 201 \times 10 \mu = \boxed{2.01 \text{ mA}} \#$$

$$I_E = \left(I_S + \frac{I_S}{\beta_F} \right) \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

$$\Rightarrow 2.01 \text{ m} = \left(10^{-17} + \frac{10^{-17}}{200} \right) \left[e^{\frac{V_{BE}}{25 \text{ m}}} - 1 \right]$$

$$\Rightarrow V_{BE} = \boxed{0.82 \text{ V}} \#$$

P6.2

a)

$$\alpha_F = \frac{I_C}{I_E} = \frac{\beta_F I_B}{I_E}$$

$$\alpha_F = \frac{\beta_F}{1 + \beta_F} \Rightarrow \alpha_F + \alpha_F \beta_F = \beta_F$$

$$\Rightarrow \alpha_F = (1 - \alpha_F) \beta_F \Rightarrow \beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

$$\frac{I_B}{I_E} = \frac{\alpha_F}{\beta_F} = \boxed{1 - \alpha_F} \#$$


b) 5% error for $\alpha_F \Rightarrow \alpha_F > 0.90$

$$\frac{\beta_F}{1 + \beta_F} > 0.95 \Rightarrow \boxed{\beta_F > 19} \#$$

1% error for $\alpha_F \Rightarrow \alpha_F > 0.94$

$$\frac{\beta_F}{1 + \beta_F} > 0.99 \Rightarrow \boxed{\beta_F > 99} \#$$

P6.3
(a)
(b)

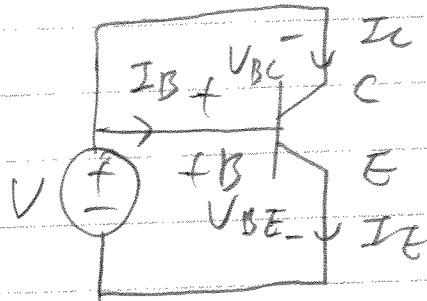

(c) $V = 0.64V$, $I_C = 275\mu A$, $I_B = 4\mu A$

$$I_C = \beta_F I_B \Rightarrow \boxed{\beta_F = 68.75} \quad \#$$

$$\beta_R = \frac{\alpha_R}{1 - \alpha_R} = \frac{0.5}{1 - 0.5} = \boxed{1} \quad \#$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow 275\mu = I_S e^{\frac{0.64}{25m}}$$

$$\Rightarrow I_S = \boxed{2.09 \times 10^{-15} A} \quad \#$$

P6.4

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.995}{1 - 0.995} = 199$$

$$I_B + I_C = 100\mu A \Rightarrow (1 + 199) I_B = 100\mu A$$

$$\Rightarrow \boxed{I_B = 0.5\mu A}$$

$$\Rightarrow \boxed{I_C = 99.5\mu A} \quad \#$$

P6.5

$$I_C = \beta_F I_B = \beta_{F0} \left(1 + \frac{V_{CE}}{V_A}\right) I_B$$

$$I_C = 240 \mu A \text{ for } V_{CE} = 5V$$

$$I_C = 265 \mu A \text{ for } V_{CE} = 10V$$

$$\begin{cases} 240 \mu = \beta_{F0} \left(1 + \frac{5}{V_A}\right) \times 3 \mu \\ 265 \mu = \beta_{F0} \left(1 + \frac{10}{V_A}\right) \times 3 \mu \end{cases}$$


$$\Rightarrow V_A = 43V, \beta_{F0} = 71.66$$

#

P6.6

(a)

$$\beta_F = 50, V_{BE} = 0.7V$$

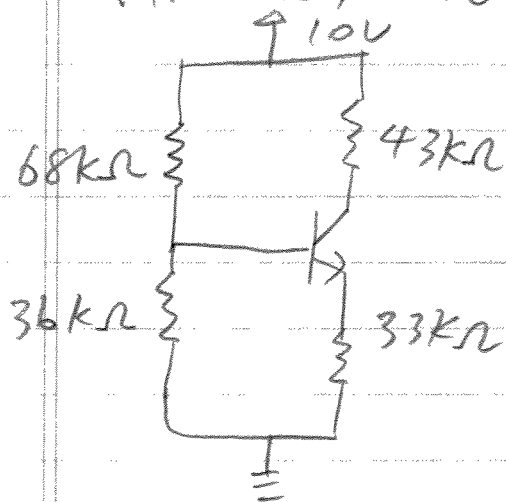

$$V_B = \frac{36}{36 + 68} \times 10 = 3.46V$$

$$R_{eq} = 36k\Omega // 68k\Omega = 23.54k\Omega$$


$$I_B = \frac{3.46 - 0.7}{23.54k + (50 + 1) \times 33k} = 1.62 \mu A$$

$$I_C = \beta_F I_B = 81 \mu A$$

$$V_{CE} = 10 - 43k \times 81 \mu - 33k \times (81 \mu + 1.62 \mu) = 3.79V$$

$$Q \text{ point } (3.79V, 81 \mu A)$$

#

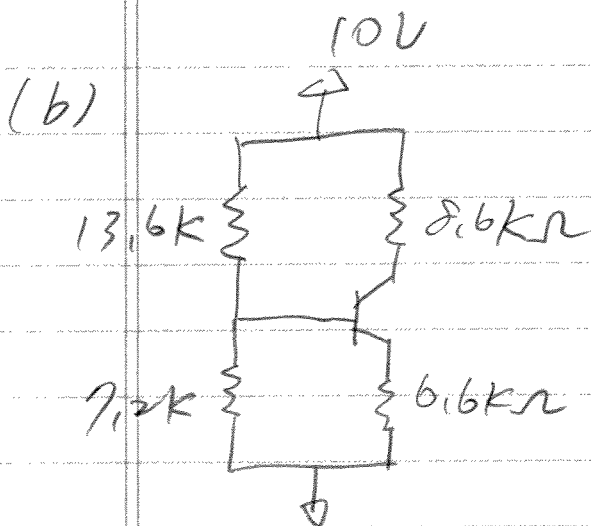

p.4

$$V_B = 10 \times \frac{7.2}{7.2 + 13.6} = 3.46 \text{ V}$$

$$R_{eq} = 13.6 \text{ k} \parallel 7.2 \text{ k} = 4.7 \text{ k}\Omega$$


$$I_B = \frac{3.46 - 0.7}{4.7 \text{ k} + (50 + 1) \times 6.6 \text{ k}} = 8.08 \mu\text{A}$$

$$I_C = 50 \times I_B = 404.336 \mu\text{A}$$

$$V_{CE} = 10 - 8.6 \text{ k} \times 404.34 \mu - 6.6 \text{ k} \times (8.03 \mu + 404 \mu) = 3.8 \text{ V}$$

Q point (3.8 V, 404.34 μA)

#

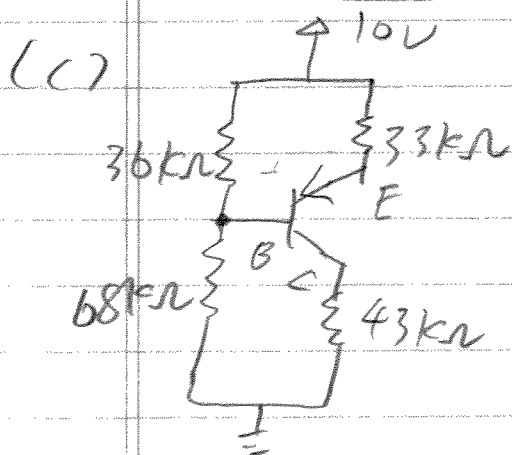

$$V_B = 10 \times \frac{68}{68 + 36} = 6.54 \text{ V}$$

$$R_{eq} = 36 \text{ k} \parallel 68 \text{ k} = 23.54 \text{ k}\Omega$$

$$I_B = \frac{10 - 6.54 - 0.7}{23.54 \text{ k} + (51) \times 33 \text{ k}} = 1.61 \mu\text{A}$$


$$I_C = 50 \times I_B = 80.86 \mu\text{A}$$

$$V_{CE} = 10 - 33 \text{ k} \times (1.61 \mu + 80.86 \mu) - 80.86 \mu \times 43 \text{ k} = 3.8 \text{ V}$$

Q point (3.8 V, 80.86 μA)

#

(10)

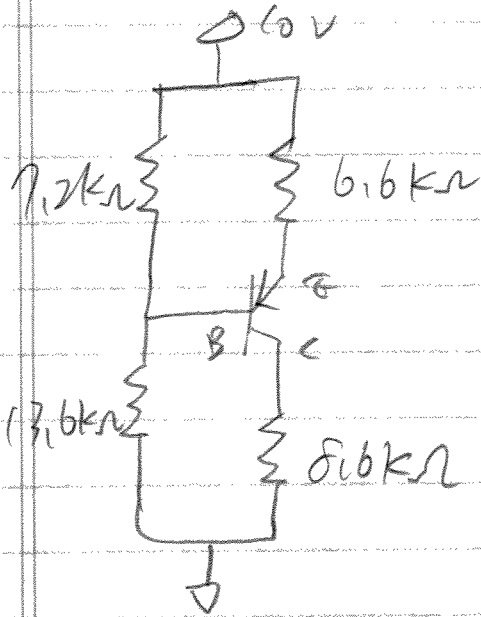

$$V_B = 10 \times \frac{13.6}{13.6 + 7.2} = 6.54V$$

$$R_{eq} = 7.2k \parallel 13.6k = 4.7k\Omega$$

$$I_B = \frac{10 - 6.54 - 0.7}{4.7k + 6.6k \times 51} = 8.09 \mu A$$


$$I_C = 50 \times I_B = 404.34 \mu A$$

$$\begin{aligned} V_{EC} &= 10 - 6.6k \times (404.34 \mu + 8.09 \mu) \\ &\quad - 8.6k \times (404.34 \mu) \\ &= 3.8V \end{aligned}$$

Q point (3.8V, 404.34μA)

#


P6.7

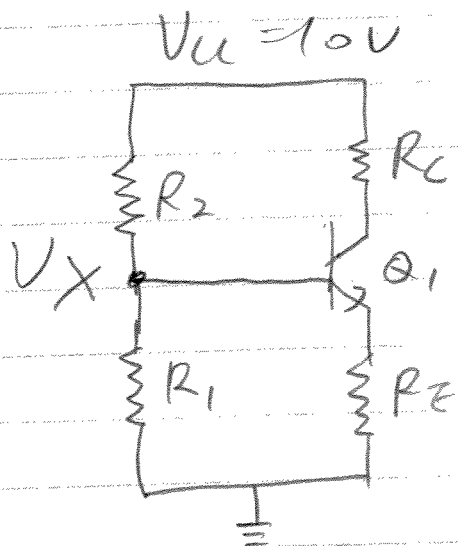

$$R_1 = 6.2 \text{ k}\Omega, R_2 = 12 \text{ k}\Omega$$

$$R_C = 5.1 \text{ k}\Omega, R_E = 7.5 \text{ k}\Omega$$

$$\beta_F = 100, V_{CC} = 10 \text{ V}$$

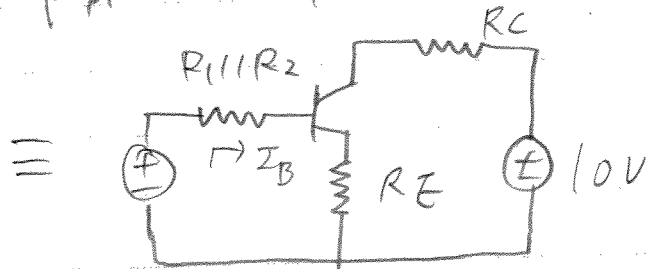

$$V_X = V_{CC} \times \frac{R_1}{R_1 + R_2} = 10 \times \frac{6.2}{6.2 + 12} = 3.4 \text{ V}$$

$$R_1 \parallel R_2 = 6.2 \text{ k} \parallel 12 \text{ k} = 4.08 \text{ k}\Omega$$

$$I_C = \beta_F I_B = 100 \times \frac{3.4 - 0.7}{4.08 \text{ k} + 101 \times 7.5 \text{ k}} = 354.5 \mu\text{A}$$

$$V_{CE} = 10 - 354.5 \times 10^{-6} \times 5.1 \times 10^3$$

$$- 354.5 \times 10^{-6} \times \frac{101}{100} \times 7.5 \times 10^3$$

$$= 5.5 \text{ V}$$

Q-point: (5.5V, 354.5μA)


#

P6.8

$$I_C = 1 \text{ mA}, V_{CE} = 5 \text{ V}, V_E = 2 \text{ V}$$

$$V_{CC} = 12 \text{ V}, \beta_{AF} = 100$$

$$V_{BE, \text{on}} = 0.7 \text{ V}$$

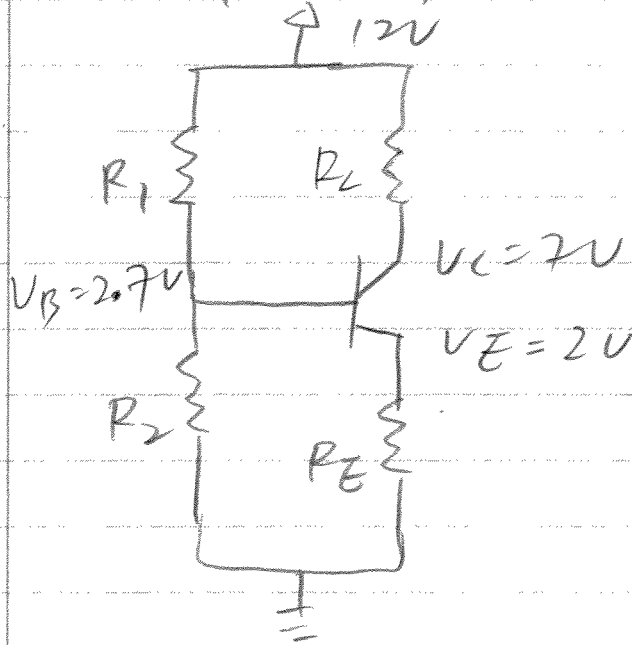

$$R_C = \frac{12 - 7}{10^{-3}} = 5 \text{ k}\Omega$$

$$R_E = \frac{2}{I_B + I_C} = \frac{2}{10^{-3}(1 + \frac{1}{100})}$$

$$\approx 1.98 \text{ k}\Omega$$

$$I_B = \frac{I_C}{\beta_{AF}} = 10 \mu\text{A} = \frac{12 - 2.7}{R_1} - \frac{2.7}{R_2}$$

$$\text{Choose } R_2 = 50 \text{ k}\Omega$$

$$R_1 = 145.3 \text{ k}\Omega$$

$$R_1 = 145.3 \text{ k}\Omega$$

$$R_2 = 50 \text{ k}\Omega$$

$$R_C = 5 \text{ k}\Omega$$

$$R_E = 1.98 \text{ k}\Omega$$

#