

EECS 311: PS7 Solution

P.1

P7.1

$I_D \propto (V_{SG} - |V_{tp}|)^2$ @ saturation region

$$\frac{50}{200} = \frac{(3 - |V_{tp}|)^2}{(5 - |V_{tp}|)^2}$$

$$\Rightarrow |V_{tp}| = 1 \text{ or } 3.66 (\times)$$

Since this is PMOS device, $V_{tp} < 0$

$$\Rightarrow \boxed{V_{tp} = -1V} \#$$


$$I_D = \frac{1}{2} K_p (V_{SG} - |V_{th}|)^2$$

$$200 \mu A = \frac{1}{2} K_p (5 - 1)^2$$

$$\Rightarrow \boxed{K_p = 25 \mu A/V^2} \#$$

P7.2

(a)

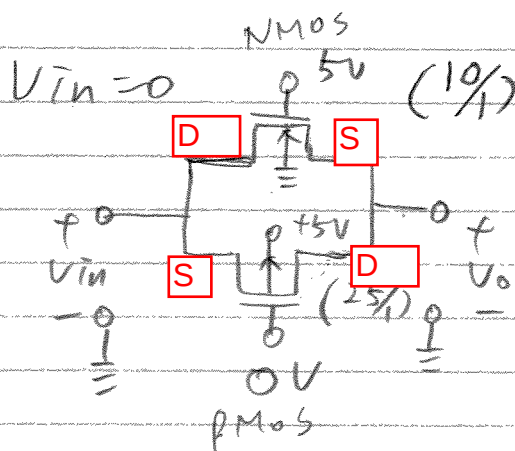

for $V_{in} = 0V$

$$NMOS: \boxed{V_{GS} - V_{th} > 0}$$

$\Rightarrow$ NMOS is on

$$PMOS: \boxed{V_{SG} - V_{th} < 0}$$

$\Rightarrow$ PMOS is off

$$R_{on} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{th})}$$

$$= \frac{1}{100 \mu A/V^2 \times 10 \times (5 - 0.75)}$$

$$= \boxed{235 \Omega} \#$$

(b) for $V_{in} = 5V$

NMOS: NMOS is off.

PMOS: PMOS is on. $V_{SG} = 5V$, $V_D = 5V$

$$R_{on} = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right) (V_{SG} - |V_{th,p}|)} = \frac{40 \times 10^{-6} \times 25 \times (5 - 0.75)}{1} = \boxed{1.25 k\Omega}$$

p7.3

PMOS, $V_{BS} = 4V$, $V_{GS} = -1.5V$, $V_{DS} = -4V$
 $(\frac{W}{L}) = \frac{25}{1}$, region of operation?

$$V_{TP} = -0.75 - 0.5(\sqrt{4 + 0.6} - \sqrt{0.6}) = -1.43$$

$$V_{SD} = 4 > V_{SG} - |V_{TP}| = 1.5 - 1.43 = 0.07$$

Saturation region #

$$I_D = \frac{1}{2} \times 40 \mu A \times \left(\frac{25}{1}\right) (1.5 - 1.43)^2$$

$$= \boxed{2.45 \mu A} \#$$

p7.4 NPN transistor, $I_C = 1mA$, $I_B = 0.1mA$, $\beta_A = 100$
 $\beta_R = 10$ $I_S = 10^{-15} A$, $V_T = 25mV$



$$\alpha_R = \frac{\beta_R}{\beta_R + 1} = \frac{10}{11}$$

$$V_{CEsat} = V_T \ln \left[\left(\frac{1}{\alpha_R} \right) \frac{1 + \frac{I_C}{(\beta_R + 1) I_B}}{1 - \frac{I_C}{\beta_A I_B}} \right]$$

$$= 25mV \ln \left[\frac{11}{10} \times \frac{1 + \frac{1m}{11 \times 0.1m}}{1 - \frac{1m}{100 \times 0.1m}} \right]$$

$$= 25mV \ln \left[\frac{11}{10} \times \frac{1 + 0.909}{1 - 0.1} \right]$$

$$= \boxed{21.2 mV} \#$$

P7.5

$$V_{BE} = 0.7 \text{ (V)}$$

$$v_{be}(t) = 0.008 \sin(\omega_0 t) \text{ (V)}$$

$$V_{CE} = 5 \text{ (V)}$$

$$v_{ce}(t) = -1.7 \sin(\omega_0 t + \pi) \text{ (V)}$$

P7.6


$$v_{gs}(t) = 0.5 \sin(\omega_0 t) \text{ (V)}$$

$$V_{GS} = 3.5 \text{ (V)}$$

$$V_{DS} = 4.8 \text{ (V)}$$

$$v_{ds}(t) = +0.1 - 2 \sin(\omega_0 t + \pi) \text{ (V)}$$

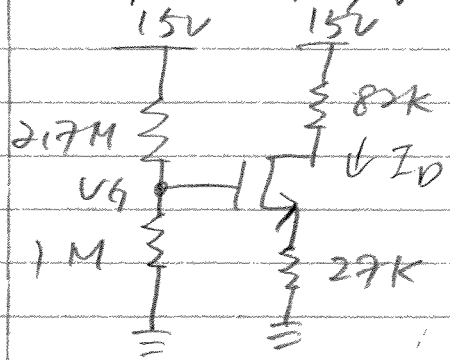P7.7 $K_n = 250 \mu A/V^2$, $V_{th} = 1V$, $\lambda = 0$



$$V_G = \frac{1}{1+2.7} \times 15 = 4.05V$$

(a) Assume the transistor is in saturation region

$$I_D = \frac{1}{2} K_n (V_{GS} - V_{th})^2$$

$$\Rightarrow I_D = \frac{1}{2} \times 250 \mu (4.05 - I_D \times 27K - 1)^2$$

$$\boxed{I_D = 83 \mu A} \quad \# \text{ check if it's in saturation (V)}$$

$$I_D = \frac{1}{2} \times 250 \times 10^{-6} \times [(4.05 - 27 \times 10^3 I_D) - 1]^2$$

$$I_D = \boxed{83.43 \mu A} \text{ or } 152.94 \mu A$$

$$\frac{83.433 - 83}{83} \times 100\% = \boxed{0.52\%} \quad \#$$


$$I_D = \frac{1}{2} \times 250 \times 10^{-6} \times [(4.05 - 27 \times 10^3 I_D) - 0.95]^2$$

$$I_D = \boxed{84.384 \mu A} \text{ or } 156.219 \mu A$$

$$\frac{84.384 - 83}{83} \times 100\% = \boxed{1.67\%} \quad \#$$

P7.8
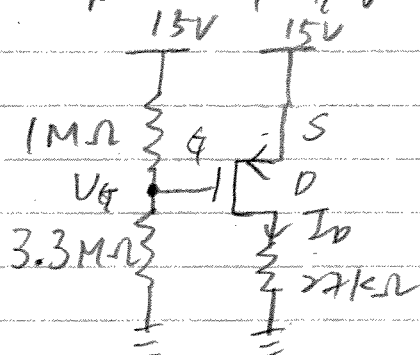
$$K_p = 100 \mu\text{A}/\text{V}^2, V_{tp} = -1\text{V}, \lambda = 0$$



$$V_G = \frac{3.3}{3.3+1} \times 15 = 11.51\text{V}$$

(a) Assume the transistor is in saturation region.

$$I_D = \frac{1}{2} K_p (V_{SG} - |V_{tp}|)^2$$

$$\Rightarrow I_D = \frac{1}{2} \times 100 \mu \times (15 - 11.51 - 1)^2$$

$$= \boxed{310 \mu\text{A}} \#$$

$$V_D = 27\text{k} \times 310 \mu = 8.37\text{V}$$

$$V_{SD} = 15 - 8.37 = 6.63, V_{SG} - |V_{tp}| = (15 - 11.51) - 1$$

$$V_{SD} > V_{SG} - |V_{tp}| \Rightarrow \text{Saturation.} = 2.49$$

(b)

$$I_D = \frac{1}{2} \times 105 \mu \times (2.49)^2$$

$$= \boxed{325.5 \mu\text{A}} \#$$

$$\frac{(325.5 - 310)}{310} \times 100\% = \boxed{5\%}$$

(c)

$$I_D = \frac{1}{2} \times 100 \mu \times [(15 - 11.51) - 0.95]^2$$

$$= \boxed{322.58 \mu\text{A}}$$

$$\frac{(322.58 - 310)}{310} \times 100\% = \boxed{4.06\%}$$

#