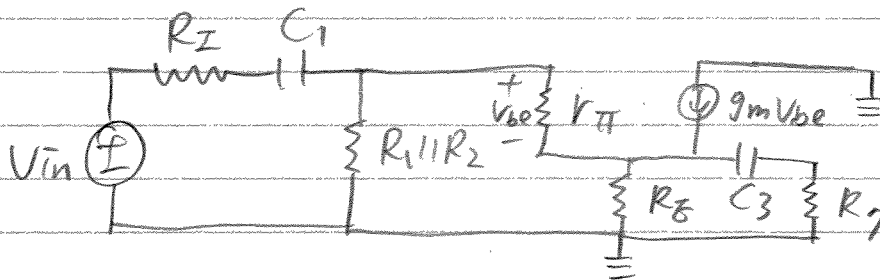


# EECS 311 PS9 Solution


P7.1

P.1

a) Low frequency



midband:

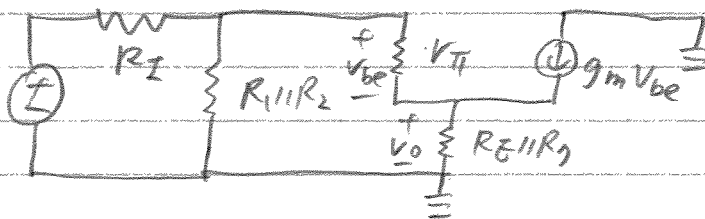

b) SCL:

$$C_1: R_{1,eq} = R_I + [R_1 \parallel R_2 \parallel (r_{\pi} + (1 + g_m r_{\pi}) R_E)]$$

$$C_3: R_{3,eq} = R_7 + (R_E \parallel \frac{1}{g_m})$$

$$C_1 = 4.7 \mu F, C_3 = 10 \mu F, R_1 = 100 k\Omega, R_2 = 300 k\Omega$$

$$R_3 = 13 k\Omega, R_I = 2 k\Omega, R_7 = 100 k\Omega$$

$$g_m = \frac{I_C}{V_T}, \beta_0 = g_m r_{\pi} = 100, I_C = 0.25 mA, V_{CC} = 12V$$

$$f_L = \left( \frac{1}{R_{1,eq} C_1} + \frac{1}{R_{3,eq} C_3} \right) \frac{1}{2\pi} \approx \boxed{0.623 kHz} \quad \#$$


$$A_v = \frac{R_{in}}{R_I + R_{in}} \frac{(1 + \beta_0)(R_E \parallel R_7)}{r_{\pi} + (1 + \beta_0)(R_E \parallel R_7)} \approx \boxed{0.964 \frac{V}{V}} \quad \#$$

P7.2

$$\omega_L = \frac{1}{R_{1eg}C_1} + \frac{1}{R_{3eg}C_3} = 2\pi f_L = 20\pi$$

$$C_3 = \frac{(20\pi - \frac{1}{R_{1eg}C_1})^{-1}}{R_{3eg}} \approx \boxed{0.187 \mu F} \quad \#$$


P7.3

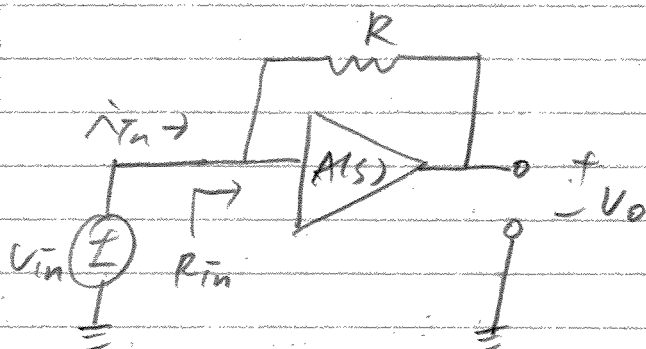

$$R_{in} = \frac{V_{in}}{i_{in}} = \frac{R}{1-A(s)} \quad \#$$

$$i_{in} = \frac{V_{in} - V_{out}}{R} = \frac{V_{in}(1-A(s))}{R}$$

P7.4

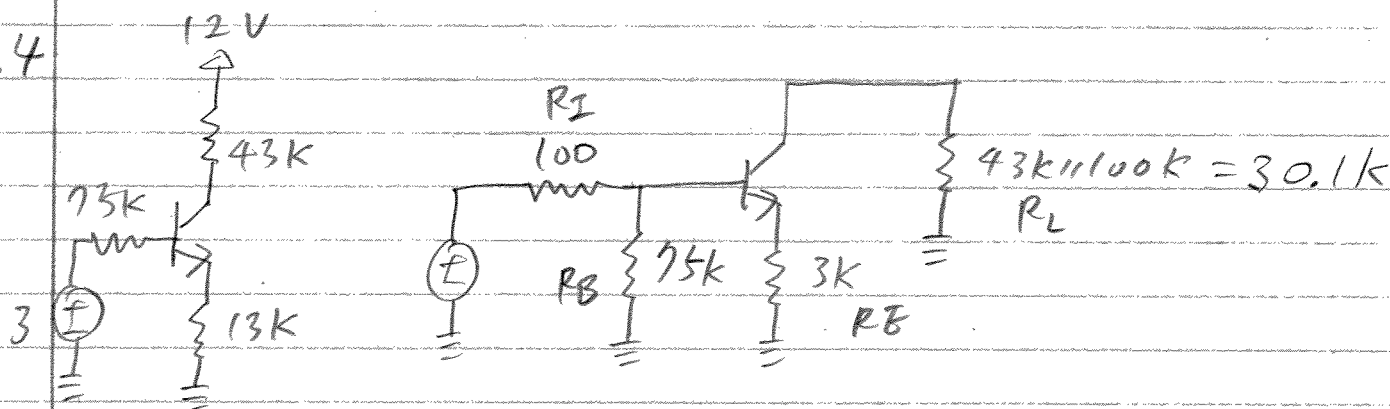

$$I_C = 100 \times \frac{3 - 0.7}{75k + 101 \times 13k} = 0.166 \text{ mA}$$

$$V_{CE} = 12 - 43k \times I_C - 13k I_E = 2.68 \text{ V}$$

$$g_m = \frac{1}{25m} \times 0.166 \text{ m} = 6.64 \text{ mS}$$

$$r_{\pi} = \frac{100}{6.64 \text{ m}} = 15.1 \text{ k}\Omega$$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu} = \frac{6.64 \text{ m}}{2\pi \times 300 \times 10^6} - 0.5 \times 10^{-12} = 3.52 \text{ pF}$$

OCLC

From Table 16.2

$$r_{\pi 0} = r_{\pi} \parallel [r_x + (R_I \parallel R_B)], \quad R_B = R_1 \parallel R_2$$

$$= 15.1k \parallel (300 + (100 \parallel 75k)) = 390 \Omega$$

$$C_{TB} = \frac{C_{\pi}}{1 + g_m R_E} + C_{\mu} \left( 1 + \frac{g_m R_L}{1 + g_m R_B} \right) + (C_u + C_L) \frac{R_L}{r_{\pi 0}}$$

$$= \frac{3.52p}{1 + 6.64m \times 3k} + 0.5p \left[ 1 + \frac{6.64m \times 30.1k}{1 + 6.64m \times 3k} \right] + \left( \frac{30.1k \Omega}{390} \right)$$

$$\approx 44 pF$$

$$f_H = \frac{1}{2\pi(390)(44p)} = 9.27 MHz$$

SLTL

$$R_{1s} = 100 + 75k \parallel [300 + 15.1k + (101 \times 3k)] = 60.8k \Omega$$

$$R_{2s} = 10k \parallel \left( 3k + \frac{15.1k + 99.9}{101} \right) = 2.4k \Omega$$

$$R_{3s} = 43k + 100k = 143k \Omega$$


$$f_L \approx \frac{1}{2\pi} \left[ \frac{1}{(60.8k)(1\mu F)} + \frac{1}{(2.4k)(2.2\mu)} + \frac{1}{(143k)(0.1\mu)} \right]$$

$$= 43.9 Hz$$

$$A_{mid} = - \frac{60.7k}{60.8k} \times \frac{(6.64m)(30.1k)}{1 + (6.64m)(3k)} = \boxed{-9.5} \quad \#$$

$$GBW = 9.54 \times (9.27M - 43.9) \approx \boxed{88 MHz} \quad \#$$

P9.5  
(a)

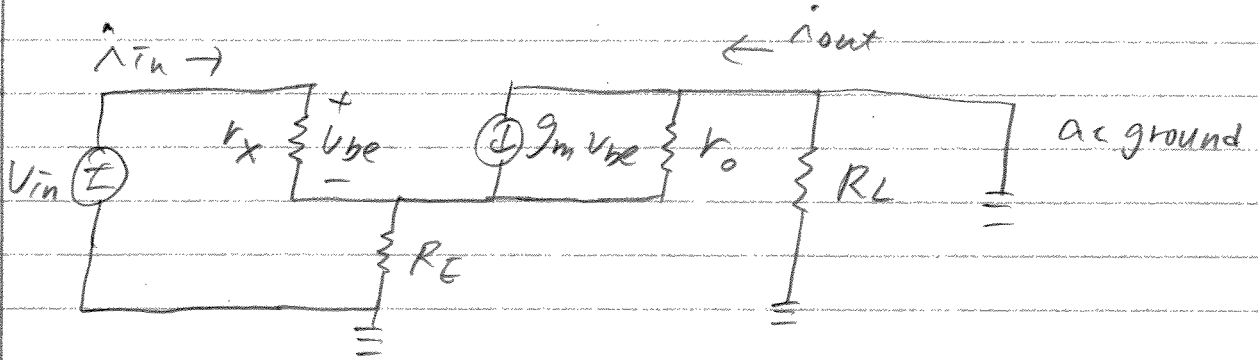

KCL:

$$\hat{i}_{in} + g_m V_{be} = \frac{V_{in} - V_{be}}{R_E \parallel r_o}, \quad V_{be} = \hat{i}_{in} r_\pi$$

$$\hat{i}_{in} \left( 1 + g_m r_\pi + \frac{r_\pi}{R_E \parallel r_o} \right) = \frac{V_{in}}{R_E \parallel r_o}$$

$$R_{in} = \frac{V_{in}}{\hat{i}_{in}} = \boxed{r_\pi + (1 + g_m r_\pi)(R_E \parallel r_o)} \quad \#$$


$$\hat{i}_{out} = g_m V_{be} - \frac{(V_{in} - V_{be})}{r_o}$$

$$\boxed{V_{be} = \hat{i}_{in} r_\pi = \frac{r_\pi V_{in}}{r_\pi + (1 + \beta_o)(R_E \parallel r_o)} = \frac{r_\pi V_{in}}{R_{in}}}$$

$$\hat{i}_{out} = V_{in} \left( \frac{\beta_o}{R_{in}} - \frac{1}{r_o} + \frac{r_\pi}{R_{in} r_o} \right)$$

$$G_m = \frac{\hat{i}_{out}}{V_{in}} = \frac{\beta_o r_o - R_{in} + r_\pi}{r_o R_{in}}$$
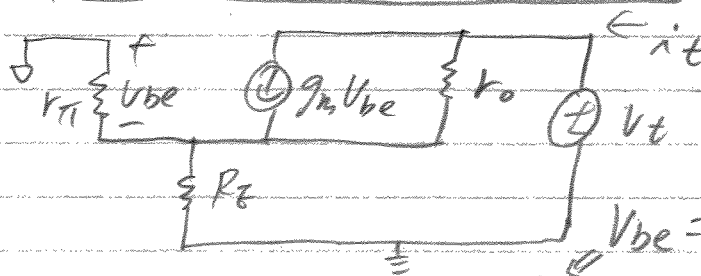
$$= \boxed{\frac{\beta_o r_o - (1 + \beta_o)(R_E \parallel r_o)}{r_o (r_\pi (1 + \beta_o)(R_E \parallel r_o))}} \quad \#$$



$$\hat{i}_t = \frac{-V_{be}}{r_\pi \parallel R_E} = g_m V_{be} + \frac{V_t + V_{be}}{r_o}$$

$$V_{be} = -\hat{i}_t (r_\pi \parallel R_E)$$

$$\hat{i}_t = -g_m (r_\pi \parallel R_E) \hat{i}_t + \frac{V_t - \hat{i}_t (r_\pi \parallel R_E)}{r_o}$$

$$R_{out} = \frac{V_t}{\hat{i}_t} = \boxed{r_o [1 + g_m (r_\pi \parallel R_E)] + (r_\pi \parallel R_E)} \quad \#$$

$$\begin{aligned}
 b) \quad R_{in} &= r_{\pi} + (1 + g_m r_{\pi}) (R_E \parallel r_o) \\
 &\approx r_{\pi} + (1 + g_m r_{\pi}) R_E \quad (r_o \gg R_E) \\
 &\approx r_{\pi} + g_m r_{\pi} R_E \quad (\beta_o = g_m r_{\pi} \gg 1) \\
 &\approx \boxed{r_{\pi} (1 + g_m R_E)} \quad \#
 \end{aligned}$$

$$\begin{aligned}
 G_M &= \frac{\beta_o r_o - (1 + \beta_o) (R_E \parallel r_o)}{r_o (r_{\pi} + (1 + \beta_o) (R_E \parallel r_o))} \\
 &\approx \frac{\beta_o r_o - \beta_o R_E}{r_o (r_{\pi} + \beta_o R_E)} \quad (r_o \gg R_E, \beta_o \gg 1) \\
 &\approx \frac{\beta_o (r_o - R_E)}{r_o (r_{\pi} + \beta_o R_E)} \approx \frac{\beta_o r_o}{r_o (r_{\pi} + \beta_o R_E)} \quad (r_o \gg R_E) \\
 &\approx \frac{g_m r_{\pi}}{r_{\pi} + g_m r_{\pi} R_E} \approx \boxed{\frac{g_m}{1 + g_m R_E}} \quad \#
 \end{aligned}$$


Conditions used:  $r_o \gg R_E$  &  $\beta_o = g_m r_{\pi} \gg 1$

$$\begin{aligned}
 c) \quad R_{out} &= r_o [1 + g_m (r_{\pi} \parallel R_E)] + (r_{\pi} \parallel R_E) \\
 &\approx r_o [1 + g_m R_E] + R_E \quad (r_{\pi} \gg R_E) \\
 &\approx \boxed{r_o (1 + g_m R_E)} \quad \# \quad (r_o \gg R_E)
 \end{aligned}$$

P7.6 Ignored  $r_o$ 

$$a) A_v = \frac{V_A}{V_{in}} \times \frac{V_{out}}{V_A} = \frac{R_{in}}{R_B + R_{in}} \times (-G_m R_{out})$$
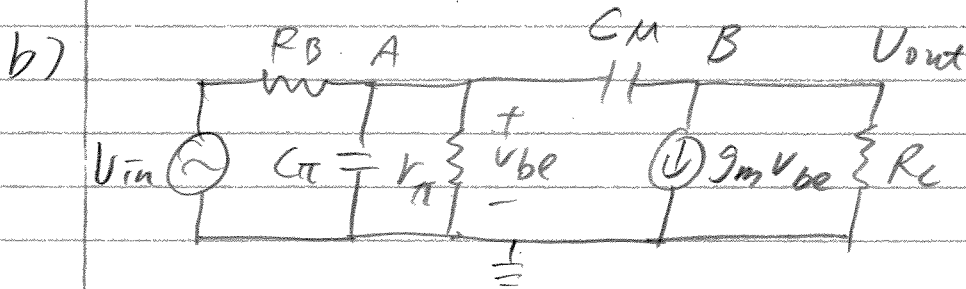
$$\approx \left[ \frac{-r_{\pi}(1 + g_m R_E)}{R_B + r_{\pi}(1 + g_m R_E)} \times \frac{g_m R_C}{1 + g_m R_E} \right] \#$$



$$\left. \begin{aligned} C_A &= C_{\pi} + C_{\mu}(1 - A_v) \\ C_B &= C_{\mu}(1 - A_v^{-1}) \end{aligned} \right\} A_v \text{ from part a)} \#$$

$$c) R_{A,eq} = R_B \parallel r_{\pi}$$

$$R_{B,eq} = R_C$$


$$f_H = \frac{1}{2\pi} \left( \frac{1}{R_{A,eq} C_A + R_{B,eq} C_B} \right) \#$$

$$d) A_v \approx -1389 \text{ V/V}$$

$$f_H \approx 75 \text{ kHz}$$

(see attached)

e)

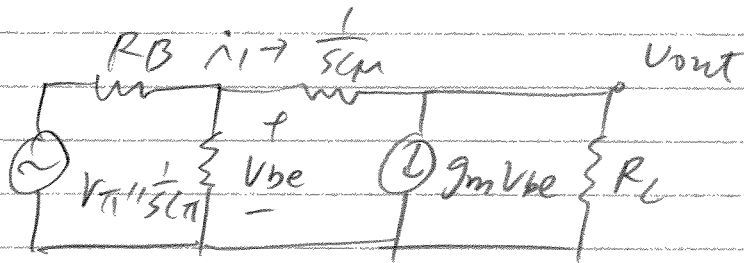

$$\text{KCL } i_1 = g_m V_{be} + \frac{V_{out}}{R_C}$$

$$\text{KCL } \frac{V_{in} - V_{be}}{R_B} = i_1 + \frac{V_{be}}{r_{\pi} \parallel \frac{1}{sC_{\pi}}}$$

$$\begin{aligned} \frac{V_{in}}{R_B} &= g_m V_{be} + \frac{V_{out}}{R_C} + \frac{V_{be}}{r_{\pi} \parallel \frac{1}{sC_{\pi}}} + \frac{V_{be}}{R_B} \\ &= V_{be} \left( g_m + \frac{1}{r_{\pi} \parallel \frac{1}{sC_{\pi}}} + \frac{1}{R_B} \right) + \frac{V_{out}}{R_C} \quad (1) \end{aligned}$$

$$\text{Ohm's Law } V_{be} - \frac{i_1}{sC_{\mu}} = V_{out}$$

$$V_{be} = V_{out} + \frac{g_m}{sC_{\mu}} V_{be} + \frac{V_{out}}{sR_C C_{\mu}}$$

$$\begin{aligned} V_{be} \left( 1 - \frac{g_m}{sC_{\mu}} \right) &= V_{out} \left( 1 + \frac{1}{sR_C C_{\mu}} \right) \\ &= \frac{sC_{\mu} - g_m}{sC_{\mu}} \end{aligned}$$

$$\begin{aligned} \Rightarrow V_{be} &= V_{out} \left( \frac{sR_C C_{\mu} + 1}{sR_C C_{\mu}} \right) \frac{sC_{\mu}}{sC_{\mu} - g_m} \\ &= V_{out} \frac{(sR_C C_{\mu} + 1)}{R_C (sC_{\mu} - g_m)} \quad (2) \end{aligned}$$

Plug (2) into (1)

$$\begin{aligned} \frac{V_{in}}{R_B} &= V_{out} \left[ \frac{sR_C C_{\mu} + 1}{R_C (sC_{\mu} - g_m)} \left( g_m + \frac{1}{r_{\pi} \parallel \frac{1}{sC_{\pi}}} + \frac{1}{R_B} \right) + \frac{1}{R_C} \right] \\ \frac{V_{out}}{V_{in}} &= \left\{ R_B \left[ \frac{sR_C C_{\mu} + 1}{R_C (sC_{\mu} - g_m)} \left( g_m + \frac{1}{r_{\pi} \parallel \frac{1}{sC_{\pi}}} + \frac{1}{R_B} \right) + \frac{1}{R_C} \right] \right\}^{-1} \end{aligned}$$

f) plots attached.

#

```

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #1
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

R1 = 100e3;
R2 = 300e3;
Ri = 2e3;
Re = 13e3;
R7 = 100e3;
Bf = 100; % current gain, A/A
Af = Bf/(Bf+1);
Vt = 0.026; % thermal voltage @ room temp.
Ic = 0.25e-3;

gm = Ic/Vt;
rpi = Bf/gm;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Midband gain
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Rin = (1/R1 + 1/R2 + 1/(rpi+(1+Bf)*Re))^-1;
RL = (1/Re + 1/R7)^-1;
Gain = (Rin/(Ri+Rin))*((1+Bf)*RL/(rpi+(1+Bf)*RL))

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% SCTC - fL
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C1 = 4.7e-6;
C3 = 10e-6;
Re_eq1 = Ri+Rin;
Re_eq3 = R7 + (1/Re + gm)^-1;

FL = (1/(Re_eq1*C1) + 1/(Re_eq3*C3))/(2*pi) %Hz

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #2
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C3 = ((20*pi - (1/(Re_eq1*C1)))^-1)/Re_eq3

clc;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #4
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Vcc = 12;
R1 = 10e3;
R2 = 30e3;
Ri = 250;
rx = 350;
Re1 = 200;
Re2 = 1100;
Rc = 4.3e3;
R3 = 47e3;
Vbeon = 0.7;

```



```

Bf = 100; % current gain, A/A
Af = Bf/(Bf+1);
Vt = 0.026; % thermal voltage @ room temp.

% DC bias

Vb = R1*Vcc/(R1+R2)
Ve = Vb-Vbeon
Ie = Ve/(Re1+Re2);
Ic = Af*Ie
Vc = Vcc - (Ic*Rc) % check for FAR mode

gm = Ic/Vt;
rpi = Bf/gm;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Midband gain
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Rin = (1/R1 + 1/R2 + 1/(rpi+rx+(1+Bf)*Re1))^-1;
Rout = (1/Rc + 1/R3)^-1;
Gain = -(gm/(1+gm*Re1))*(Rout) * (Rin/(Ri+Rin))

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% SCTC - fL
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C1 = 5e-6;
C2 = 1e-6;
C3 = 4.7e-6;
Re_eq1 = Ri+Rin;
Re_eq2 = R3+Rc;
Re_eq3 = Re1 + (1/gm);

FL = (1/(Re_eq1*C1) + 1/(Re_eq2*C2) + 1/(Re_eq3*C3))/(2*pi) %Hz

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% OCTC - fH
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Cu = 1e-12;
ft = 200e6;
Cpi = (gm/ft) - Cu

GS=1/Ri+1/R1+1/R2;
Rs=1/GS;
Rpi_eq = 1/(1/rpi+(1+gm*Re1)/(Rs+Re1))

Rin = 1/(1/Ri + 1/R1 + 1/R2 + 1/(rpi+rx+(1+Bf)*Re1));
Rout = 1/(1/Rc + 1/R3);
GM = gm/(1+gm*Re1);
Ru_eq = Rin + Rout*(1+GM*Rin);

FH = 1/(2*pi*(Rpi_eq*Cpi + Ru_eq*Ccu))

```

```

Bf = 100; % current gain, A/A
Af = Bf/(Bf+1);
Vt = 0.026; % thermal voltage @ room temp.

% DC bias

Vb = R1*Vcc/(R1+R2)
Ve = Vb-Vbeon
Ie = Ve/(Re1+Re2);
Ic = Af*Ie
Vc = Vcc - (Ic*Rc) % check for FAR mode

gm = Ic/Vt;
rpi = Bf/gm;

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% Midband gain
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Rin = (1/R1 + 1/R2 + 1/(rpi+rx+(1+Bf)*Re1))^-1;
Rout = (1/Rc + 1/R3)^-1;
Gain = -(gm/(1+gm*Re1))*(Rout) * (Rin/(Ri+Rin))

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% SCTC - fL
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

C1 = 5e-6;
C2 = 1e-6;
C3 = 4.7e-6;
Re_eq1 = Ri+Rin;
Re_eq2 = R3+Rc;
Re_eq3 = Re1 + (1/gm);

FL = (1/(Re_eq1*C1) + 1/(Re_eq2*C2) + 1/(Re_eq3*C3))/(2*pi) %Hz

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% OCTC - fH
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

Cu = 1e-12;
ft = 200e6;
Cpi = (gm/ft) - Cu

GS=1/Ri+1/R1+1/R2;
Rs=1/GS;
Rpi_eq = 1/(1/rpi+(1+gm*Re1)/(Rs+Re1))

Rin = 1/(1/Ri + 1/R1 + 1/R2 + 1/(rpi+rx+(1+Bf)*Re1));
Rout = 1/(1/Rc + 1/R3);
GM = gm/(1+gm*Re1);
Ru_eq = Rin + Rout*(1+GM*Rin);


FH = 1/(2*pi*(Rpi_eq*Cpi + Ru_eq*Ccu))

```

```

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #6
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

```

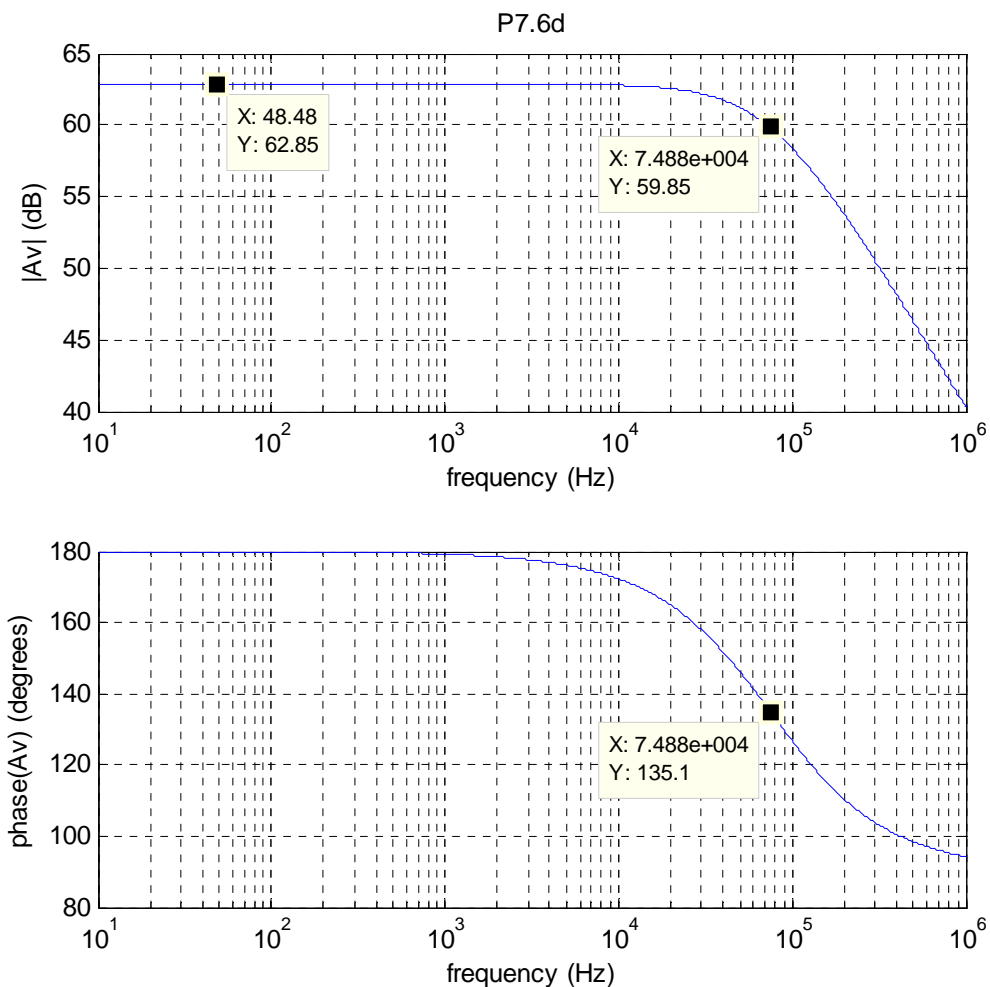

```

Rb = 1e3;
Rc = 50e3;
Bf = 100;
Cu = 2e-12;
Cje = 0; %no depletion cap, just consider diffusion cap for B-E junction
Ic = 1e-3;
Tf = 500e-12;
Vt = 0.026;

gm = Ic/Vt;
rpi = Bf/gm;
Cpi = gm*Tf;

Av = -gm*Rc*(rpi/(Rb+rpi));
CA = Cpi + Cu*(1-Av);
CB = Cu*(1-(1/Av));
RAeq = (1/Rb + 1/rpi)^-1;
RBeq = Rc;

fH = (1/(RAeq*CA + RBeq*CB))/(2*pi)

f = logspace(1,6,10000);

```

```



Gain = Av./(1+(j*f./fH));
subplot(2,1,1);
semilogx(f,20*log10(abs(Gain)));
grid on
xlabel('frequency (Hz)');
ylabel('|Av| (dB)');
title('P7.6d');
subplot(2,1,2);
semilogx(f,angle(Gain)*180/pi);
grid on
xlabel('frequency (Hz)');
ylabel('phase(Av) (degrees)');

```

```

%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%
% #6e
%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%%

```

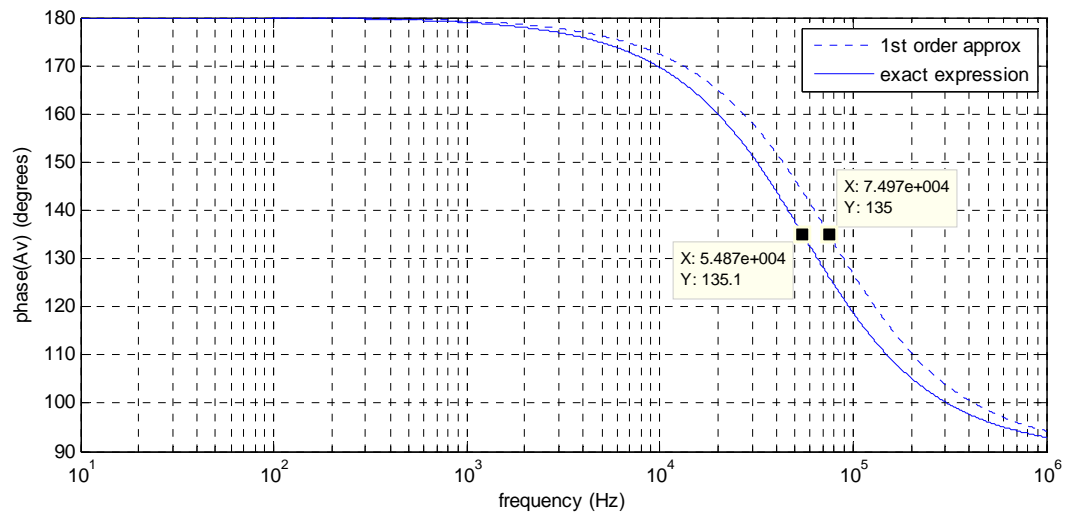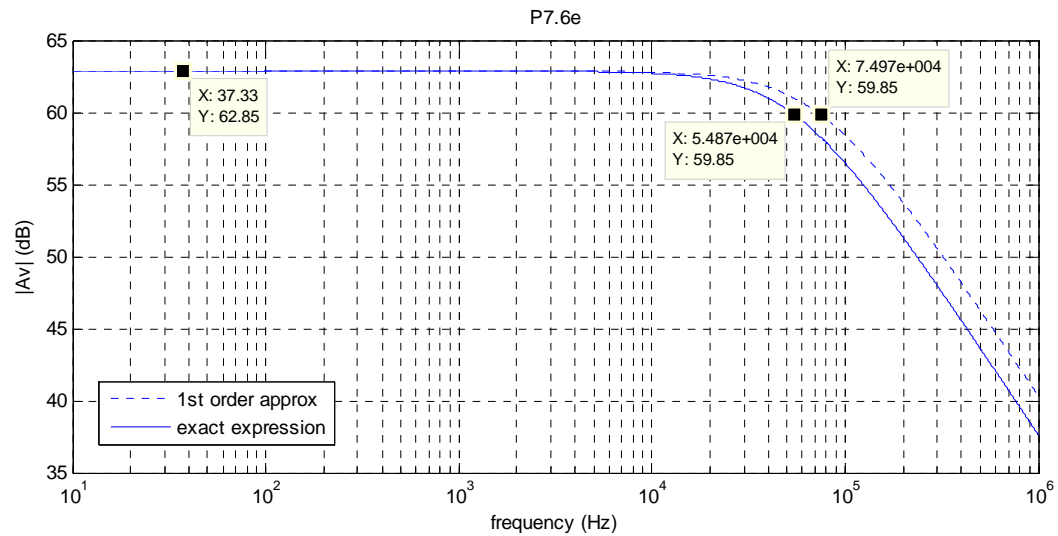

```

Gain_e = 1./ (Rb.*(((1+j*2*pi.*f.*Rc*Cu)./(Rc.*(j*2*pi.*f.*Cu-
gm))).*(gm+((1/rpi)+j*2*pi.*f.*Cpi)+(1/Rb)))+(1/Rc)));
subplot(2,1,1);
semilogx(f,20*log10(abs(Gain)),':');
hold on
semilogx(f,20*log10(abs(Gain_e)));
hold off
grid on
xlabel('frequency (Hz)');
ylabel('|Av| (dB)');
title('P7.6e');
legend('1st order approx','exact expression');
subplot(2,1,2);
semilogx(f,angle(Gain)*180/pi,':');
hold on
semilogx(f,angle(Gain_e)*180/pi);
hold off
grid on
xlabel('frequency (Hz)');
ylabel('phase(Av) (degrees)');
legend('1st order approx','exact expression');

```