

# EECS 373

## Design of Microprocessor-Based Systems

Robert Dick  
University of Michigan

Lecture 15: Interface circuits and wireless

9 March 2017

# Outline

- Context and review
- Power supplies
- Voltage regulators
- Signal conditioning
- Wireless communication

## Context and review

- Relationships among power, temperature, and reliability.
- PCB power integrity.
- Several mechanical devices.
- H bridges.
- Shaft encoders.

# Outline



- ~~Context and review~~
- Power supplies
- Voltage regulators
- Signal conditioning
- Wireless communication

# Power supplies

- Goals (Why?).
  - Always stably output desired voltage.
  - V requirements may change w. time.
- Reality
  - Available voltage wrong sometimes or always.
  - High parasitics.
    - $L \rightarrow di/dt$  = droops/spikes w. current var.

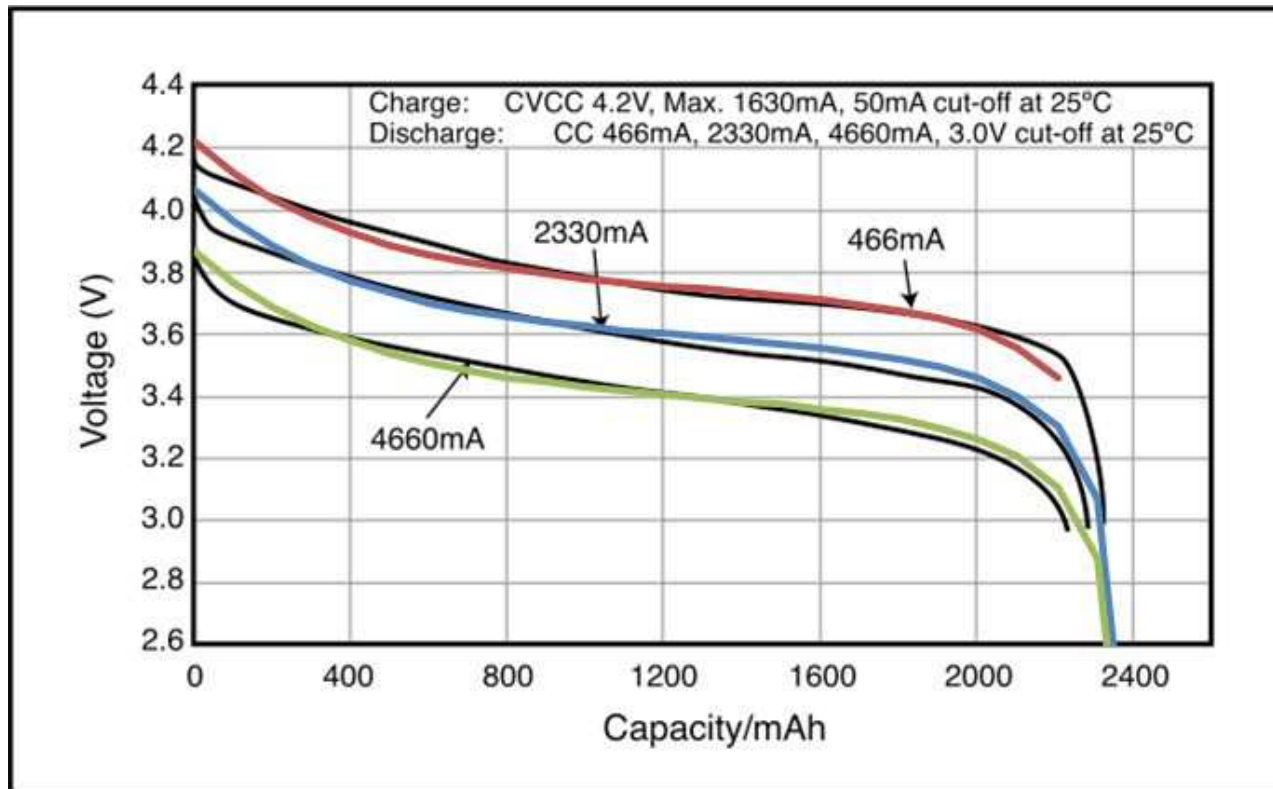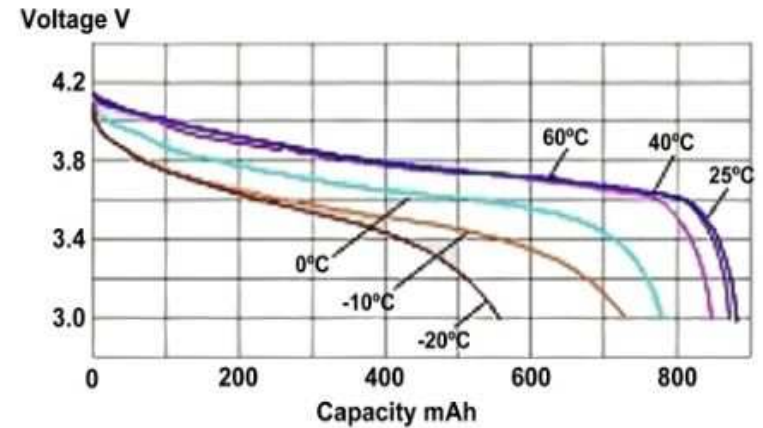
# Battery discharge curve

- Beware startup peak.
- Load matters.
  - Series R.
- T matters.



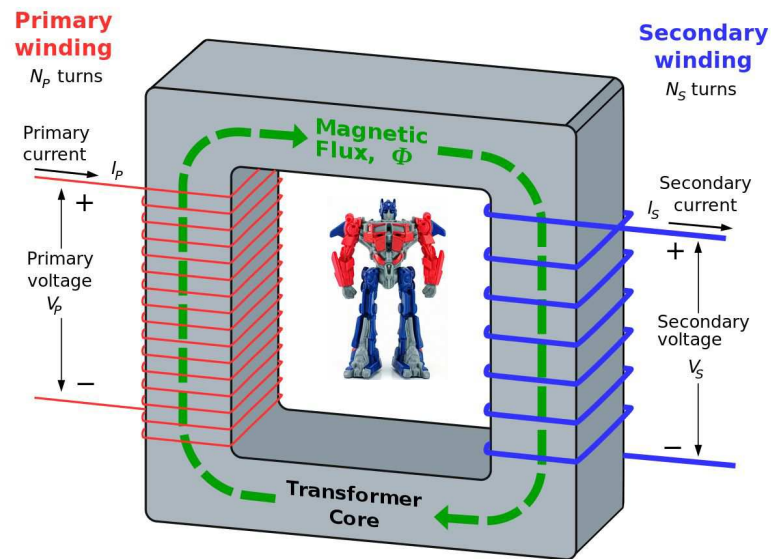
# AC-AC

- Winding ratio.
  - Step up or down voltage.
- Expensive and bulky.


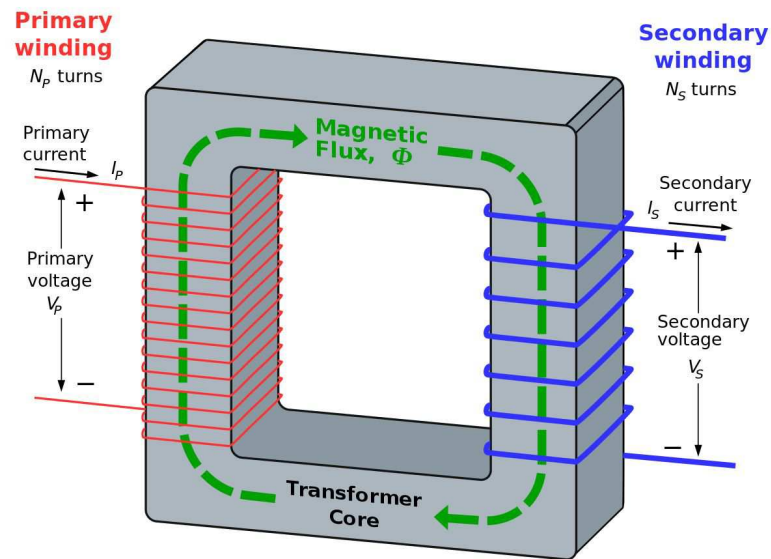
# AC-AC



- Winding ratio.
  - Step up or down voltage.
- Expensive and bulky.




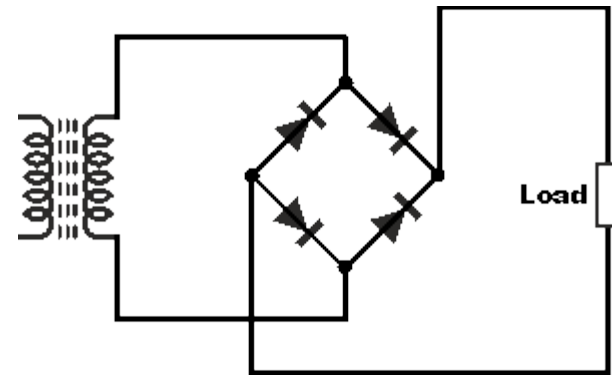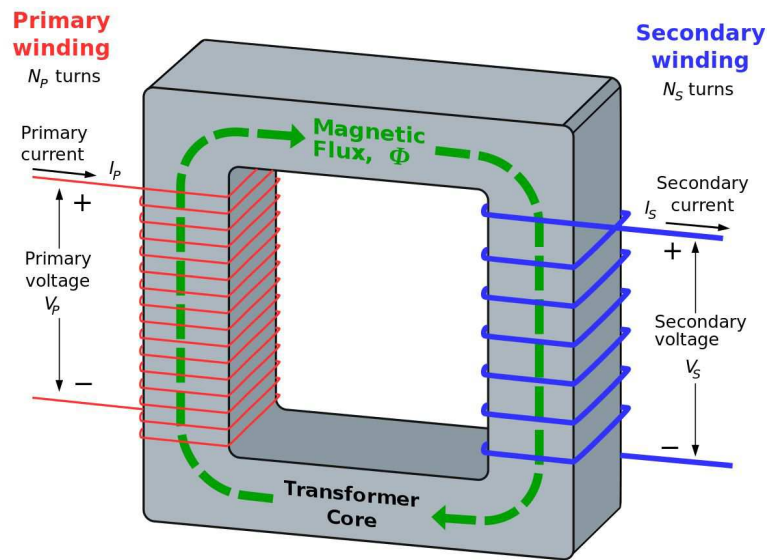
# AC-DC

- Need DC.
- Full-wave rectifier.
- What does this do to waveform?
- How to make stable? C.
- Tolerate changing input V? Zener.



# Outline

- ~~Context and review~~
- ~~Power supplies~~
- Voltage regulators
- Signal conditioning
- Wireless communication

## Linear DC-DC

- Simple, Zener-based.
- Inefficient for large  $V$  conversion.
- Will give reading material for review.

## Charge pump DC-DC

- Charge C.
- Stack with source.
- Repeat.
- Not great for high power.
- Good for communication.
- Can control charging period to control V.

# Buck switching DC-DC

- Efficient.
- Step-down, only.
- Max output =  $V_{in} - V_{loss}$ .

# Buck-boost switching DC-DC

- Efficient.
- Step up or down.
  - $0X \rightarrow 2X$ .
- Inverting.


# None

- Don't always need regulator.
- They're only around 85% efficient.
- Terrible for usually-sleeping systems.
- Built-in battery C is useful.
- Can components can tolerate full swing?
  - Consider Lilon start-up peak!

See

<http://robertdick.org/publications/kim07oct.html>

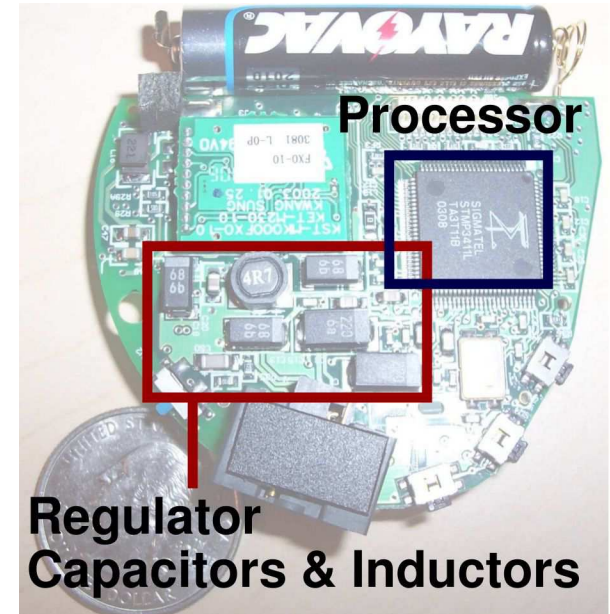Will post many other regulator references to website today.



# Outline


- ~~Context and review~~
- ~~Power supplies~~
- ~~Voltage regulators~~
- Signal conditioning
- Wireless communication



# Signal conditioning


- Why? Bare sensor characteristics clash with ADC.
- Problems with many sensor outputs.
  - High internal resistance.
  - Voltage range mismatch.
  - Unwanted frequencies.
  - Fluctuating near-DC offset.
- Solutions.
  - Low-pass/high-pass/notch filters.
  - Amplifiers.

# Filter order

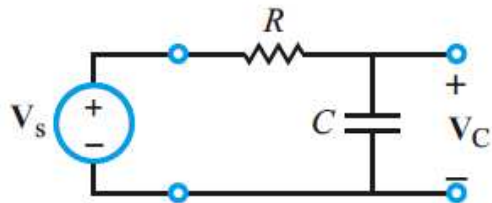


(a)

First-order filter

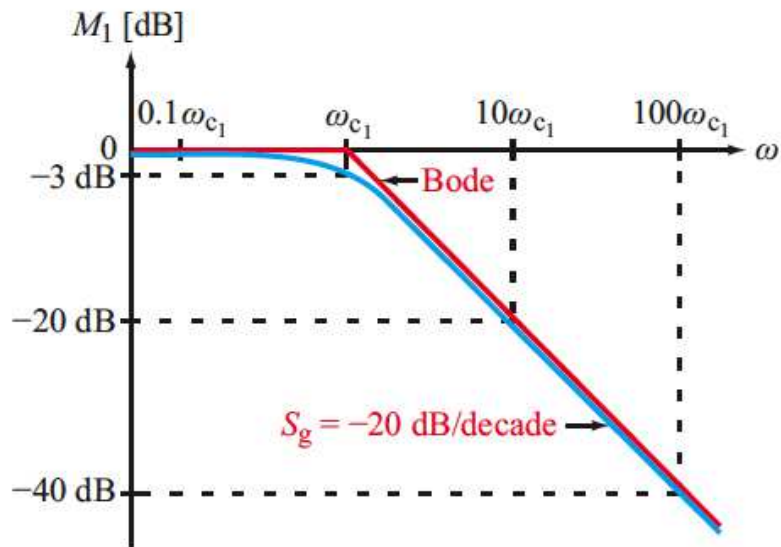


(b)

Response of first-order filter

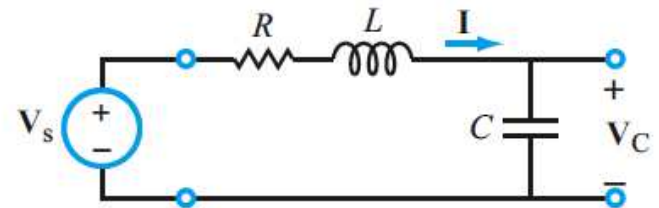

(c)



Second-order filter

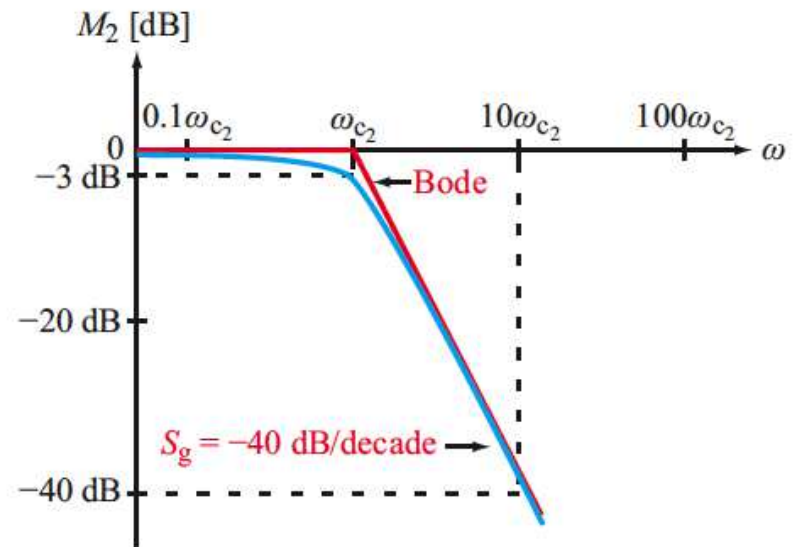

(d)

Response of second-order filter

# Realistic op-amp model

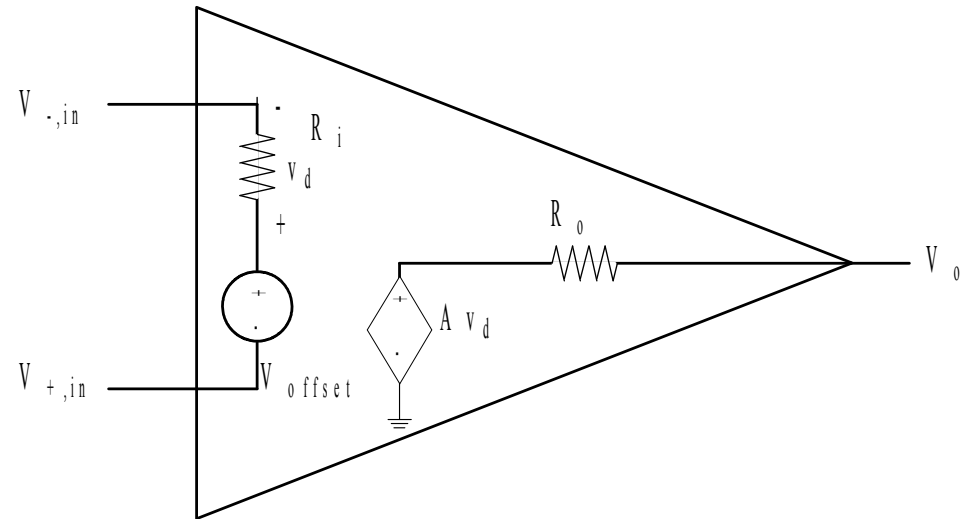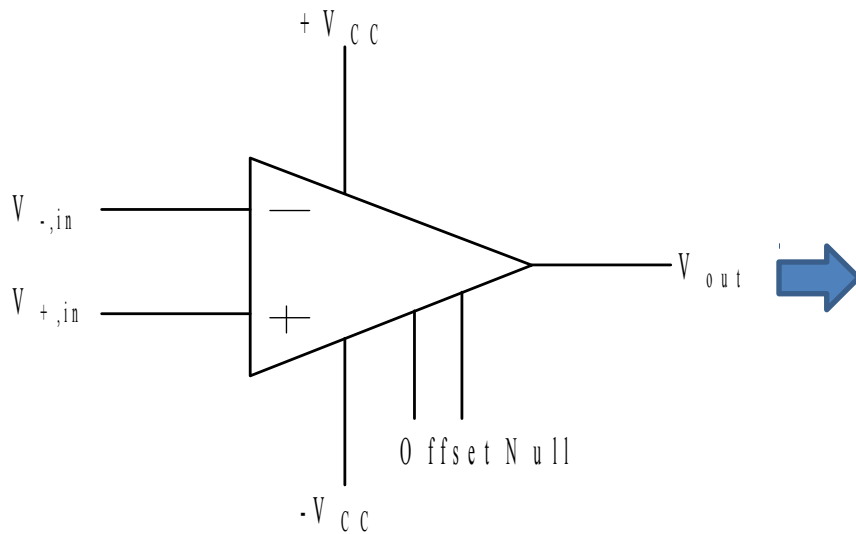


$R_i = 2 \text{ M}\Omega$   
 $V_{offset} = 4 \text{ mV}$   
 $A = 20\text{M}$   
 $R_o = 75 \text{ }\Omega$


- Nonlinear behavior not represented in model.
- **Consider power supply V.**

$R_i < \infty$   
 $V_{offset} \neq 0 \text{ V}$   
 $A < \infty$   
 $R_o > 0 \text{ }\Omega$

# Ideal op-amp model

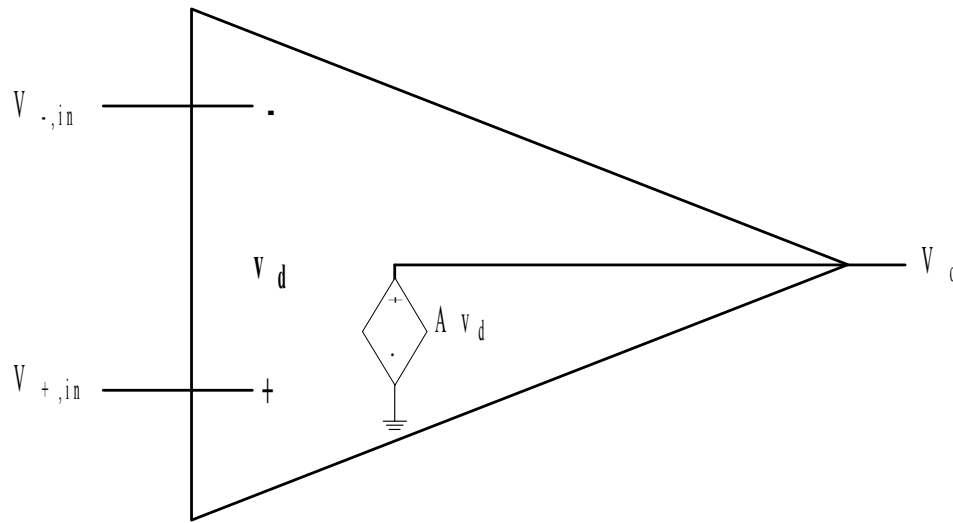

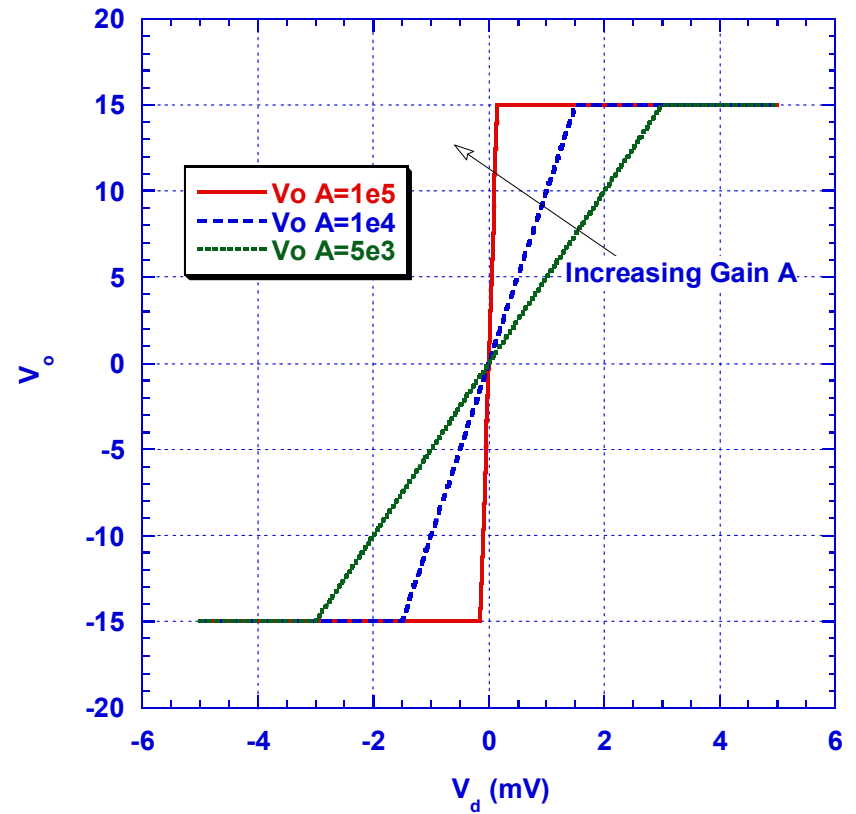
$R_i \rightarrow \infty$   
 $V_{offset} = 0 \text{ V}$   
 $A \rightarrow \infty$   
 $R_o = 0 \Omega$




# Op-amp “Golden Rules”
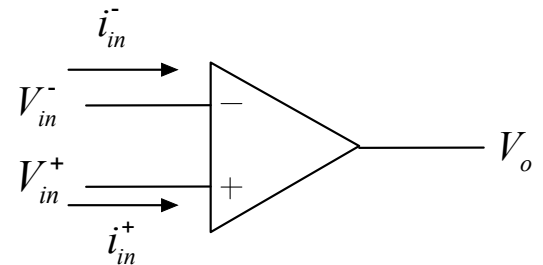
## For negative feedback


- Gain is infinite so input voltages equal.
- Input resistance infinite so input current zero.



# Nodal analysis for noninverting case

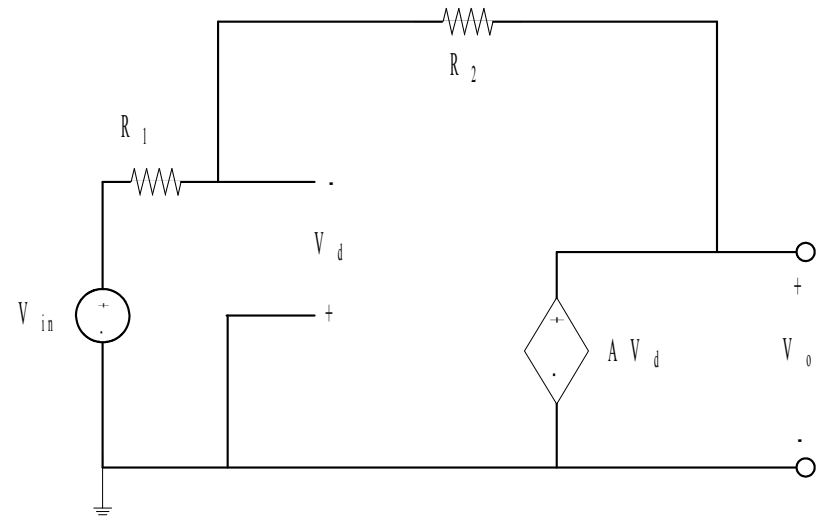


# First-order active lowpass filter

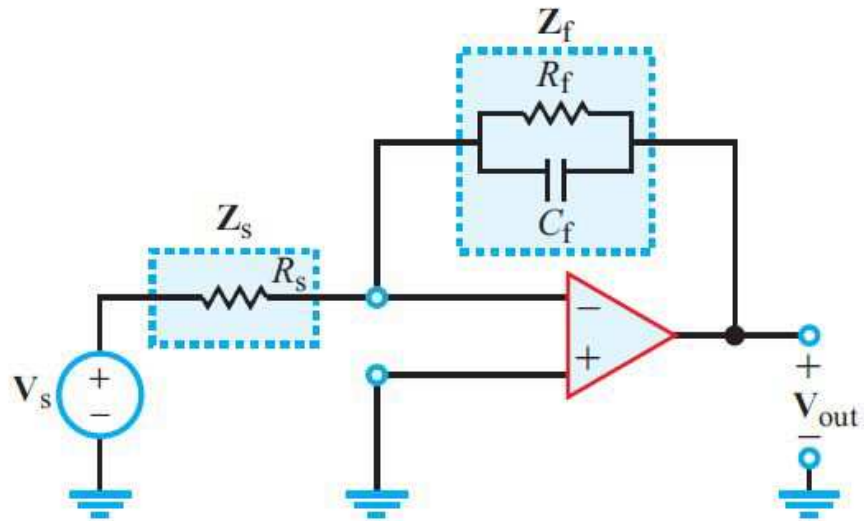

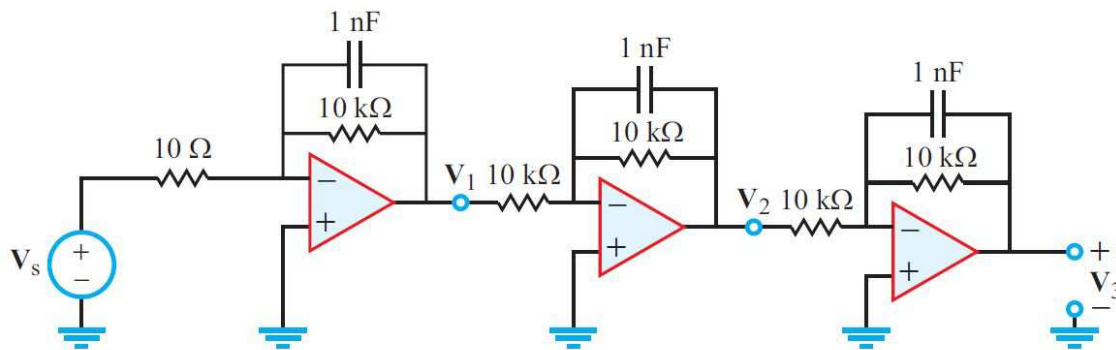
# Cascading of active filters


Create a higher-order filter by cascading.



(a) Circuit diagram

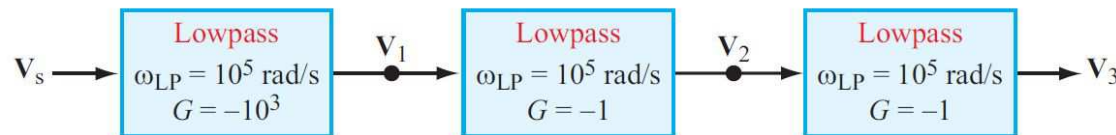

(b) Block diagram


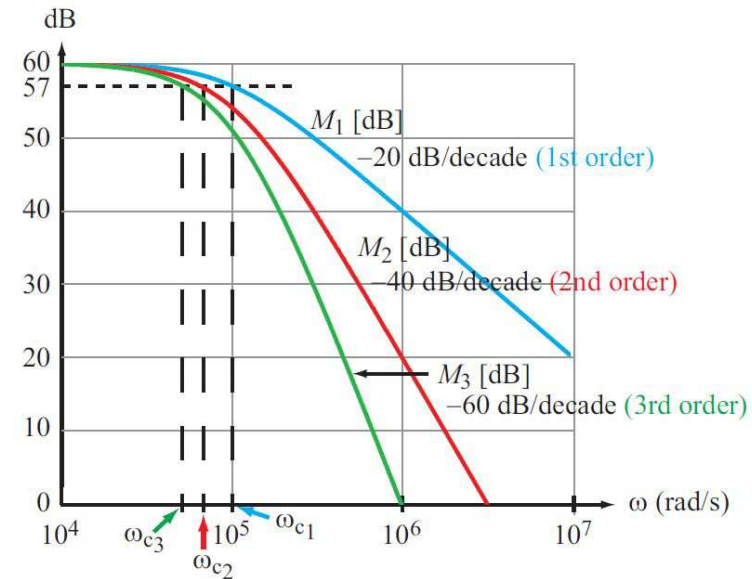


(c) Transfer function plots





# Cascading active filters

Create band filters by cascading.

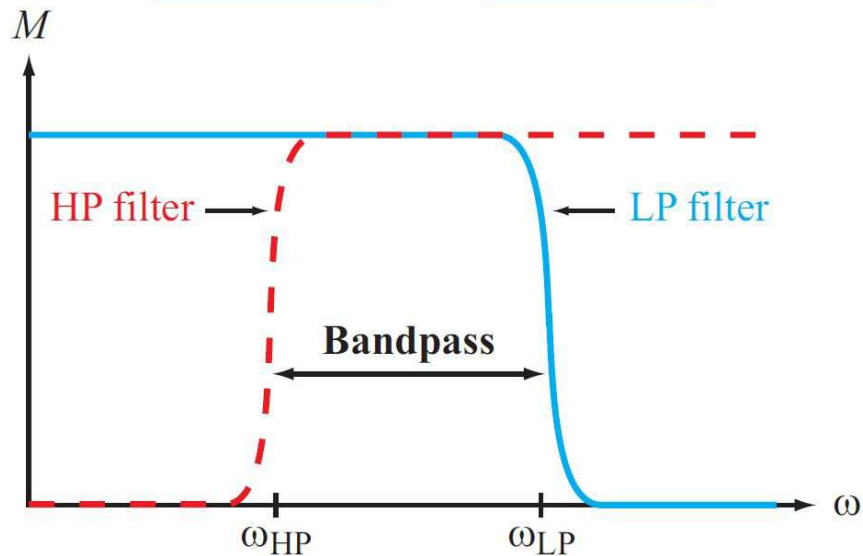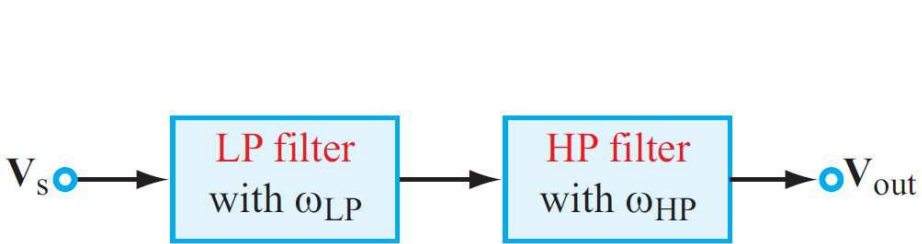

(a) Bandpass filter

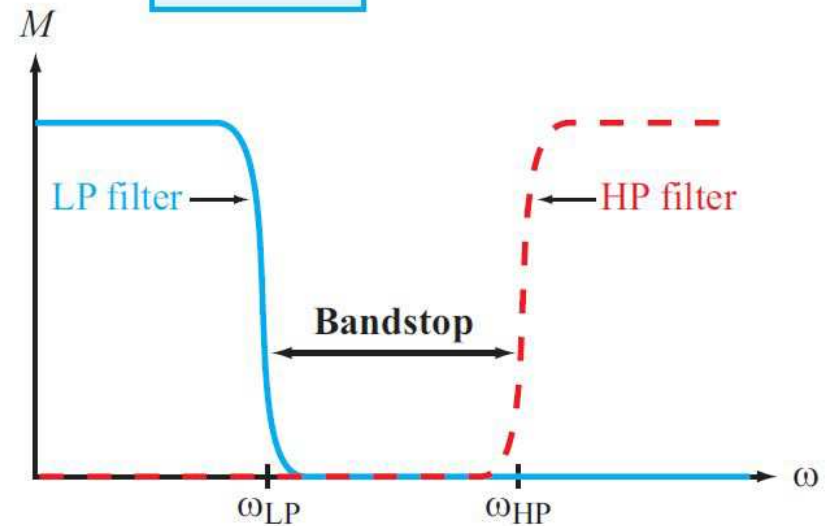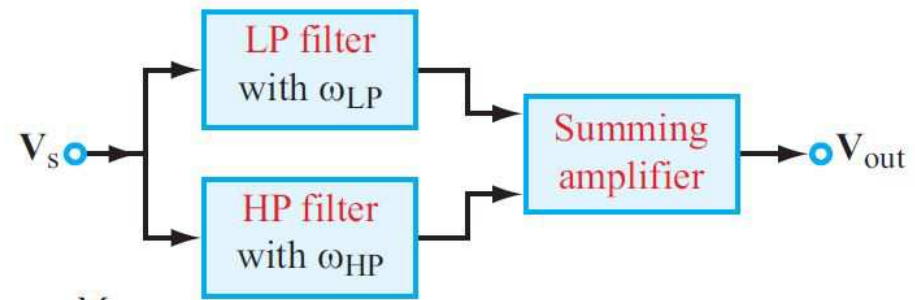

(b) Bandreject filter

# Instrumentation amplifiers

- Amplifies differential signal.
- Rejects ground (common-mode) noise.
- Most designs use multiple op amps.

# References

- Paul Horowitz and Winfield Hill, “The Art of Electronics.”
- Howard M. Berlin, “Design of OP-AMP Circuits.”
- Any decent introductory circuits book.
- Application notes from op amp manufacturers.

# Outline

- ~~Context and review~~
- ~~Power supplies~~
- ~~Voltage regulators~~
- ~~Signal conditioning~~
- **Wireless communication**

# Wireless communication

- Reliability.
- Power.

# Wireless environment

- Noise.
- Absorption.
- Reflection.
- Multipath.
- Environmental conditions.

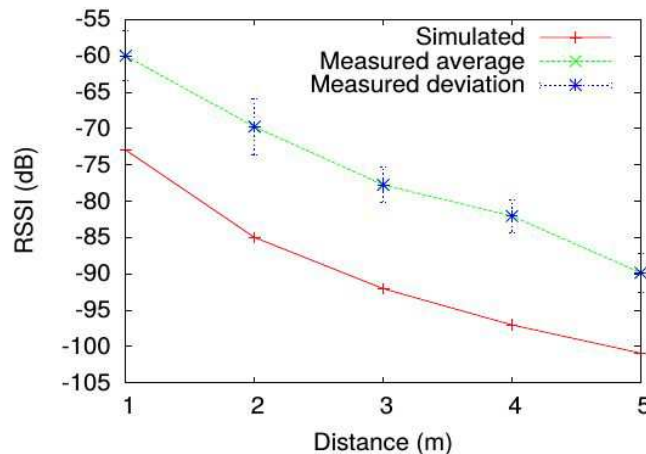


Figure 6.10: Comparison of measured and simulated RSSIs with nodes sitting on the ground.


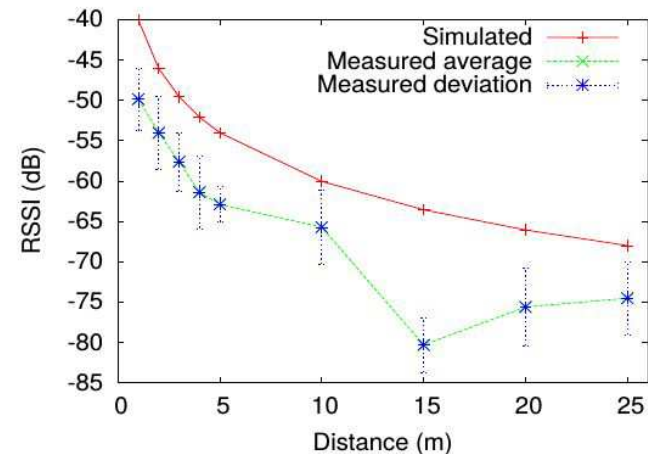
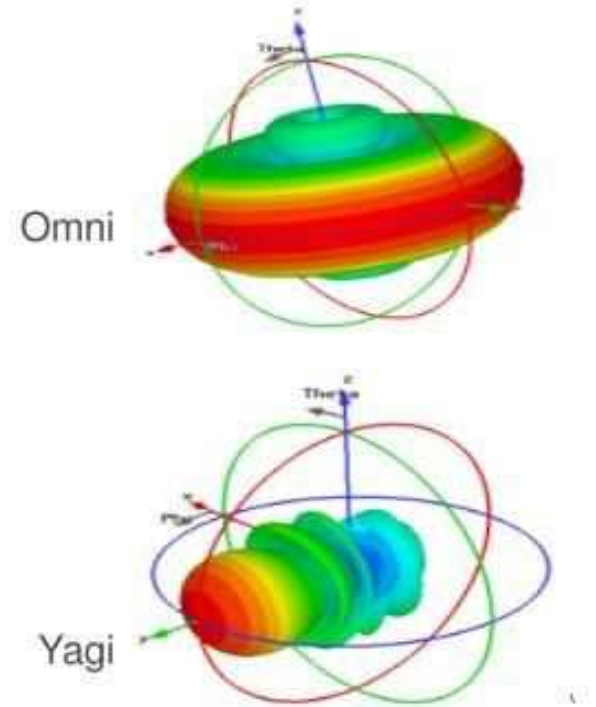


Figure 6.11: Comparison of measured and simulated RSSIs with nodes raised 0.95 m from ground.

# Anisotropic radiation patterns

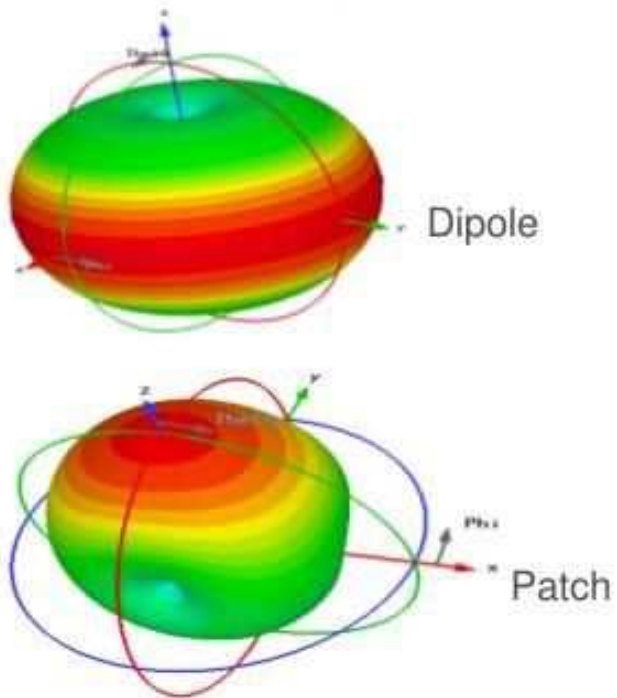


Credit to fpvlair.com for image.

# Wireless motion

- Antenna motion.
- Conductive material motion.

Table 2.3: Classification Performance

Environment	Sensitivity (%)	Specificity (%)
Office I	99.6	96.5
Office II	100.0	87.7
Cafeteria	91.4	86.6
Outdoor	95.9	61.1

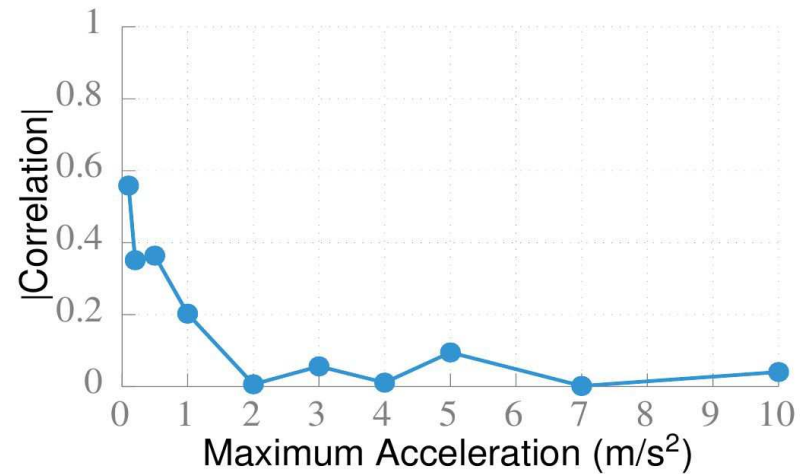



# Communication power

1. Antenna.
2. Electronics.

# Radiated energy

- Radiated power depends on distance.
  - Hit target SNR at receiver.
  - For given rate,  $P_r \propto d^\alpha$ ,  $\alpha \approx 3-4$ .
- Small antennas may be inefficient.
- Power into amp often  $\approx 4$  times transmitter power.

## Communication energy

- Circuit energy is roughly constant and independent of distance.
  - On order of 1-10mW.
- For large distances, transmission energy dominates.
- For short distance, circuit energy should also be considered.

## Communication energy

**Example:** For a particular radio the power consumption while on is 2mW. When transmitting at a peak power of 10mW the power amplifier has an energy efficiency of 25%.

What is total power while transmitting?

# Communication power and multi-hop

- Are two hops better than one?
- Superlinear increase in energy with distance.
- Constant energy hit regardless of distance.

# Processing vs. transmitting

- For motes, transmitting 1-bit costs same as executing  $\approx 1,000$  processor instructions.
- Can save on transmission costs by intelligently processing data before transmitting!
- Data aggregation/fusion.

# Dynamic power management

- Dynamic power management also useful for communication power.
- Turn radio off when nothing to send/receive.
- Note while off can **not** receive.
- Taking into account DPM can change transceiver trade-offs.
  - Better to send fast and sleep or slow?

# Hibernation

When to wake up?

Possibilities

1. At regular intervals.
  - Need synchronization.
2. Trigger by stimulus.
  - E.g., heat-sensitive circuit.