



# EECS 373

## Design of Microprocessor-Based Systems

Robert Dick  
University of Michigan

Lecture 15: Interface circuits and wireless

9 March 2017

### Outline

- Context and review
- Power supplies
- Voltage regulators
- Signal conditioning
- Wireless communication

1

2

### Context and review

- Relationships among power, temperature, and reliability.
- PCB power integrity.
- Several mechanical devices.
- H bridges.
- Shaft encoders.

### Outline

- Context and review
- Power supplies
- Voltage regulators
- Signal conditioning
- Wireless communication

3



4

### Power supplies

- Goals (Why?).
  - Always stably output desired voltage.
  - V requirements may change w. time.
- Reality
  - Available voltage wrong sometimes or always.
  - High parasitics.
    - $L \rightarrow dI/dt = \text{droops/spikes w. current var.}$
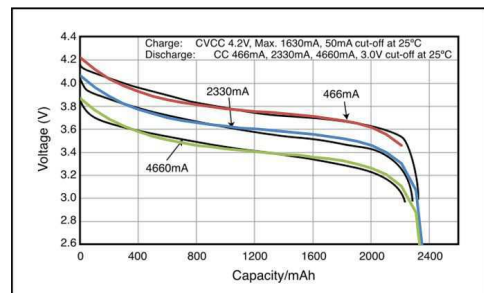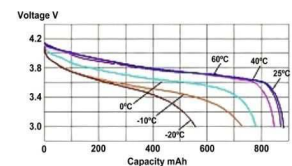
### Battery discharge curve

- Beware startup peak.
- Load matters.
  - Series R.
- T matters.




5

6
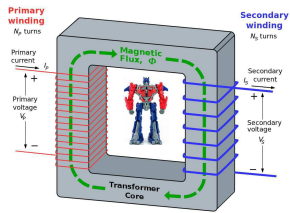
## AC-AC


- Winding ratio.
- Step up or down voltage.
- Expensive and bulky.



7
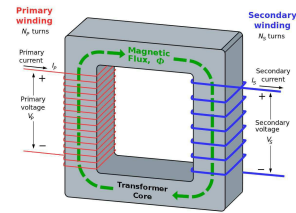
## AC-AC


- Winding ratio.
- Step up or down voltage.
- Expensive and bulky.



8
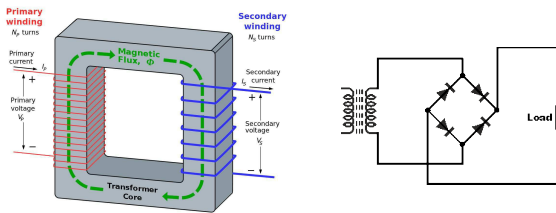
## AC-DC

- Need DC.
- Full-wave rectifier.
- What does this do to waveform?
- How to make stable? C.
- Tolerate changing input V? Zener.



9

## Outline

- Context and review
- Power supplies
- [Voltage regulators](#)
- Signal conditioning
- Wireless communication

10

## Linear DC-DC

- Simple, Zener-based.
- Inefficient for large V conversion.
- Will give reading material for review.

## Charge pump DC-DC

- Charge C.
- Stack with source.
- Repeat.
- Not great for high power.
- Good for communication.
- Can control charging period to control V.

11

12

## Buck switching DC-DC

- Efficient.
- Step-down, only.
- Max output =  $V_{in} - V_{loss}$ .

13


## Buck-boost switching DC-DC

- Efficient.
- Step up or down.
  - $0X \rightarrow 2X$ .
- Inverting.

14
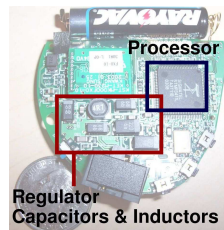
## None

- Don't always need regulator.
- They're only around 85% efficient.
- Terrible for usually-sleeping systems.
- Built-in battery C is useful.
- Can components can tolerate full swing?
  - Consider Lilon start-up peak!



See

<http://robertdick.org/publications/kim07oct.html>

Will post many other regulator references to website today.

15

## Outline


- Context and review
- Power supplies
- Voltage regulators
- Signal conditioning
- Wireless communication

16

## Signal conditioning


- Why? Bare sensor characteristics clash with ADC.
- Problems with many sensor outputs.
  - High internal resistance.
  - Voltage range mismatch.
  - Unwanted frequencies.
  - Fluctuating near-DC offset.
- Solutions.
  - Low-pass/high-pass/notch filters.
  - Amplifiers.

## Filter order

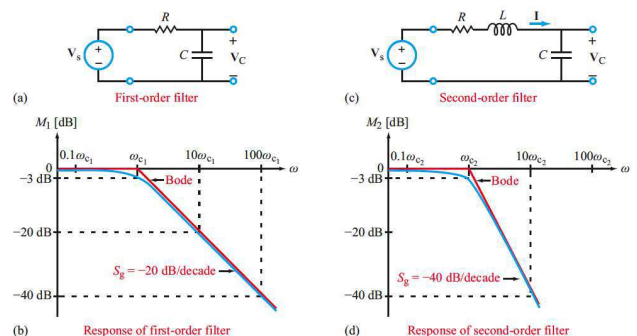

17

## Realistic op-amp model

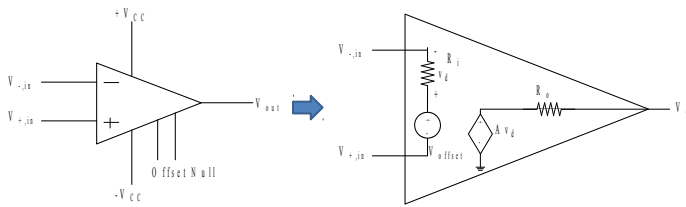


$R_i = 2 \text{ M}\Omega$   
 $V_{\text{offset}} = 4 \text{ mV}$   
 $A = 20\text{M}$   
 $R_0 = 75 \Omega$


- Nonlinear behavior not represented in model.
- Consider power supply  $V$ .

$R_i < \infty$   
 $V_{\text{offset}} \neq 0 \text{ V}$   
 $A < \infty$   
 $R_0 > 0 \Omega$

## Ideal op-amp model

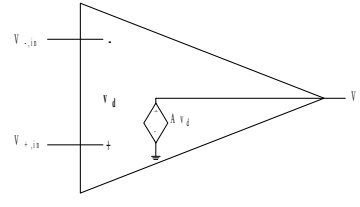

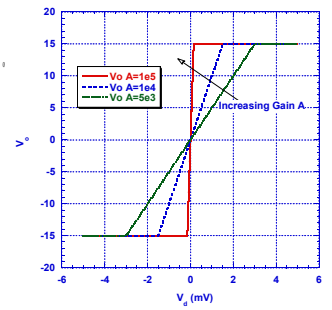$R_i \rightarrow \infty$   
 $V_{\text{offset}} = 0 \text{ V}$   
 $A \rightarrow \infty$   
 $R_0 = 0 \Omega$





## Op-amp “Golden Rules”


For negative feedback

- Gain is infinite so input voltages equal.
- Input resistance infinite so input current zero.

## Nodal analysis for noninverting case

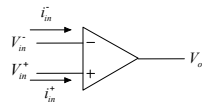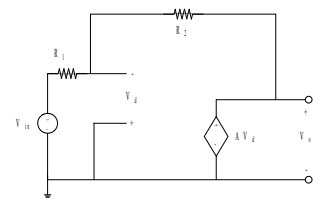


## First-order active lowpass filter

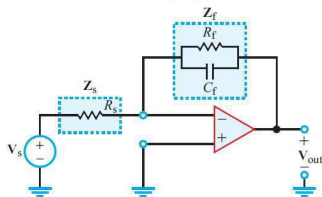

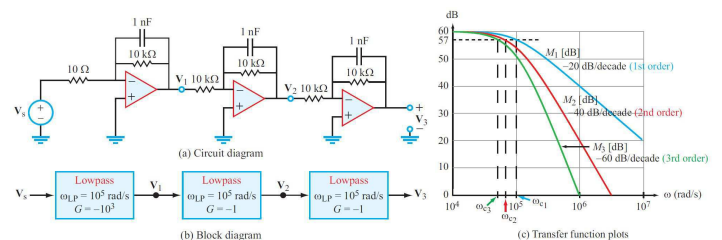
## Cascading of active filters

Create a higher-order filter by cascading.



## Cascading active filters

Create band filters by cascading.

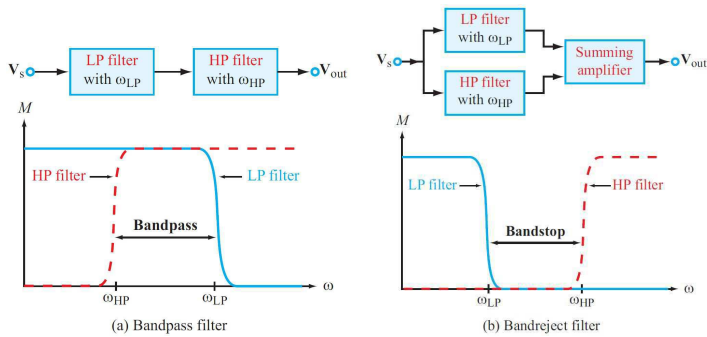

26

## Instrumentation amplifiers

- Amplifies differential signal.
- Rejects ground (common-mode) noise.
- Most designs use multiple op amps.

## References

- Paul Horowitz and Winfield Hill, "The Art of Electronics."
- Howard M. Berlin, "Design of OP-AMP Circuits."
- Any decent introductory circuits book.
- Application notes from op amp manufacturers.

## Outline

- Context and review
- Power supplies
- Voltage regulators
- Signal conditioning
- Wireless communication

27

## Wireless communication

- Reliability.
- Power.

## Wireless environment

- Noise.
- Absorption.
- Reflection.
- Multipath.
- Environmental conditions.

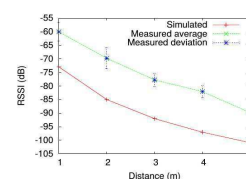


Figure 6.10: Comparison of measured and simulated RSSIs with nodes sitting on the ground.


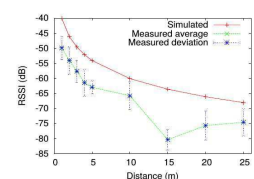


Figure 6.11: Comparison of measured and simulated RSSIs with nodes raised 0.95 m from ground.

29

30

## Anisotropic radiation patterns

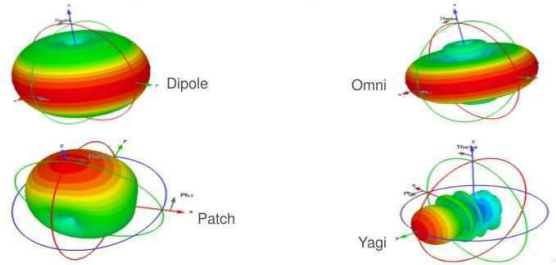

Credit to fpvlair.com for image.


31

## Wireless motion

- Antenna motion.
- Conductive material motion.

Table 2.3: Classification Performance

Environment	Sensitivity (%)	Specificity (%)
Office I	99.6	96.5
Office II	100.0	87.7
Cafeteria	91.4	86.6
Outdoor	95.9	61.1

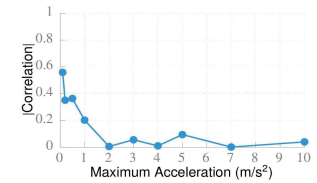

32

## Communication power

1. Antenna.
2. Electronics.

## Radiated energy

- Radiated power depends on distance.
  - Hit target SNR at receiver.
  - For given rate,  $P_r \propto d^\alpha$ ,  $\alpha \approx 3-4$ .
- Small antennas may be inefficient.
- Power into amp often  $\approx 4$  times transmitter power.

## Communication energy

- Circuit energy is roughly constant and independent of distance.
  - On order of 1-10mW.
- For large distances, transmission energy dominates.
- For short distance, circuit energy should also be considered.

## Communication energy

**Example:** For a particular radio the power consumption while on is 2mW. When transmitting at a peak power of 10mW the power amplifier has an energy efficiency of 25%.

What is total power while transmitting?

## Communication power and multi-hop

- Are two hops better than one?
- Superlinear increase in energy with distance.
- Constant energy hit regardless of distance.

## Processing vs. transmitting

- For motes, transmitting 1-bit costs same as executing  $\approx 1,000$  processor instructions.
- Can save on transmission costs by intelligently processing data before transmitting!
- Data aggregation/fusion.

## Dynamic power management

- Dynamic power management also useful for communication power.
- Turn radio off when nothing to send/receive.
- Note while off can **not** receive.
- Taking into account DPM can change transceiver trade-offs.
  - Better to send fast and sleep or slow?

## Hibernation

When to wake up?

Possibilities

1. At regular intervals.
  - Need synchronization.
2. Trigger by stimulus.
  - E.g., heat-sensitive circuit.