

Homework 1 Solutions


1 Combinational Logic Review

1a)

a	b	c	b'c'	bc'	ab'c	b'c' + bc' + ab'c
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	1	0	0	1	0	1
0	1	1	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	0	1	1
1	1	0	0	1	0	1
1	1	1	0	0	0	0

1b)

$$c' + ab'$$

 


1c)

2a)

io0	io1	s	p
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

2b)

$io0*s' + io1*s$

 



3a)

a	b	ci	co	s	co'
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	1	0

3b)

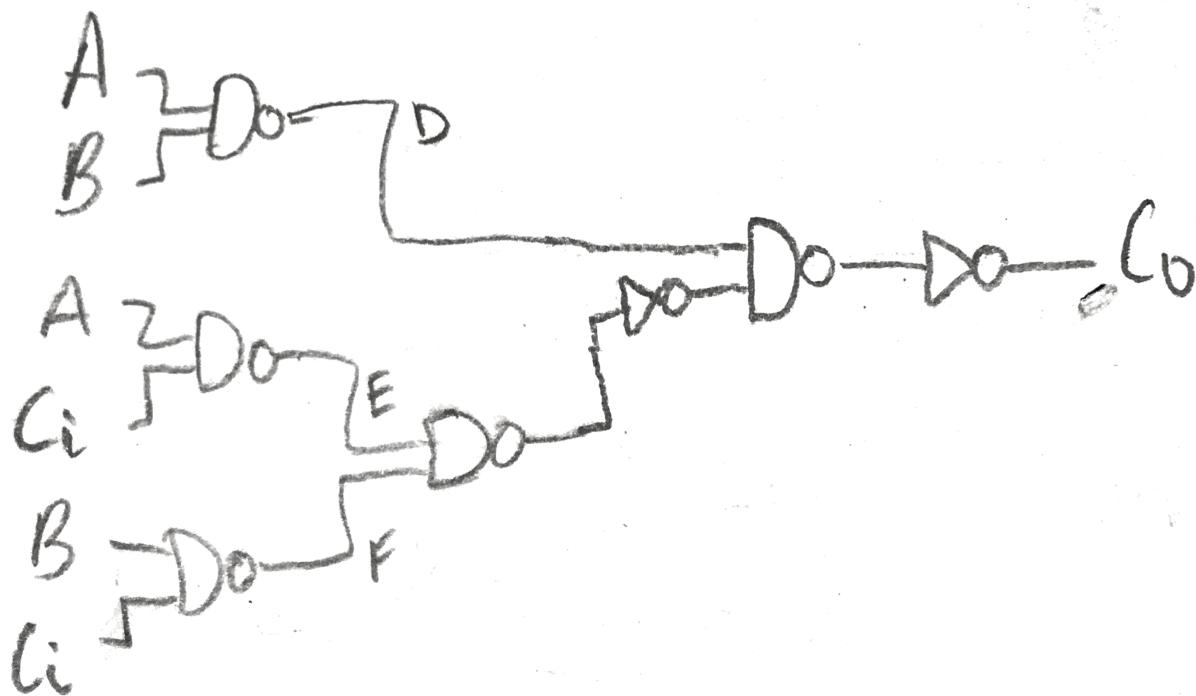With generating s, and generating co with all NANDs (I think this is more optimized, by a bit):



 

Generating co with all NORs:

2 Verilog for Combinational Logic

4a)

To determine proper parentheses use, see http://www.ee.ed.ac.uk/~gerard/Teach/Verilog/manual/Appendices/op_prec.html for the order of operations.

You could also use logical operators (&&, ||, !) instead of bitwise (&, |, ~). Brehob prefers using bitwise for logic like this. Using them interchangeably is inappropriate (but would still work in this instance).

```
assign p = (~a)&b | ~(a&(~c)) | (b^c);
```

4b)

```
assign p = (s & io1) | (~s & io0);
```

5a)

```
module MUX21 (io0, io1, s, p);
```

```

input io0, io1, s;
output P;
wire P;

assign p = (s == 1)? io1: io0;
// alternatively
// assign p = (s & io1) | (~s & io0);

endmodule // end of MUX21 module

```

5b)

```

module MUX41 (io0, io1, io2, io3, s0, s1, p);

input io0, io1, io2, io3, s0, s1;
output p;
wire w0, w1;

MUX21(io0, io1, s0, w0);
MUX21(io2, io3, s0, w1);
MUX21(w0, w1, s1, p);

endmodule // end of MUX41 module

```

6a)

```

module MUX21 (io, io1, s, p);

input io0, io1, s;
output reg p;

always @*
begin
    p = (s == 1)? io1 : io0;
end

endmodule // end of MUX21 module

```

6b)

```


module MUX41 (io0, io1, io2, io3, s0, s1, p);

input io0, io1, io2, io3, s0, s1;
wire w0, r1;
// also acceptable: reg r0, r1;
output p;

MUX21(io0, io1, s0, w0);


```

Figure 1: D flip-flop.

 

 8)

The reset part here caused people a lot more grief than was intended. A number of you came



up with really cool ways of handling the reset signal. The intent was to just use a flip-flop with a reset. A number of you came up with some very impressive and creative solutions while using only full-adders and flip-flops without a reset.

4 Verilog for Sequential Logic

9a)

3 bits used - the minimum would be 2.

9b)

Only two state variables are required (state, and next_state). Each one needs to be two or 3 bits wide.

9c)

The assign statement version is a lot shorter, but harder to get and much harder to manipulate if the state machine needs minor changes. On the whole, the case-statement version is strongly preferred - less error-prone, easier to debug and modify.

11g)

If the input to an inverter is Hi-Z, then the input wire is essentially being left to float. Therefore, the output is unknown.

12a)

An open-collector bus design is one where a device's output either connects to ground or it connects to nothing. If any device on the bus connects to ground, the wire is at ground. But if none of them do, the wire will float (HiZ).

12b)

The pull-up resistor prevents the wire from floating if no device is connected to ground. Now, the default state is the wire being at a "1", through the pull-up resistor.

12c)

To send a 0, a device output would be in a "0" state (and everyone else should drive nothing, although it doesn't matter what they drive - they can only drive "0", which would accomplish the same objective). That would pull the wire to "0".

12d)

To send a 1, a device output would be in the "HiZ" state as well as all of the other devices). This would allow the pull-up resistor to bring the bus up to a "1".

12e)

When the device output is not attempting to drive the bus, then it would be in "HiZ" to allow other devices to choose to drive the bus to "0".