

A Low Power Low Frequency Sample and Hold Circuit for Implantable Pacemaker

Fu Sun, Ali Ahmed and Guan Huang

**Department of Electrical Engineering and Computer Science
University of Michigan, Ann Arbor, MI 48109-2122, USA**




Outline

- **What is sample and hold circuit?**
- **Motivation: why low power?**
- **Specs and Target**
- **Design Topology**
- **Simulation Results and Analysis**
- **Summary**




Sample and Hold Circuit

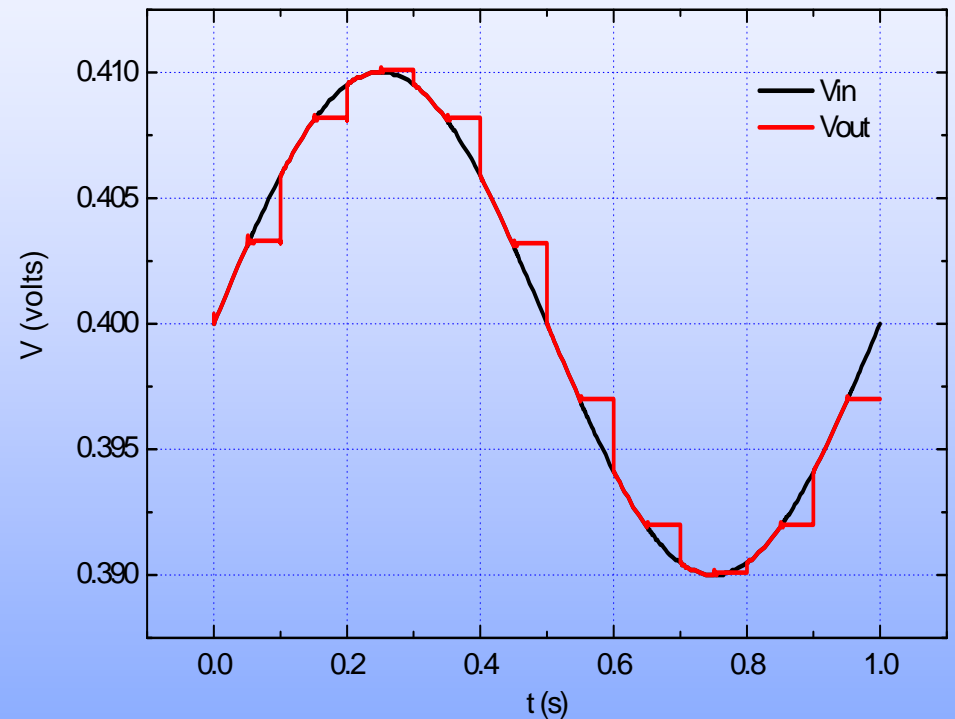- Sample the input signal
- Hold the signal steady for a period of time until the next stage can process the signal





Why Low Power?

 

- Remain In body for 5 -10 years
- To avoid frequently changing of battery by surgery.



Targets

- Power: nano Watts
- Leakage current: fA
- Error signal: uV




Our solutions

- Power supply: 0.7 Volts
- Subthreshold operation
- Leakage cancellation circuit




Block Diagram

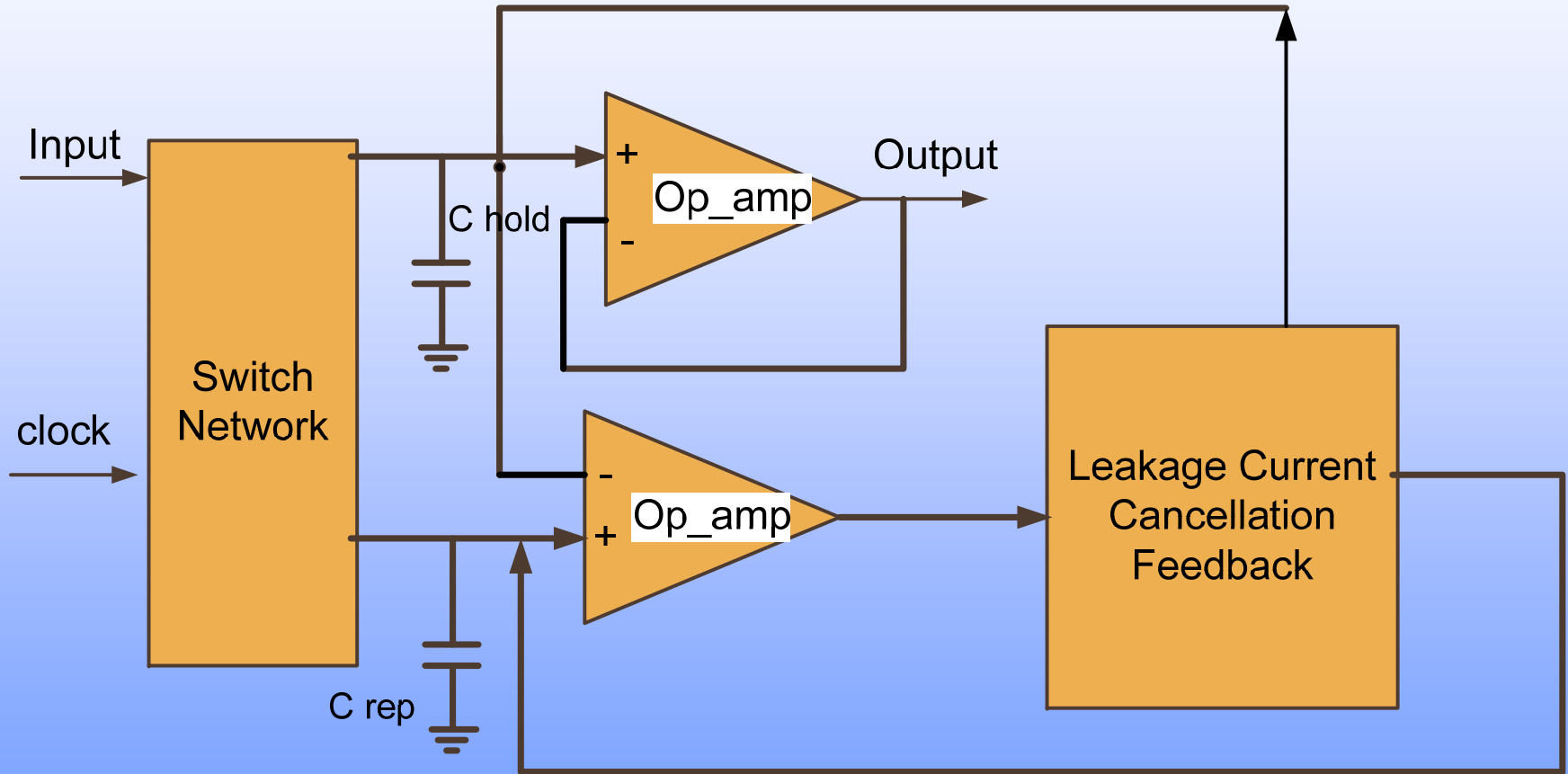




Op-amp

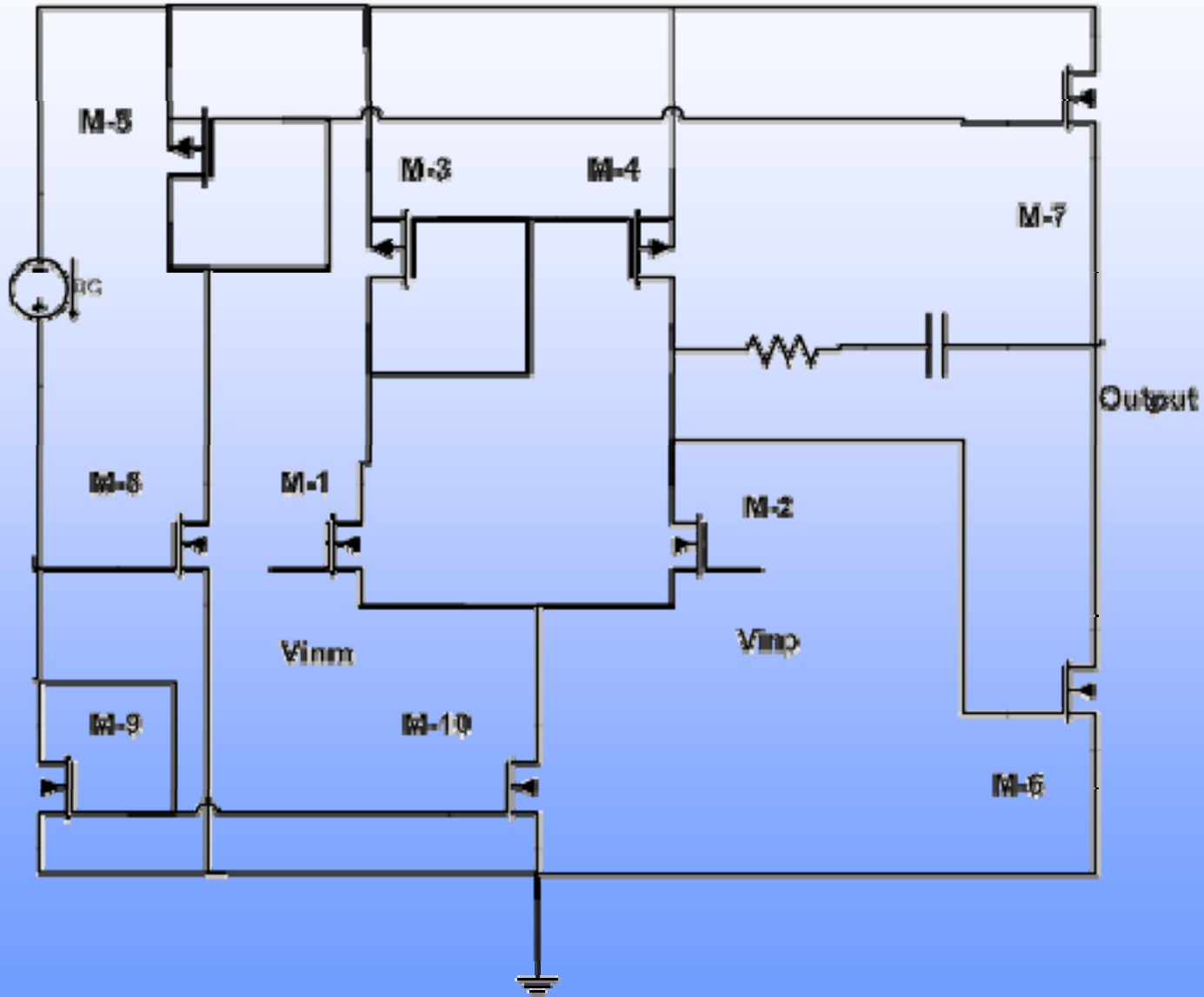



Op-amp simulation

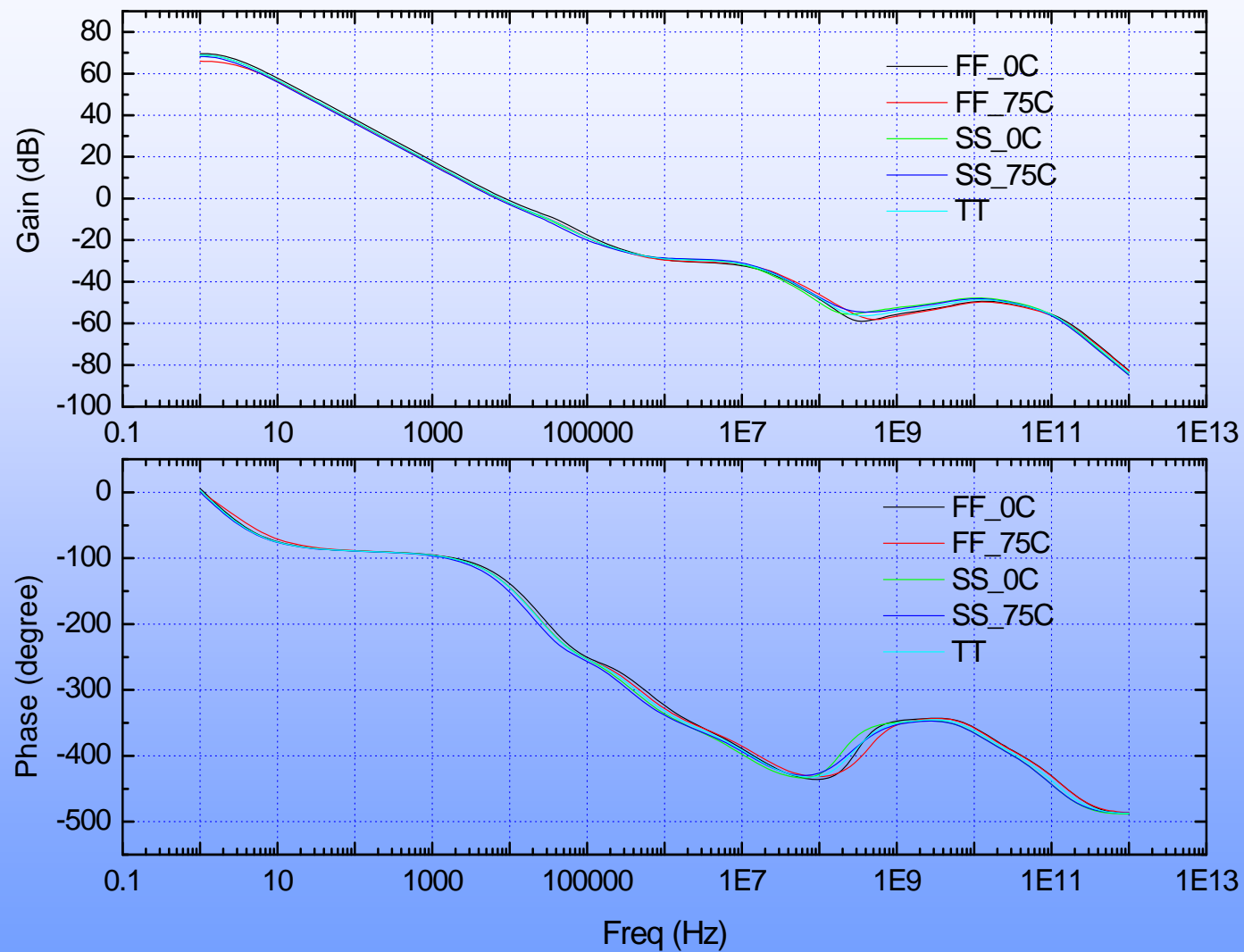




Leakage Current Cancellation

Advantages:

- Reduces Voltage drift during hold time
- Reduces the size of the capacitor, effectively reducing the area of the layout




Operation

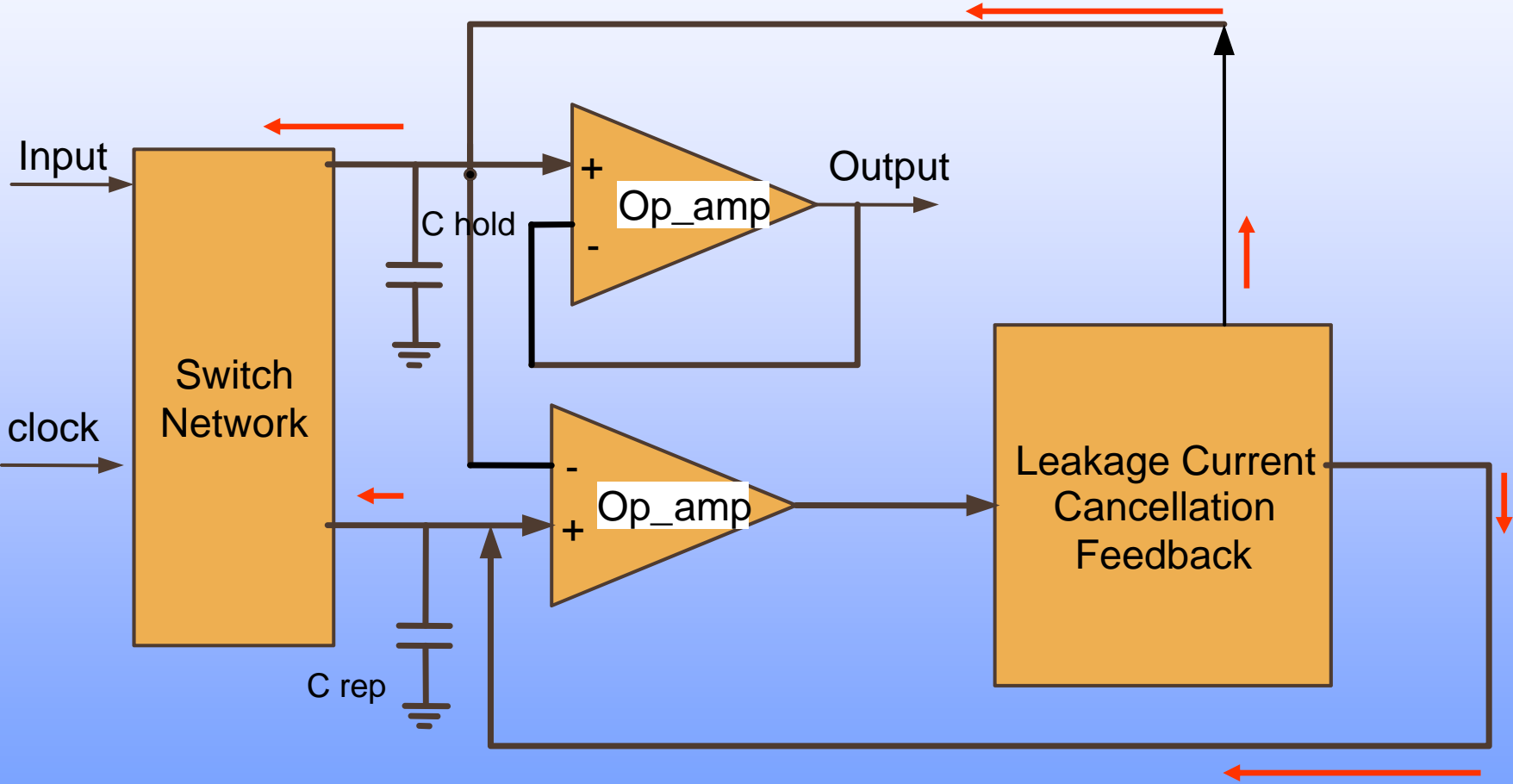




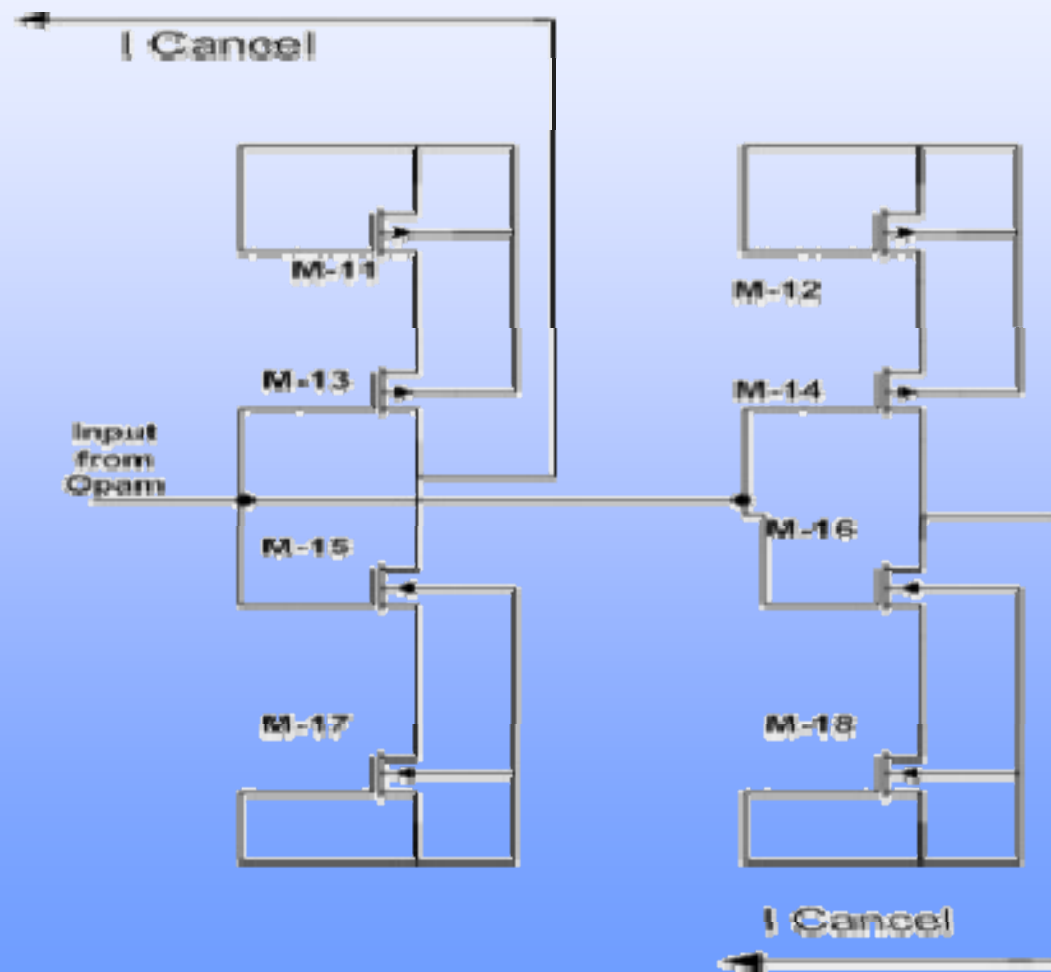
Detailed Circuit Diagram of Leakage Current Cancellation Circuitry





 Variation of cancellation current with input voltage of leakage circuitry



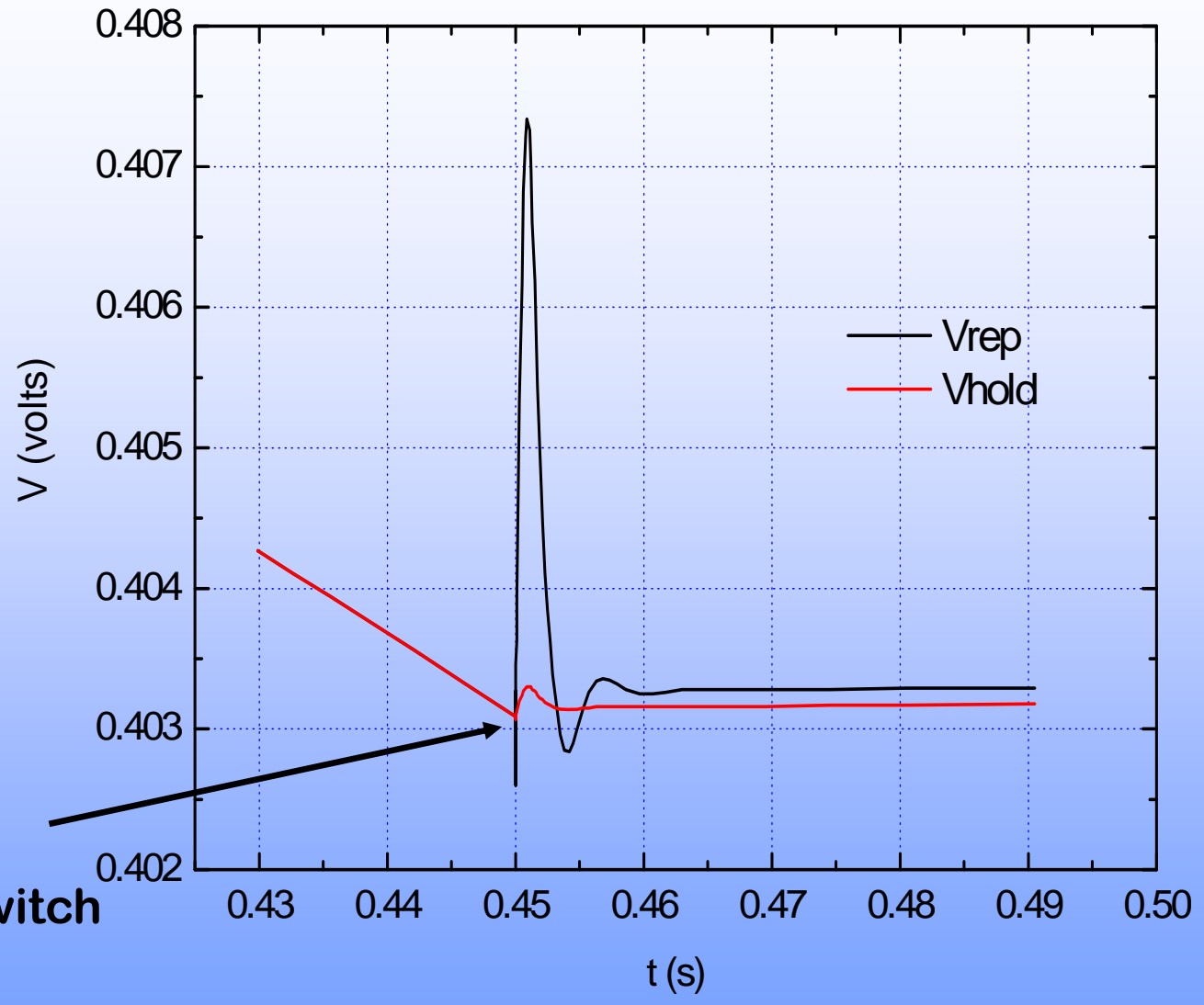

**Hold time
Starts (switch
turns off)**


The variation of voltages on C_{rep} and C_{hold} during hold mode (left)



Layout


Leakage Cancellation

Switch Network

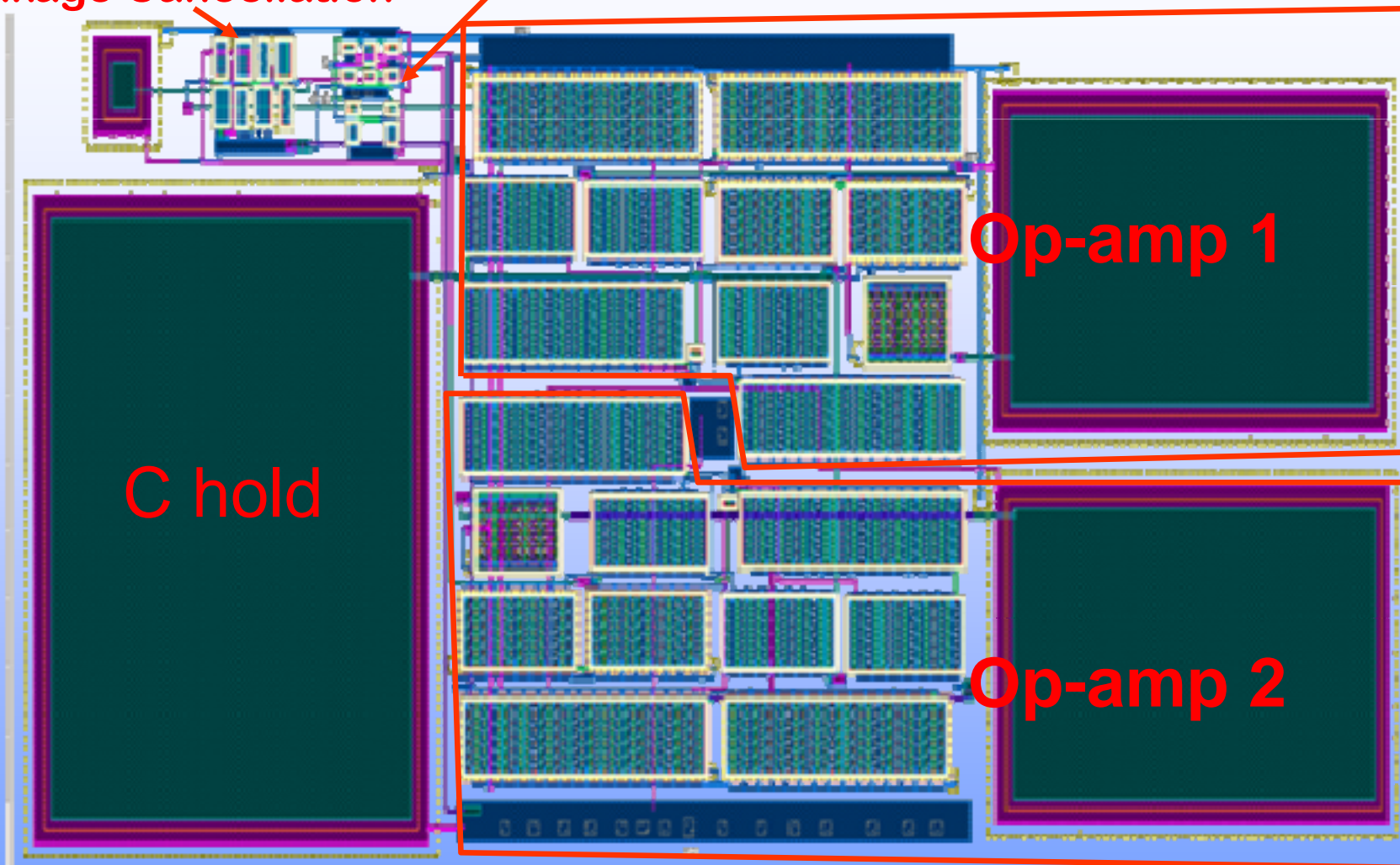




Simulation Results

 

Output of S/H circuit at 37C (upper) and zoom-in plot of hold period showing the settling time (bottom)



Simulation Results

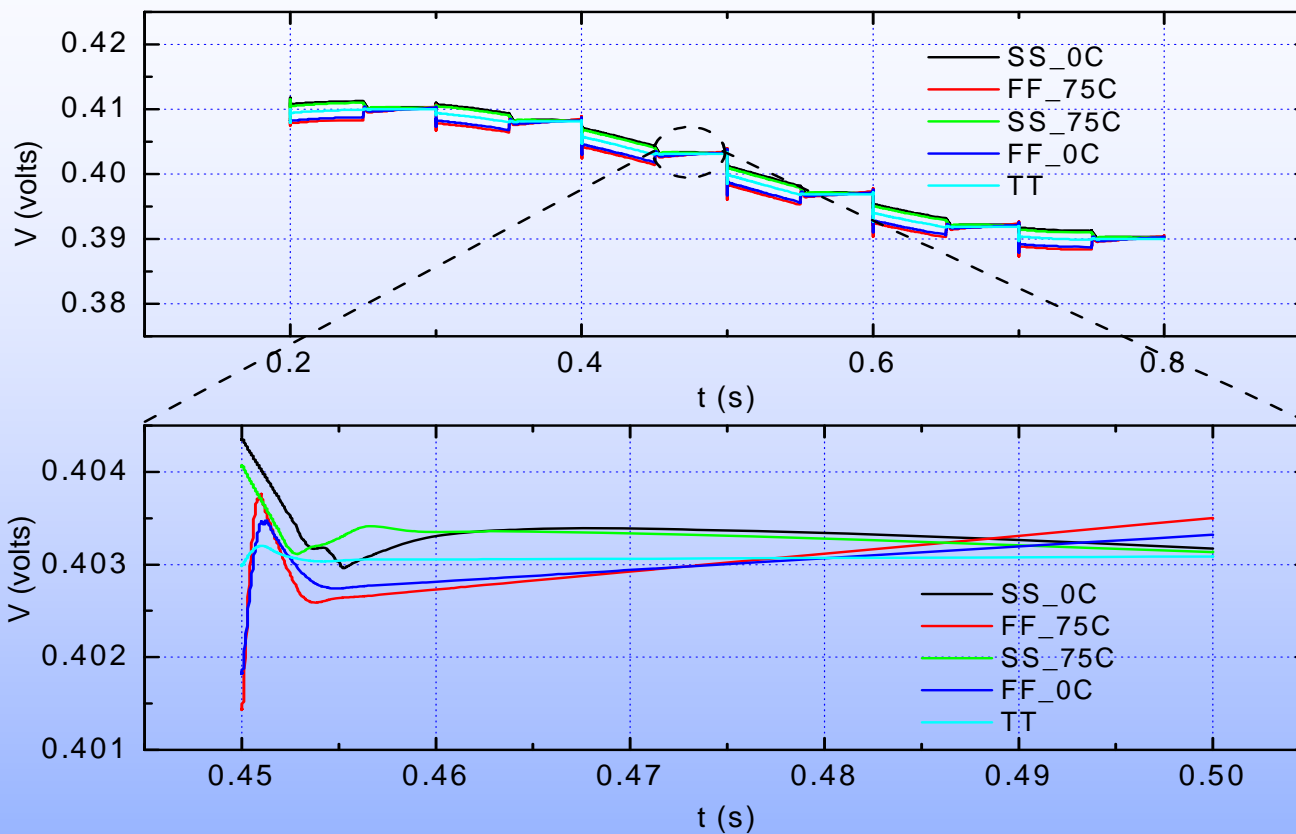

Corner simulation of the S/H circuit over 32°C to 42°C



Conclusion

Specification	Our work	Other's work
Power	92.9nW	~150nW
Leakage current after cancellation	4fA	10fA
Settling time	4ms	??
Hold capacitor	10pF	1pF



Thank you!

Questions?