



Class D High Power Audio Amplifier

December 5, 2007

Mohammad Adeel

Farah Shariff


BoQiang Xiao

Contents

- Motivation
- Design Goals
- System Overview
- Individual Stage Design
- Layout
- Results
- Challenges
- Questions

Motivation

 - Why Class D?
- Class D Features
 - Switching Amplifier
 - Pulse Width Modulation (PWM)
- High Power / High Efficiency
- Driver for speakers and headphones
- Portable Audio Applications
 - Cell Phones, PDAs, GPS





Texas Instruments Class D Amplifier

Design Goals

- Peak Output Power ≥ 1 Watt
- Efficiency ≥ 85 %
- THD ≤ 0.5 %
- Bandwidth = 20 Hz to 20 kHz
- Maximum Input Swing = 2.5 V_{ppk}
- Maximum Output Swing = 5 V_{ppk}
- Power Dissipation = 75 to 150 mWatts


System Overview

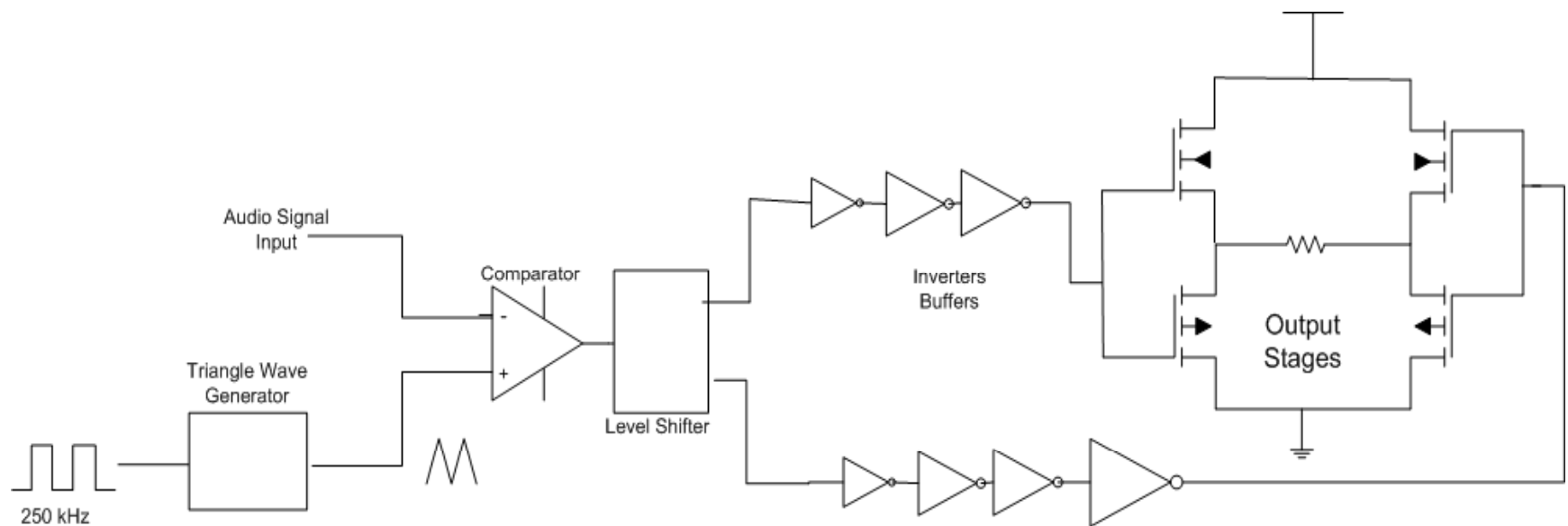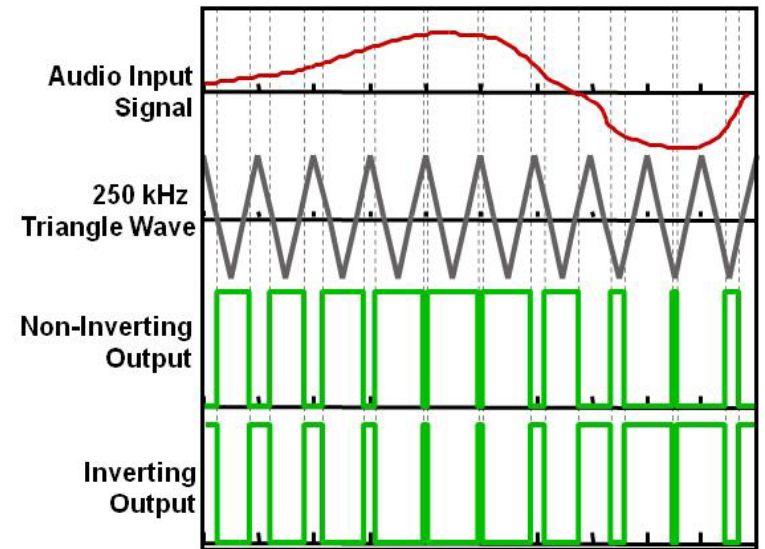- Triangle Wave Generator
- Comparator
- Level Shifter
- Output Stages



Triangle Wave Generator

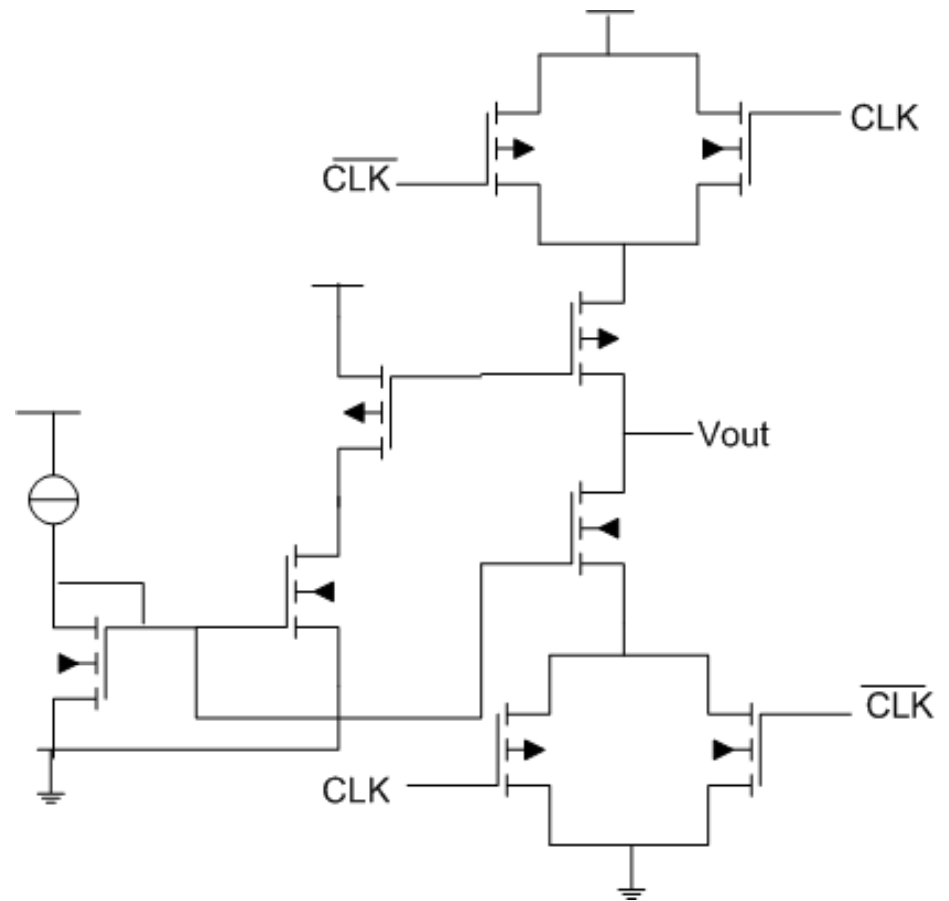- $V_{IN} = 250\text{kHz}$ squarewave CLK
- System of Current Mirrors
- Output Mirrors acting as Push-Pull Architecture
- Slew Rate to linearize V_{rise} & V_{fall}
- Transmission Gates to switch between charge / discharge




$$I_{SS} = I_C = C \, dv/dt$$

Comparator

- Multiple Potential Architectures
 - One / Two Stage
 - Telescopic / Folded Cascode
 - Gain Boosting
- Two stage design selected
 - High Gain
 - MHz range Bandwidth
 - Average Power Consumption
- Trade off between Gain – BW


$$A_v = -g_m (r_{01} // r_{02}) \propto I_D^{-\frac{1}{2}}$$
 
$$r_0 = \frac{1}{\lambda I_D} \propto L$$




Level Shifter

 - High Speed Architecture
- SE Input, Double-Ended Output
- High Dynamic Shift
- Delay ~ picoseconds
- Inverters sized for equal transitions




Output Buffer Stages

 

- PWM Speaker Drivers
- Inverter Chain
 - Lowest Cross Conduction
 - Minimum and equal Rise / Fall Times
 - Minimum Delay
- BTL – 2x the voltage swing

$$F = C_{out} / C_{in}$$
$$N = \frac{\log(F)}{\log(f_{opt})} \text{ with } f_{opt} = 3.6$$

Layout

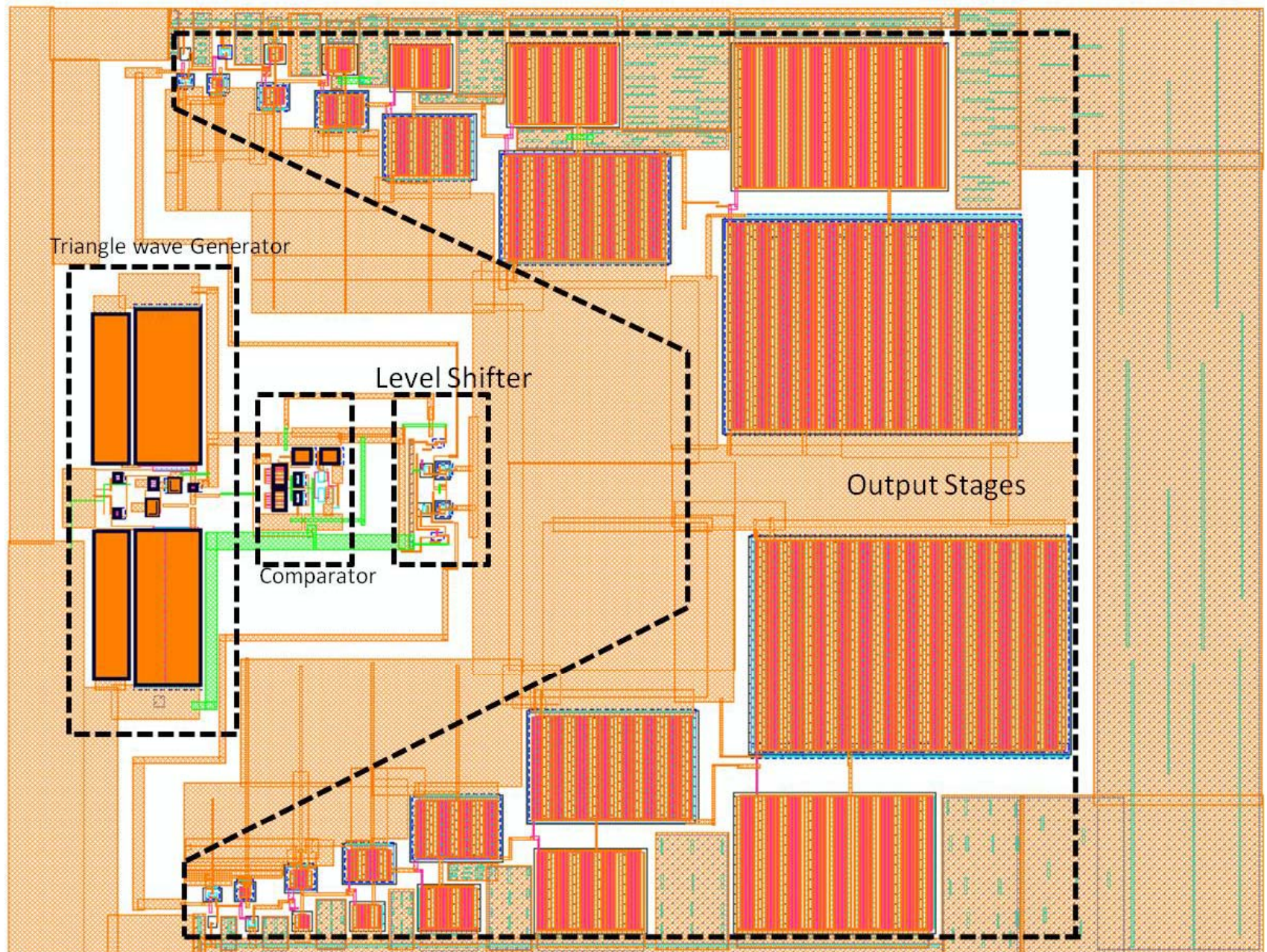

Results

 


Table 1: System Results

 



Table 2: Temperature Variation

$$THD (\%) = \frac{P_2 + P_3 + P_4 + \dots P_N}{P_1}$$



where P_1 is at the audio frequency

$$Eff. (\%) = \frac{P_{LOAD}}{V_{dd2.5} * I_{dd2.5} + V_{dd5} * I_{dd5}}$$



Results (cont.)

 

THD Analysis with DC Offset

  

THD Analysis with out DC Offset

  

PWM and Reconstructed Signal

Design Challenges

- Designing for two supply rails
 - How to Level Shift?
- Triangle Wave Generator sizing
 - Intricate tweaking to minimize nonlinearity in the slewing
- Input Pre-Amplifier
 - DC bias matching and high voltage swing
- Comparator Sizing
 - Gain bandwidth compromises
- Simulation Time
 - CAEN disk quota restrictions



Questions

Mohammad Adeel

Farah Shariff

BoQiang Xiao