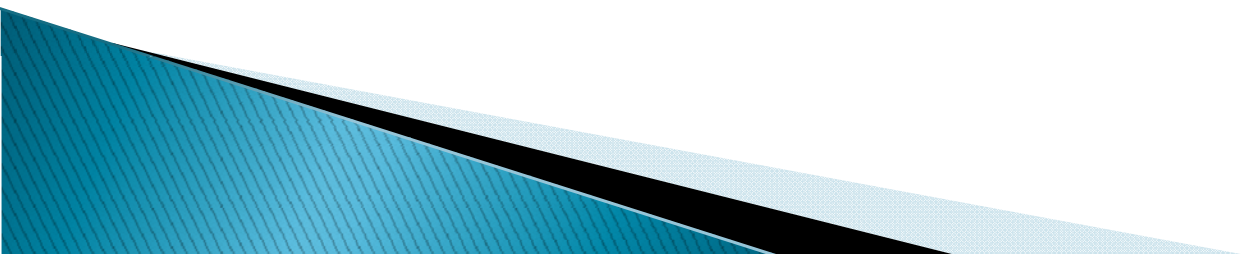


EECS413 Final Project
Group 7


A CMOS LNA and Mixer for FM Receivers

Mao-Ter Chen, Wei-Ling Chiang, Yohan Kim



Introduction

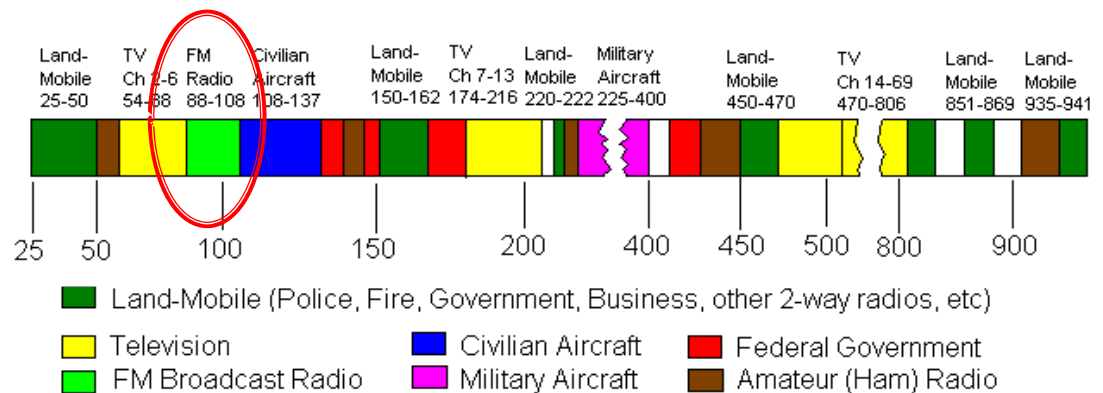- ❖ Continuous demand for high performance, low power RF circuits
- ❖ CMOS provides a favorable environment to integrate analog and digital on a single chip
- ❖ FM Band (88 – 108MHz)



Legend:
■ Land-Mobile (Police, Fire, Government, Business, other 2-way radios, etc)
■ Television
■ FM Broadcast Radio
■ Civilian Aircraft
■ Military Aircraft
■ Federal Government
■ Amateur (Ham) Radio


Design goals

LNA:


- ❖ Input matching network (50Ω)
- ❖ Enough gain to overcome noise in later stages
- ❖ Low Power
- ❖ Linearity

MIXER:

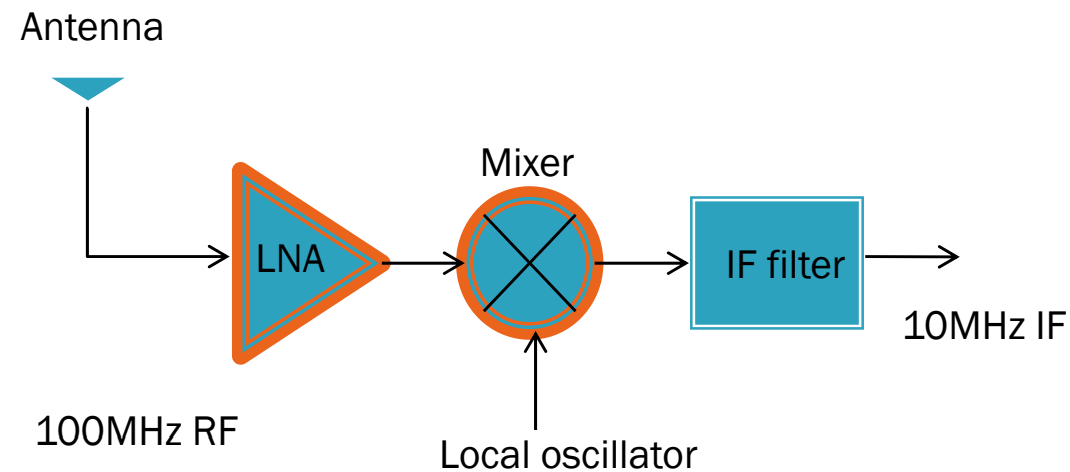- ❖ Translate the RF signals with minimal distortion
- ❖ High gain, low power consumption




LNA– Choosing Topology

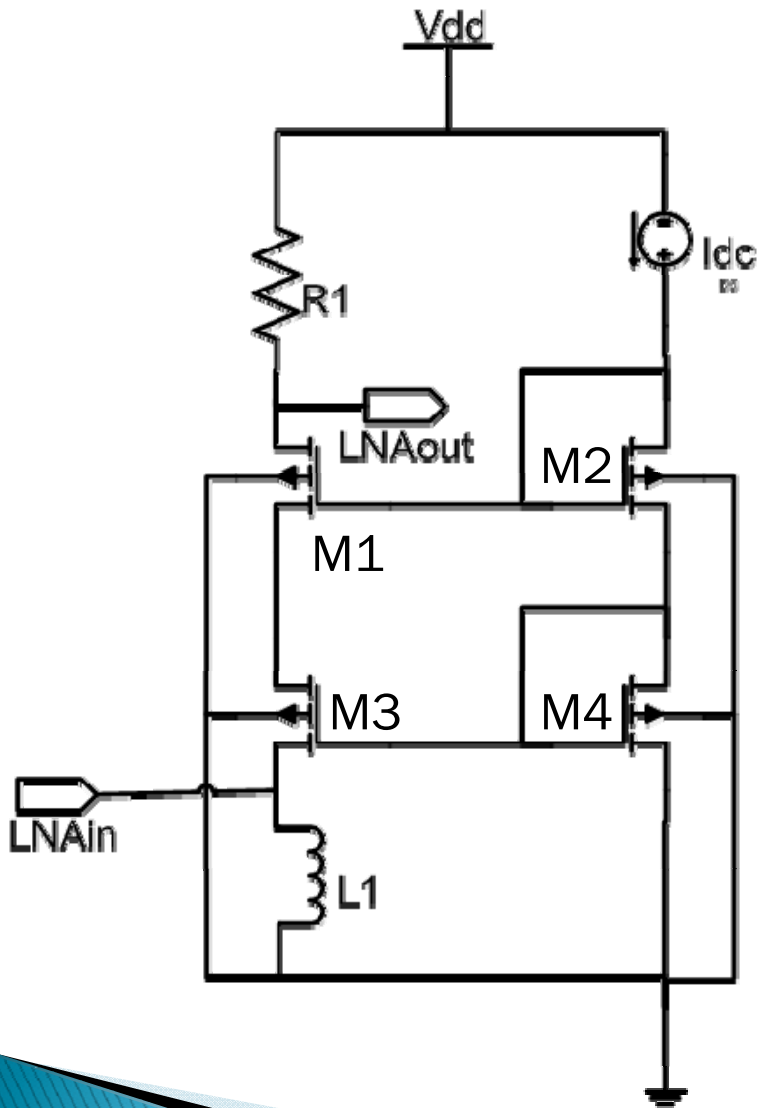

- ❖ Why 2 stage cascode common gate?
- ❖ Isolation from output to input and better power supply noise rejection
- ❖ Increase output impedance

LNA-Input impedance

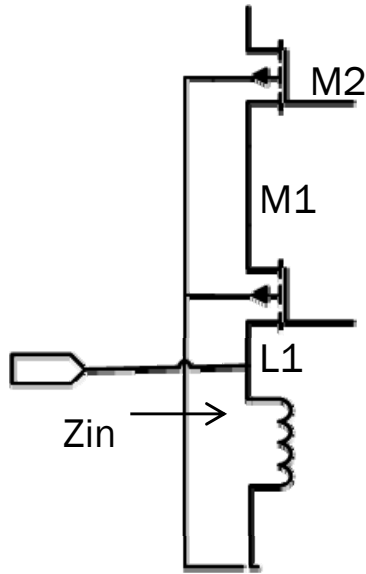- ❖ In RF applications, impedance is usually 50Ω (matched to antenna)




$$Z_{in} = \frac{sL}{sL(g_m + sC_{gs1}) + 1} = 50$$

- ❖ Assume C_{gs} equals to 10pF ,

$$\omega_0^2 = \frac{1}{L_2 C_{gs}} = \frac{1}{10^{-11} \times L_2} = (2\pi \times 100 \times 10^6)^2$$

$$\Rightarrow L_2 = 253.3\text{nH} \rightarrow \text{off-chip}$$

LNA - Gain

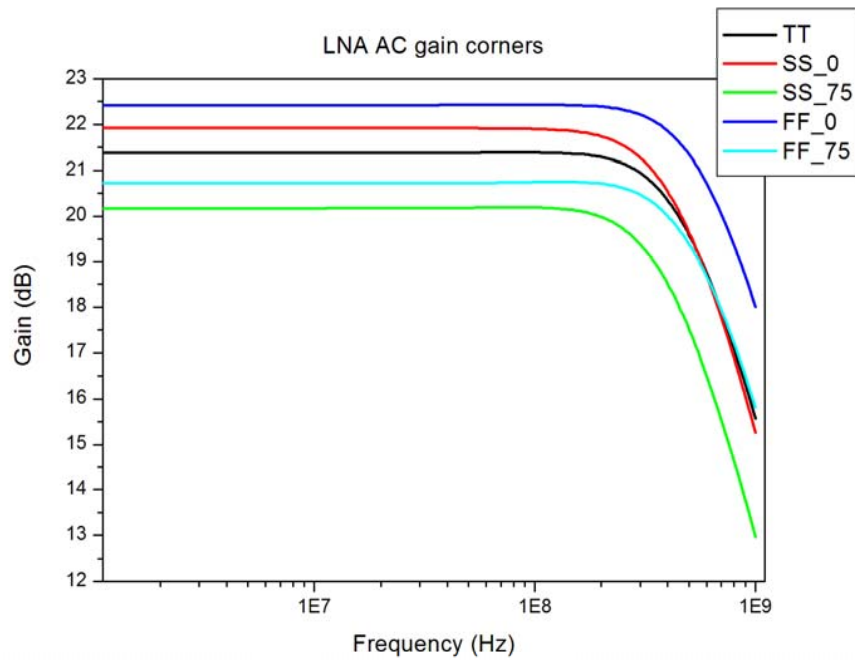

❖ Gain $A_v = \frac{g_{m3}g_{m1}R_1}{g_{m1} + sC_{gs1}} \approx g_{m3}R_1$


Too high: early mixer saturation and bad linearity

Too small: NF of whole system increase

❖ Ideally, $A_v = 15 \square 20dB$

❖ Our design: $A_v = g_m R_l = 20 \log(0.022 \times 600) = 22dB$

S-Parameter and stability


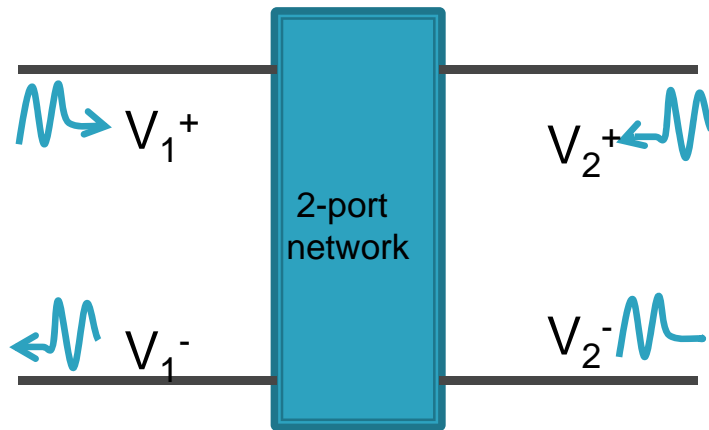


$$S_{ij} = \left. \frac{V_i^-}{V_j^+} \right|_{V_k^+ = 0 \text{ for } k \neq j}$$


❖ For unconditional stability,

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} > 1$$


$$|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1$$

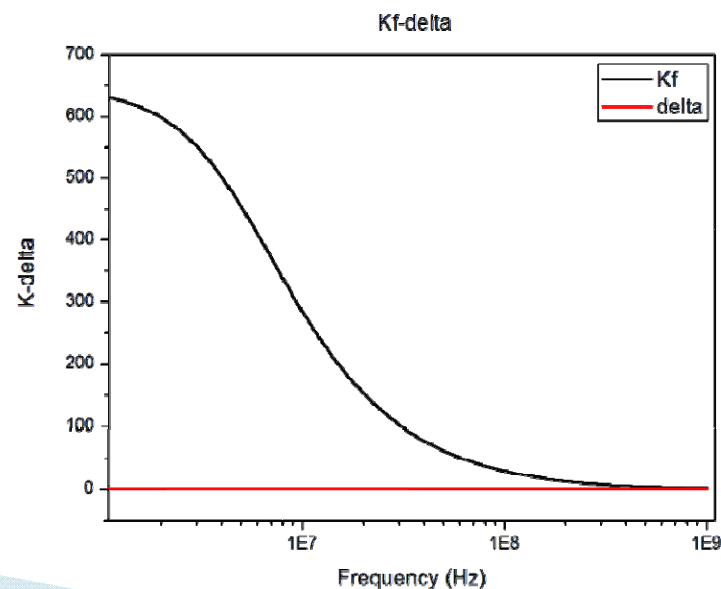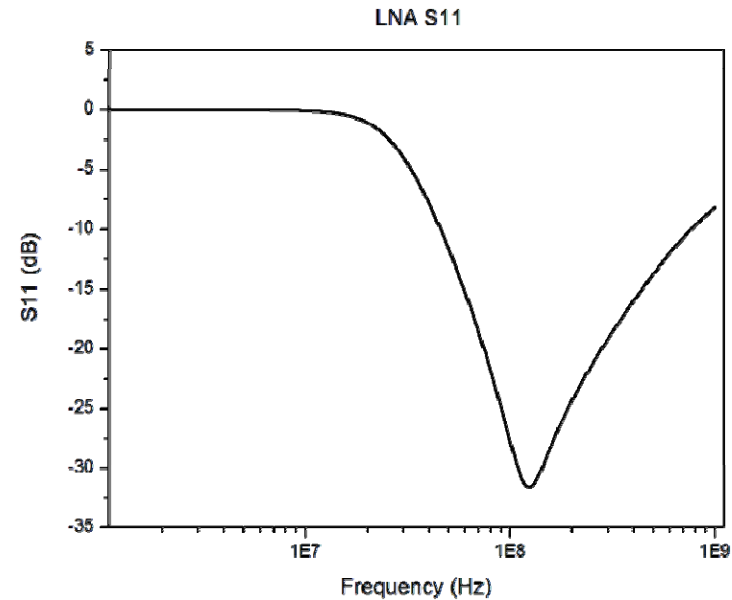

Mixer—down conversion

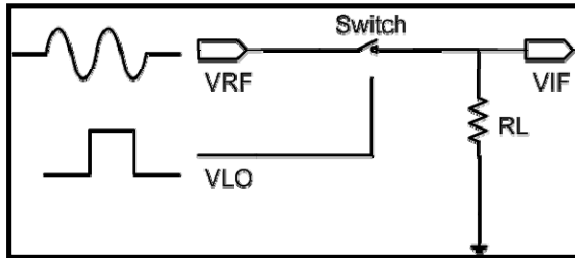


❖ Simple switch as a mixer

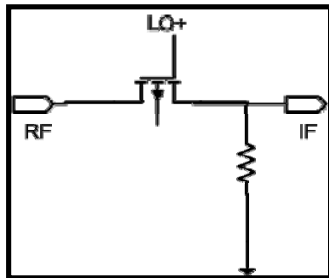


❖ Implementation with NMOS

$$V_{IF}(t) = KV_{RF}(t)V_{LO}(t) = K \cos 2\pi f_{RF}t \cos 2\pi f_{LO}t$$

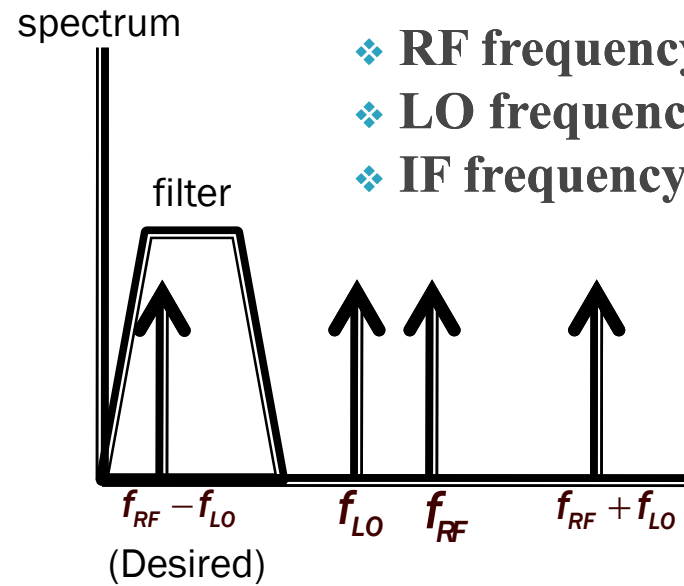
$$= \frac{K}{2} [\cos 2\pi(f_{RF} - f_{LO})t + \cos 2\pi(f_{RF} + f_{LO})t]$$




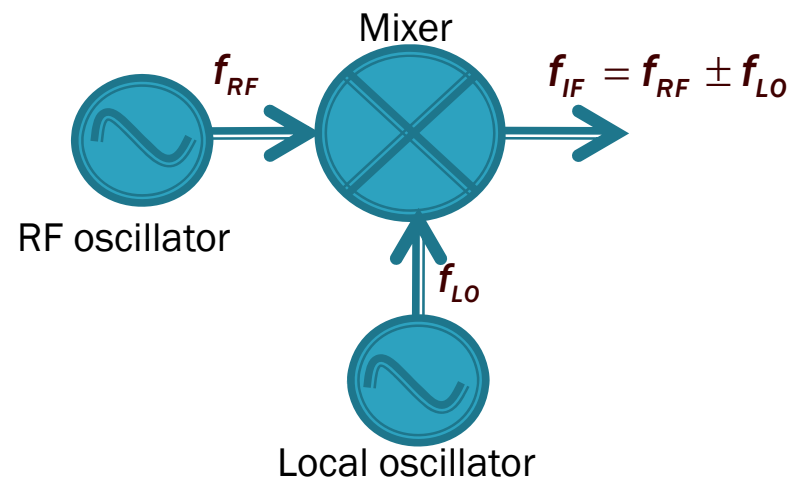
- ❖ RF frequency = 100MHz
- ❖ LO frequency = 90MHz
- ❖ IF frequency = 10MHz



Mixer Topology

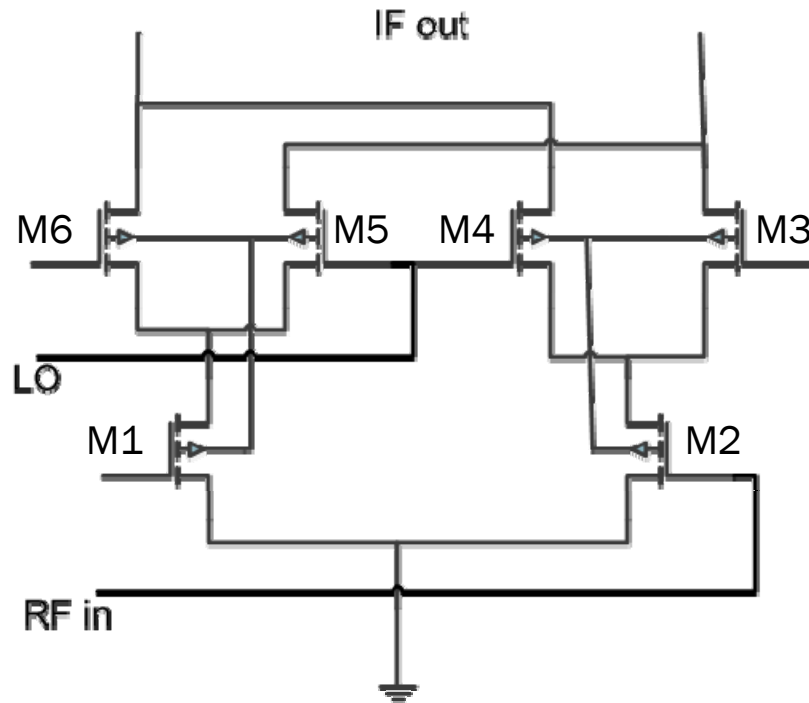

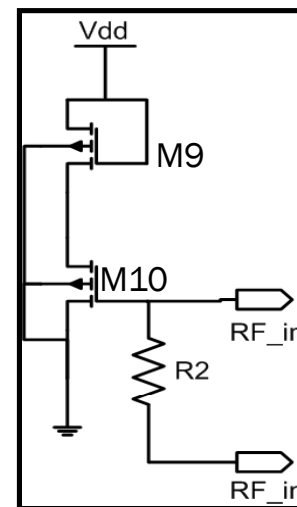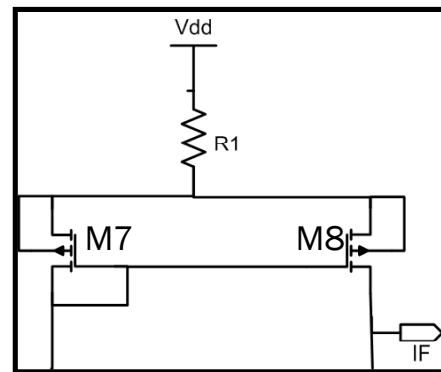- ❖ Active double balanced mixer Gilbert Cell
- ❖ Rejection of LO coupling
- ❖ Single-ended I/O port



- ❖ DC bias circuit
- ❖ Current mirror
- ❖ R1 for output voltage level

Input signal setting

❖ For RF input:


$$V_{RF} = 1\text{mV}$$

❖ For LO input:



$$V_{LO} = 0/1.0\text{V (peak to peak)}$$

❖ M1 and M2 are chosen long and wide transistors

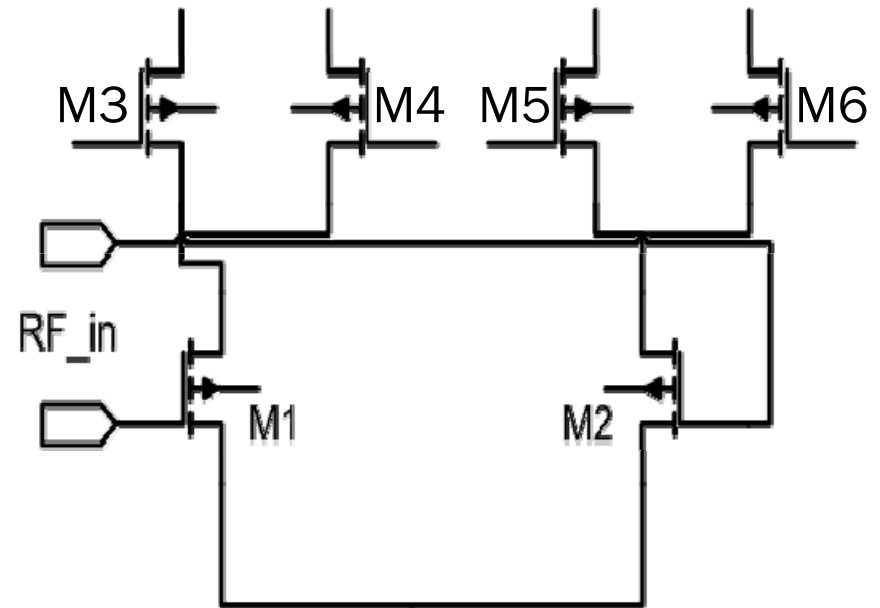❖ Switch transistors (M3~M6) are set appropriately





Transient simulation and Spectrum

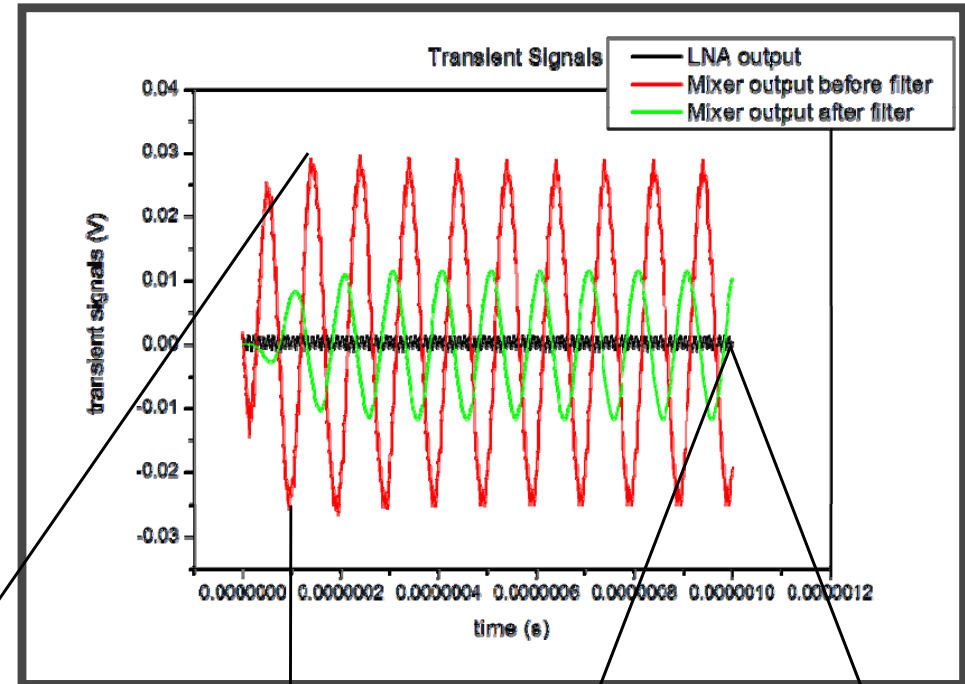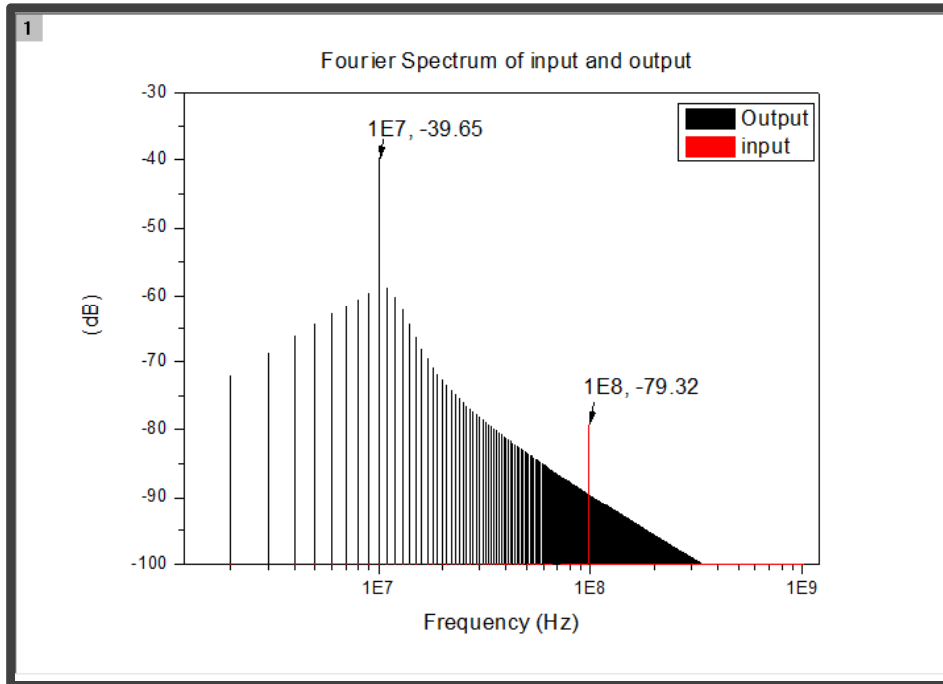


❖ Total Gain = $-39.65 - (-79.32) = 39.67\text{dB}$

❖ Minus DC level

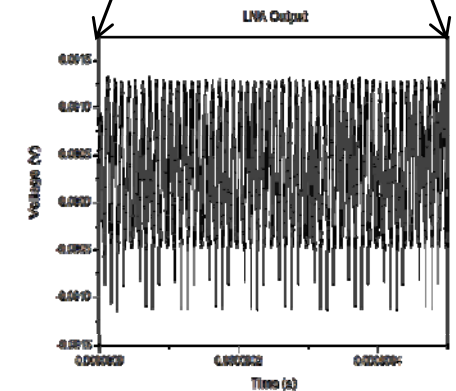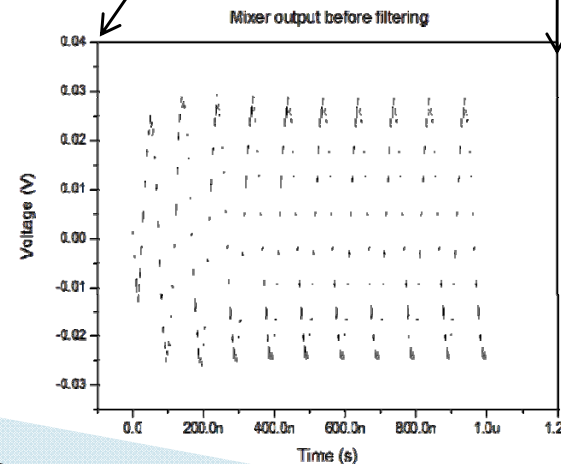


System Performance - Noise figure

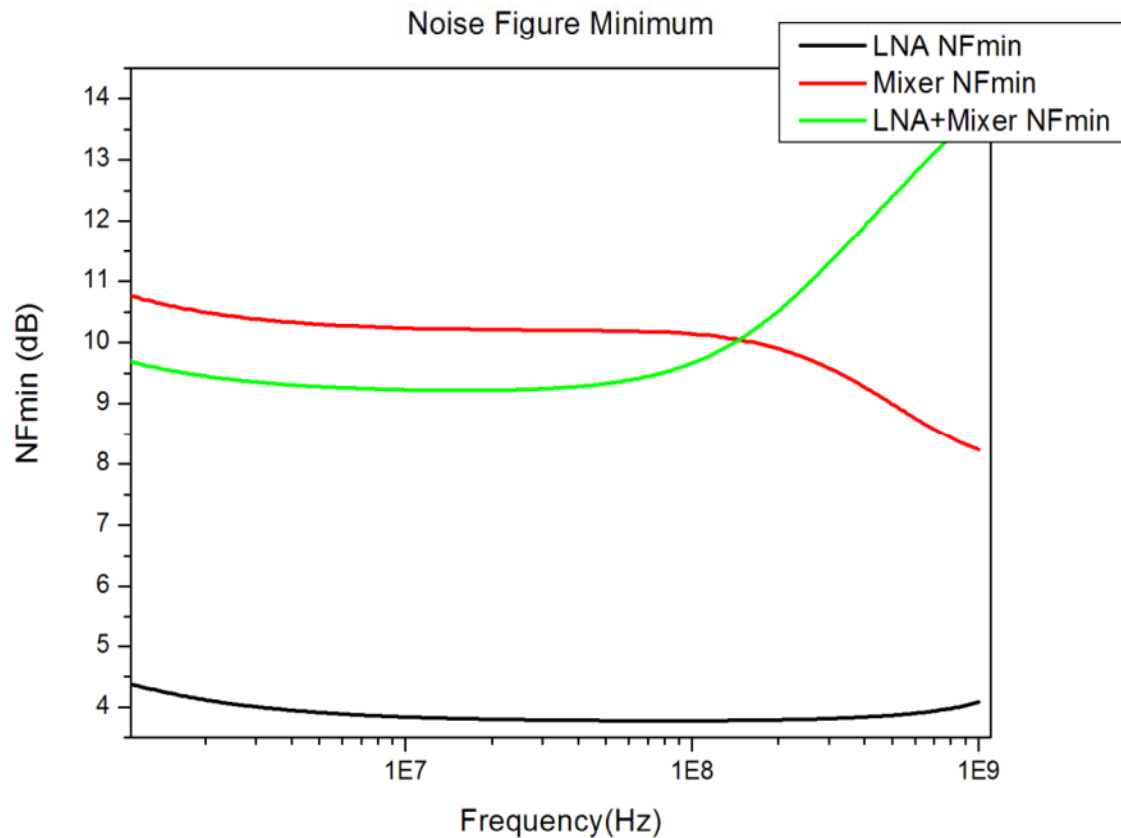


LNA: 3.77 dB
Mixer: 10.14 dB

$$NF_{total} = NF_1 + \frac{NF_2 - 1}{G_1} + \frac{NF_3 - 1}{G_1 G_2} \dots + \frac{NF_n - 1}{G_1 G_2 \dots G_{n-1}}$$

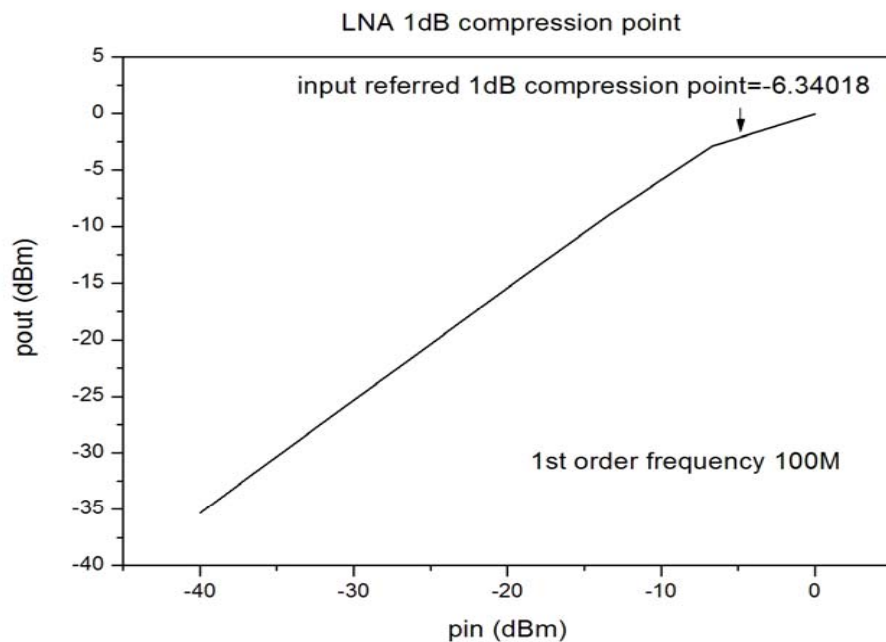System Performance - 1dB compression point




❖ LNA 1dB-compression level

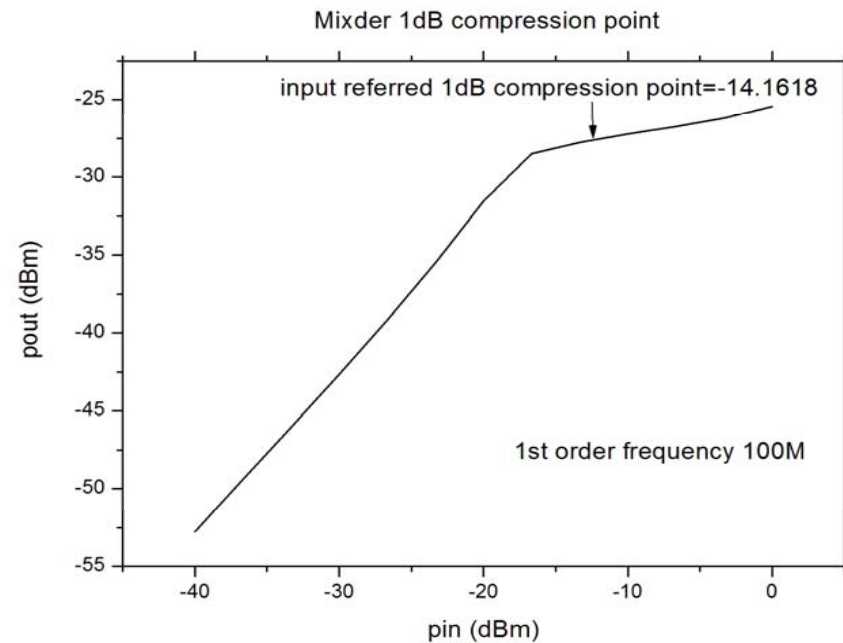




❖ Mixer 1dB-compression level

System Schematic and Layout

LNA

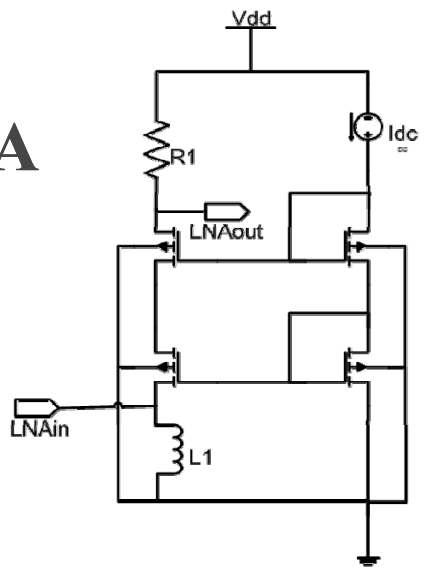

Mixer

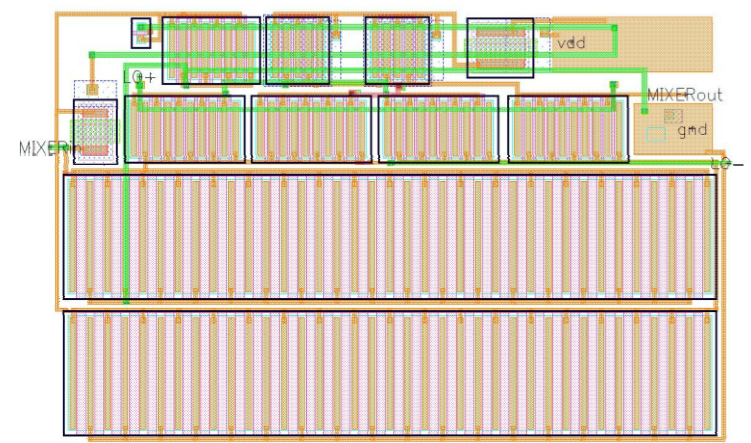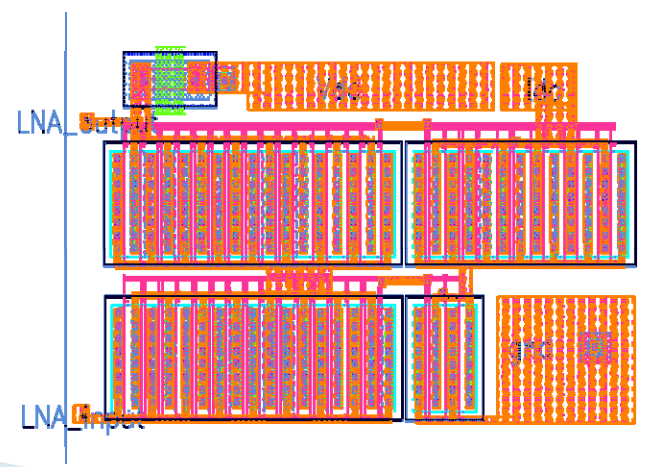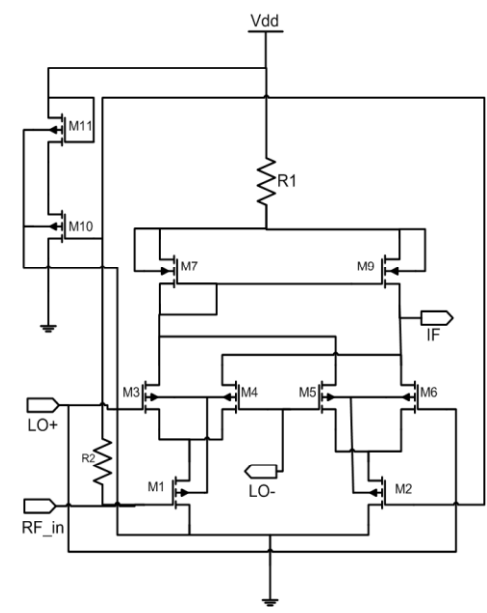


Total specifications

LNA	This work	Karanicolas, A.N.
Power dissipation	3.9mW	20mW
Noise figure	3.77dB	1.9dB
AC Gain	22dB	15dB
Input 1dB compression level	-6.34dBm	-15.2dBm
Reflection coefficient $ s_{11} $	-27.7dB	-
RF frequency	100MHz	900MHz

MIXER	This work	Zencir et al.
Power dissipation	3.105mW	5.4mW
Noise figure	10.14dB	5.8dB
Voltage gain	20.4dB	20.8dB
Input 1dB compression level	-14.16dBm	-21dBm
RF frequency	100MHz	435MHz

Conclusion

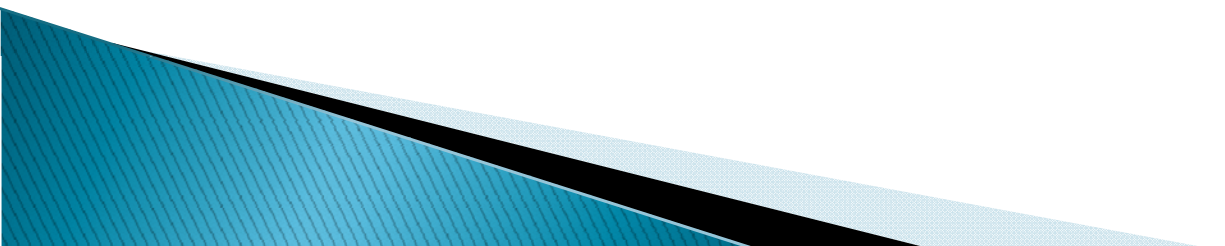- ▶ System satisfies most of initial project specifications
 - Bandwidth, power consumption, gain...
 - ▶ Possible improvements:
 - Mixer noise figure, on-chip inductor design
 - ▶ Introduction to CMOS RF design
- 

Thank You!