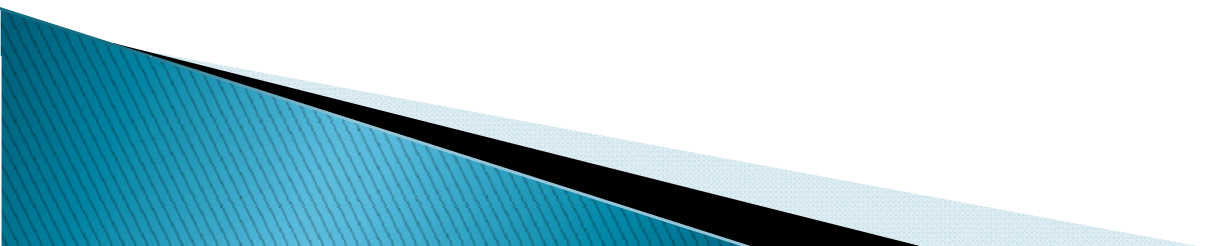



# SRAM Sense Amplifier

Sheeba Gandhi  
Fei Xu  
Neal Moyer

# Introduction


- Sense amplifiers are important circuit elements in memory design
  - The aim of the project is to design a high yield and high speed voltage sense amplifier to detect change in data and the data bar lines during a read operation.
  - The fault detection circuit is also designed to detect the validity of the data presented to the sense amplifier.
- 

# Block Diagram

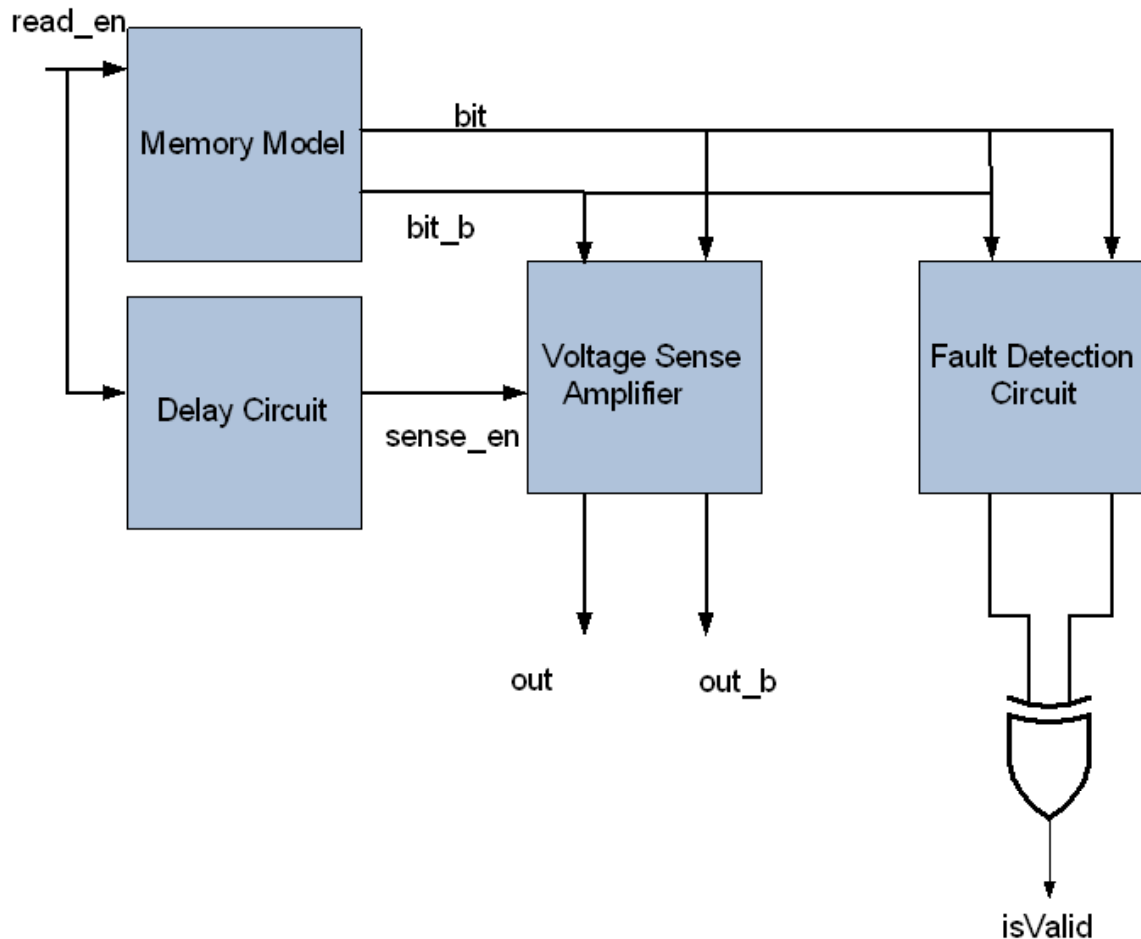

- Memory Model simulates the input to the sense and the fault detection circuit
- Delay circuit provides the enable signal so that the input signal difference is above the noise threshold.


# Memory Model

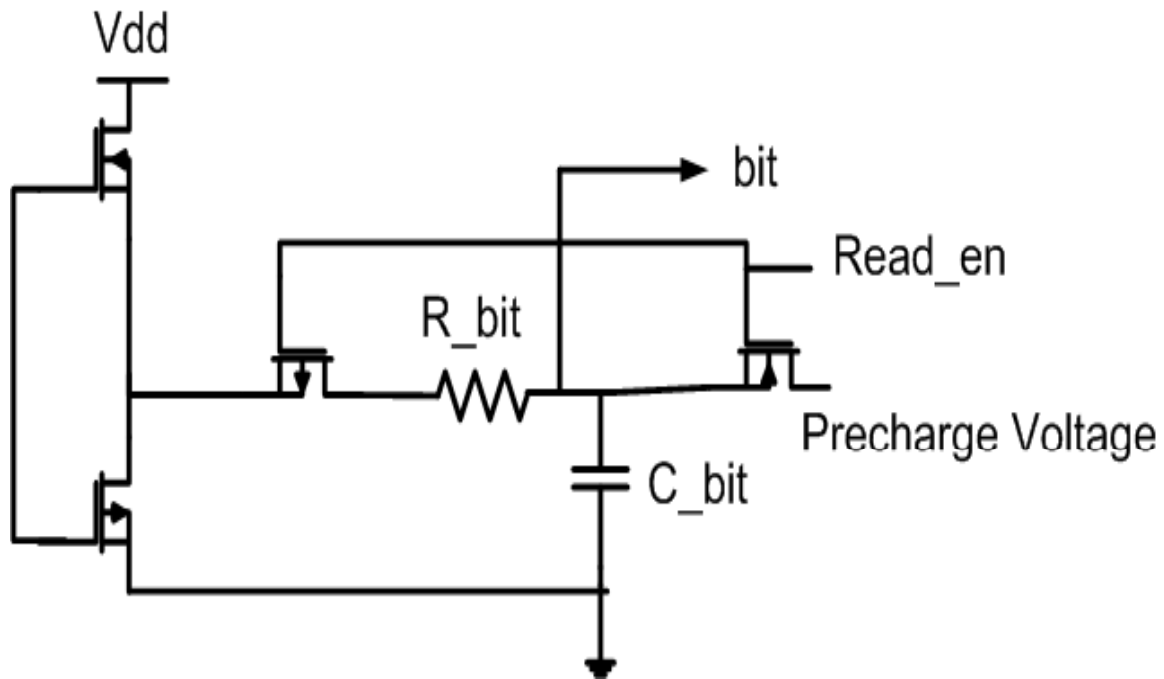

- ▶ Bit Line resistance and capacitance calculated for 512 word SRAM cell
- ▶ Precharge voltage was set to 1.15 V

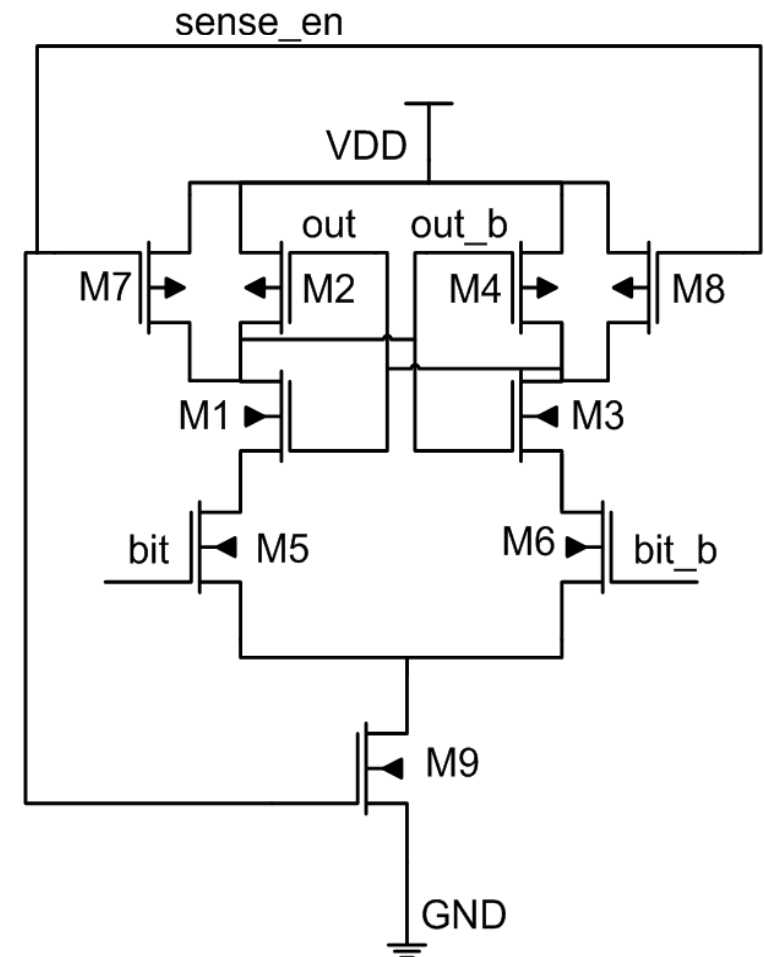
# Sense Amplifier

- Outputs precharged to VDD
- M9 foot enabled, M7, M8 precharge stopped
- M5, M6 inputs control bias currents,  $\Delta V_{out}$
- M1, M2, M3, M4 cross-coupled inverters drive full-rail swing at  $V_{out}$
- Offset voltage issues/mitigation techniques




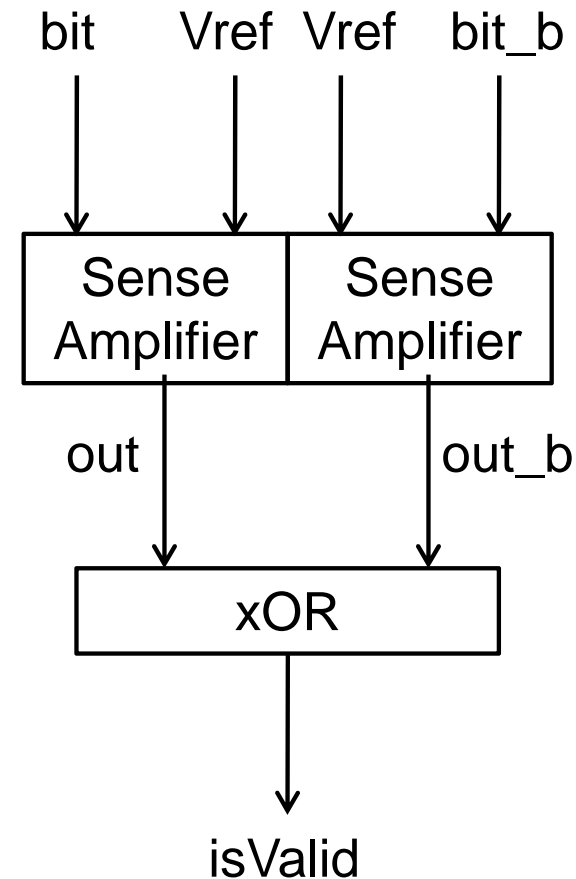
# Fault Detection

- ▶ Want to find bit errors ( $\text{bit} == \text{bit}_b$ )
- ▶ Two sense amplifiers with  $V_{\text{ref}}$  (1.15 V) input
- ▶ Sense bit/bit\_b lines independently
- ▶ Results are xORed to check if data is valid



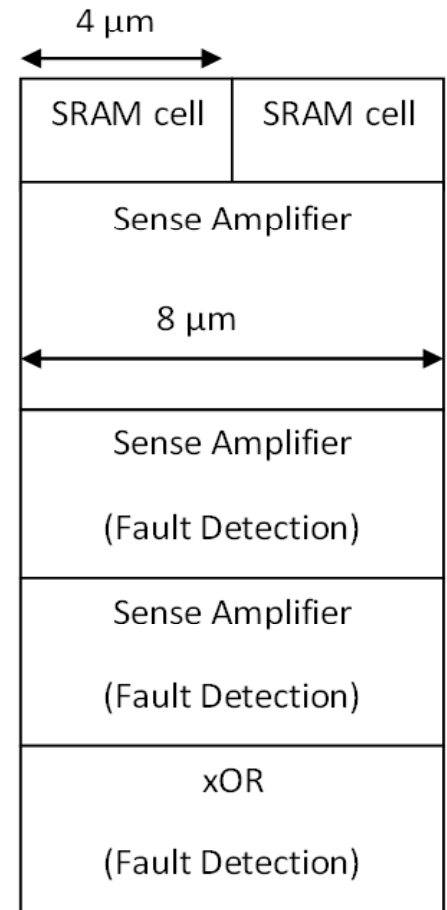 
# Floorplan

- ▶ 2X bit-slice, can stack 2 vertically
- ▶ Only 1 VDD, 1 GND rail
- ▶ Very regular topology
- ▶ Attaches to bottom of SRAM core




# Transient Results

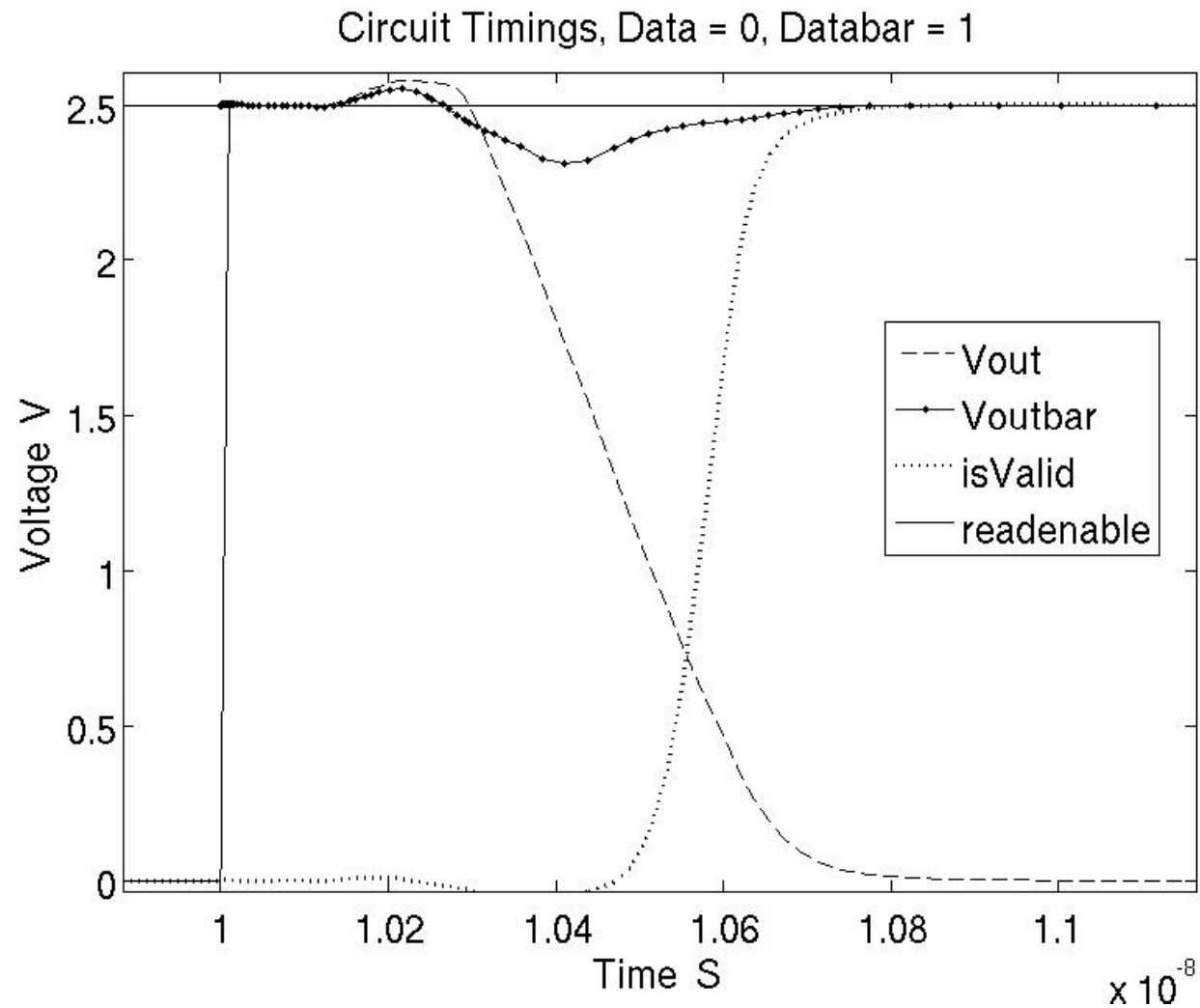



# Critical Voltage Comparison

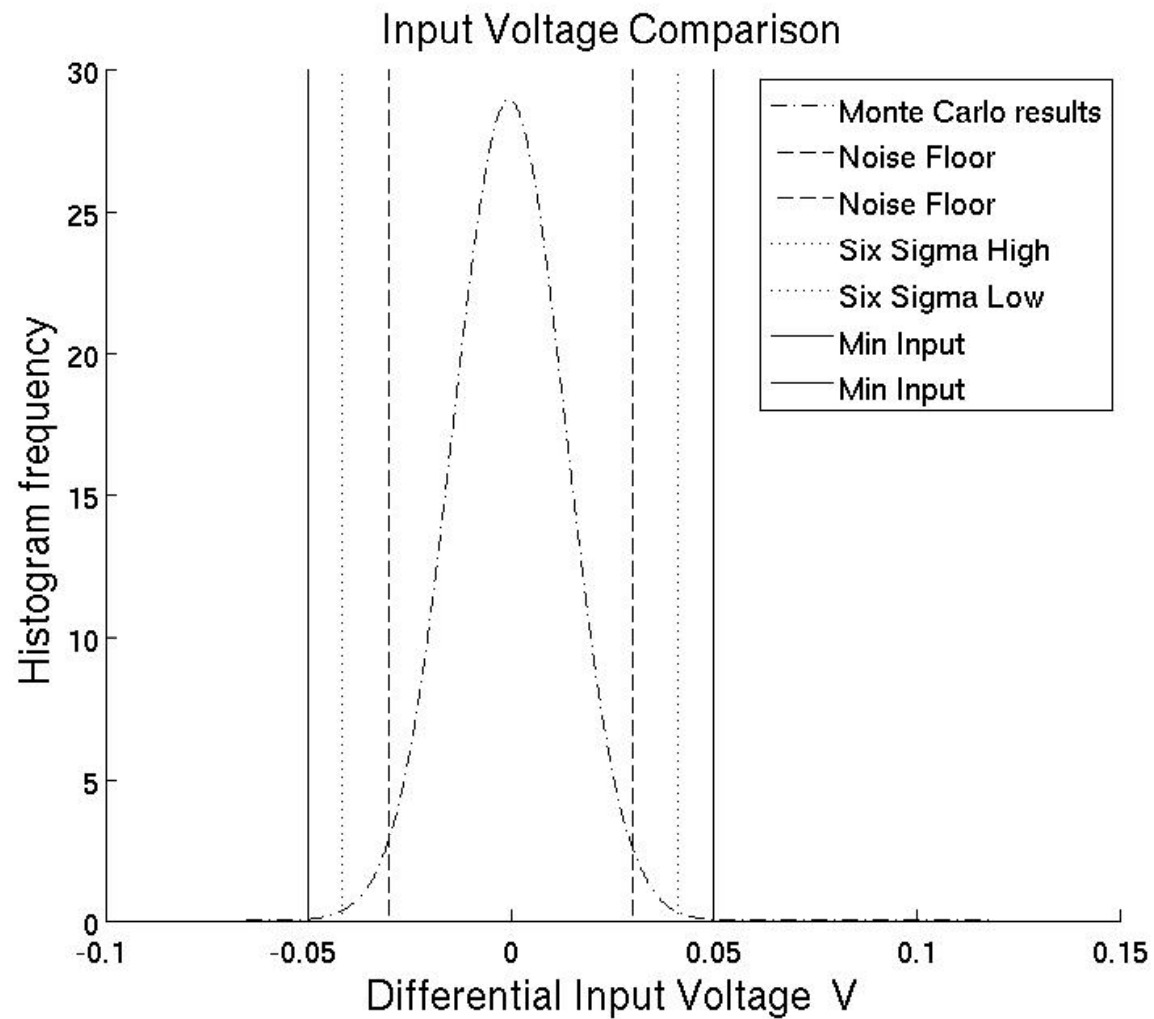

# Important Timings / Voltages

Characteristics	Simulated Results
Read enable- sense enable delay	200 ps
Read enable- data output delay	475 ps
Read enable- fault detection delay	575 ps
XOR delay	100 ps
Sense amplifier differential Input	250 mV
Fault detection differential Input	50 mV
Noise Floor	30 mV
6 $\sigma$ offset voltage	$\pm 40$ mV