

# Discussion 3

Wei-Hsiang Ma

2009/09/29

# Today

- Presentation given by 2 groups from last semester
- CAD4

# CAD4 requirements

- No metal4 and metal5 until datapath assignment
- Implement ADD, SUB, CMP, AND, OR, XOR, and immediate form of those functions
- Remember to implement the sign/zero extends
- Bit-slice width match with RF
- The VDD and GND metal2 power grid should use the same track as RF.

# Logic functions

- 2 ways to implement the logic functions
  - Muxing: higher power, faster
  - Utilize part of the adder: lower power, slower.  
(Sum= A xor B xor C, Carry=AB+AC+BC)
    - XOR: output from sum, cin=0 for every bit
    - AND: output from Cout, cin=0
    - OR: output from Cout, cin=1

# PSR

## (Processor Status Register )

- Have signals ready for PSR
- PSR conditions: (Cn= carry out of MSB)
  - C: carry ( Cn for ADD, Cn\_b for SUB)
  - F: overflow (Cn xor Cn-1)
  - Z: isZero (Nor bits of ALU output)
  - N: negative (Cn xor Cn-1 xor Sn-1) (signed)
  - L: low (Cn\_b) (unsigned)

More detail, please look at “427 Baseline Arch.”

# Future CAD/Discussion

- CAD Assignments
  - CAD4 is ALU (Custom)
  - CAD5 is Shifter (Custom)
  - CAD6 is Program Counter (Verilog)
- Discussion
  - 10/6: Baseline Architecture/ Verilog
  - 10/13: Tutorial2: Verilog/ Synthesis
  - 10/27: Tutorial2: Auto Place & Route (APR)
  - 11/3: Tutorial2.5: Integration

Q