

Discussion 4

Wei-Hsiang Ma

2009/10/06



Today

- Baseline Architecture
- Synthesis Flow
- Verilog


Architecture

- The architecture I am going to show you is the baseline architecture for EECS427
- Feel free to modify it, but it has to be working
- The slides are newly made by your GSI, if you see something wrong, please tell me.
- Hope you have a better understanding about the architecture.


ADDI/SUBI/CMPI/ANDI/ORI/XORI

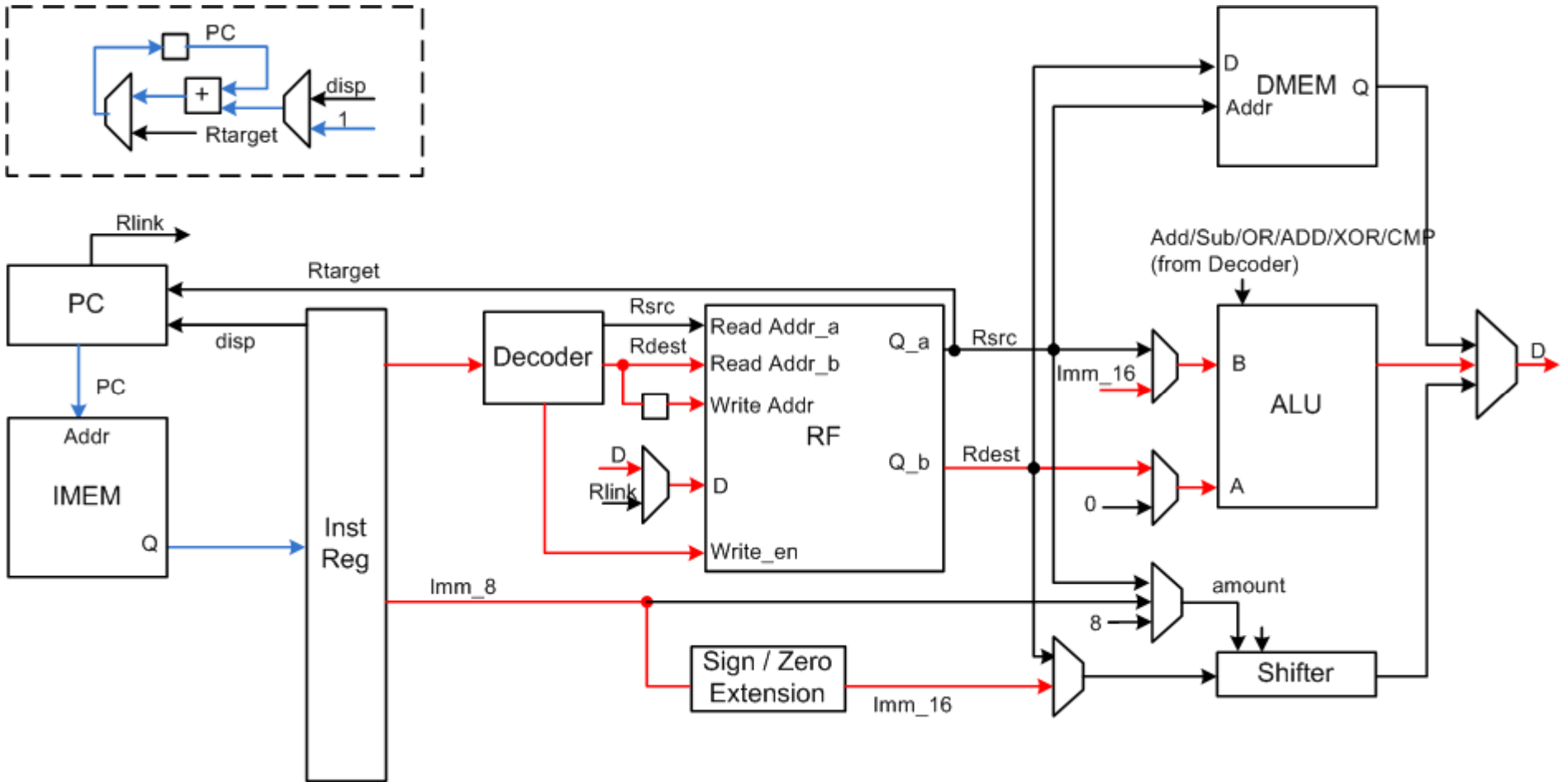 


MOV

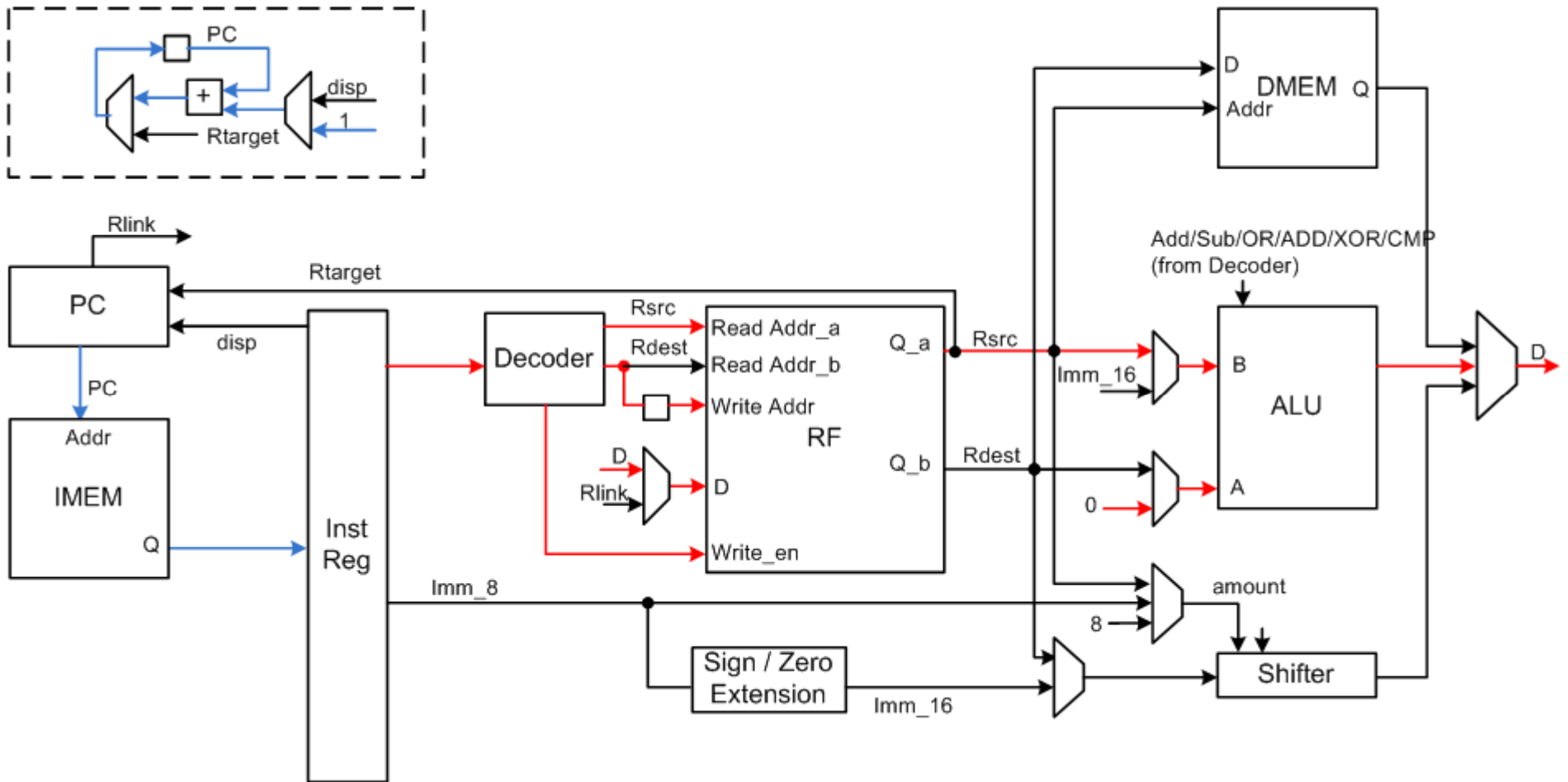


MOVI

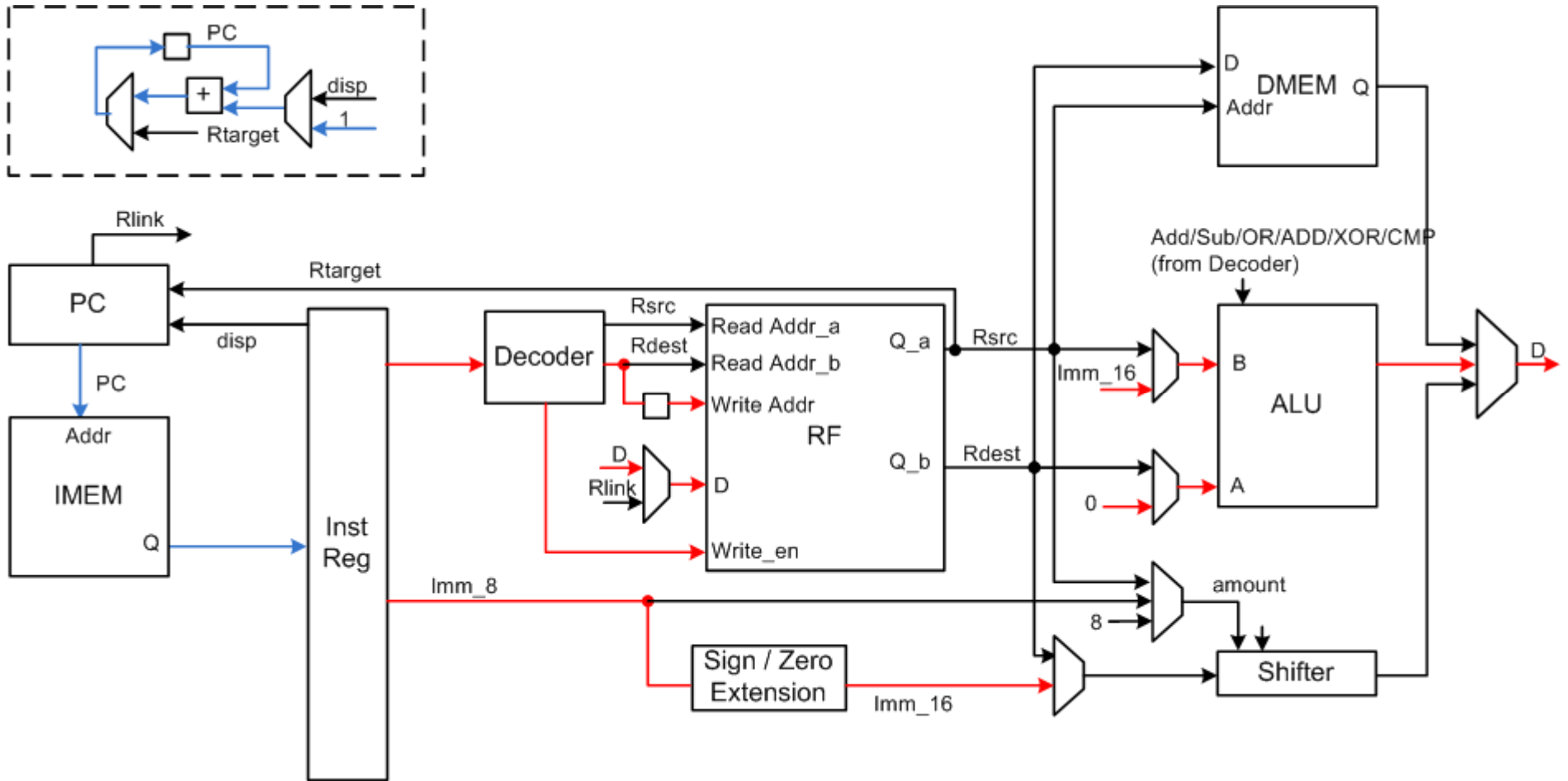


LSH/ASHU

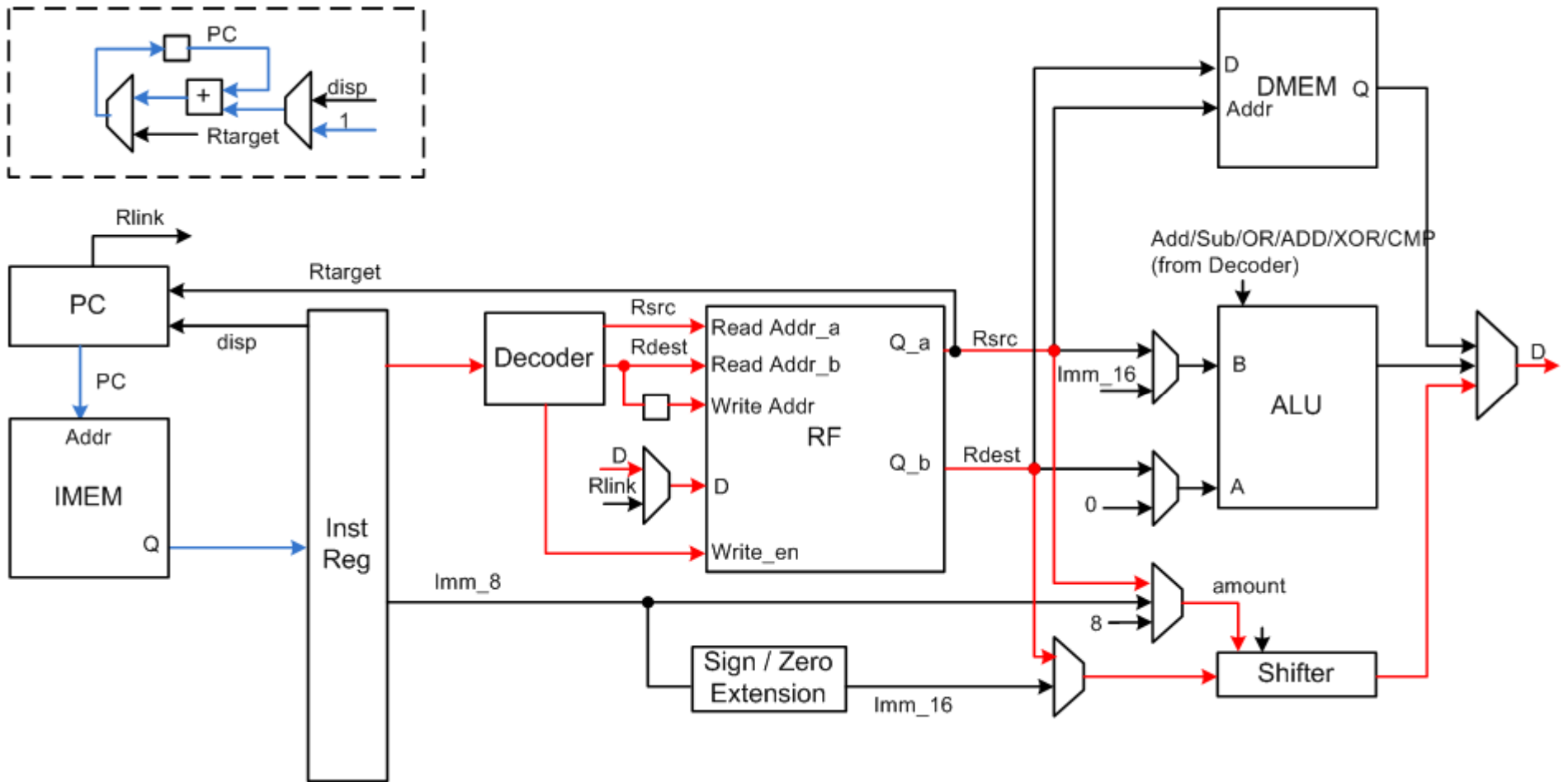


LSHI/ASHUI

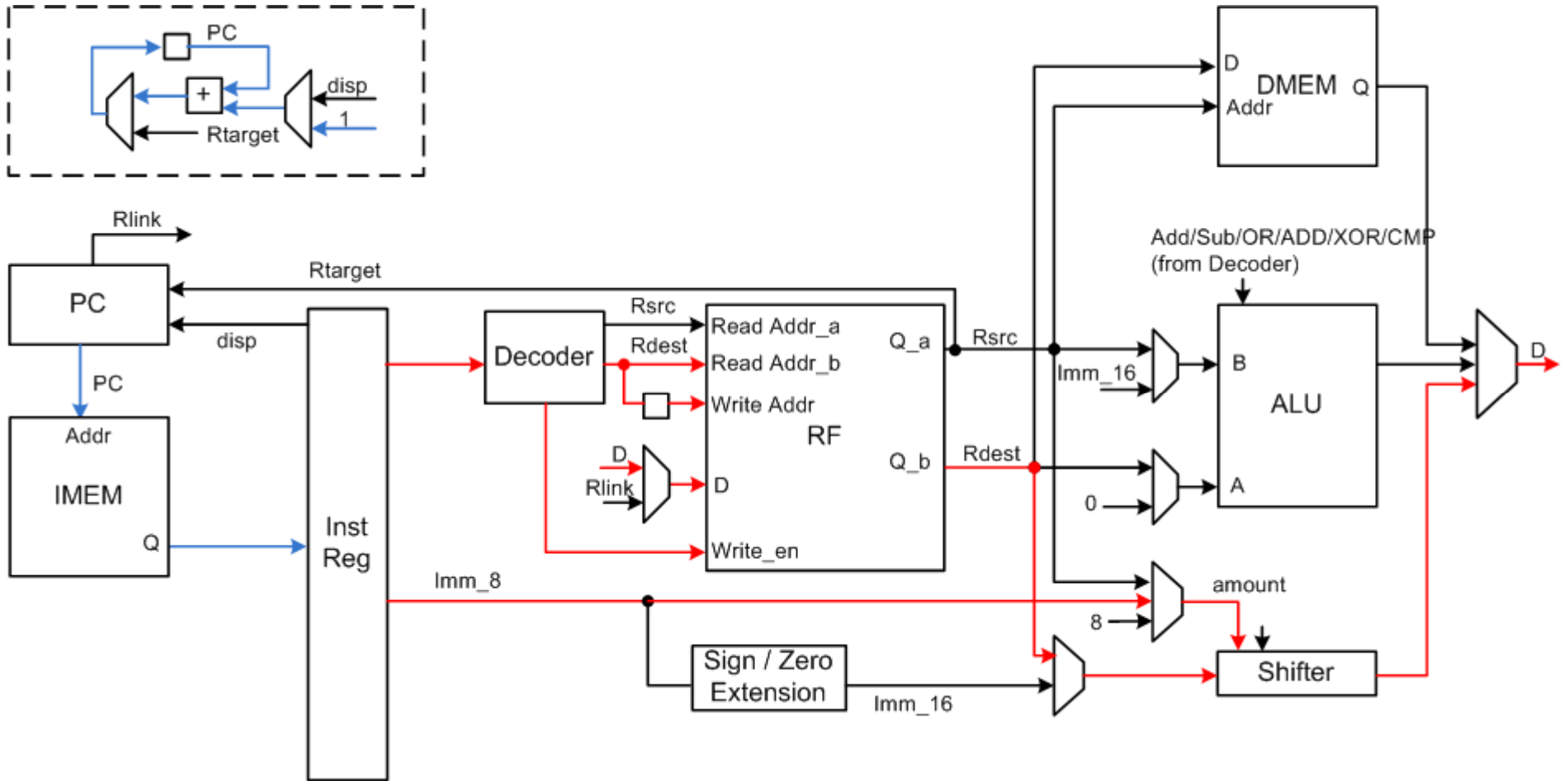


LUI

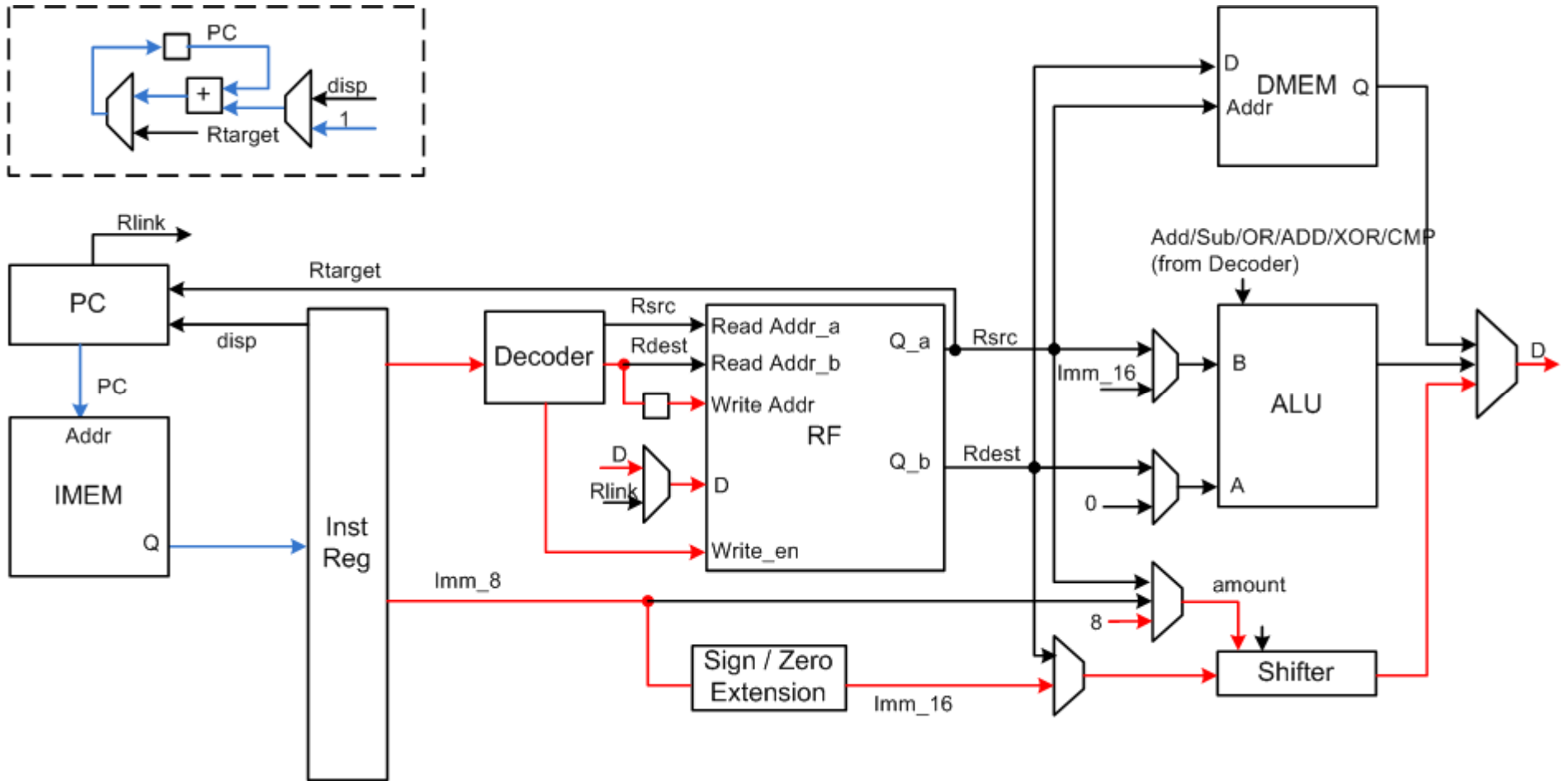


LOAD

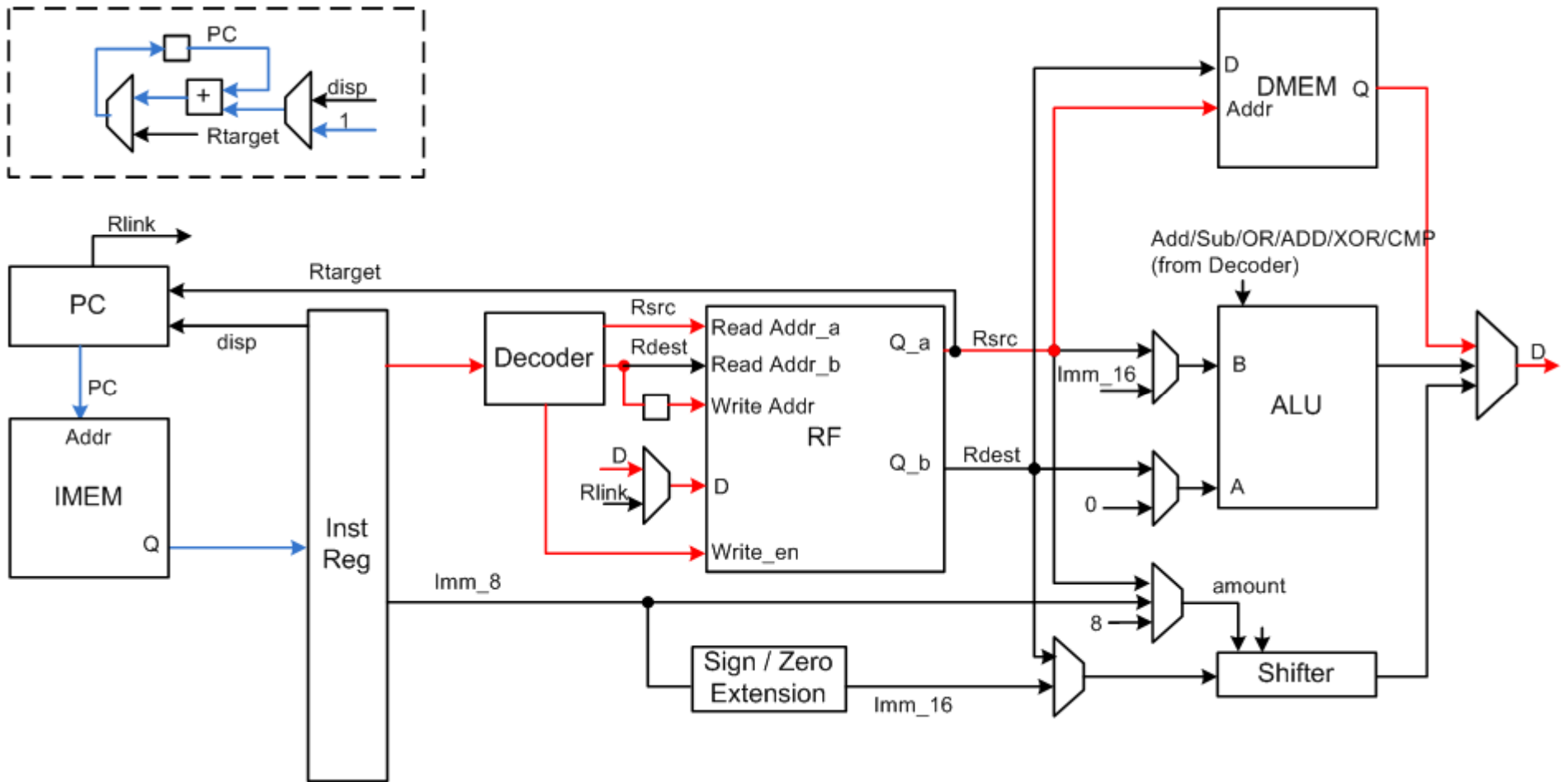


STOR

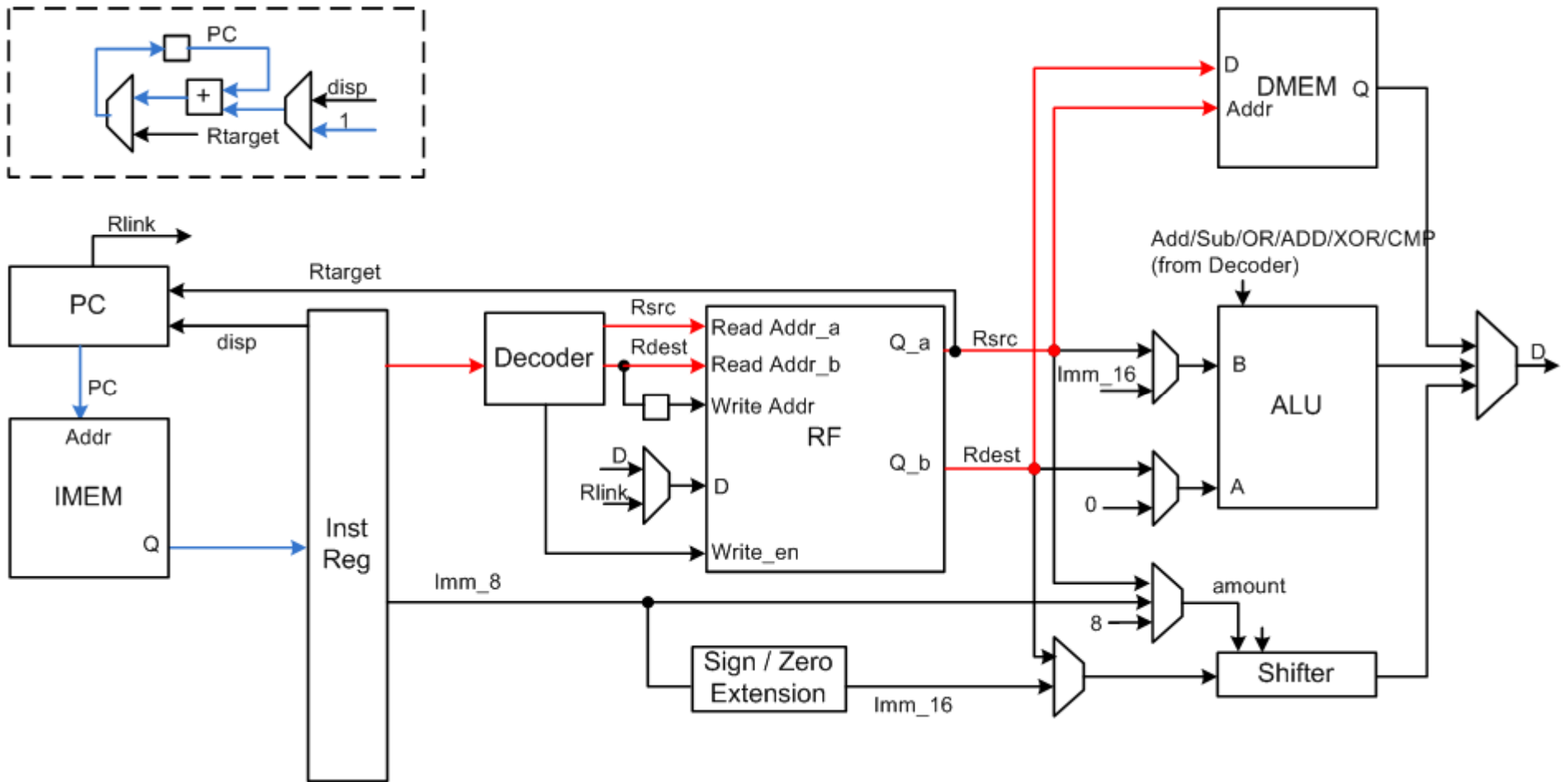

Bcond

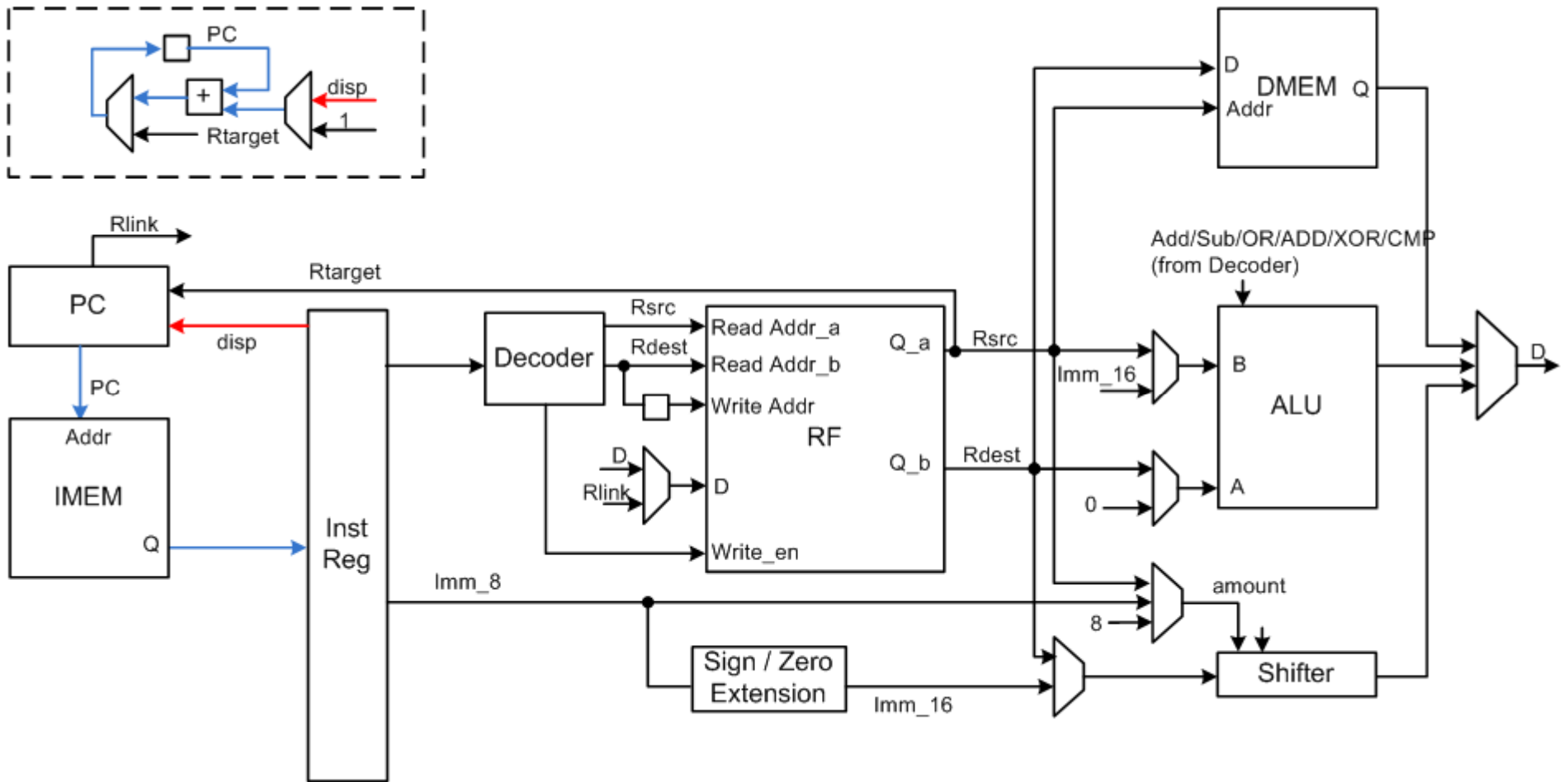


JAL

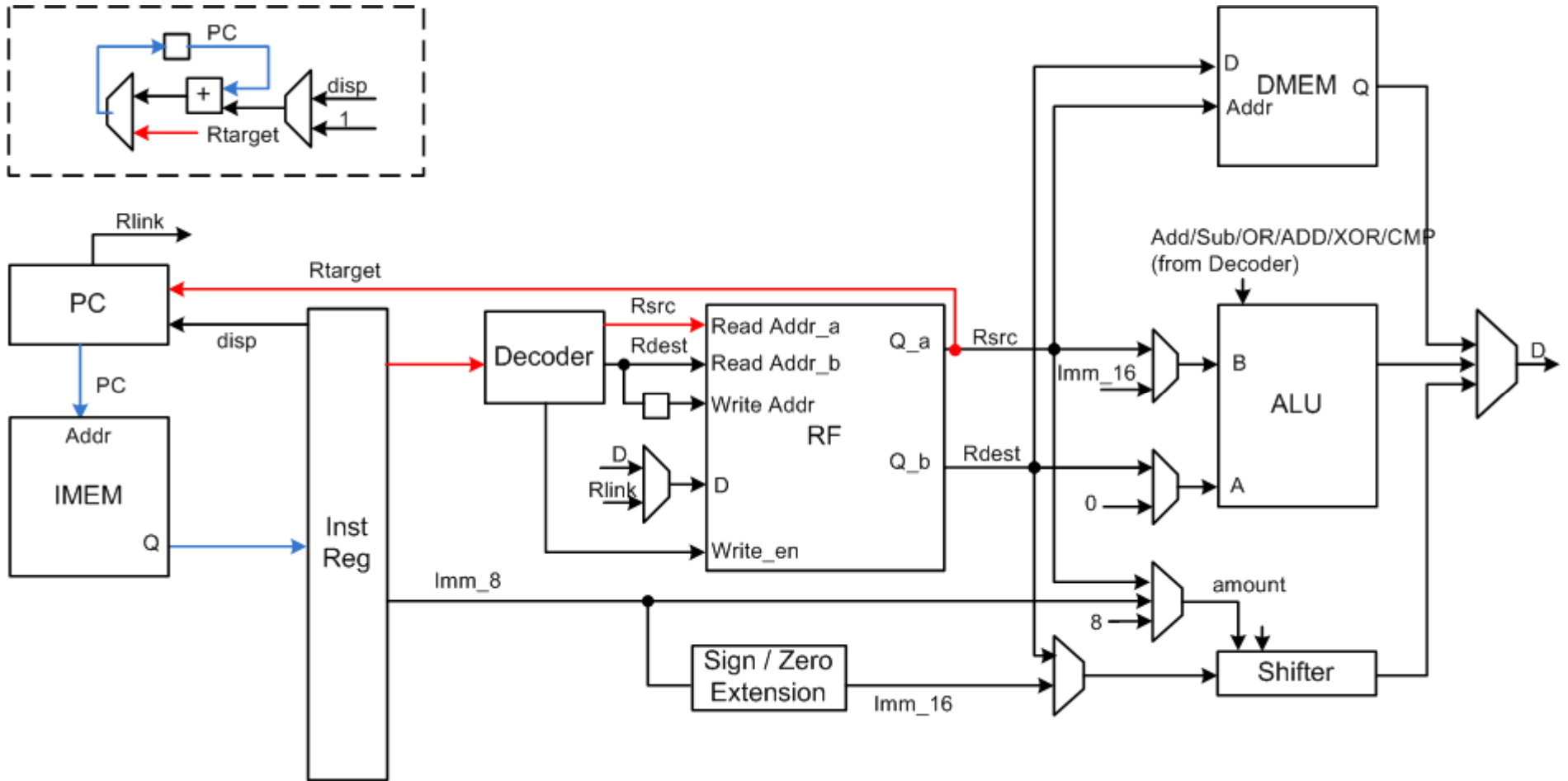

What else?

- Data Hazard
 - Inst0: $r1 + r3 \Rightarrow r1$
 - Inst1: $r1 + r5 \Rightarrow r1$
- Scan
 - Scan out some intermediate data
 - Scan in instructions I-MEM
- Global Reset
 - How does your processor start?

Synthesis Flow

 

```
add2.v  
  
module add2 (Y, A, B);  
input [1:0] A, B;  
output [1:0] Y;  
  
assign Y[1:0] = A[1:0] + B[1:0];  
  
endmodule
```

```
Std Cells:  
  
INVX1TR  
INVX2TR  
AND2X1TR  
AND2X2TR  
OR2X1TR  
OR2X2TR
```

```
Constrains:  
  
set input delay  
set output delay  
set output load  
set clock period
```

```
add2.nl.v  
  
module add2 (Y, A, B);  
input [1:0] A, B;  
output [1:0] Y;  
  
XORX2X1TR I1 (.Y(Y[0]), .A(A[0]), .B(B[0]));  
AND2X2TR I0 (.Y(C0), .A(A[0]), .B(B[0]));  
XOR3X2TR I2 (.Y(Y[1]), .A(A[1]), .B(B[1]), .C(C0));  
  
endmodule
```

- Synthesis tools will choose the size of the std cell according to the design constrains

Verilog (Sequential Logic)

<u>DFF without RESET</u>	<u>DFF with Sync RESET</u>	<u>DFF with Async RESET</u>
<pre>module DFF (Q, Q_b, D, CK); input D, CK; output Q, Q_b; reg Q, Q_b; always @(posedge CK) begin Q <= D; Q_b <= ~D; end endmodule</pre>	<pre>module DFF (Q, Q_b, D, CK, R); input D, CK,R; output Q, Q_b; reg Q, Q_b; always @(posedge CK) begin if (R == 1'b0) begin Q <= 1'b0; Q_b <= 1'b1; end else begin Q <= D; Q_b <= ~D; end end endmodule</pre>	<pre>module DFF (Q, Q_b, D, CK, R); input D, CK,R; output Q, Q_b; reg Q, Q_b; always @(posedge CK or negedge R) begin if (R == 1'b0) begin Q <= 1'b0; Q_b <= 1'b1; end else begin Q <= D; Q_b <= ~D; end end endmodule</pre>

- Tips:
 - Declare Q, Q_b as register
 - Use Non-Blocking assignment “<=“
 - All non-blocking assignments happen at the same time

Verilog (Combinational Logic)

<u>Use Assign</u>	<u>Use Always block</u>
<pre>module mult (Y, A, B); input [1:0] A, B; output [3:0] Y; assign Y = A * B; endmodule</pre>	<pre>module mult (Y, A, B); input [1:0] A, B; output [3:0] Y; reg [3:0] Y; always@* begin Y = A * B; end endmodule</pre>


- Tips for using always block
 - Declare Y as register, even though it is not.
 - Use Blocking assignment “=”
 - Blocking assignments are processed in order (C-style)

Verilog (Seq + Com Logic)

```
module mult (Y, A, B, CK);  
input [1:0] A, B;  
input CK;  
output [3:0] Y;  
  
reg [3:0] Y;  
wire [3:0] temp;  
  
assign temp = A * B;  
  
always @(posedge CK)  
begin  
Y <= temp;  
end  
endmodule
```

FSM

```
module FSM (A, clk, reset, state);  
  
input A;  
input clk, reset;  
output [1:0] state;  
  
reg [1:0] state;  
  
always@(posedge clk)  
begin  
    if (reset == 1'b0)  
    begin  
        state <= 2'b00;  
    end  
    else  
    begin  
        case (state)  
        2'b00:  
        begin  
            if (A == 1'b1) state <=2'b00;  
            else state <= 2'b01;  
        end  
        2'b01:  
        begin  
            if (A == 1'b1) state <=2'b00;  
            else state <= 2'b10;  
        end  
        2'b10:  
        begin  
            if (A == 1'b1) state <=2'b00;  
            else state <= 2'b10;  
        end  
        endcase  
    end  
end  
  
endmodule
```

 

FSM

```
module FSM (A, clk, reset, state);

input A;
input clk, reset;
output [1:0] state;

reg [1:0] state;

always@(posedge clk)
begin
    if (reset == 1'b0)
    begin
        state <= 2'b00;
    end
    else
    begin
        case (state)
        2'b00:
        begin
            if (A == 1'b1) state <=2'b00;
            else state <= 2'b01;
        end
        2'b01:
        begin
            if (A == 1'b1) state <=2'b00;
            else state <= 2'b10;
        end
        2'b10:
        begin
            if (A == 1'b1) state <=2'b00;
            else state <= 2'b10;
        end
        endcase
    end
end

endmodule

reg we_en0, we_en1, we_en2;
always@ *
begin
    case (state)
    2'b00:
    begin
        we_en0 = 1'b1;
        we_en1= 1'b0;
        we_en2= 1'b1;
    end
    2'b01:
    begin
        we_en0 = 1'b1;
        we_en1= 1'b0;
        we_en2= 1'b0;
    end
    2'b10:
    begin
        we_en0= 1'b0;
        we_en1= 1'b0;
        we_en2= 1'b1;
    end
    endcase
end
```

Others

- While, forever, initial,... => only used in testbench

Verilog Simulation

- Create “**functional**” view
- Paste your behavioral code into the “**functional**” view
- Create an empty “**schematic**” view
- When doing NCverilog simulation, choose “**functional**” instead of “**schematic**”
- Modify your testbench and simulate it

Demo

- Verilog simulation