

---

# EECS 427

## Lecture 15: Timing, Latches, and Registers

Reading: Chapter 7


---

## Reminders

- CAD assignments
  - CAD7 is due Thursday at noon
- ECE Graduate Symposium
  - Poster session in ECE Atrium on Friday
- HW4 (detailed proposal) is due Tuesday 11/17 (one day extension)
  - You should have completed your schematic design and simulation and started block layouts by then
  - Send your proposal (in Word or LaTeX) by email to the Zhengya, cutoff time: 11:59 pm on 11/17
- Quiz 2 on Monday 11/23?
  - Your chance to improve your performance in Quiz 1
  - The other option: review session (problem solving, Q&A) on Monday 11/23 in class, Quiz 2 on Tuesday 11/24 5:40 pm – 7:00 pm during the discussion slot
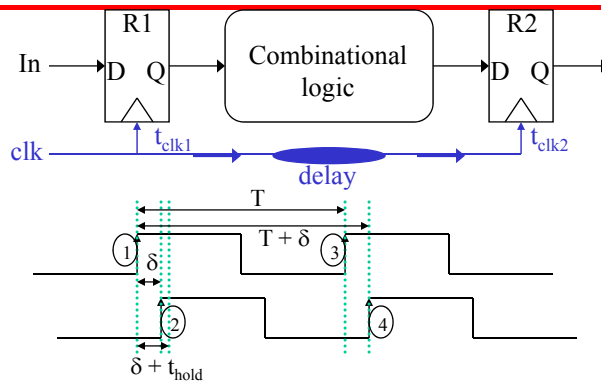
## Positive Clock Skew

- Clock and data flow in the same direction



$$T: T + \delta \geq t_{cq,max} + t_{logic,max} + t_{su} \quad \text{so} \quad T \geq t_{cq,max} + t_{logic,max} + t_{su} - \delta$$

$$t_{hold}: t_{hold} + \delta \leq t_{logic,min} + t_{cq,min} \quad \text{so} \quad t_{hold} \leq t_{logic,min} + t_{cq,min} - \delta$$

- Positive skew: Improves performance, but makes  $t_{hold}$  harder to meet. If  $t_{hold}$  is not met (race conditions), the circuit malfunctions independent of the clock period!

EECS 427 F09


Lecture 15

Irwin and Narayanan

3
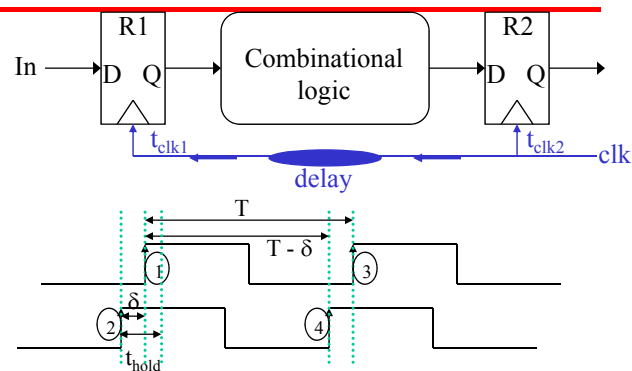
## Negative Clock Skew

- Clock and data flow in opposite directions



$$T: T - \delta \geq t_{cq,max} + t_{logic,max} + t_{su} \quad \text{so} \quad T \geq t_{cq,max} + t_{logic,max} + t_{su} + \delta$$

$$t_{hold}: t_{hold} - \delta \leq t_{logic,min} + t_{cq,min} \quad \text{so} \quad t_{hold} \leq t_{logic,min} + t_{cq,min} + \delta$$

- Negative skew: Degrades performance, but  $t_{hold}$  is easier to meet (eliminating race conditions)

EECS 427 F09


Lecture 15

Irwin and Narayanan

4
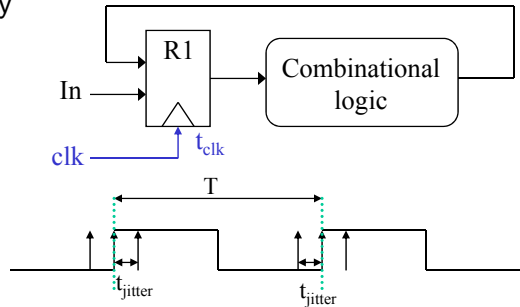
# Clock Jitter

- Jitter causes  $T$  to vary on a cycle-by-cycle basis




$$T : T - 2t_{\text{jitter}} \geq t_{\text{cq,max}} + t_{\text{logic,max}} + t_{\text{su}} \quad \text{so} \quad T \geq t_{\text{cq,max}} + t_{\text{logic,max}} + t_{\text{su}} + 2t_{\text{jitter}}$$

$$t_{\text{hold}} : t_{\text{hold}} + 2t_{\text{jitter}} \leq t_{\text{logic,min}} + t_{\text{cq,min}} \quad \text{so} \quad t_{\text{hold}} \leq t_{\text{logic,min}} + t_{\text{cq,min}} - 2t_{\text{jitter}}$$

- Jitter directly reduces the performance of a sequential circuit
- Jitter makes race condition worse
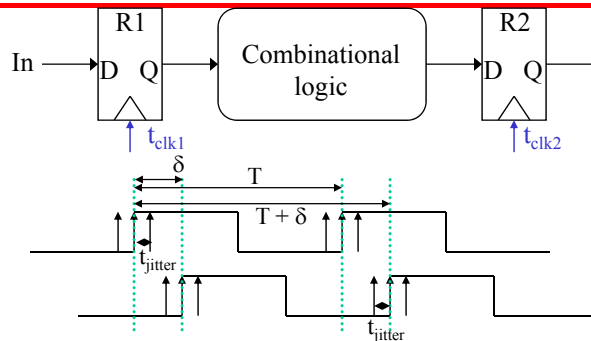
# Combined Impact of Skew and Jitter


- Constraints on the minimum clock period ( $\delta > 0$ )



$$T \geq t_{\text{cq,max}} + t_{\text{logic,max}} + t_{\text{su}} - \delta + 2t_{\text{jitter}} \quad t_{\text{hold}} \leq t_{\text{logic,min}} + t_{\text{cq,min}} - \delta - 2t_{\text{jitter}}$$


- Positive skew with jitter: Degrades performance, and makes  $t_{\text{hold}}$  even harder to meet. (The acceptable skew is reduced by jitter.)

# Register-Based Timing

 


Representation after  
M. Horowitz, VLSI Circuits 1996.

# Registers and Dynamic Logic

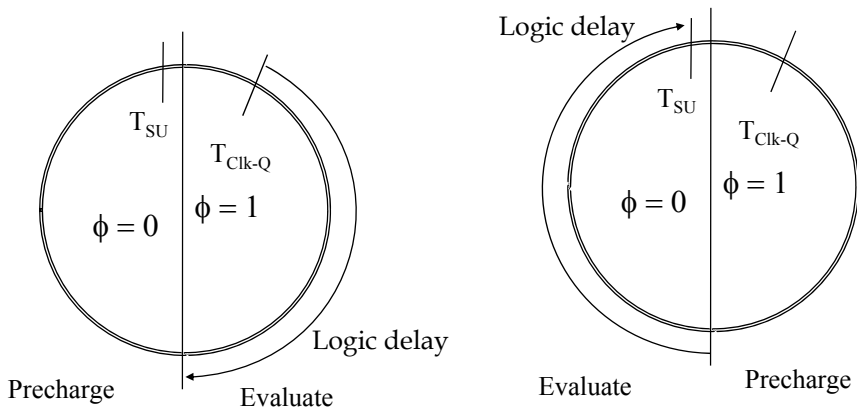

Registers are used only with static logic

# Latch timing

 


When data arrives to transparent latch

Latch is a 'soft' barrier

When data arrives to closed latch

Data has to be 're-launched'


# Domino Logic with Latch Timing

 


Harris, JSSC97

# Master-Slave Register


Multiplexer-based latch pair

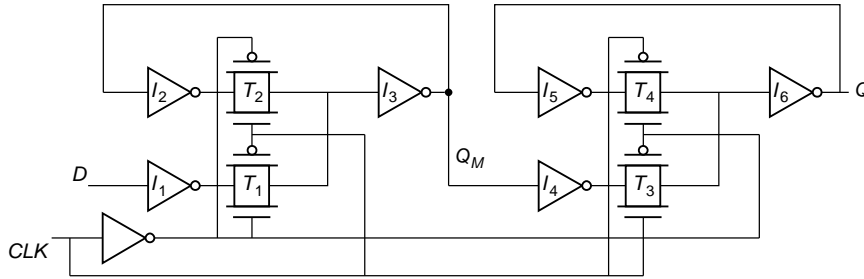


# Setup Time

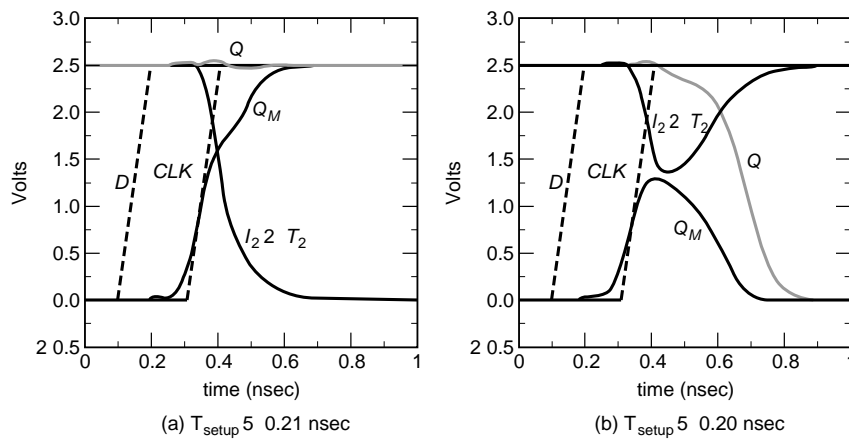


# Reduced Clock Load

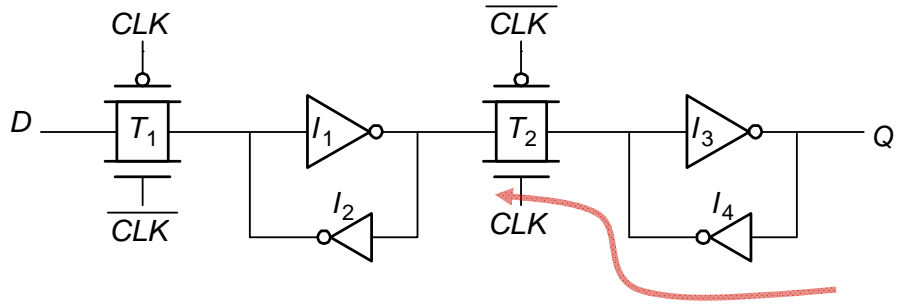

# Avoiding Clock Overlap

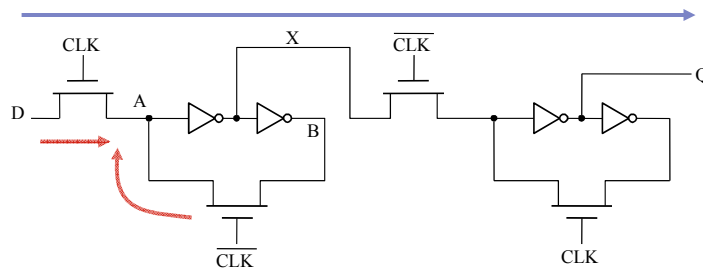


(a) Schematic diagram

 


(b) Overlapping clock pairs

# Dynamic Latch


Static

 

Dynamic (charge-based)

 


# C<sup>2</sup>MOS

 


"Keepers" can be added to make circuit pseudo-static


# In insensitive to Clock-Overlap

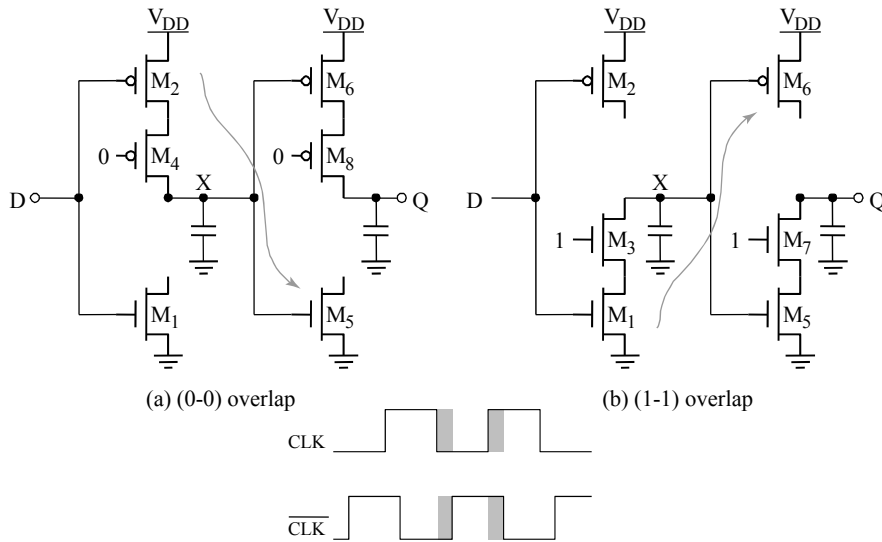

# TSPC

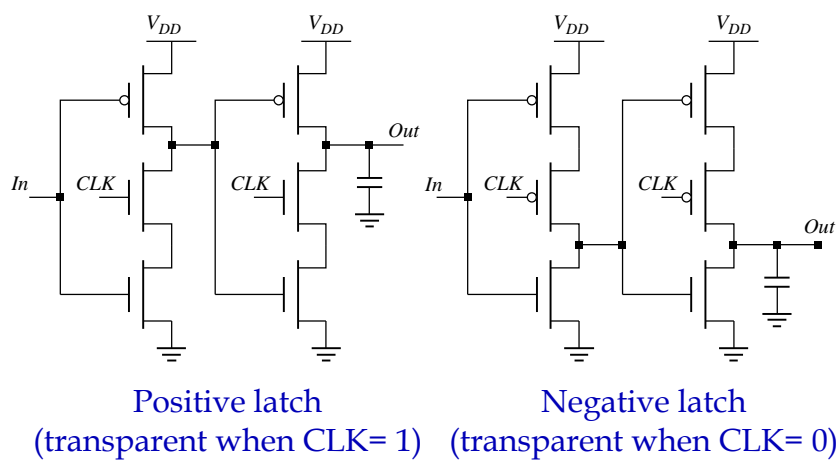


# Including Logic in TSPC

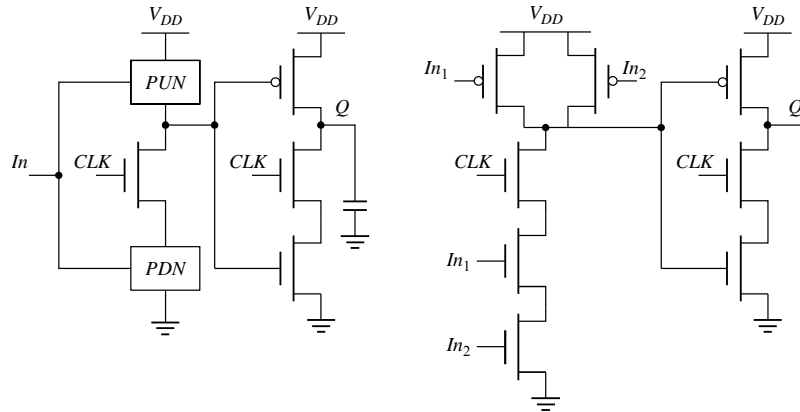

Example: logic inside the latch

AND latch


# TSPC Register

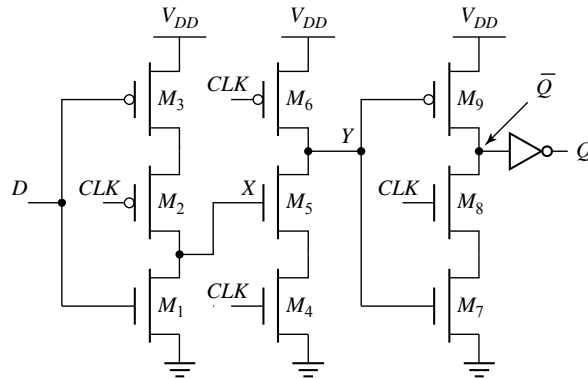


# Pulse-Triggered Latches

Ways to design an edge-triggered sequential cell:


Master-Slave Latches

 

Pulse-Triggered Latch

 


# Pulsed Latches

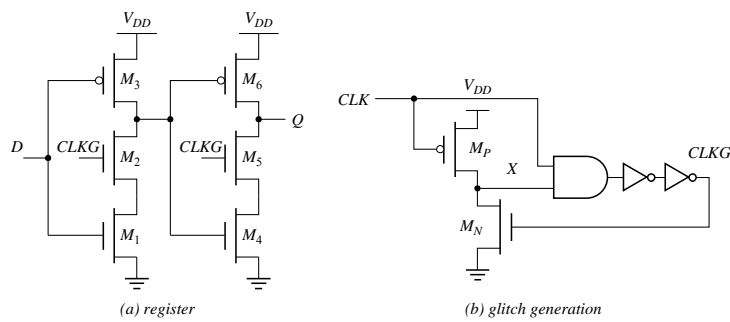

(a) register


(b) glitch generation

 

(c) glitch clock
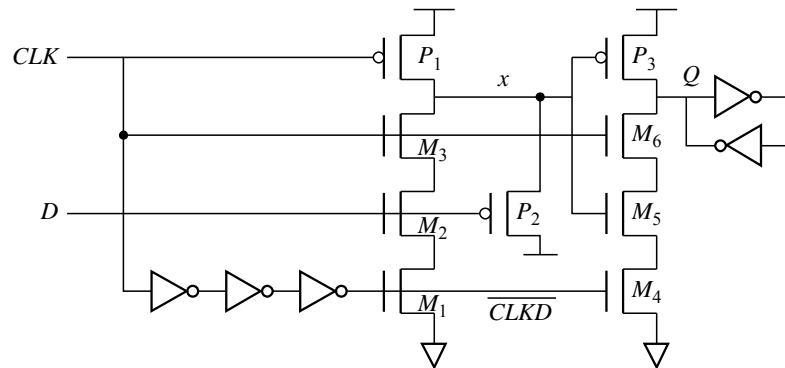
# Pulsed Latches

Hybrid Latch - Flip-flop (HLFF), AMD K-6 and K-7 :




EECS 427 F09

Lecture 15

23

# Hybrid Latch-FF Timing

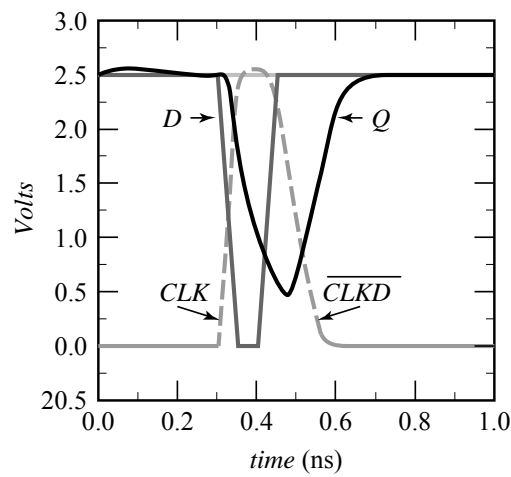

EECS 427 F09

Lecture 15

24

# Latch-Based Pipeline

