
EECS 427

Lecture 8: Adders

Readings: 11.1-11.3.3

Reminders

- HW3 – project initial proposal: due Wednesday 10/7
 - You can schedule a half-hour appointment with me to discuss your initial proposal before submission
 - Email your initial proposal (one per group) in doc format to zhengya@eecs.umich by 7 pm on Wednesday night
 - Limit your write-up to 4 pages maximum. Keep it brief and clear.
- Quiz 1 on Wednesday 10/14
 - Samples (with solutions) from past terms are posted
 - Half-lecture review next Monday
- CAD4 is due Wednesday 10/14
 - You can submit it by Thursday 10/15 at noon


Last Time

- Dynamic circuits – high performance
 - Dynamic logic – non-ratioed, dynamic power only, no static current, higher activity, low noise margin
 - Domino logic – can be safely cascaded, only non-inverting logic
 - Footless domino – ripple precharge, delayed clock, extra power
 - Dual-rail domino – both inverting and non-inverting outputs
 - NP CMOS – cascade n- and p- evaluation networks

Overview


- Full adder
 - Mirror adder
 - Transmission-gate adder
 - Manchester carry chain
- Adder topologies
 - Ripple carry
 - Carry bypass
 - Carry select
 - Carry lookahead
- Carry lookahead adder
 - Kogge-Stone
 - Radix 2 or Radix 4
 - Sparse tree, Brent-Kung

Full Adder

 

A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

The Binary Adder

 

$$\begin{aligned}
 S &= A \oplus B \oplus C_i \\
 &= \overline{A}\overline{B}C_i + \overline{A}B\overline{C}_i + A\overline{B}\overline{C}_i + ABC_i \\
 C_o &= AB + BC_i + AC_i
 \end{aligned}$$

Express Sum and Carry as a function of P, G, D

Define 3 new variables which ONLY depend on A, B WHY?

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A \oplus B$$


$$\text{Delete} = \overline{A} \overline{B}$$

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and C_o based on D and P

The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{adder} = (N-1)t_{carry} + t_{sum}$$

Goal: Make the fastest possible carry path circuit

Complementary Static CMOS Full Adder

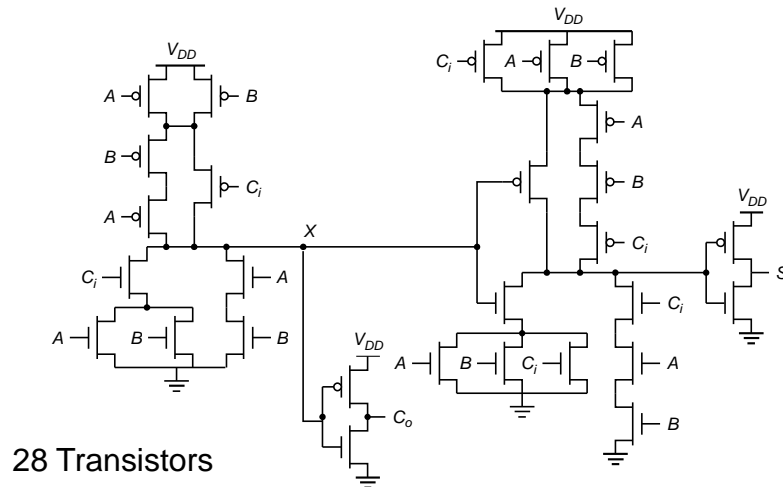


EECS 427 F09

Lecture 8

9

Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

EECS 427 F09

Lecture 8

10

 
Minimize Critical Path by Reducing Inverting Stages Along Carry Path



Exploit Inversion Property


Allows us to remove inverter in carry chain → at what cost?

A Better Structure: Mirror Adder

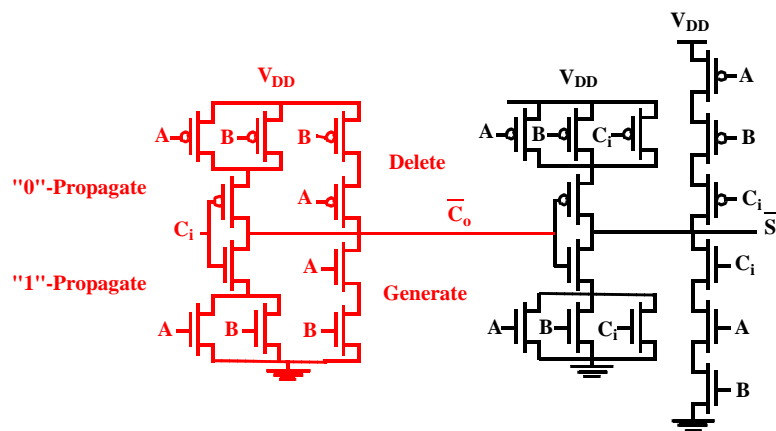

24 transistors

Mirror Adder Layout

 

EECS 427 F09

Lecture 8

13

Mirror Adder Details


- NMOS and PMOS chains are **completely symmetric**.
Maximum of 2 series transistors in carry generation
- In layout \rightarrow critical to minimize capacitance at node C_o .
Reduction of junction capacitances is particularly important
- Capacitance at node C_o is composed of 4 junction capacitances, 2 internal gate capacitances, and 6 gate capacitances in connecting adder cell
- Transistors connected to C_i are closest to output
- Only optimize transistors in carry stage for speed
Transistors in sum stage can be small

EECS 427 F09


Lecture 8

14


Sizing Mirror Adder

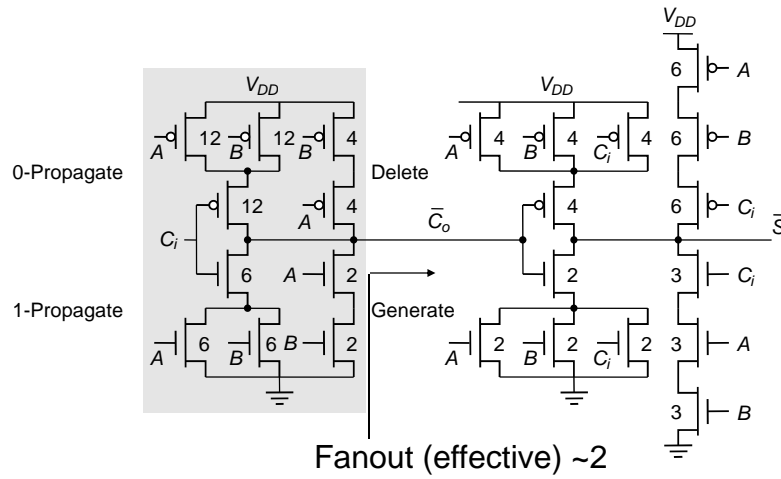

Transmission Gate Full Adder

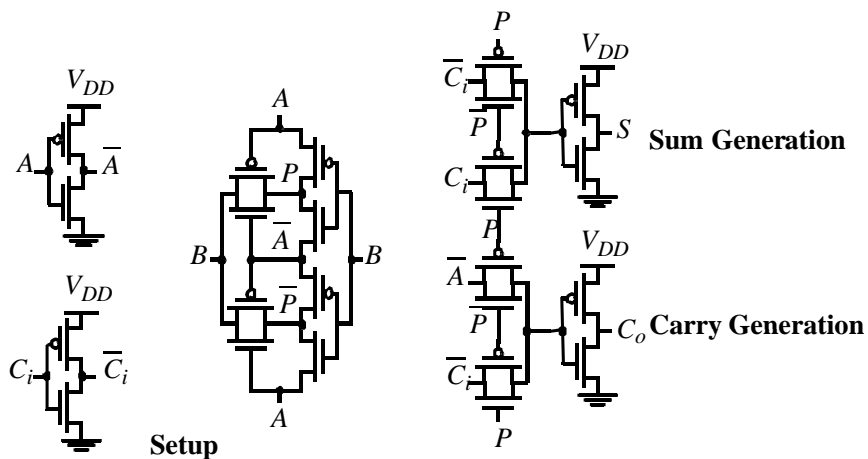

Manchester Carry Chain

 


EECS 427 F09

Lecture 8

17

Manchester Carry Chain

 - Implement P with pass-transistors
- Implement G with pull-up OR kill (delete) with pull-down (note inversion)
- Use dynamic logic to reduce complexity and speed up




EECS 427 F09

Lecture 8


18

Carry-Bypass Adder

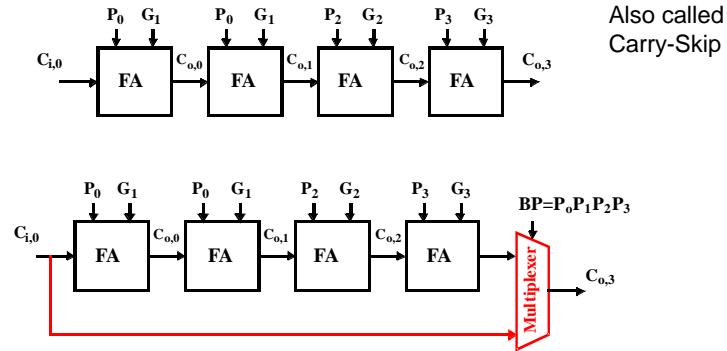

Idea: If $(P_0 \text{ and } P_1 \text{ and } P_2 \text{ and } P_3 = 1)$
 then $C_{o3} = C_{i,0}$, else "delete" or "generate"


Carry-Bypass Adder (cont.)

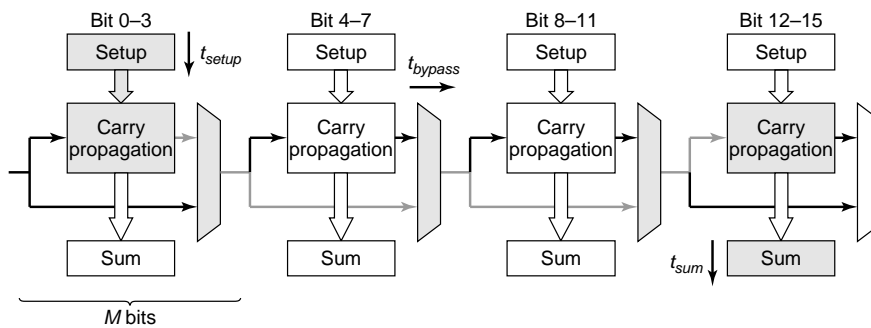


$$t_{adder} = t_{setup} + M t_{carry} + (N/M - 1) t_{bypass} + (M - 1) t_{carry} + t_{sum}$$

Inner blocks do not contribute to worst-case delay since they have time to compute while bits 0-3 are propagating (assuming they have a generate or delete)

Carry Ripple versus Carry Bypass

 


Carry-Select Adder

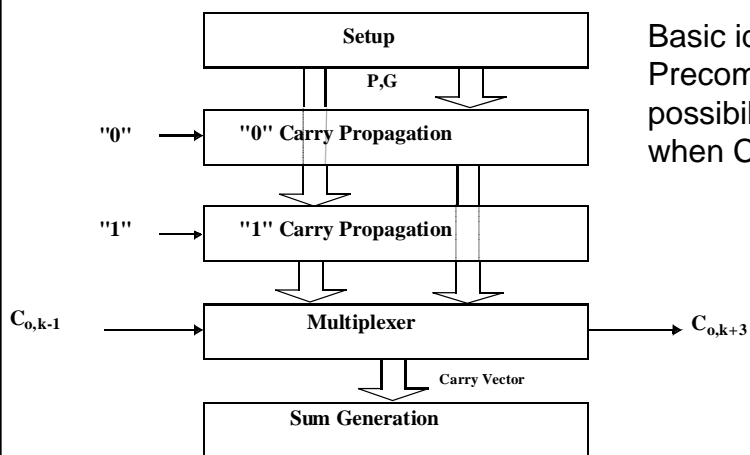


Basic idea:
Precompute both possibilities, choose when C_{in} available

Carry Select Adder: Critical Path

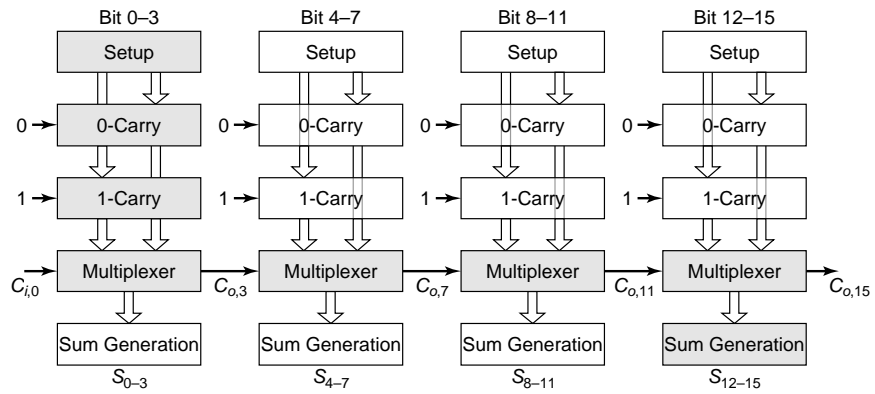


$$t_{add} = t_{setup} + Mt_{carry} + (N/M)t_{mux} + t_{sum}$$

Linear Carry Select

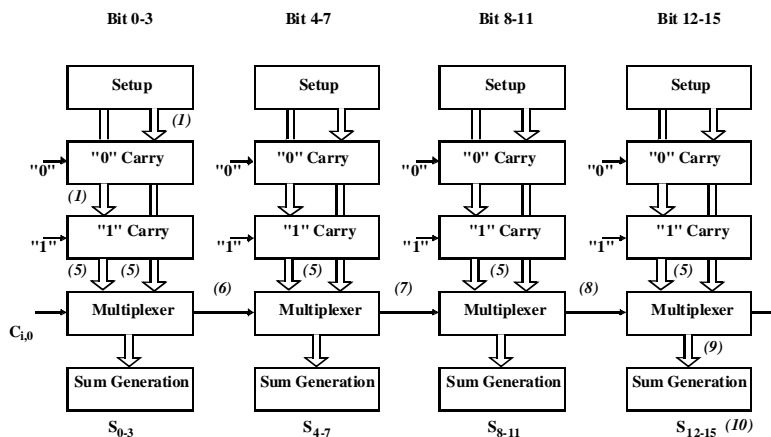


$$t_{add} = t_{setup} + M^*t_{carry} + (N/M)t_{mux} + t_{sum}$$

Square Root Carry Select

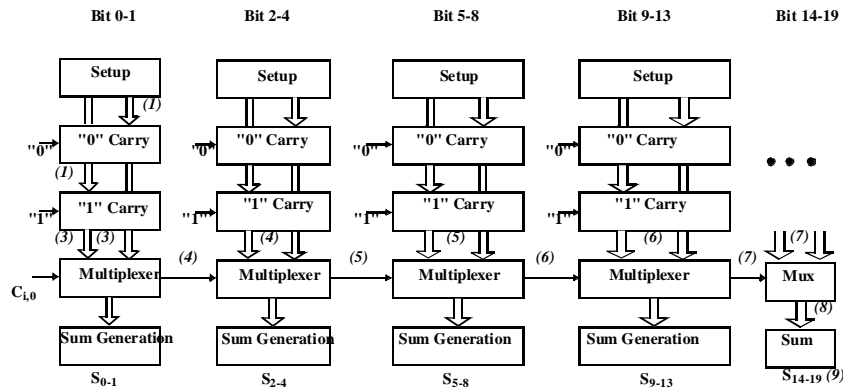


$$t_{add} = t_{setup} + Mt_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$

Adder Delays - Comparison

 

Lookahead - Basic Idea

 

$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$

EECS 427 F09

Lecture 8

27


4-bit Lookahead Adder

Expanding Lookahead equations:

$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}C_{o,k-2})$$

All the way:
 
$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}(\dots + P_1(G_0 + P_0C_{i,0})))$$




EECS 427 F09


Lecture 8

28

Logarithmic Lookahead Adder

 

$$t_p \sim N$$

 

$$t_p \sim \log_2(N)$$

Carry Lookahead Trees

$$C_{0,0} = G_0 + P_0 C_{i,0}$$

$$C_{0,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$C_{0,2} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0}$$

$$= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{0,0}$$


Can continue building the tree hierarchically.

In general

$$G_{j:k} = G_j + P_j G_{j-1:k}$$


$$P_{j:k} = P_j P_{j-1:k}$$

Tree Adder

 

16-bit radix-2 Kogge-Stone tree


Domino Adder

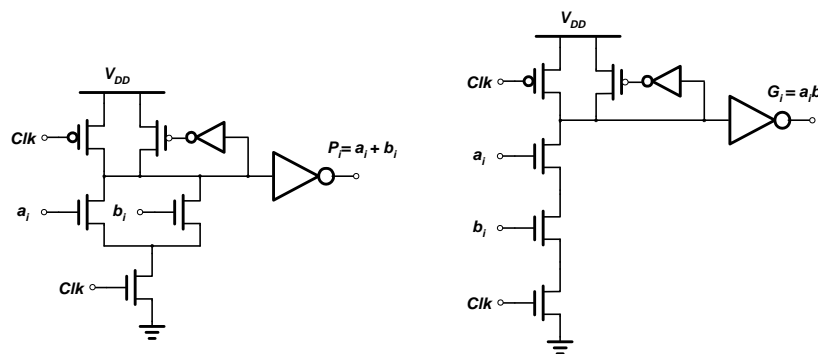

Propagate

Generate

Domino Adder

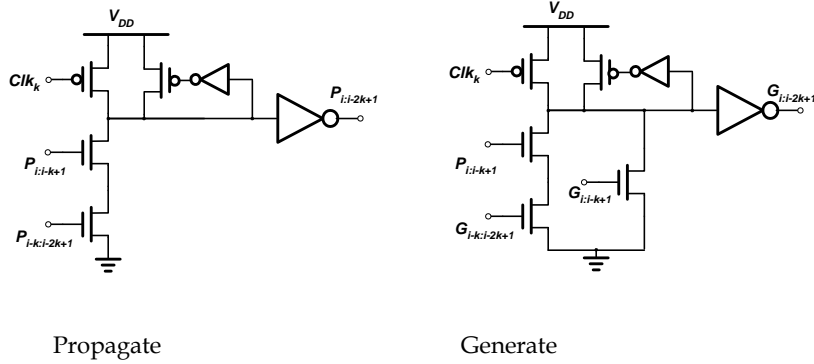


EECS 427 F09

Lecture 8

33

Domino Sum

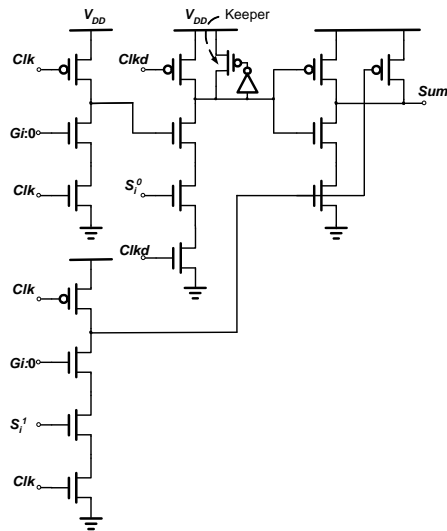


EECS 427 F09

Lecture 8


34

Tree Adder

 


16-bit radix-4 Kogge-Stone Tree

Sparse Tree

 

16-bit radix-2 sparse tree with sparseness of 2

Tree Adder

 

Brent-Kung Tree

Radix 2 vs. Radix 4

- Fanout consideration
 - Easier to drive large fanouts with Radix-2
 - Radix-4 has fewer stages and could have speed advantage when driving low fanouts
- Wire length consideration
 - Radix-4 has longer wires (64 bits: crosses 48 bit slices vs. 32 in radix-2). Fewer logic stages precedes large wireload.
- Logic consideration
 - Radix-2 has lower stack heights

Full vs. Sparse Trees

- Not all the carries are calculated in sparse trees
 - Only every 2nd, 4th, etc.
 - Reduced (uneven) input capacitance
 - Fewer transistors and wires
 - Lower power
- Sparse tree adders need to recover missing carries
 - Ripple (extra gate delay)
 - Precompute (extra fanout)
 - Complex precomputation can get into the critical path

Overview

- Full adder
 - Mirror adder – size it carefully
 - Transmission-gate adder – efficient XOR implementation
 - Manchester carry chain – long RC chain
- Adder topologies
 - Ripple carry – simple, small adders
 - Carry bypass – skip in groups
 - Carry select – precomputation to shorten the critical path
 - Carry lookahead – compute carry-in for higher order bits to shorten the critical path
- Carry look-ahead adder
 - Kogge-Stone – full tree, regular interconnect, consistent fanout, large area and high power
 - Radix 2 or Radix 4 – tradeoff between gate complexity and tree depth
 - Sparse tree, Brent-Kung – fewer gates, fewer wires, some high-fanout gates slows down the performance