

Assignment

Create schematics, symbols, and layouts for an inverter and a 2-input nand gate. Using these symbols and layouts, create a schematic, symbol, and layout for a 2:1 mux using 3 2-input nand gates and 1 inverter. Perform design-rule-checks (DRC) and a layout-vs.-schematic (LVS) check on the layouts of the inverter, 2-input nand, and 2:1 mux. Then, get accurate propagation delays for the 2:1 mux by extracting parasitic capacitances from the layout and simulating the circuit with HSpice.

You probably will not use any of these cells in your final project, so don't be concerned about choosing the "right" cell height or choosing optimal transistor sizes. Try to minimize area and feel free to use all layers except Metal 4 and Metal 5. While layout area will be considered in grading, do not spend a lot of time optimizing the layout to save on area.

The first two cad assignments are to be done on your own. You may discuss use of the cad tools and basic layout concepts with other students, but your design, particularly your layout, should be created by yourself.

Description

- Create a directory in your class account called **cad1**. All of your files will need to be in this directory in order to be graded.
- Make the **schematics** and **symbols** for the inverter and 2-input nand using *Composer*. Follow the naming guidelines in the inverter tutorial (i.e. don't call the nand "nand" or the inverter "inv"). Be sure to use the pmos/nmos transistors from the NCSU_ANALOG_LIBRARY. Call the inverter ports **in** and **out**. Call the nand ports **in0**, **in1**, and **out**.
- **Simulate** the inverter and nand in NC Verilog and verify correct functionality. Test all possible inputs for both gates. Create the input stimulus as you did in the inverter tutorial by editing the testfixture.verilog file to forces the inputs.
- Follow the guidelines of *The Design and Simulation of an Inverter* to create layouts for the inverter and 2-input nand. Make sure that you use the same names to label the inputs and outputs of the gates in *VLE* that are used on the symbol. Keep in mind when designing these gates that they will be used in the layout of the 2:1 mux. Examples of things to keep in mind:
 - (1) How will you route between the 4 cells?
 - (2) How will you place the cells to create a 2:1 mux?
 - (3) Where will you place your input and output ports?

For example, you could place all your cells in a straight line or in a square. **Choose a configuration that minimizes interconnect length.**

- Perform a Design Rules Check (**DRC**) on the layouts of the inverter and nand gates. For directions please refer to *The Design and Simulation of an Inverter*.
- Perform a Layout Versus Schematic (**LVS**) on the layouts of the inverter and nand gates. Save the LVS reports to the files **lvs_<component_name>.rep**. For directions please refer to *The Design and Simulation of an Inverter*.
- Make the **schematics** and **symbols** for the 2:1 mux and call it **mux2**. Create the 2:1 mux by instantiating 3 of your nand gates and 1 inverter.
- **Simulate** the 2:1 mux in NC Verilog and verify correct functionality. Force values on the two inputs and select such that all possible input combinations are accounted for.
- Follow the guidelines of *The Design and Simulation of an Inverter* to create layout for the 2:1 mux. **The only structures that you may use in the 2:1 mux are the cells created earlier in this CAD assignment and metal1, metal2, metal3, or polysilicon to connect those cells.** Make sure that you use the same names to label the inputs and outputs of the 2:1 mux in *VLE* that are used on the symbol. Also try to minimize your use of upper metal layers.
- Perform a Design Rules Check (**DRC**) on the layouts of the 2:1 mux, saving the DRC reports.

- Perform a Layout Versus Schematic (**LVS**) on the layout of the 2:1 mux, again, saving the report.
- Extract the capacitance values from the 2:1 mux. For directions, please refer to *The Design and Simulation of an Inverter*.
- Use HSpiceS to simulate the circuit in the spice domain. Refer to the inverter tutorial for details as to how to use it. Prior to doing this, set the output capacitance to 25fF to represent the load on the mux.

Requirements

For the first CAD experiment, you need to have the following files in the directory **cad1**:

- inverter, 2-input nand and 2:1 mux schematics and layouts.
- Waveform files for all NC Verilog simulations. (All three circuits)
- Wave .png of the critical path waveforms generated by HSpice.
- LVS report for the inverter, 2-input nand, and 2:1 mux.
- Include a README file containing the full path names for all of the cells the grader is to look at, and any comments you wish to pass on to the grader. Include in the file the maximum rise and fall times. List the nodes between which the rise and fall delays were maximum, what that delay was, and explain why that path was the maximum. Provide a brief paragraph describing any relevant points in your design. Any comments will be taken into consideration when your assignments are graded.

For this and future cad assignments, follow these submission guidelines:

- Call the README file README (not readme, readthis, info, cad1_readme, etc.)
- lvs reports: lvs_<component_name>.rep
- spice waveforms: spice_<component_name>_<description>.png Where <description> is a brief description of the measurement (e.g. falltime, risetime, falldelay, risedelay)
- NC verilog waveforms: nc_<component_name>.ps. Make sure this waveform shows proper digital functionality of your design and explain in the readme why this input set was sufficient i.e. covered all possible input combinations exhaustively.

Deadline

You have to complete the first CAD assignment by **Friday, Jan 12, 2007, 7pm.**