EECS 427 Lecture 11: Shifters / CAD5 Reading: 11.5

Shift types

- Logical
 - Shift in 0s
 - left shifts pretty much always logical
 - Left shift is multiplication by 2ⁿ
- Rotate
 - Useful in some coding and crypto applications
 - Shift in the bits that were shifted out
 - Data preserving
 - Shifts can be rotates followed by bitwise mask

More shift types

- Arithmetic
 - Shift "in" the high bit
 - Sometimes use the carry control bit instead
 - Useful for lots of things besides the obvious divide by 2ⁿ (and round down)
 - In particular, conditional generation of masks based on sign of value
 - Absolute value:
 - rb = ra sra ra 15
 - ra = ra xor rb
 - ra = ra rb

Shift Examples

- Arithmetic vs. logical shift (Start with 1101)
 - Logical shift (baseline op for us)
 - Logical shift right by 1: 0110 _ Shift in 0s for logical
 - Logical shift right by 2: 0011 \int right shifts
 - Logical shift left by 1: 1010
 - \succ Shift in 0s for left shifts
 - Logical shift left by 2: 0100 \int
 - Arithmetic shift (not baseline)
 - Arithmetic left shifts same as logical
 - Arithmetic right shift by 1: 1110 \carcol Repeat sign of MSB for
 - Arithmetic right shift by 2: 1111 \int arithmetic right shifts

Barrel Shifter



4x4 barrel shifter



Barrel Considerations

- Buffer should really have weak feedback (for full swing)
- Shown choices for horiz / diagonal / vertical lines not the only ones
- How to implement shifts in both directions?
 - This turns out to be nice for barrel because one direction only requires a triangle, and the two triangles can be fit together to form a square
- Fast for A through, but B goes through decoder
- Size becomes a problem at more bits

The Binary Shifter Concept



Logarithmic Shifter



0-7 bit Logarithmic Shifter



Log Shifter Considerations

- Wiring pattern looks very similar to koggestone adder
- No decoding needed
- How to handle both directions?
 - Use binary shifters with connections in both directions?
 - Some way to avoid that?
- How to implement those small muxes?
 - Use pass transistors like barrel shifter?

Other Spins on Shifters

- Log₄ instead of log₂ (cross between barrel / log)
 - Advantage: Fewer stages of pass transistors
 - Disadvantage: must re-encode the control bits
 - Ex: 16 bits \rightarrow 4 stages for log₂ vs. only 2 stages for log₄
- Rotate instruction could be an ISA addition
 - 11010101 → rotate right by 5 bits → 10101110
 - Both shift directions can be rotations with appropriate masking
- Reverse order shifters do the big shifts first
 - Helpful because the big shifts have larger wire capacitances
 - Elmore delay is reduced by having large caps charged through the least resistance (fewest pass transistors)

CAD5

- Logical "left shift" is only required instruction
- Shift amount could be negative though which means right shift is hidden in there too.
- Log shifter is harder. Much less uniform, and shifting in both directions is hard
- Size should be dominated by wiring, and will "want" to be narrower than your bitslice width.
- Don't give in! Keep to your bitslice width.

Shifter Summary

Barrel shifters are area-intensive (though at 16 bits are probably no bigger) but have only 1 pass transistor per path

- Lots of junction capacitance though

- Log shifters are more versatile for wider data
- Lots of variations: log base, reverse order, pass transistor vs. T-gate
- Don't forget data dependent shifts and dealing with shifts in both directions