

# EECS 427

## VLSI Design 1

Lecture 12: Power Supply  
(This lecture is mostly derived  
from EECS 627 slides)


# Outline

- Power supply
- Packaging
- Power grid
- Package
- On-chip decoupling capacitors
- Transient analysis
- Movies

# Power supply


- Goal:
  - Supply a constant voltage (temporal/spatial) to all devices on chip
- Problem:
  - Must get current from voltage regulator to chip
- Supply system does not start from chip pins but includes board
- Supply network design is very difficult, even though small number of transistors

# From the regulator to the chip

 

## C4: Controlled Collapsed Chip Connects

# Supply network model

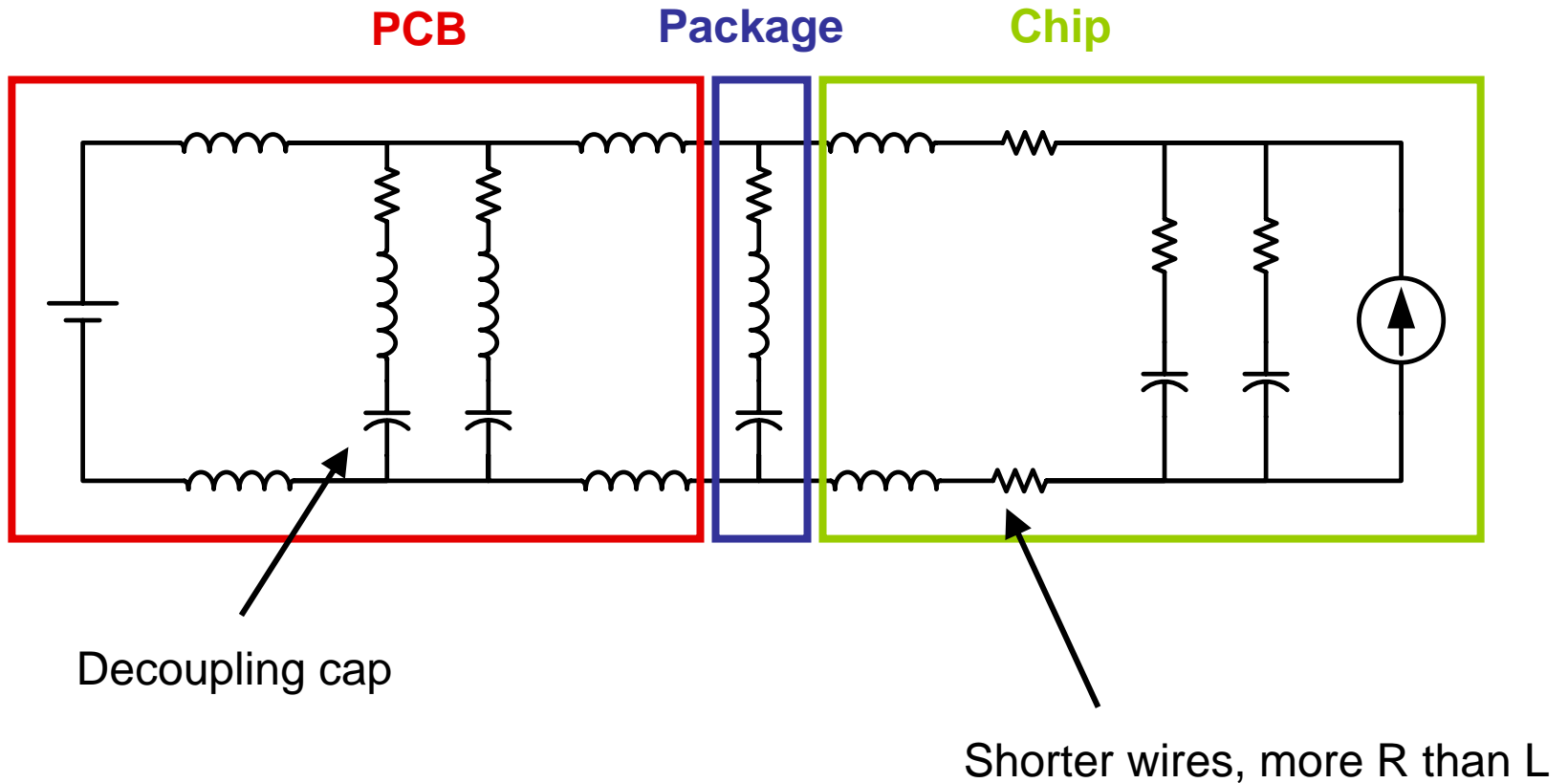

# Voltage drop (1/2)

- IR drop  $\Delta V_{IR} = IR$ 
  - Max at peak current
  - Scaling of  $I_{dc}$ 

$P \uparrow$      $V \downarrow$      $I \uparrow \uparrow$

•  $P=15W$      $V_{dd}=2.5V$

•  $P=150W$  (10x)     $V_{dd}=1.25V$  (0.5x)

}

$\Delta I = \frac{\Delta P}{\Delta V} = 20x$
- Ldi/dt drop  $\Delta V_L = L \frac{dI}{dt}$ 
  - Due to change in current
  - Scaling of  $V_{ac}$ 

$dI \uparrow$      $dt \downarrow$      $dI/dt \uparrow \uparrow \uparrow$

•  $f=200MHz$


•  $f=1GHz$  (5x)

}

$\Delta I = 7x$      $\Delta V_L = 35x$
 
# Voltage drop (2/2)

- Time of drop is different. Do not strictly add




- Pulsed noise
- DC noise (sustained)
- under/over shoot
- Supply variation both:
  - Time (temporal)
  - Area (spatial)

# Problems due to power grid noise (1/3)

- Sustained drop: Performance degradation

$$t_d \propto \frac{CV}{I} \propto \frac{1}{V_{gs} - V_t} \propto \frac{1}{V_{dd} - V_{ss} - V_t} \quad \Delta V \uparrow \rightarrow t_d \uparrow$$

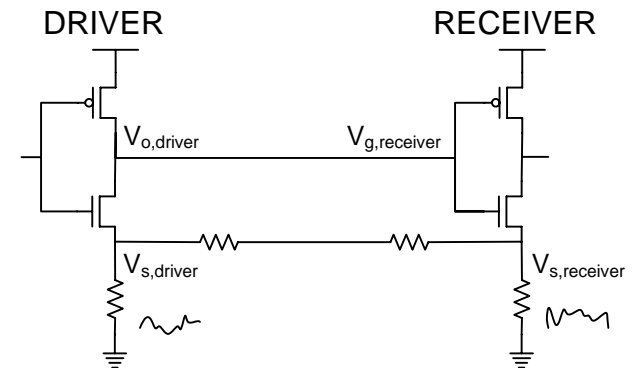- AC Noise: Functional/delay noise
  - Acts as standard noise pulse
  - Difference not absolute voltage drop
  - Uniform drop is OK







# Problems due to power grid noise (2/3)

- TDDDB: Time Dependent Dielectric Breakdown
  - Due to overshoots (inductance)
  - Hot electrons cause injection into gate oxide, may get trapped → degrade the performance of the transistor
  - Limit on  $V_{dd}$
- Electromigration
  - High current densities displace metal atoms out of place due to momentum transfer.

# Elements of power supply system - Outline


- Board
- Package
- Chip
  - Power grid
  - Decoupling cap

# Board design (1/3)


 
 


$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$\omega_r = \sqrt{\frac{1}{LC}}$$

 

# Board design (2/3)

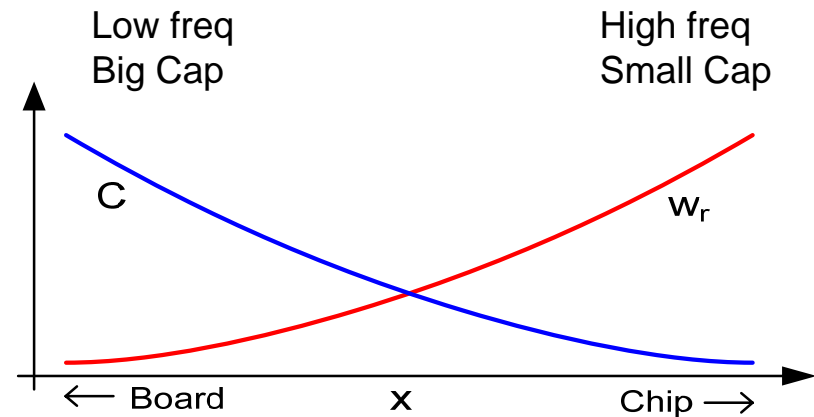  

# Board design (3/3)

- Make sure resistance is small
- Decap design: act to filter high frequency current
  - Small cap w/low  $L \rightarrow$  near chip to suppress high frequency current
    - Try to get as close to chip as possible
  - Large cap w/higher  $L \rightarrow$  further away from chip

# Package types (1/2)

- Wire bonding
  - Advantages:
    - Cheap
    - Allows for thermal expansion
  - Disadvantages:
    - High inductance (typical 5nH)
    - Limited pads (~200)
  - To reduce R → More metal layers
  - To reduce L → Lower distance from connections, bring cap closer

 


FIGURE 2-8 Typical Type-II BGA Construction

# Package types (2/2)

- Flip-chip
  - Advantages:
    - Lower inductance ( $0.1\text{nH}$ )  $\rightarrow$  lower distance
    - High number of pads ( $\sim 1000$ )


 


FIGURE 2-3 Flip-Chip Bonding


# On-Chip Power Delivery

 



 
# Power Integrity & Package

- Package design becoming increasingly complicated
- Large number of power/ground layers in current packages
- Significant Power supply variations caused by the package



 
# Power Grid design (1/2)

- Tree
  - Local grids
  - Simple
  - Metal utilization is efficient
  - Single wire failure



 
# Power Grid design (2/2)

- Grid
  - High end processor
  - Lots of metal
  - Lower resistance
  - Lines up with C4
  - Less J, better electromigration
  - Spatial variation is lower
  - Highly redundant



# Decoupling cap – Implicit (2/3)

 

$$C_{eff} = \frac{1}{2} (C_{db,N} + C_{gs,N} + C_{db,P} + C_{gs,P}) + \frac{1}{2} (C_{i,gnd} + C_{i,Vdd}) + C_{gd,N} + C_{gd,P}$$

- Depends on state of circuit
- Current injected/extracted at different locations
- Includes both device and interconnect parasitics

# Decoupling cap – Back of the envelope (3/3)

- Implicit decoupling capacitance is the capacitance that is not switching
- Assuming a switching factor of  $s$

$$P = fC_{switch}V_{dd}^2$$


$$C_{switch} = \frac{P}{fV_{dd}^2}$$

$$C_{switch} = sC_{total}$$


$$C_{decap} = (1-s)C_{total}$$

$$C_{decap} = \frac{1-s}{s} \frac{P}{fV_{dd}^2}$$

# Decoupling cap – explicit (1/3)

 


 - Reliability: Thin oxide gate can short. Yield problem
- High gate leakage




- Short only if double failure
- Gate voltage is half, less sensitive to gate failure
- Less cap

# Decoupling cap – explicit (2/3)


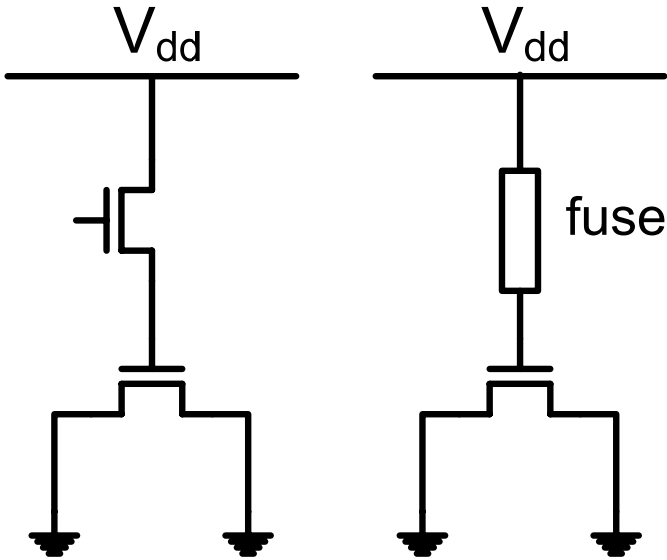


 - Turns off the cap in case of oxide failure
- Less gate leakage
- Unusable if the transistor fails



- Variation of previous

# Active decoupling cap – explicit (3/3)

  

Normal cap

$$\Delta Q = \Delta V \cdot C$$

This scheme

$$\text{Charge } Q = V_{dd} \cdot C$$

$$\text{Discharge } Q = \frac{C}{n} \cdot (V_{dd} - \Delta V)$$




$$\begin{aligned} \Delta Q &= V_{dd} \cdot C - \frac{C}{n} \cdot V_{dd} + \frac{C}{n} \cdot \Delta V \\ &= \frac{n-1}{n} C \cdot V_{dd} + \frac{C}{n} \cdot \Delta V \end{aligned}$$

For  $n=2$

$$\Delta Q = \frac{1}{2} C \cdot V_{dd} + \frac{C}{2} \cdot \Delta V$$




# Power grid model (1/3)

 

This figure does not seem correct
 
$$\Delta V(t) = IR + I \sqrt{\frac{L}{C}} e^{-\frac{R \cdot t}{2L}} \sin(\omega_r t - \theta)$$



$$\omega_r = \sqrt{\frac{1}{LC}}$$

# Power grid model (2/3)


IR-drop  $\Delta V_{IR} \propto I, R$

- Solved with more metal
- Spatial variation of voltage

Ldi/dt-drop  $\Delta V_L \propto I \sqrt{\frac{L}{C}}$

Damping  $\frac{R}{2L}$

 - Decoupling cap can only help with  $\sqrt{1/C}$
- Current step input
  - Out of reset
  - Instructions



# Power grid model (3/3)

Resonance  $\omega_r = \sqrt{\frac{1}{LC}}$

Quality factor  $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$

We do not want the system to resonate

10-15 years ago  $\omega_r > \omega_{clk}$


- Harmonics of the clock might hit  $\omega_r$
- Tune  $\omega_r$  to avoid clock harmonic

$$\omega_r \neq k\omega_{clk}$$

$k \rightarrow \text{harmonic}$

Today  $\omega_r < \omega_{clk}$

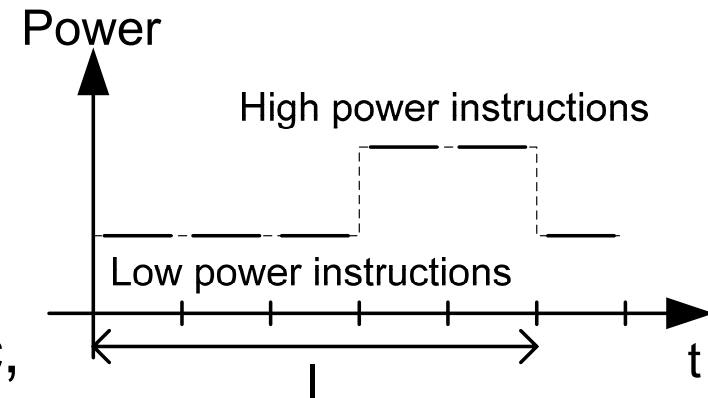- Due to circuit activity, activation frequency can be lower than  $\omega_{clk}$
- Cannot tune to avoid clock harmonic, depends on instruction stream



$$\omega_r \neq \frac{k\omega_{clk}}{l}$$

$k \rightarrow \text{harmonic}$   
 $l \rightarrow \text{loop}$

# How to fix

Reduce R: Use more metal. Tree  $\rightarrow$  Grid  $\rightarrow$  Plane

$\Delta V_{IR}$   $\downarrow$  but less damping  $Q$   $\uparrow$

Reduce L: Thin package, bondwire, flip-chip. More pads

$\Delta V_L$   $\downarrow$   $\omega_r$   $\uparrow$   $Q$   $\downarrow$  difficult to control

Increase C: Decoupling capacitance, but only  $\sqrt{C}$

$\Delta V_{IR}$   $\downarrow$   $\Delta V_L$   $\downarrow$   $Q$   $\downarrow$  Area  $\uparrow$

Decrease I: Turn modules slowly, larger reset latency

$\Delta I$   $\downarrow$   $\Delta V_{IR}$   $\downarrow$   $\Delta V_L$   $\downarrow$

# Transient Analysis Results

Design	Clk freq (MHz)	$w_r$ freq (MHz)	IR-drop (mV)	Undershoot (mV)	Overshoot (mV)
P1	200	120	101	183	100
P2	300	115	67	246	159
P3	500	90	150	345	199

- 👉 No significant increase in IR-drop as speed and power increase
- 👉 However, noise due to power transience is increasing rapidly
- 👉 Decrease in resonance frequency is of critical concern.