
EECS 427

Lecture 22: Low and Multiple-V_{dd} Design

Reading: 11.7.1

Last Time

- Low power ALUs
 - Glitch power
 - Clock gating
 - Bus recoding
- The low power design space
 - Dynamic vs static


Lecture Overview

- Low Vdd design
 - Pipelining
 - Parallel
- Multiple Vdd design
 - Concept
 - Level converter topologies
 - Dual-Vdd buffer design for global wires

Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Variable V_T	+ Variable V_T


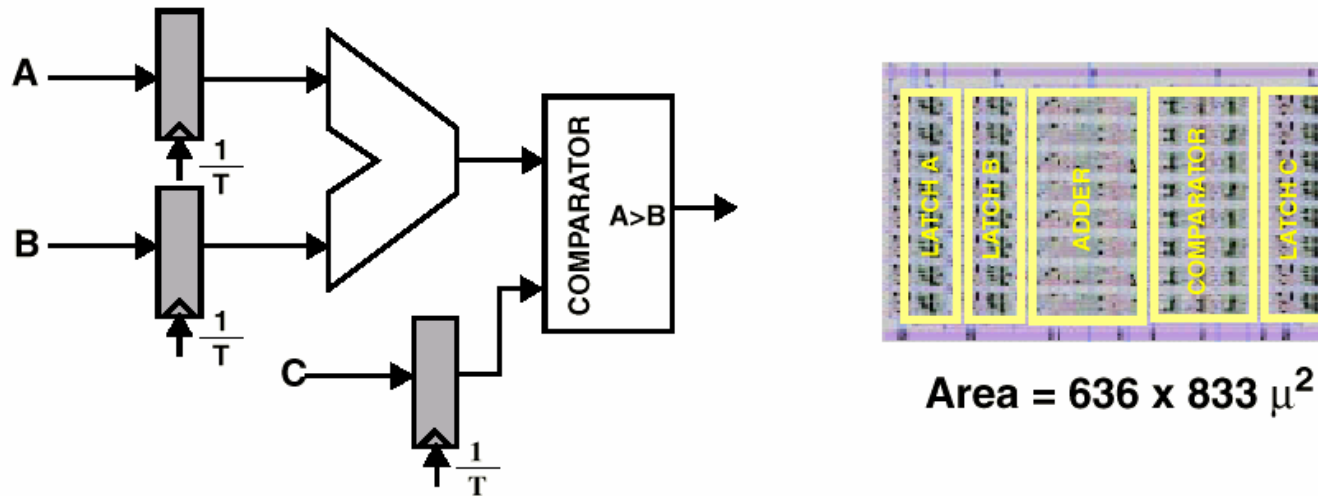
Architecture Tradeoff for Fixed-rate Processing Reference Datapath



- Critical path delay $\Rightarrow T_{\text{adder}} + T_{\text{comparator}} (= 25\text{ns})$
 $\Rightarrow f_{\text{ref}} = 40\text{Mhz}$
- Total capacitance being switched = C_{ref}
- $V_{\text{dd}} = V_{\text{ref}} = 5\text{V}$
- Power for reference datapath = $P_{\text{ref}} = C_{\text{ref}} V_{\text{ref}}^2 f_{\text{ref}}$

from [Chandrakasan92] (*IEEE JSSC*)



Parallel Datapath

  

$$\text{Area} = 1476 \times 1219 \mu^2$$

- The clock rate can be reduced by half with the same throughput $\Rightarrow f_{\text{par}} = f_{\text{ref}} / 2$
- $V_{\text{par}} = V_{\text{ref}} / 1.7$, $C_{\text{par}} = 2.15C_{\text{ref}}$
- $P_{\text{par}} = (2.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 (f_{\text{ref}}/2) \approx 0.36 P_{\text{ref}}$

Pipelined Datapath

  


Area = $640 \times 1081 \mu^2$

- Critical path delay is less $\Rightarrow \max [T_{\text{adder}}, T_{\text{comparator}}]$
- Keeping clock rate constant: $f_{\text{pipe}} = f_{\text{ref}}$
Voltage can be dropped $\Rightarrow V_{\text{pipe}} = V_{\text{ref}} / 1.7$
- Capacitance slightly higher: $C_{\text{pipe}} = 1.15 C_{\text{ref}}$
- $P_{\text{pipe}} = (1.15 C_{\text{ref}}) (V_{\text{ref}} / 1.7)^2 f_{\text{ref}} \approx 0.39 P_{\text{ref}}$

A Simple Datapath: Summary

Architecture type	Voltage	Area	Power
Simple datapath (no pipelining or parallelism)	5V	1	1
Pipelined datapath	2.9V	1.3	0.39
Parallel datapath	2.9V	3.4	0.36
Pipeline-Parallel	2.0V	3.7	0.2

How Low a Voltage can be Used?

 

- Capacitance overhead starts to dominate at “high” levels of parallelism and results in an optimum voltage


Power and Energy Design Space Revisited

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T

Supply Voltage Scaling

- How to maintain throughput under reduced supply?
- Introducing more parallelism/pipelining
 - Area increase – cost increases
 - Cost/power tradeoff
- **Multiple voltage domains**
 - Separate supply voltages for different blocks
 - Lower VDD for slower blocks
 - Cost of DC-DC converters or additional off-chip supplies, distributing multiple power supplies on-chip
- Dynamic voltage scaling – with variable throughput
- Reduce V_{th} to improve speed
 - Exponentially increased leakage eventually dominates

Delay as a Function of V_{DD}

 


$$T_d = \frac{C_L * V_{dd}}{I}$$

$$I \sim (V_{dd} - V_t)^{1.3}$$

$$\frac{T_d(V_{dd}=1.5)}{T_d(V_{dd}=2.5)} = \frac{(1.5) * (2.5 - 0.4)^{1.3}}{(2.5) * (1.5 - 0.4)^{1.3}}$$
$$\approx 1.4$$


- Decreasing V_{DD} reduces dynamic energy consumption quadratically
- But increases gate delay (decreases performance)
- Determine critical path(s) at **design time** & use high V_{DD} for transistors on those paths for speed. Use lower V_{DD} on other gates

CMOS Circuits Track Over V_{DD}

 

← Delay tracks within +/- 10% →


Changing V_{dd} and V_{th} Together

 

Contours of constant delay show that reductions in V_{th} must accompany smaller V_{dd} 's to maintain speed

Multiple V_{DD} Considerations


- How many V_{DD} ? – 2 is becoming more popular
 - Many chips already have 2 supplies (1 for core and 1 for I/O)
- When combining multiple supplies, **level converters** are required when a module at lower supply drives gate at higher supply (step-up)
 - If a gate supplied with V_{DDL} drives a gate at V_{DDH} , PMOS never turns off
 - Cross-coupled PMOS transistors perform the level conversion
 - NMOS transistors operate at reduced supply
 - Level converters are **not** needed for step-down changes in voltage

 

- Overhead of level converters can be reduced by converting at register boundaries & embedding level conversion inside the flop

Multiple Vdd Design


Conventional Design

 

Critical Path

CVS Structure

FF Level-converting F/F

 


Critical Path

Lower V_{DD} portion is shaded

“Clustered voltage scaling”


Level converting flip flops

 - Needed to restore the input to the next pipeline to V_H




Effect of CVS on path distribution

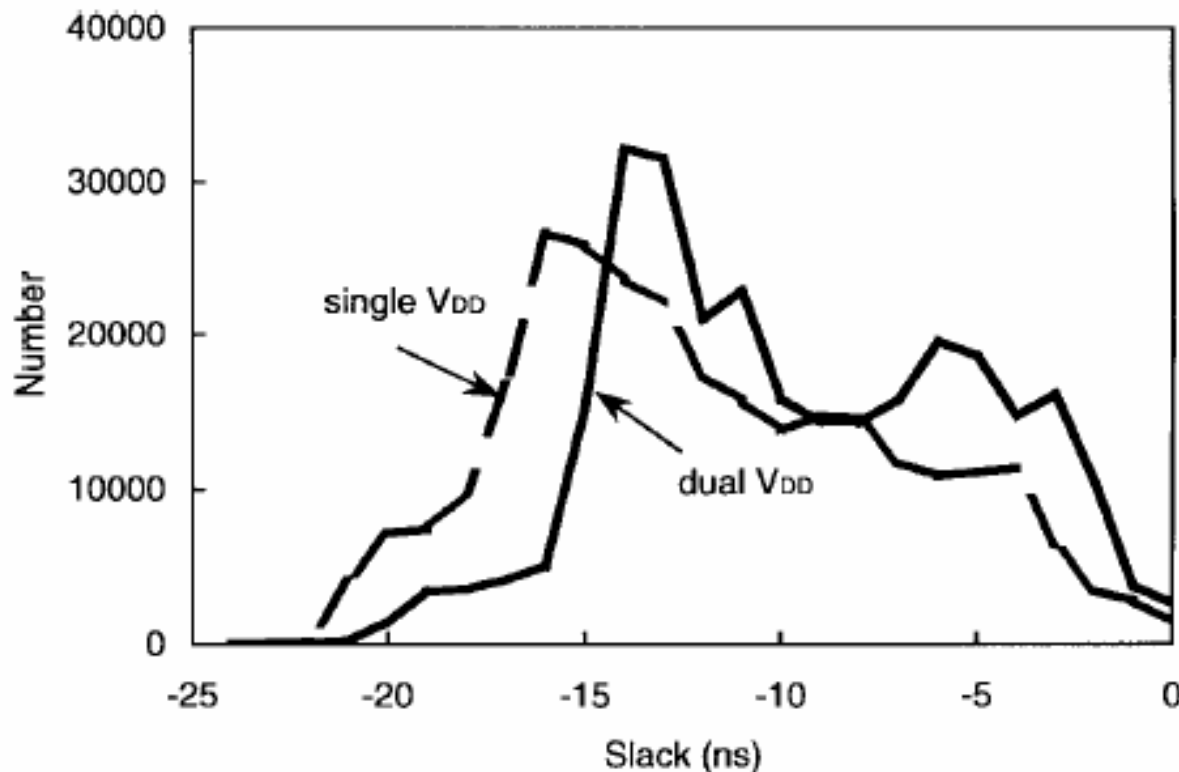- “Shift” the histogram towards the right




Delay Penalty

 - Significant delay penalty
 - Swing voltage unchanged (Linear effect)
 - Drive voltage shrinks (Quadratic effect)





Power dissipation dependence on V_L

 - Setting V_L too low results in less paths with low V_{dd} assignments




ECVS

  - No longer constrained to a monotonic voltage profile from input to output.
- Requires a level-converter to restore a higher voltage
 - Level converting buffers
 - Level converting gates
 - Level conversion is therefore not restricted to latches




ECVS allows more paths to be assigned to V_L

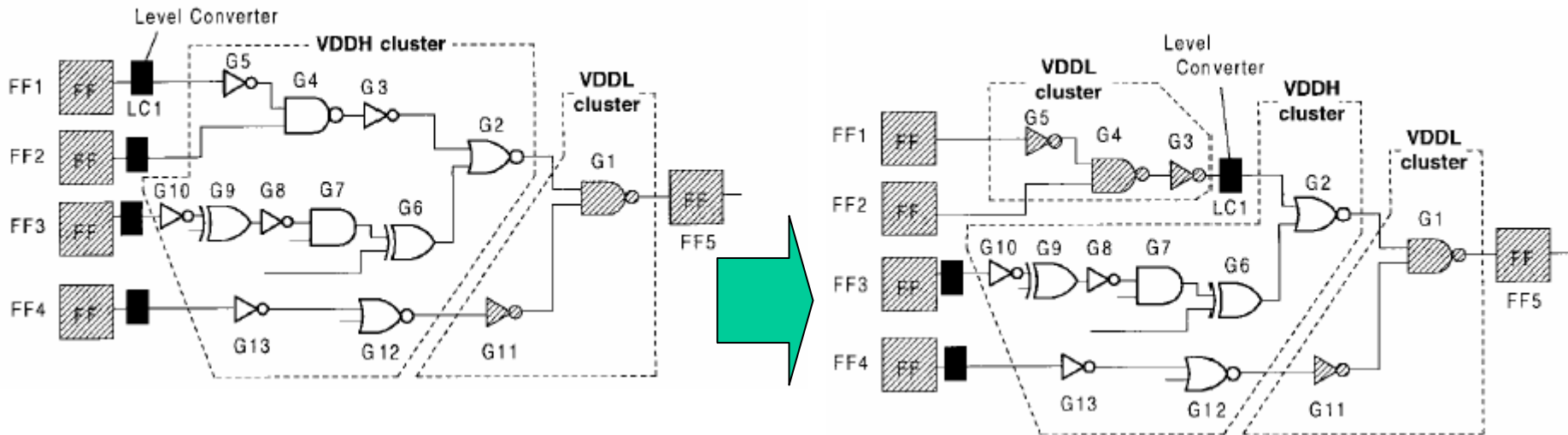- Allows delay balancing through voltage assignment
- Must pay delay and power penalty in performing every level conversion (Small clusters may not be worthwhile)
- Algorithms used for concurrent sizing-voltage assignment



Optimal choice for V_L

 
- The choice for V_L depends on the delay histogram with single V_{DD} .
- Choosing too large a V_L nullifies the effects of lower power dissipation.
- Choosing too low a V_L results in too few paths being assigned to V_L .



Existing Level Converters

- DCVS
- Pass gate (PG)


* = low- V_{th}
candidate

 

- DCVS – Higher power dissipation due to greater contention and higher transistor count
- PG – Simpler design, faster, lower power than DCVS, critical path is falling input (and output)
 - Key: Purpose of M1

Alternate LC 1 : STR1


- STR1

 


- Known high-performance design technique, with much improved results in this application space
- Keeper M4 from PG split into M4 and M5
- Reduced loading on node N and reduced contention

Alternate LCs : STR2, 3 and 4


- STR2

 

STR3

 

STR4

 


(d) STR 2: INVERTER INV FEEDS KEEPER (e) STR 3: NMOS M6 ADDED

(f) STR 4: COMBINED STR 2 & STR 3


- INV and M6 added to turn off feedback path faster and speed up critical path of the circuit

Alternate LC 5 : STR5

- STR5

 


(g) STR 5: GATE VOLTAGE OF M1 RAISED

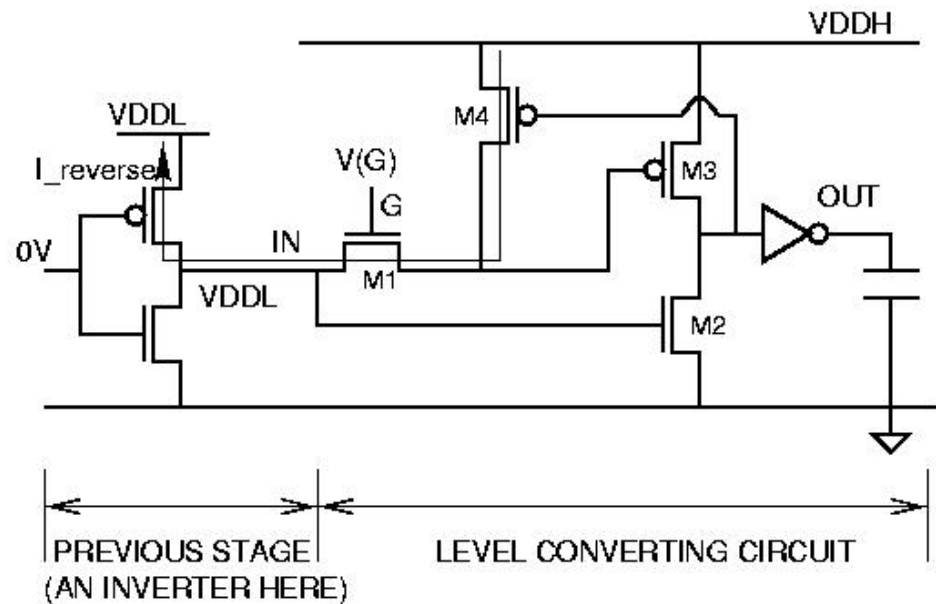

- Raised gate voltage on pass transistor boosts performance
- Leakage current I_{reverse} creates tradeoff between power and speed

Simulation Results

 - Low VDDL/High VTH
 - STR1,...,4 consume about 40-50% less energy
 - STR1 about 3-4% faster than DCVS and PG
 - STR2, 3 also slightly faster
- Low VDDL/Low VTH
 - STR1 consumes 37% and 15% lower energy than DCVS and PG respectively
- High VDDL
 - STR1 consumes 40% and 15% less energy than DCVS and PG respectively
 - STR1 and 4 faster than DCVS and PG



Summary

- Use of 2 Vdd's on a chip is growing
 - Brings up level conversion, layout, power distribution issues
- Fast, energy efficient level converter topologies are critical to maximize dual-Vdd benefit
- What else can you do with 2 supplies available?