


---

# EECS 427

## Lecture 8: Intro to adders

### Reading: 11.1 – 11.3.1


# Full Adder

 

$A$	$B$	$C_i$	$S$	$C_o$	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

# The Binary Adder

---

 

$$S = A \oplus B \oplus C_i$$

$$= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i$$

$$C_o = AB + BC_i + AC_i$$

# Express Sum and Carry as a function of P, G, D

---

Define 3 new variables which ONLY depend on A, B    WHY?

$$\text{Generate } (G) = AB$$

$$\text{Propagate } (P) = A \oplus B$$

$$\text{Delete} = \bar{A} \bar{B}$$


$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and  $C_o$  based on D and P

# The Ripple-Carry Adder

---

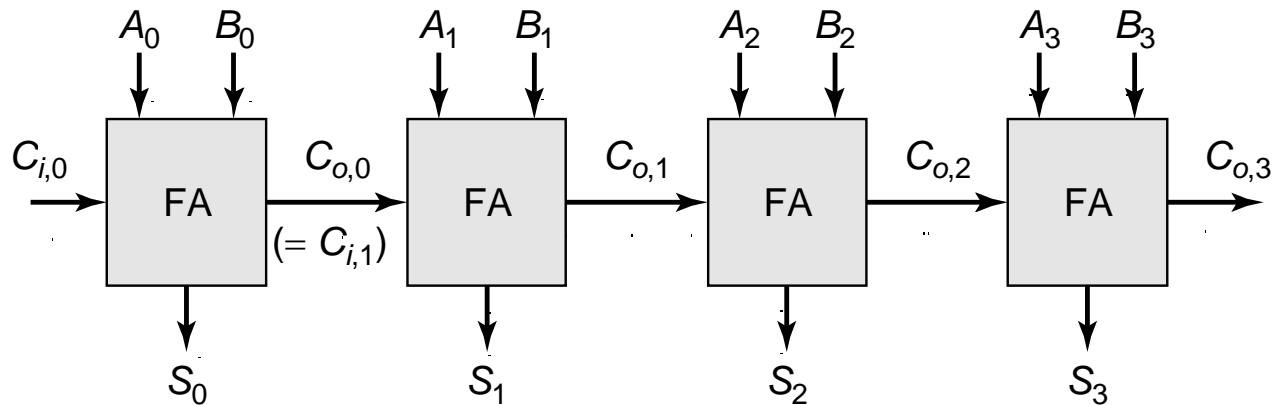


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{adder} = (N-1)t_{carry} + t_{sum}$$

**Goal: Make the fastest possible carry path circuit**


# Complementary Static CMOS Full Adder

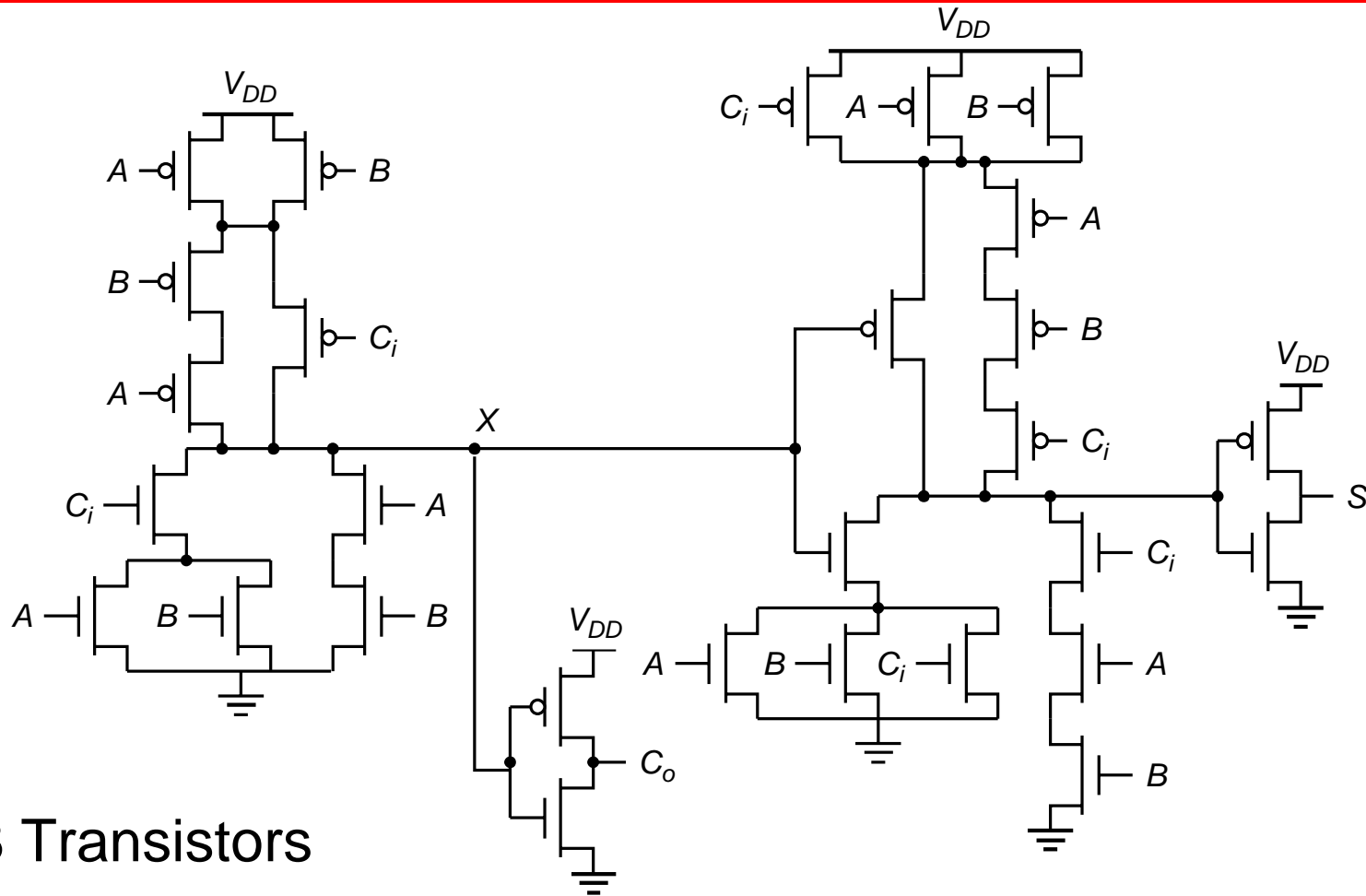

28 Transistors

# Inversion Property

---

 


$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

# Minimize Critical Path by Reducing Inverting Stages Along Carry Path

---

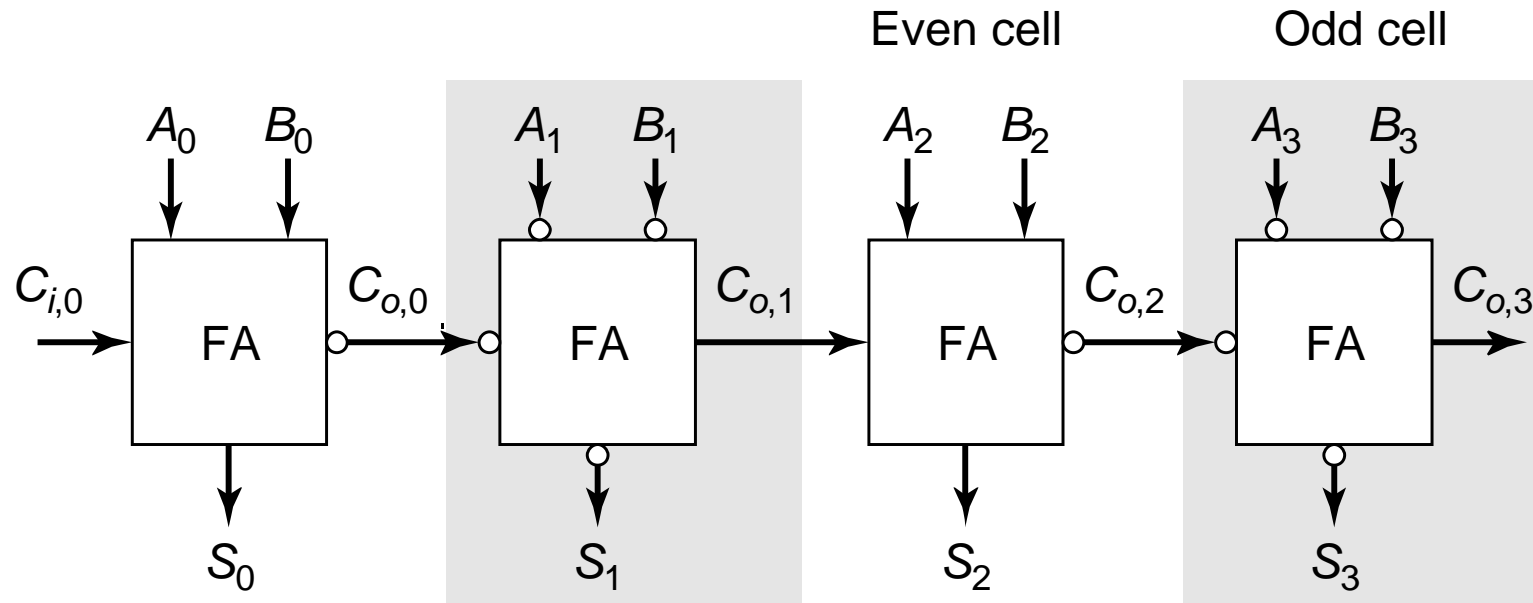


## Exploit Inversion Property


Allows us to remove inverter in carry chain  $\rightarrow$  at what cost?



# Example

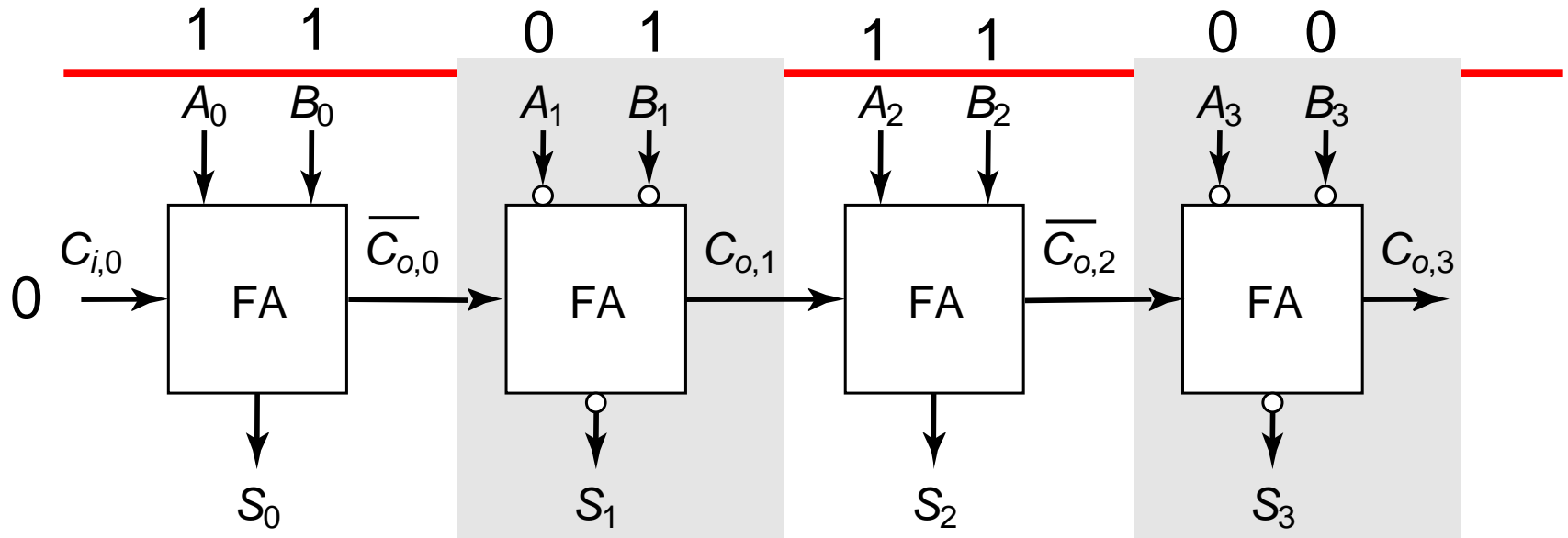

# A Better Structure: Mirror Adder

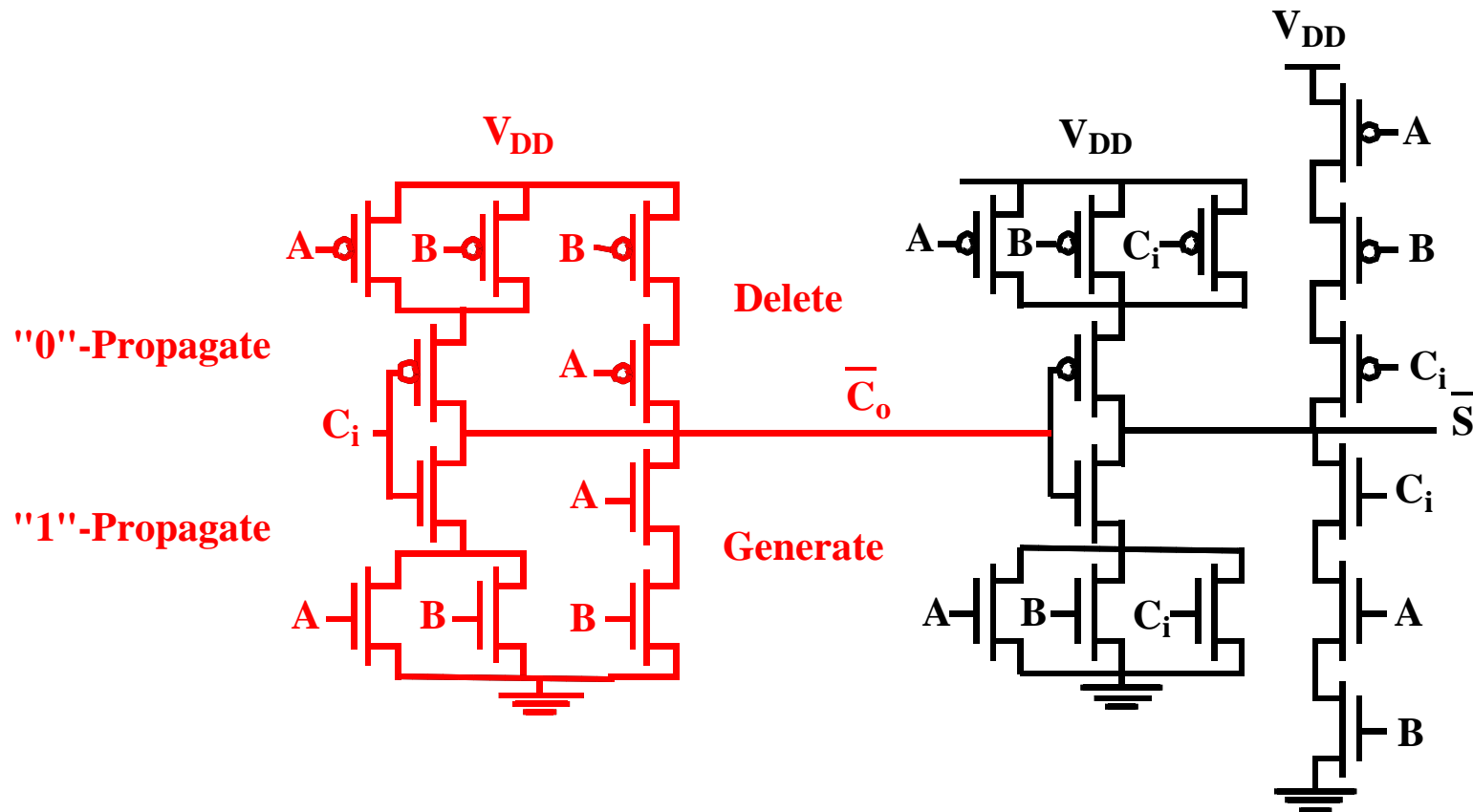

24 transistors


# Mirror Adder Details



---

- NMOS and PMOS chains are **completely symmetric**.  
Maximum of 2 series transistors in carry generation
- In layout → critical to minimize capacitance at node  $C_o$ .  
Reduction of junction capacitances is particularly important
- Capacitance at node  $C_o$  is composed of 4 junction capacitances, 2 internal gate capacitances, and 6 gate capacitances in connecting adder cell
- Transistors connected to  $C_i$  are closest to output
- Only optimize transistors in carry stage for speed  
Transistors in sum stage can be small

# Mirror Adder


Stick diagram of layout

 

 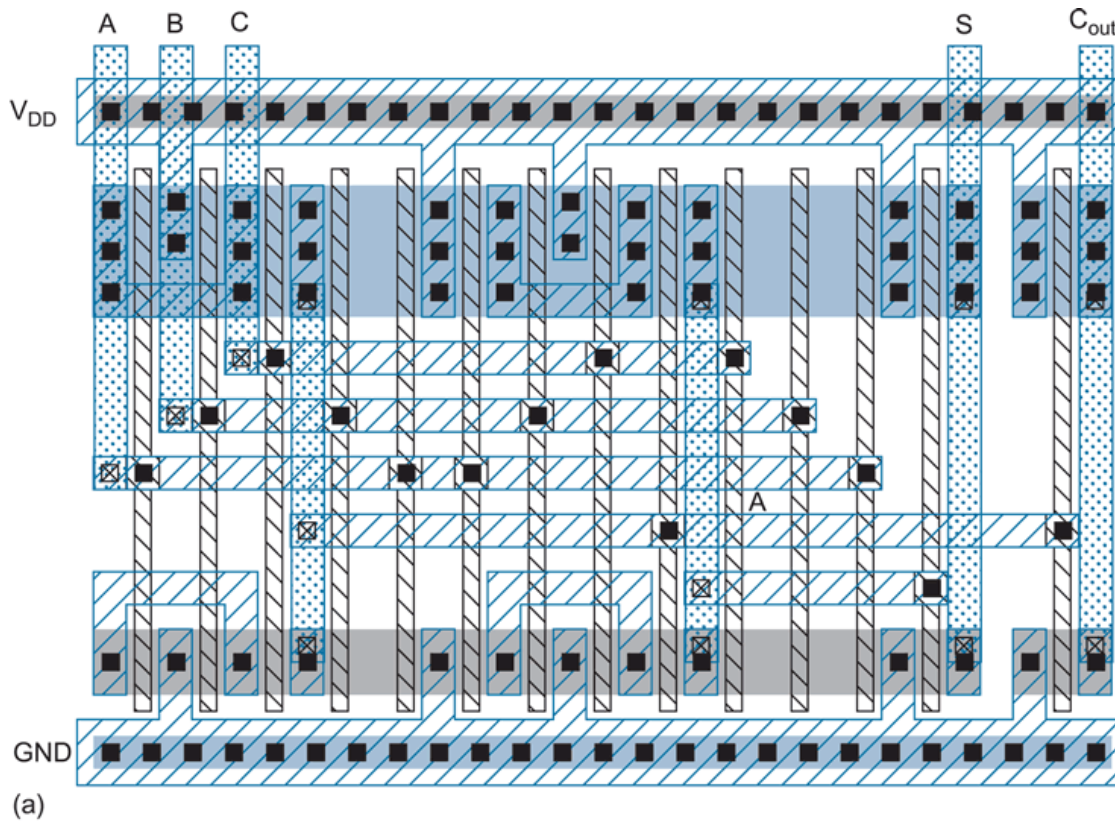

- 2 possible layouts of mirror adder
- (a) corresponds roughly to last slide's stick diagram
- Layout (b) is datapath-oriented (ex. M2 can easily run horizontally across cell)

# Sizing Mirror Adder

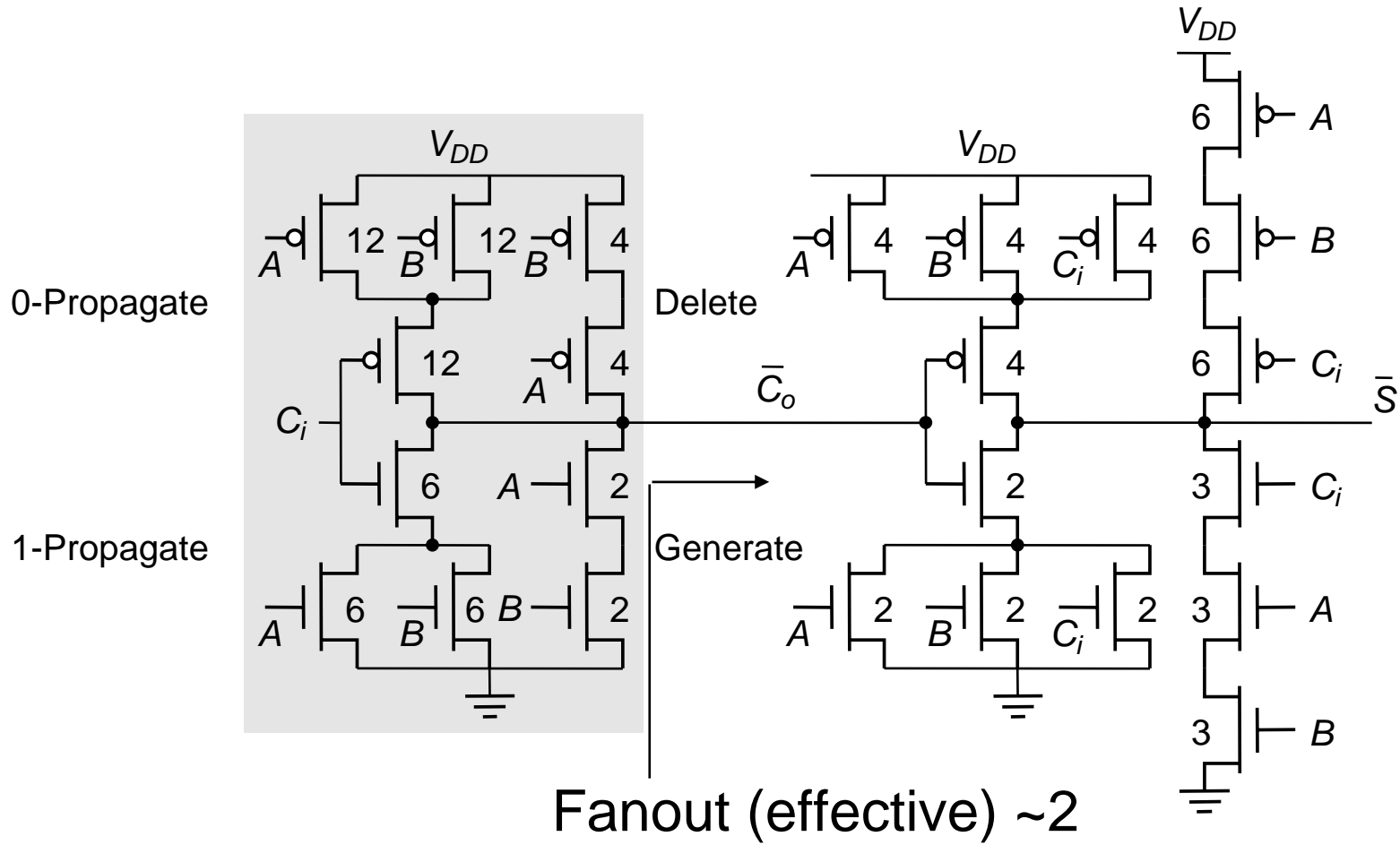

# Building from smaller gates


---

- Your ALU will need to do more than just add
- There are opportunities for sharing gates with other alu operations
- Do not feel the need to implement addition in giant monolithic gates with muxes. For example, what would mirror adder look like with P,G,D as inputs?
- XOR is the tough basic gate to make

# Transmission gate XOR


---

- Swap inverter to top for xnor gate

 




# Transmission Gate Full Adder

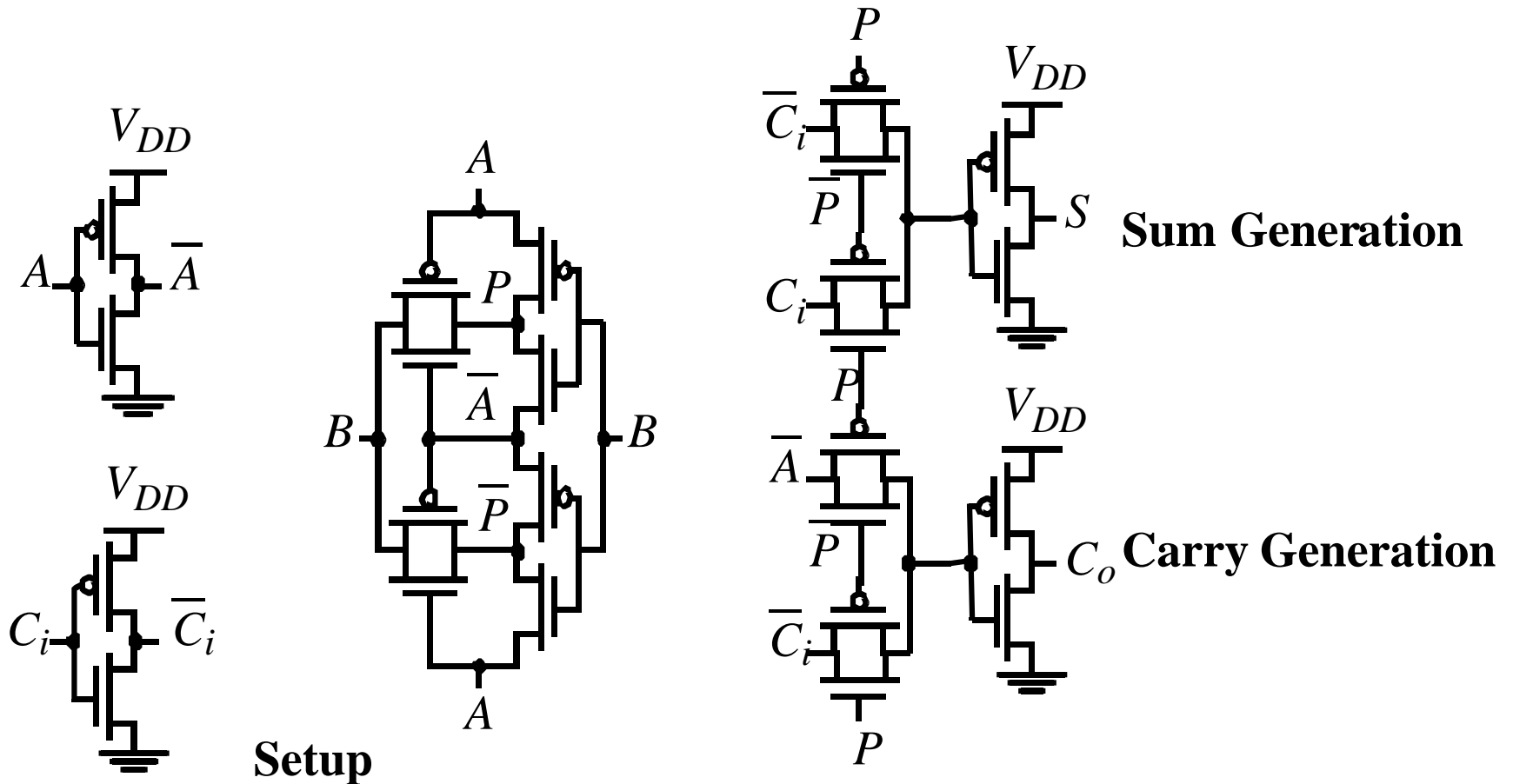


# Manchester Carry Chain

---

 


Static

 

Dynamic
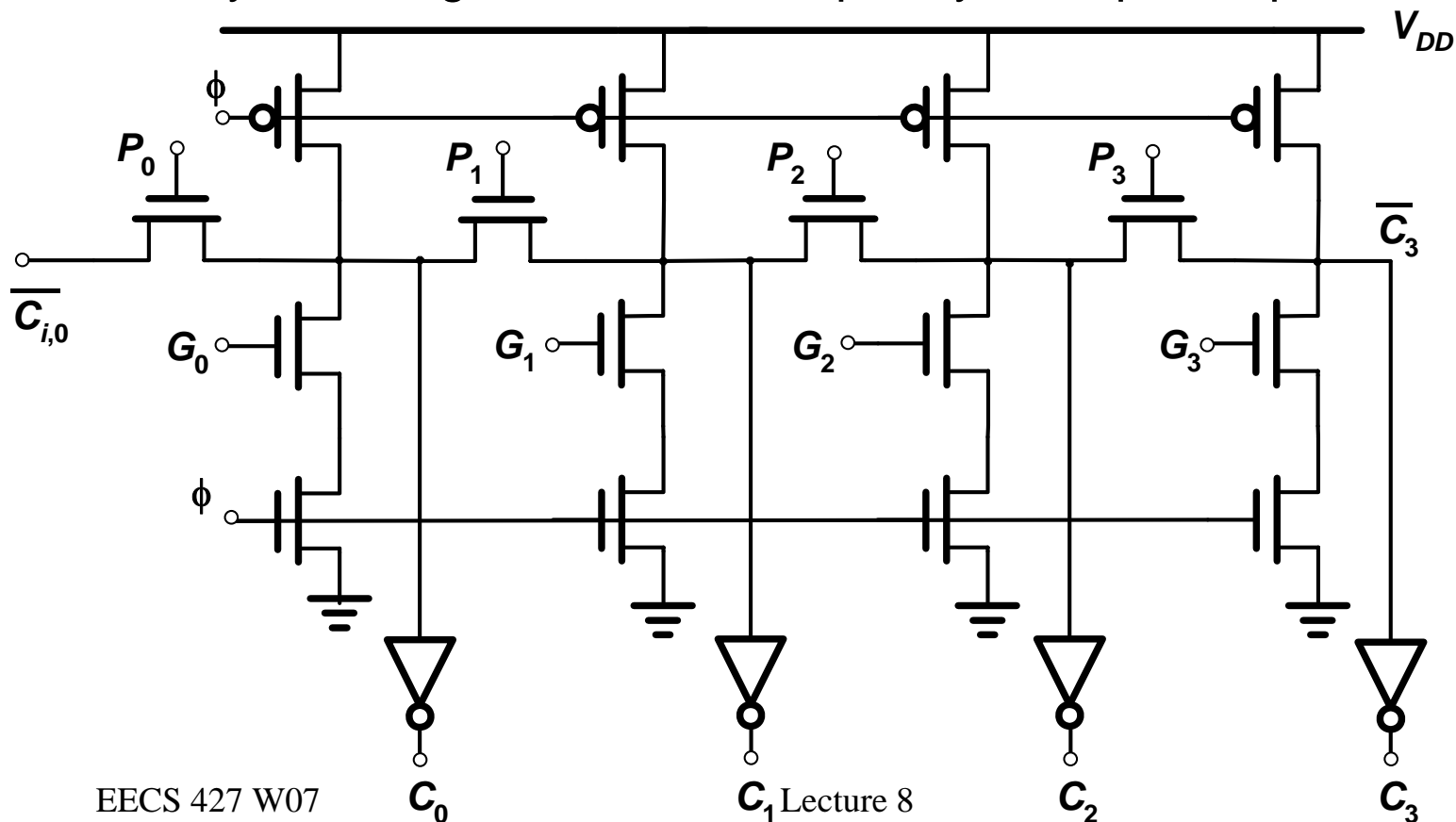
# Manchester Carry Chain

- Implement P with pass-transistors
- Implement G with pull-up OR kill (delete) with pull-down (note inversion)
- Use dynamic logic to reduce complexity and speed up




# Change the Topology

---


- Instead of speeding up carry chain, try to shorten it
- Topologies to discuss:
  - Carry bypass (skip)
  - Carry select
  - Carry lookahead
  - Log lookahead
    - Brent-kung
    - Kogge-stone

# Carry-Bypass Adder

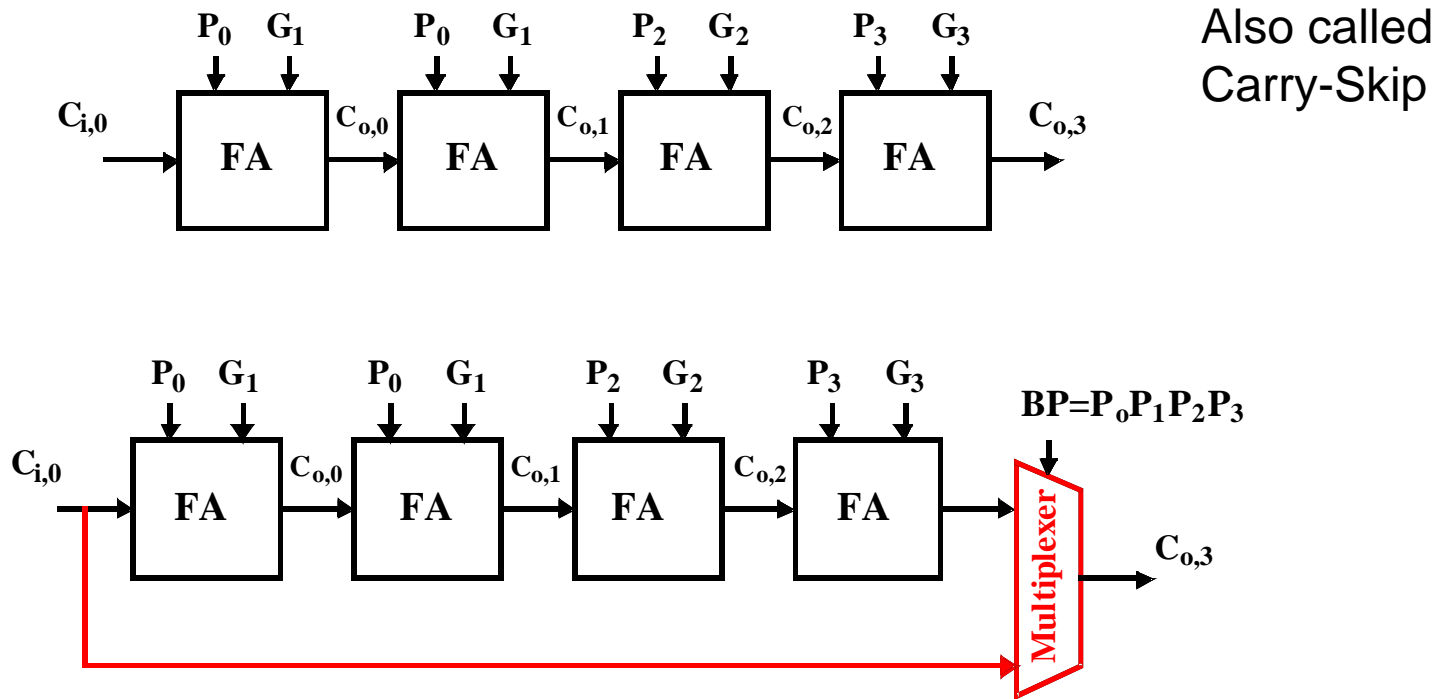

Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ )  
then  $C_{o3} = C_0$ , else “delete” or “generate”

# Carry-Bypass Adder (cont.)

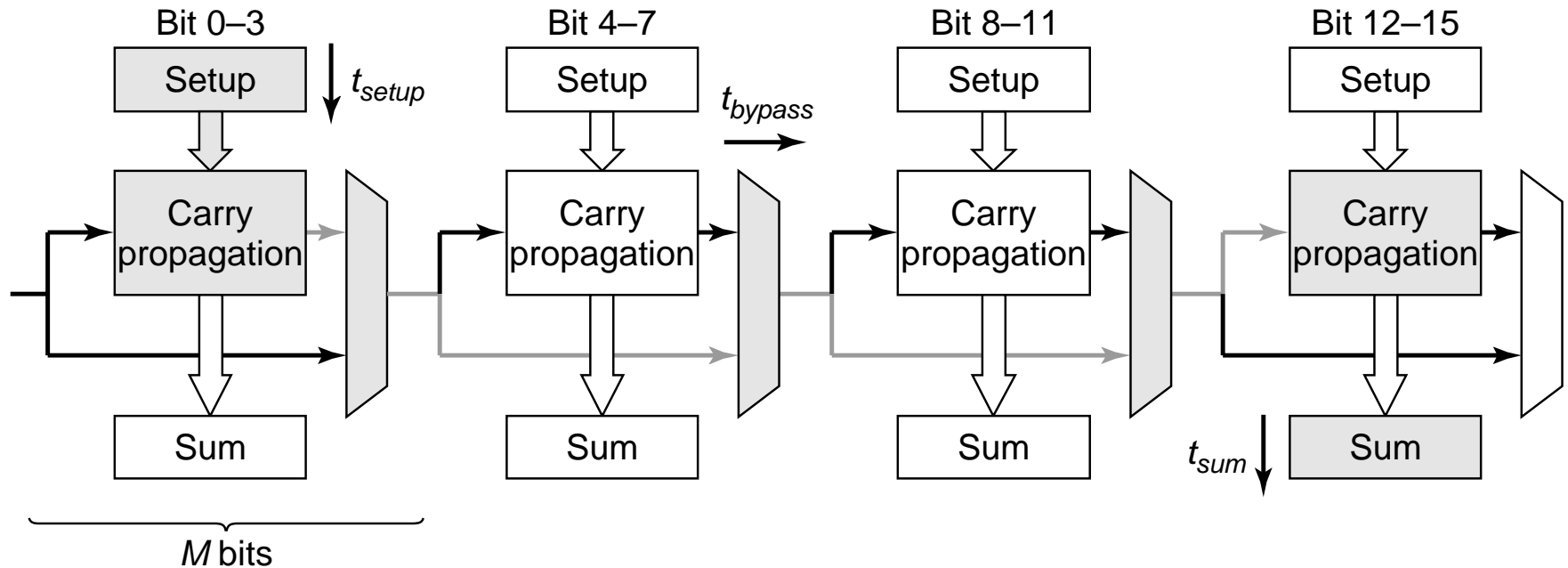

$$t_{adder} = t_{setup} + M t_{carry} + (N/M - 1) t_{bypass} + (M - 1) t_{carry} + t_{sum}$$

Inner blocks do not contribute to worst-case delay since they have time to compute while bits 0-3 are propagating (assuming they have a generate or delete)

Block sizes can be made non-uniform (HOW?)

# Carry Ripple versus Carry Bypass

---

