

Discussion 5

Wei-Hsiang Ma


2009/02/13

Today

- GSI's CAD1 / CAD2
- Synthesis Design Flow
- Verilog
- Tutorial 2 demo (page1 – page2)

GSI's CAD1

 - Tips:
 - Use “**OUTLINE**” layer to define the boundary
 - Make “**GRLOGIC**” fit the cell width
 - Overlap **VDD/VSS** labels
 - Do connections on the higher level
 - Use minimum width wire for connections
 - Area: 6um x 2.8 um




GSI's CAD2

- **Tips:**
 - Use M1 as much as possible (for cell level)
 - Use higher level metal for global signals (such as Reset)
 - Area: 12um x 3.6um



Synthesis Flow

 

add2.v

```
module add2 (Y, A, B);  
input [1:0] A, B;  
output [1:0] Y;  
  
assign Y[1:0] = A[1:0] + B[1:0];  
  
endmodule
```

Constrains:

```
set input delay  
set output delay  
set output load  
set clock period
```

Std Cells:

```
INVX1TR  
INVX2TR  
INVX3TR  
AND2X1TR  
AND2X2TR  
AND2X3TR  
OR2X1TR  
OR2X2TR  
OR2X3TR  
XOR2X1TR  
XOR2X2TR  
XOR2X3TR  
XOR3X1TR  
XOR3X2TR  
XOR3X3TR
```

add2.nl.v

```
module add2 (Y, A, B);  
input [1:0] A, B;  
output [1:0] Y;  
  
XORX2X1TR I1 (.Y(Y[0]), .A(A[0]), .B(B[0]));  
AND2X2TR I0 (.Y(C0), .A(A[0]), .B(B[0]));  
XOR3X2TR I2 (.Y(Y[1]), .A(A[1]), .B(B[1]), .C(C0));  
  
endmodule
```

- Synthesis tools will choose the size of the std cell according to the design constrains

Verilog (Sequential Logic)

<u>DFF without RESET</u>	<u>DFF with Sync RESET</u>	<u>DFF with Async RESET</u>
<pre>module DFF (Q, Q_b, D, CK); input D, CK; output Q, Q_b; reg Q, Q_b; always @(posedge CK) begin Q <= D; Q_b <= ~D; end endmodule</pre>	<pre>module DFF (Q, Q_b, D, CK, R); Input D, CK,R; output Q, Q_b; reg Q, Q_b; always @(posedge CK) begin If (R == 1'b0) begin Q <= 1'b0; Q_b <= 1'b1; end else begin Q <= D; Q_b <= ~D; end end endmodule</pre>	<pre>module DFF (Q, Q_b, D, CK, R); Input D, CK,R; output Q, Q_b; reg Q, Q_b; always @(posedge CK or negedge R) begin If (R == 1'b0) begin Q <= 1'b0; Q_b <= 1'b1; end else begin Q <= D; Q_b <= ~D; end end endmodule</pre>

- Declare Q, Q_b as register
- Use "<=" in always block

Verilog (Combinational Logic)

<u>Use Assign</u>	<u>Use Always block</u>
<pre>module mult (Y, A, B); input [1:0] A, B; output [3:0] Y; assign Y = A * B; endmodule</pre>	<pre>module mult (Y, A, B); input [1:0] A, B; output [3:0] Y; reg [3:0] Y; always@* begin Y = A * B; end endmodule</pre>

- Tips for using always block
 - Declare Y as register, even though it is not.
 - Use “= ” instead of “ <= ”

Verilog (Seq + Com Logic)

```
module mult (Y, A, B, CK);  
input [1:0] A, B;  
Input CK;  
output [3:0] Y;  
  
reg [3:0] Y;  
  
assign temp = A * B;  
  
always @(posedge CK)  
begin  
Y <= temp;  
end  
  
endmodule
```

How to verify your Verilog before synthesizing it ?

- Create “**functional**” view
- Paste your behavioral code into the “**functional**” view
- Create an empty “**schematic**” view
- When doing NCverilog simulation, choose “**functional**” instead of “**schematic**”
- Modify your testbench and simulate it

Demo

- Mult.v (behavioral verilog code)
- Behavioral simulation (NCVerilog)
- Mult.tcl (define general constrains)
- Timing.tcl (define clock constrains)
- Mult.nl.v (structural netlist)
- Mult.dc.rpt (read report)

What you should do after demo

- Go through the synthesis flow by yourself!