
EECS 427
Lecture 11: Shifters + Low-power
ALU intro
Reading: 11.5

1

Lecture Overview

- Shifters
- Low-power ALU intro
- CAD4 due Tues
- Quiz next Thurs in class
 - Example to be posted soon

2

Some Insights from ISSCC 2009

- Intel → first fully static datapath for a high performance part in >20 years on Nehalem
 - 8 cores, pairs of caches/cores can be deactivated if defects occur
 - Top-level metal is 7-8um thick for extremely low resistance
 - Significant error correction capabilities
- Micro fuel cell deposited on chip, 4x4mm
- Cyborg moth radio – UWB, piezoelectric energy scavenging

3

Last Time

- Multipliers
 - Made primarily of arrays of adders
 - Can be very slow, must be carefully optimized
- Modified Booth recoding → map multiplier to a smaller encoded version and reduce partial product count by 2X
 - 2s complement follows naturally


4

Shift Types

- Arithmetic vs. logical shift (start with 1101)
 - Logical shift (baseline op for us)
 - Logical shift right by 1: 0110 } Shift in 0s for logical right shifts
 - Logical shift right by 2: 0011 }
 - Logical shift left by 1: 1010 } Shift in 0s for left shifts
 - Logical shift left by 2: 0100 }
 - Arithmetic shift (not baseline)
 - Arithmetic left shifts same as logical
 - Arithmetic right shift by 1: 1110 } Repeat sign of MSB for arithmetic right shifts
 - Arithmetic right shift by 2: 1111 }


5

The Binary Shifter Concept

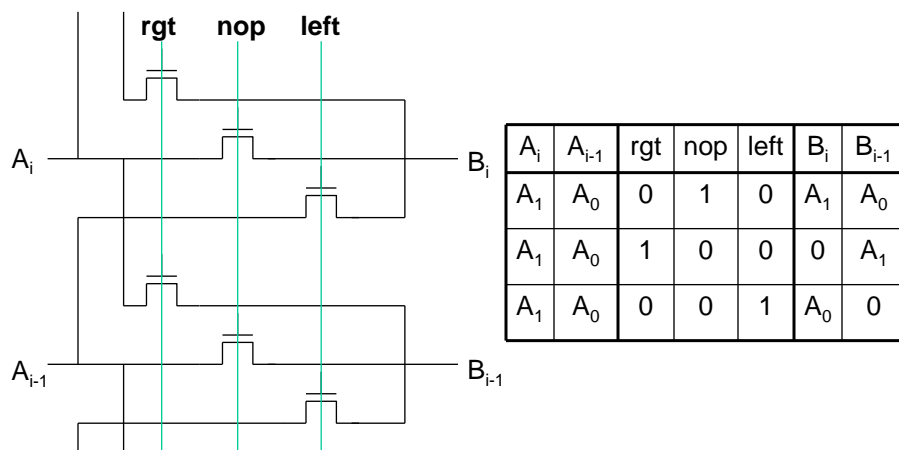

6
Thanks to: Irwin/Narayanan


Barrel Shifter

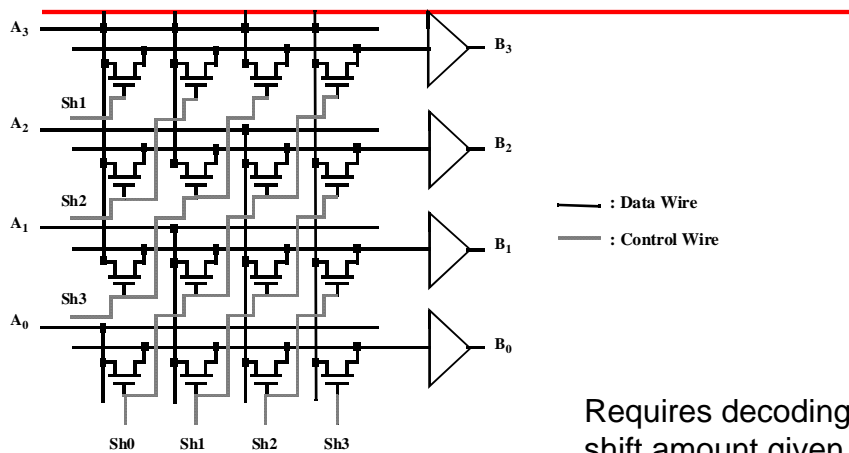

Area Dominated by Wiring

Requires decoding of shift amount given in instruction word

4x4 barrel shifter

 


Only 1 shift bit high at any time

$$\text{Width}_{\text{barrel}} \sim 2 p_m N$$


N is max shift width (15 for us), p_m is metal pitch

Logarithmic Shifter

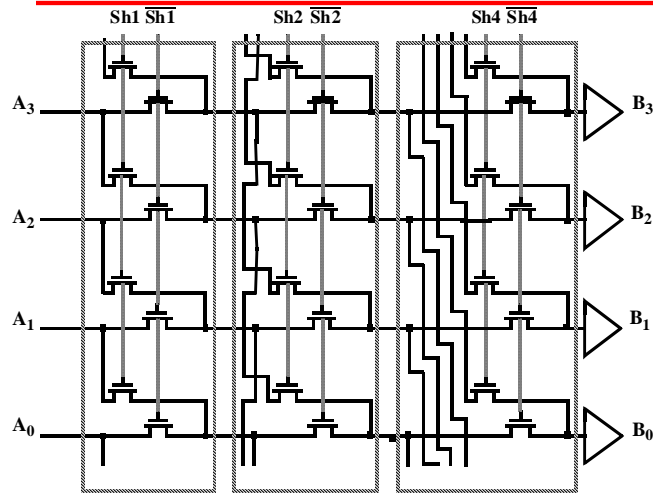

9

0-7 bit Logarithmic Shifter

 

$$width_{\log} \sim p_m (2K + (1 + 2 + \dots + 2^{K-1})) = p_m (2^K + 2K - 1)$$

$$K = \log_2 N$$

10

Other Spins on Logarithmic Shifters

- \log_4 instead of \log_2
 - Advantage: Fewer stages of pass transistors
 - Disadvantage: must re-encode the control bits
 - Ex: 16 bits \rightarrow 4 stages of pass transistors for \log_2 vs. only 2 stages for \log_4
- Can use CMOS transmission gates instead of NMOS pass transistors
- Rotate instruction – could be an ISA addition
 - 11010101 \rightarrow rotate right by 5 bits \rightarrow 10101110
- Reverse order shifters – do the big shifts first
 - Helpful because the big shifts have larger wire capacitances
 - Elmore delay is reduced by having large caps charged through the least resistance (fewest pass transistors)

11

Active Power Reduction


$$P \sim \alpha \cdot C_L \cdot V_{swing} \cdot V_{DD} \cdot f \quad E \sim \alpha \cdot C_L \cdot V_{swing} \cdot V_{DD}$$

- Reducing load capacitance
 - Technology scaling
 - Gate sizing, logic minimization, better placement tools
 - Logic families (pass transistor logic, ...)
- Reducing supply voltage
 - Quadratic impact on power
 - Impact on delay – how to maintain throughput?
- Reducing frequency – performance penalty
- Reducing switching probability (α)
 - Architecture
 - Glitching power reduction (15-20%)

12



Glitching in Static CMOS Networks

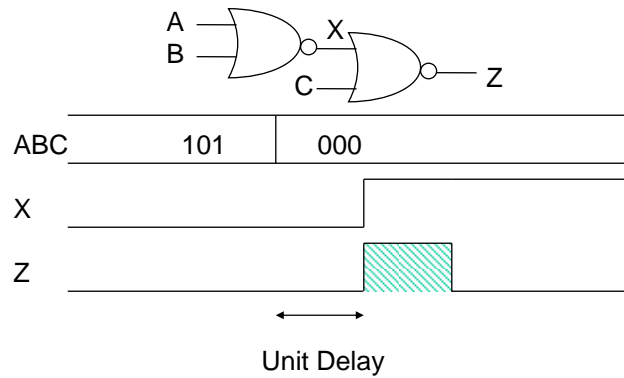- Gates have a nonzero propagation delay resulting in spurious transitions or **glitches** (hazards)
 - glitch: node exhibits multiple transitions in a single cycle before settling to the correct logic value



13


Glitching in a Ripple Carry Adder

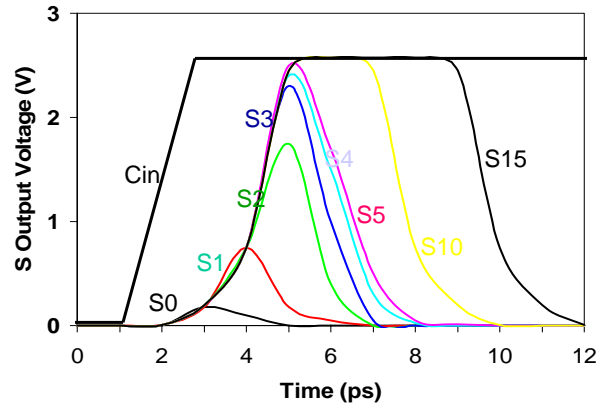 

14

Balanced Delay Paths to Reduce Glitching

 
- Glitching is due to mismatches in path lengths in a logic network
- If all input signals of a gate change simultaneously, no glitching occurs



Equalize the lengths of timing paths through logic

15

Circuit-Level Activity Encoding

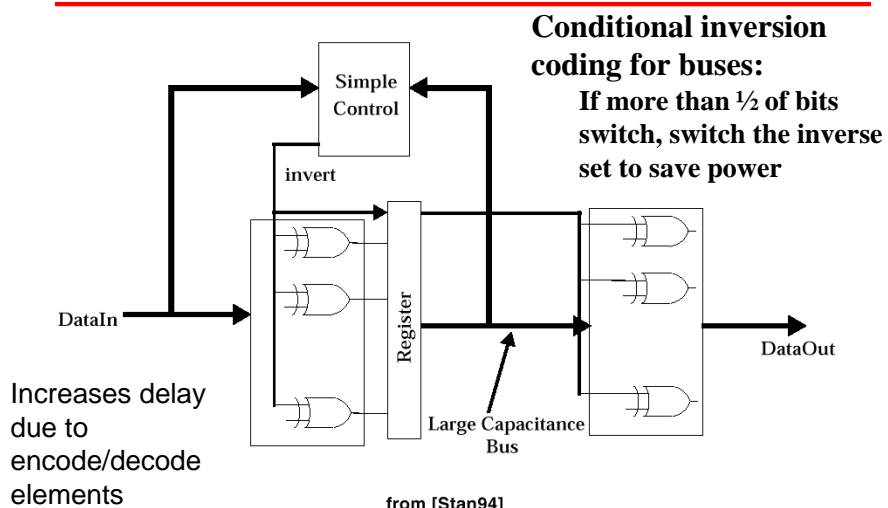


from [Stan94]
 (1994 International Workshop on Low-power Design)

16

Clock Gating

- Most popular method for power reduction of clock signals and functional units
- Turn off clock to idle functional units
 - Ex. floating point units
 - need logic to generate **disable** signal
 - increases complexity of control logic
 - consumes power
 - timing critical to avoid clock glitches at OR gate output
 - additional gate delay on clock signal
 - OR gate can replace a buffer in the clock distribution tree

 

Irwin/Narayanan 17

Summary

- Barrel shifters are area-intensive but have only 1 pass transistor per path
 - Lots of junction capacitance though
- Log shifters are more versatile for wider data
 - Various choices: log base, reverse order, pass transistor vs. T-gate, buffering
- Low-power design
 - Can focus on reducing any # of things from switching activity to cap to voltage
 - Extremely important today; everyone cares about power

18