

---

EECS 427  
Lecture 12: Low-power ALUs  
Reading: 11.7.1

1

## Lecture Overview

---

- Low power design
  - Parallel vs. pipelined datapaths for lower power
  - Multi-Vdd design
- Quiz in class on Thursday
  - Open notes/book

2

## Last Time

---

- Barrel shifters are area-intensive but have only 1 pass transistor per path
  - Lots of junction capacitance though
- Log shifters are more versatile for wider data
  - Various choices: log base, reverse order, pass transistor vs. T-gate, buffering
- Low-power design
  - Can focus on reducing any # of things from switching activity to cap to voltage
  - Extremely important today; everyone cares about power

3

## Active Power Reduction

---

$$P \sim \alpha \cdot C_L \cdot V_{swing} \cdot V_{DD} \cdot f \quad E \sim \alpha \cdot C_L \cdot V_{swing} \cdot V_{DD}$$

- Reducing load capacitance
  - Technology scaling
  - Gate sizing, logic minimization, better placement tools
  - Logic families (pass transistor logic, ...)
- Reducing supply voltage
  - Quadratic impact on power
  - Impact on delay – how to maintain throughput?
- Reducing frequency – performance penalty
- Reducing switching probability ( $\alpha$ )
  - Architecture
  - Glitching power reduction (15-20%)

4

## Two types of processing


---

- Fixed-rate processing (signal processing for multimedia or communications)
  - Stream-based computation
  - No advantage in obtaining throughput in excess of the real-time constraint
- Variable-rate or burst-mode computation (general purpose computation)
  - Mostly idle (or low-load) with bursts of computation
  - Faster is better

5

## Architecture Tradeoff for Fixed-rate Processing Reference Datapath

---

 


- Critical path delay  $\Rightarrow T_{\text{adder}} + T_{\text{comparator}} (= 25\text{ns})$   
 $\Rightarrow f_{\text{ref}} = 40\text{Mhz}$
- Total capacitance being switched =  $C_{\text{ref}}$
- $V_{\text{dd}} = V_{\text{ref}} = 5\text{V}$
- Power for reference datapath =  $P_{\text{ref}} = C_{\text{ref}} V_{\text{ref}}^2 f_{\text{ref}}$

from [Chandrakasan92] (IEEE JSSC)

6


## Parallel Datapath

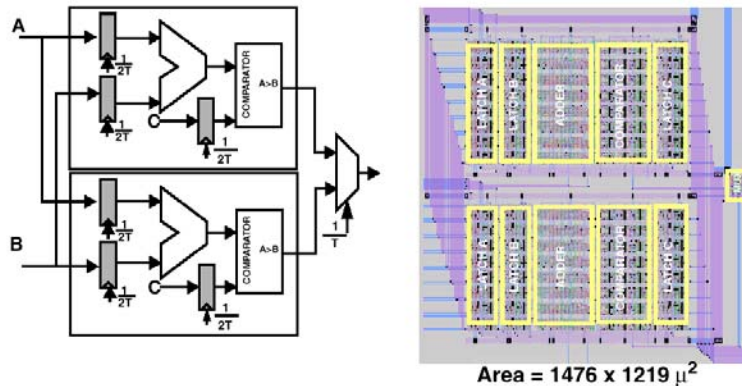

- The clock rate can be reduced by half with the same throughput  $\Rightarrow f_{\text{par}} = f_{\text{ref}} / 2$
- $V_{\text{par}} = V_{\text{ref}} / 1.7$ ,  $C_{\text{par}} = 2.15C_{\text{ref}}$
- $P_{\text{par}} = (2.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 (f_{\text{ref}}/2) \approx 0.36 P_{\text{ref}}$

7

## Pipelined Datapath

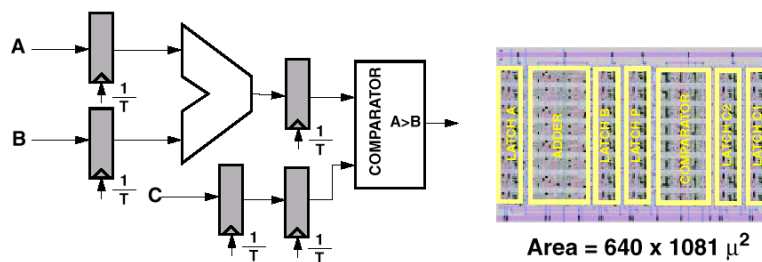

- Critical path delay is less  $\Rightarrow \max [T_{\text{adder}}, T_{\text{comparator}}]$
- Keeping clock rate constant:  $f_{\text{pipe}} = f_{\text{ref}}$   
Voltage can be dropped  $\Rightarrow V_{\text{pipe}} = V_{\text{ref}} / 1.7$
- Capacitance slightly higher:  $C_{\text{pipe}} = 1.15C_{\text{ref}}$
- $P_{\text{pipe}} = (1.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 f_{\text{ref}} \approx 0.39 P_{\text{ref}}$

## A Simple Datapath: Summary


---

Architecture type	Voltage	Area	Power
Simple datapath (no pipelining or parallelism)	5V	1	<b>1</b>
Pipelined datapath	2.9V	1.3	0.39
Parallel datapath	2.9V	3.4	0.36
Pipeline-Parallel	2.0V	3.7	<b>0.2</b>

9

## How Low a Voltage can be Used?

---

 

- Capacitance overhead starts to dominate at “high” levels of parallelism and results in an optimum voltage

10


## Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced $V_{dd}$ Sizing Multi- $V_{dd}$	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- $V_T$	Sleep Transistors Variable $V_T$	+ Variable $V_T$

## Supply Voltage Scaling

- How to maintain throughput under reduced supply?
- Introducing more parallelism/pipelining
  - Area increase – cost increases
  - Cost/power tradeoff
- **Multiple voltage domains**
  - Separate supply voltages for different blocks
  - Lower VDD for slower blocks
  - Cost of DC-DC converters or additional off-chip supplies, distributing multiple power supplies on-chip
- Dynamic voltage scaling – with variable throughput
- Reduce  $V_{th}$  to improve speed
  - Exponentially increased leakage eventually dominates

## Delay as a Function of $V_{DD}$

 


$$T_d = \frac{C_L * V_{dd}}{I}$$

$$I \sim (V_{dd} - V_t)^{1.3}$$

$$\frac{T_d(V_{dd}=1.5)}{T_d(V_{dd}=2.5)} = \frac{(1.5) * (2.5 - 0.4)^{1.3}}{(2.5) * (1.5 - 0.4)^{1.3}} \approx 1.4$$


- Decreasing  $V_{DD}$  reduces dynamic energy consumption quadratically
- But increases gate delay (decreases performance)
- Determine critical path(s) at **design time** & use high  $V_{DD}$  for transistors on those paths for speed. Use lower  $V_{DD}$  on other gates

## CMOS Circuits Track Over $V_{DD}$

 

← Delay tracks within +/- 10% →
 
## Changing $V_{dd}$ and $V_{th}$ Together




Contours of constant delay show that reductions in  $V_{th}$  must accompany smaller  $V_{dd}$ 's to maintain speed

15
 
## Multiple $V_{DD}$ Considerations

- How many  $V_{DD}$ ? – 2 is becoming more popular
  - Many chips already have 2 supplies (1 for core and 1 for I/O)
- When combining multiple supplies, **level converters** are required when a module at lower supply drives gate at higher supply (step-up)
  - If a gate supplied with  $V_{DDL}$  drives a gate at  $V_{DDH}$ , PMOS never turns off
    - Cross-coupled PMOS transistors perform the level conversion
    - NMOS transistors operate at reduced supply
  - Level converters are **not** needed for step-down changes in voltage




- Overhead of level converters can be reduced by converting at register boundaries & embedding level conversion inside the flop


Irwin/Narayanan 16

# Multiple Vdd Design

## Conventional Design

 

## CVS Structure

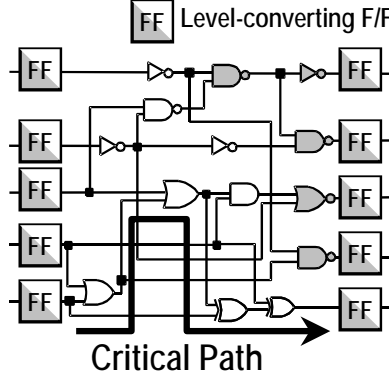

Lower  $V_{DD}$  portion is shaded  
 "Clustered voltage scaling"


M.Takahashi, ISSCC'98.

17

# Existing Level Converters

- DCVS (2 slides ago)
- Pass gate (PG)


\* = low- $V_{th}$   
 candidate

 

- DCVS – Higher power dissipation due to greater contention and higher transistor count
- PG – Simpler design, faster, lower power than DCVS, critical path is falling input (and output)
  - Key: Purpose of M1

18


## Alternate LC: STR1

 

- Known high-performance design technique, with much improved results in this application space
- Keeper M4 from PG split into M4 and M5
- Reduced loading on node N and reduced contention

19

## Alternate LC: STR5

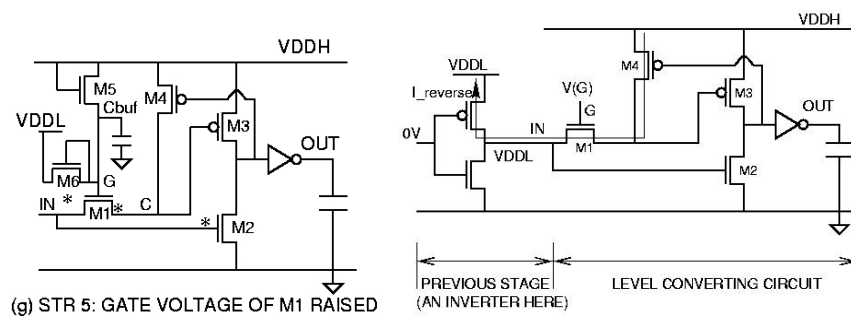


- Raised gate voltage on pass transistor boosts performance
- Leakage current  $I_{\text{reverse}}$  creates tradeoff between power and speed

20
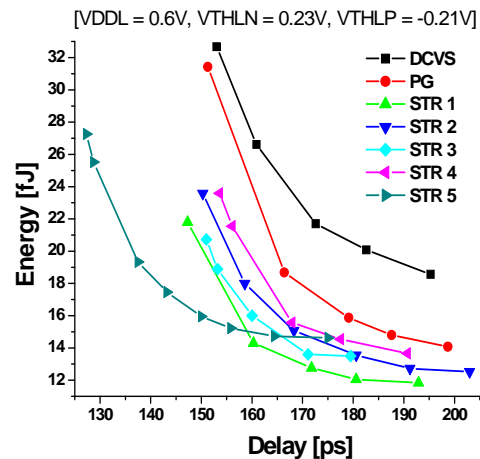
## Simulation Results

- STR1 consumes about 40-50% less energy
- STR1 about 3-4% faster than DCVS and PG
- STR5 best overall, especially at fast speeds
  - Gains diminish at low switching activities due to reverse leakage
- Overall: Delay of LCs is <2 F04 delays



21

## Summary

- If voltage is scalable, parallelism and pipelining are good levers to reduce dynamic power
  - For a fixed voltage, pipelining is *bad* for power though
- Multi-Vdd is a powerful knob to exploit path imbalances
  - Complicated: level conversion, layout, power distribution issues

22