
EECS 427
Lecture 17: Memory core and
peripherals
Reading: 12.1-12.3

1

Overview


- SRAM and DRAM basics
- Decoders
- Sense amplifiers
- Our focus is mainly on SRAM

- HW 4 due now

2

A Typical Memory Hierarchy

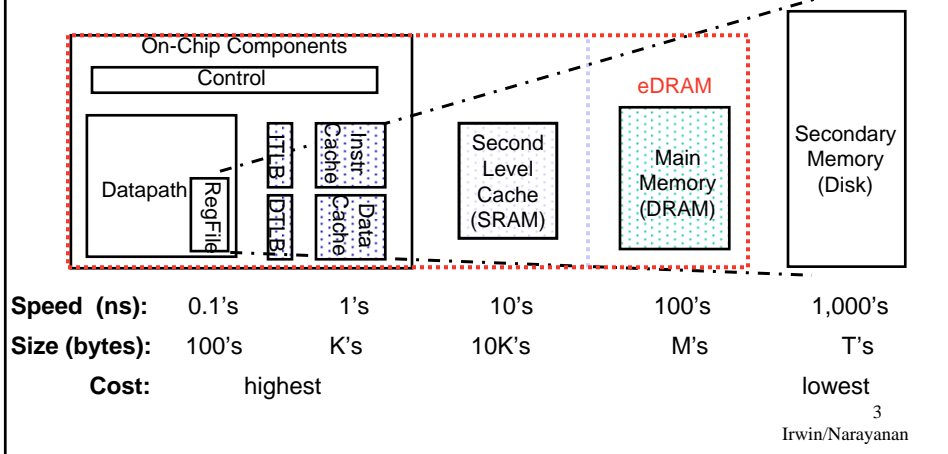
- By taking advantage of the principle of locality:
 - Present the user with as much memory as is available in the cheapest technology
 - Provide access at the speed offered by the fastest technology



Read-write Memory Review

- SRAM
 - Data is stored as long as power is supplied
 - Relatively large cells, 6-transistors, lower density (vs. DRAM)
 - Fast – use closer to computation
 - Compatible with CMOS technology
- DRAM
 - Data must be periodically refreshed
 - Small cells, 1 transistor, VERY dense
 - Slower, use in larger main memories
 - Process not compatible with standard CMOS

1-Transistor DRAM cell review

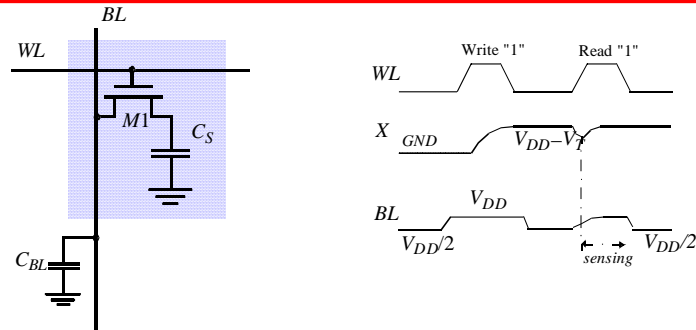


Write: C_S is charged or discharged by asserting WL and BL.
Read: Charge redistribution takes place between bit line and storage capacitance

$$\Delta V = V_{BL} - V_{PRE} = (V_{BIT} - V_{PRE}) \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.

5


CMOS 6T SRAM cell review

 

6

 
Example layout

- Freescale 65nm cell, $0.69\mu\text{m}^2$



7

Stability: Read Upset

 


Read-disturb (read-upset): must carefully limit the allowed voltage rise on I_Q to a value that prevents the read-upset condition from occurring while simultaneously maintaining acceptable circuit speed and area constraints

8


SRAM Sizing

 - High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell



9


Example 65 nm Sizing

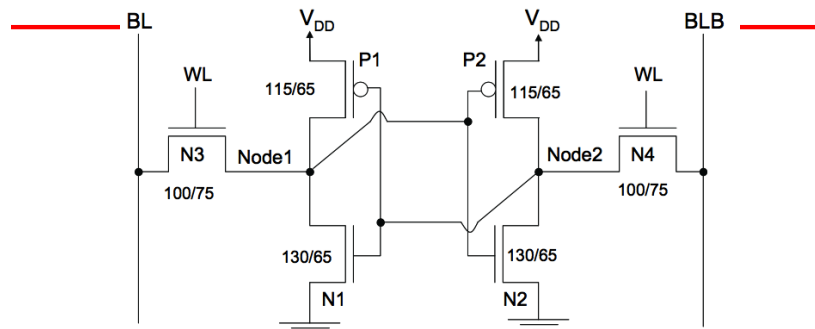

High Read Stability and Low Leakage Cache Memory Cell
Zhiyu Liu; Kursun, V.;
[Circuits and Systems, 2007. ISCAS 2007. IEEE International Symposium on](#)
27-30 May 2007 Page(s):2774 - 2777


10

Stability: Read Upset

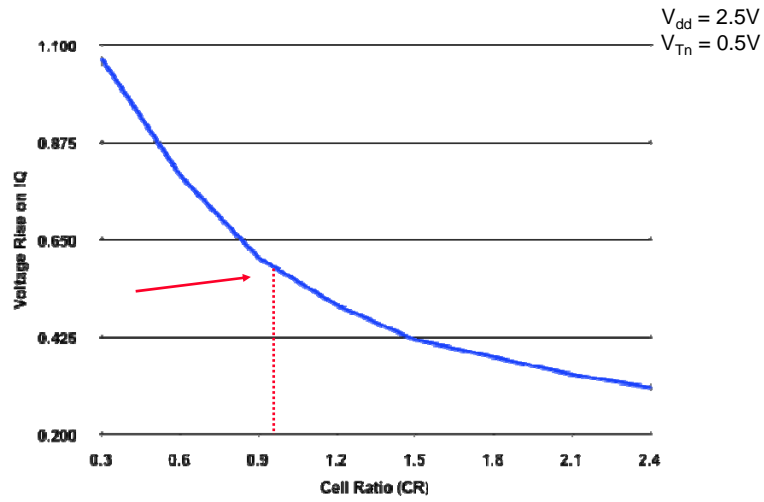


11

Growth in DRAM Chip Capacity

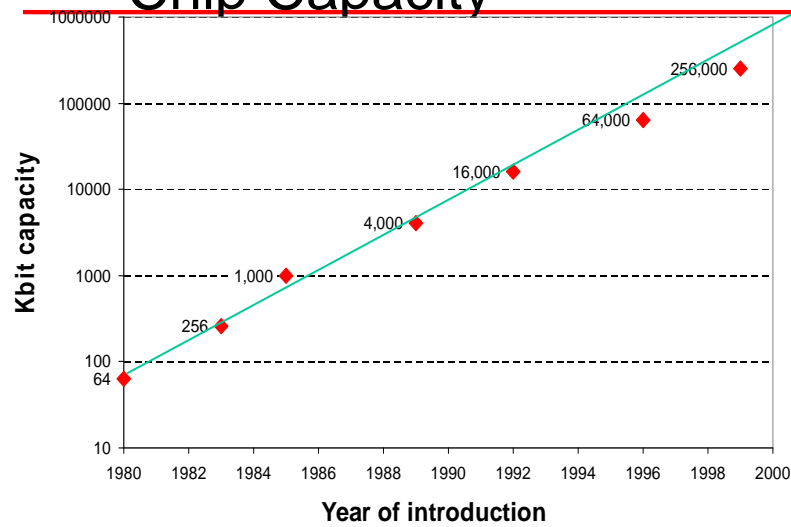


12

1D Memory Architecture

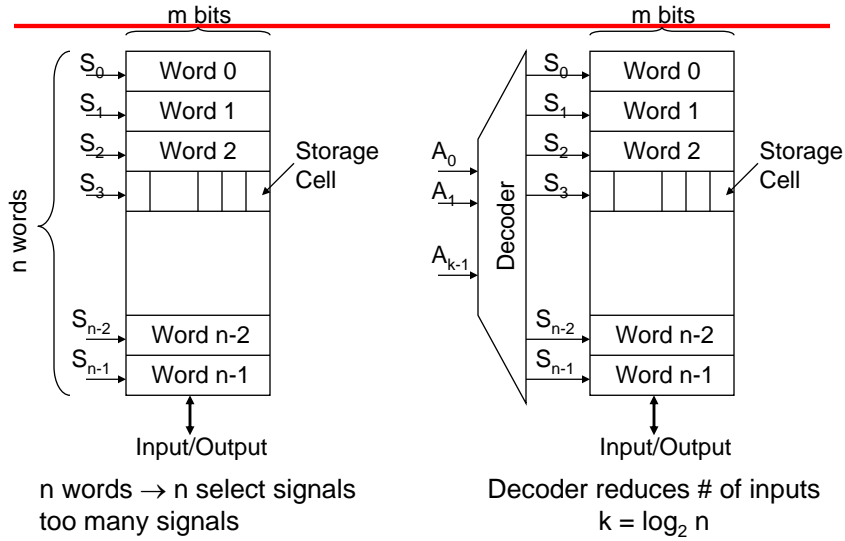

2D (array) Memory Architecture

 Problem: ASPECT RATIO or HEIGHT \gg WIDTH




Can put column decode above/before sense amps instead

Total memory access time consists of many components

- Row decode
- Word line drivers
- Cell driving bit line cap
- Sense amp delay
- Column decode
- Output driving circuitry

(which dominate?)

3D Memory Architecture

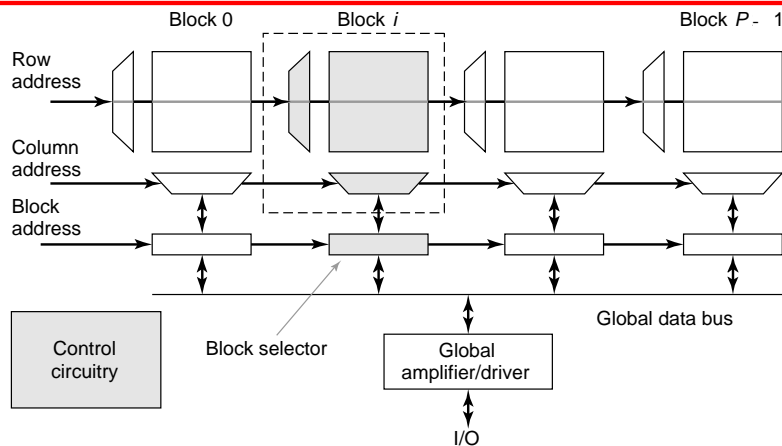

Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings

15

Peripheral Components of Memories

Decoders (both row & column)

Sense Amplifiers

Not discussing:

Input/Output Buffers

Control / Timing Circuitry

16

Row Decoders (M to 2^M)

**Simplest visualization: Collection of 2^M complex logic gates
Organized in regular and dense fashion**

(N)AND Decoder

$$WL_0 = \bar{A}_0 \bar{A}_1 \bar{A}_2 \bar{A}_3 \bar{A}_4 \bar{A}_5 \bar{A}_6 \bar{A}_7 \bar{A}_8 \bar{A}_9$$

$$WL_{511} = \bar{A}_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 A_9$$

NOR Decoder


$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{A_0 + \bar{A}_1 + \bar{A}_2 + \bar{A}_3 + \bar{A}_4 + \bar{A}_5 + \bar{A}_6 + \bar{A}_7 + \bar{A}_8 + \bar{A}_9}$$

17

Hierarchical Decoders

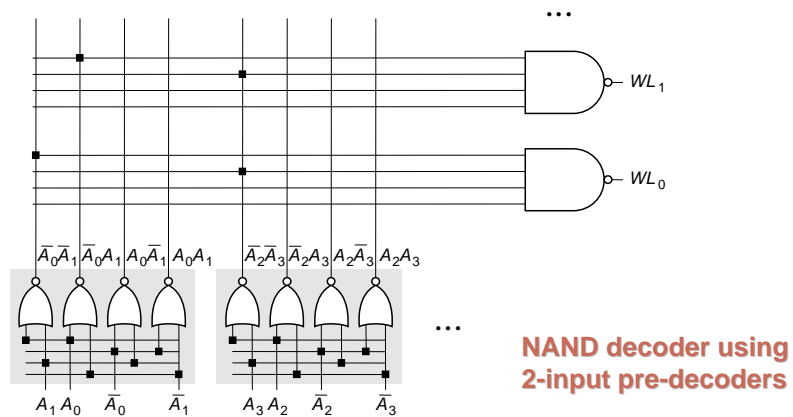Multi-stage implementation improves performance




18

Decoder design goals


- Only 1 critical transition
 - 1 signal must go HIGH, going low again is not as crucial
- Can skew the gate sizing
- Can use dynamic logic with precharge

19

Dynamic Decoders

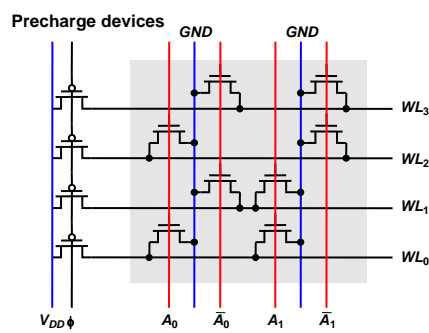

2-input NOR decoder

 


2-input NAND decoder

NOR is faster but consumes more power since all but one word line pulls down each cycle

20

 4-input pass-transistor based **column** decoder




Often use PMOS pass transistors instead since BLs precharge high (speed penalty)

Advantages: speed (Decode portion doesn't add to overall memory access time)
 Only one extra transistor in signal path
Disadvantage: Large transistor count

21

4-to-1 tree based **column** decoder

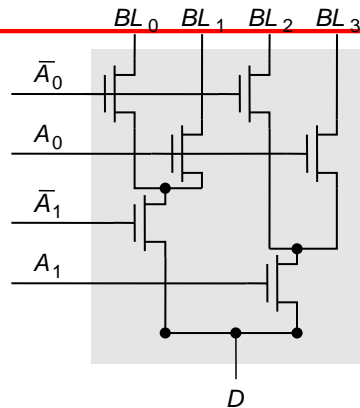

Number of devices drastically reduced
 Delay increases quadratically with # of sections; prohibitive for large decoders
Solutions: buffers
 progressive sizing
 combination of tree and pass transistor approaches


22

Sense Amplifiers

$$t_p = \frac{C \times \Delta V}{I_{av}}$$

(b/c of large arrays) large C → **make ΔV as small as possible**
small I_{av} → **devices must be small for density**


Idea: Use Sense Amplifier

 

23


Differential Pair Amp

 - Differential pair requires no clock
- But always dissipates static power



24

SRAM sense amp design

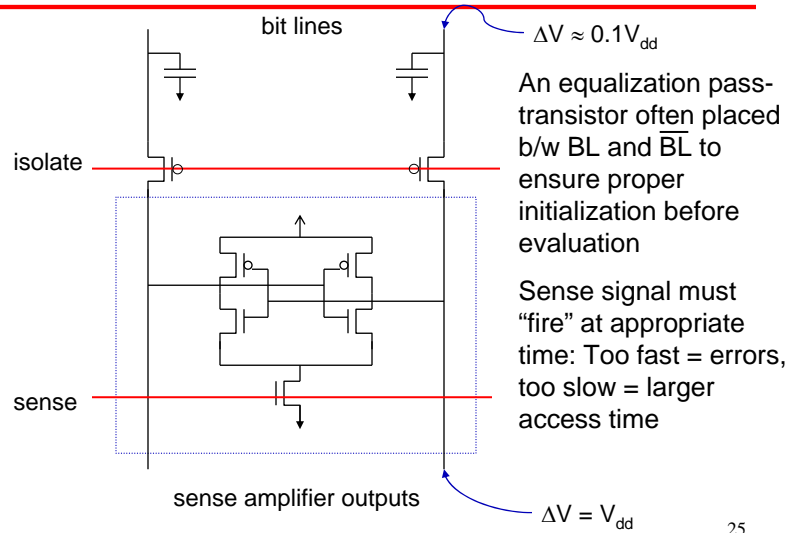

25

Irwin/Narayanan

Summary

- Memory performance is critical to overall system performance
 - Memory hierarchy develops based on speed and size requirements
- On-chip SRAM very common today
 - 6T SRAM cells have become very compact
 - Complete memory architecture involves arrays + row/column decoders, sense amps, output drivers

26