
EECS 427

Lecture 5: Interconnect review

Reading: 4.3.1, 4.3.2, 4.4.1-4.4.3,
9.3.3

Last Time


- Power/energy in CMOS
 - Sources we will focus on are dynamic (caps) and leakage (subthreshold currents)
 - Much more later in the class on low-power design techniques
- Dynamic logic
 - Used sparingly, when speed is critical
 - Increases power, design complexity, poor noise properties compared to CMOS
 - Revisit today

Overview

- Wiring or interconnections and their performance impact
 - Contribute to delay, RC
 - Coupling capacitance between wires
- Design strategies to deal with large RC or C delays
 - Repeaters and cascaded/tapered buffer chains


Monotonicity

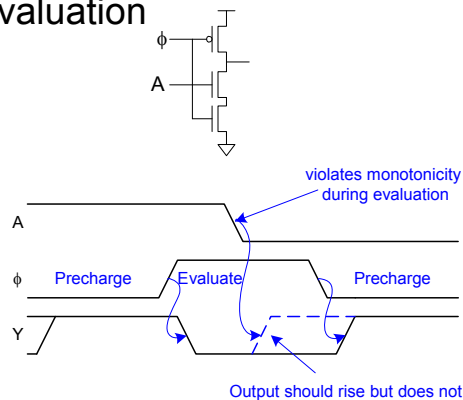- Dynamic gates require *monotonically rising* inputs during evaluation
 - 0 -> 0
 - 0 -> 1
 - 1 -> 1
 - But not 1 -> 0




Monotonicity Woes

 - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!




Monotonicity Woes

 - But dynamic gates produce monotonically falling outputs during evaluation
- Illegal for one dynamic gate to drive another!



Domino Gates

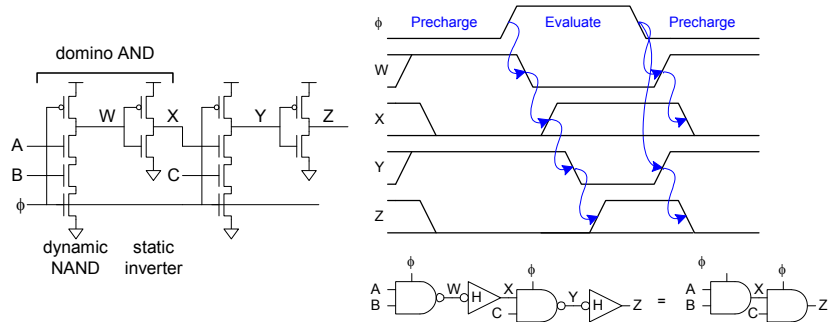- Follow dynamic stage with inverting static gate
 - Dynamic / static pair is called domino gate
 - Produces monotonic outputs




EECS 427 W09

7

Domino Optimizations

 
- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially but precharge in parallel
- Thus evaluation is more critical than precharge
- Skewed static stages can perform added logic



EECS 427 W09

8


Keepers: A must-have

 

- Keeper helps with charge leakage, charge sharing
 - But – fights evaluation initially
- Must be kept very weak; often use $L > L_{min}$ and $W = W_{min}$
- Avoid truly floating nodes!


Transistors vs. Wires

 - Cross section of modern technology is mostly dominated by wires.



Reverse Scaling of Interconnects

 - Gate delays reduce with technology scaling
- Global interconnect delays increase with scaling
 - Interconnects must be included in analysis and optimization



Interconnect Parasitics

- Classes of parasitics
 - Capacitance
 - Resistance
 - Inductance (627 focuses on this)
- Impact of interconnect parasitics
 - Increases propagation delay
 - Energy dissipation and power distribution
 - Reliability and signal integrity

Interconnect Modeling


- Lumped capacitance model is what we use for device/gate analysis
- Lumped RC model
 - For simple one segment RC:
 - 50% Delay = $0.69 \cdot RC$
 - 10-90% Slew = $2.2 \cdot RC$
- Distributed RC line model
 - More accurate for interconnect analysis
 - 50% Delay = $0.38 \cdot RC$
 - 10-90% Slew = $0.9 \cdot RC$

Design Rules of Thumb

- RC delays should be considered when t_{pRC} is a sizable fraction of the unloaded gate delay (t_{pgate}) of the driver
- Ex: in our technology $t_{pgate} \sim 40\text{-}60\text{ps}$ (inverters)
- Resistance of a 500um line at $0.08 \Omega/\text{square}$:
- Cap: roughly $2\text{pF}/\text{cm}$
- Need wires of length $\sim 400\text{um}$ to have appreciable RC
- Also compare R_{wire} to R_{eq} of driver

How to reduce RC delay

 
- Since RC delay is quadratic with length, reducing length is key
- Note: $2^2 = 4$ and $1+1 = 2$ but $1^2 + 1^2 = 2$



EECS 427 W09

15

Repeaters

 


Repeater

Repeater = strong driver (usually an inverter or pair of inverters for non-inverting polarity) placed along a long RC line to “break up” the line and reduce delay

We need to determine optimal # of repeaters and their size based on wire and device delay properties


Repeaters Impact

 


17

Coupling Capacitance

 - To reduce interconnect resistance, thickness is not scaled as aggressively as the width of the interconnect




- Tall wires (high aspect ratios)

 

EECS 427 W09



18

Capacitive Cross Talk

 


$$\Delta V_Y = \frac{C_{XY}}{C_Y + C_{XY}} \Delta V_X$$

Capacitive Cross Talk

 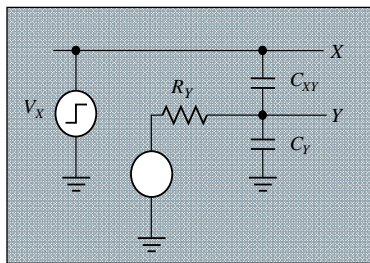

Keep time-constant small (size up driver of node Y)

Impact of Crosstalk on Delay

 

DELAY DEPENDENT UPON
ACTIVITY IN NEIGHBORING
WIRES! (very important today)


Miller Effect

- Both terminals of capacitor are switched in opposite directions ($0 \rightarrow V_{dd}, V_{dd} \rightarrow 0$)
- Effective voltage is doubled and additional charge is needed (from $Q=CV$)

EECS 427 W09

23

Structured Predictable Interconnect

 

Example: Dense Wire Fabric ([Khatri])


Trade-off:

- Cross-coupling capacitance 40x lower, 2% delay variation
- Large increase in area and overall capacitance

EECS 427 W09

24


How to Design Large Transistors

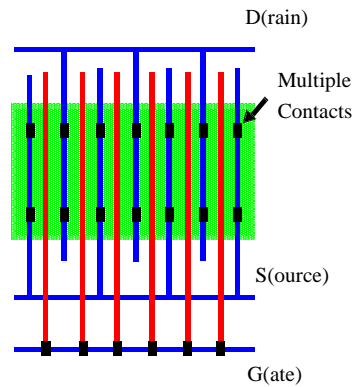

Reduces diffusion capacitance
Reduces gate resistance

Many small transistors in parallel


Driving Large Capacitances

 

$$t_p = \frac{C_L V_{swing}}{I_{av}}$$

- Transistor Sizing
- Cascaded Buffers

Using Cascaded Buffers

 


0.25 μm process
 $C_{in} = 2.5 \text{ fF}$
 $t_{p0} = 30 \text{ ps}$

$F = C_L/C_{in} = 8000$
 $f_{opt} = 3.6 \text{ N} = 7$
 $t_p = 0.76 \text{ ns}$

(See Section 5.4)

Delay as a Function of F and N

 

Output Driver Design

0.25 μm process, $C_L = 20 \text{ pF}$

Transistor Sizes for optimally-sized cascaded buffer $t_p = 0.76 \text{ ns}$

Stage	1	2	3	4	5	6	7
W_n (μm)	0.375	1.35	4.86	17.5	63	226.8	816.5
W_p (μm)	0.71	2.56	9.2	33.1	119.2	429.3	1545.5

Transistor Sizes of redesigned cascaded buffer $t_p = 1.8 \text{ ns}$

Stage	1	2	3
W_n (μm)	0.375	7.5	150
W_p (μm)	0.71	14.4	284

Repeaters vs. Cascaded Buffer Chains

- Repeaters are used to drive long RC lines
 - Breaking up quadratic dependence of delay on line length is the goal
 - Typically sized identically
- Cascaded buffers are used to drive large capacitive loads, where there is no parasitic resistance
 - We put all buffers at the beginning of the load
 - This would be pointless for a long RC wire since the wire RC delay would be unaffected and dominate the total delay

Summary

- Wires provide connectivity but also pose delay, noise, power problems
- Long wires can be partitioned using repeaters
- Coupling capacitance impacts both delay and noise; delay more critical
- Can cascade inverters to drive a large capacitive load like an I/O pad
 - Size each gate 3 or 4 times bigger than the last
- Next time: project discussion + getting started on logical effort