

---

EECS 427  
Lecture 9: Adders  
Reading: 11.3.2 – 11.3.3 (limited  
carry lookahead coverage)

1

---

## Last Time

- Finished logical effort
- Adder intro
  - Ripple carry adder is simplest design but slow (delay grows linearly with # of bits)
  - Standard CMOS implementation is ugly
  - Key point: Inputs (A and B) are available at time zero, carry in is not

2

# Lecture Overview


---

- Better full adder design
- Better adder architectures vs. ripple carry adder (RCA)
- HW3 due Tuesday by beginning of class
  - Initial project proposal, only a brief description required
  - Can email it to me, or turn in hard copy in lecture
- Tuesday lecture on multipliers to be covered by Jerry Kao
  - ISSCC

3

## Complementary Static CMOS Full Adder Revisited


---

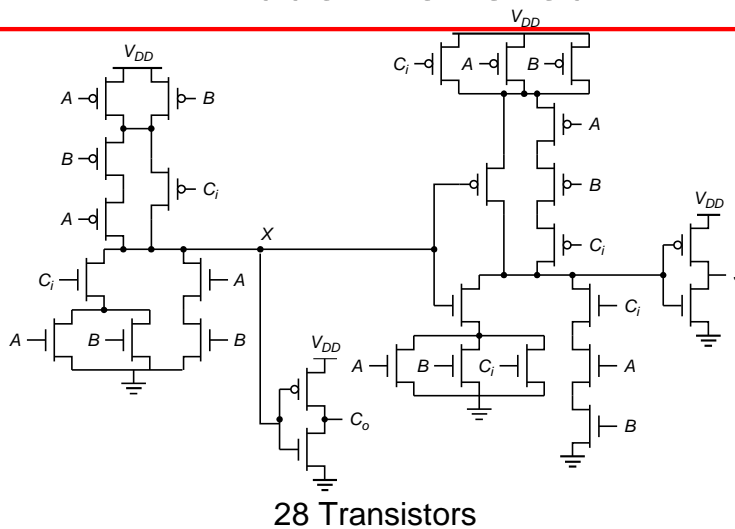

4

# Inversion Property

---

 


$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

5

# Minimize Critical Path by Reducing Inverting Stages Along Carry Path

---

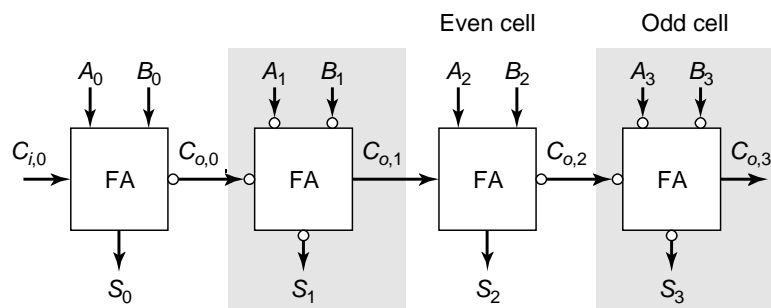


## Exploit Inversion Property

Allows us to remove inverter in carry chain → at what cost?

6

## A Better Structure: Mirror Adder

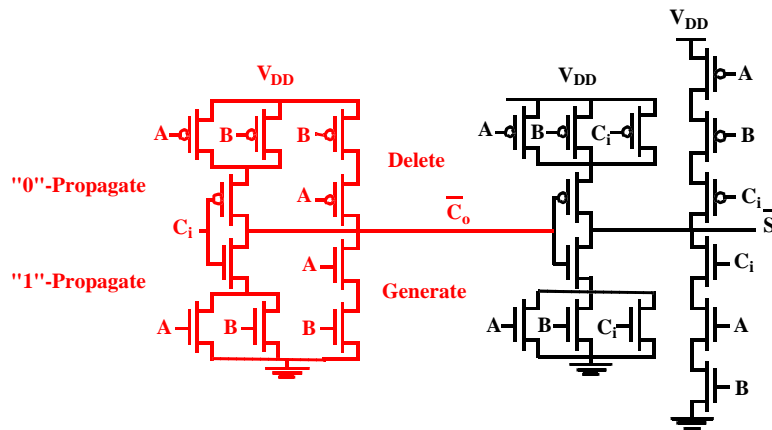

24 transistors

7


## Mirror Adder Details

- NMOS and PMOS chains are **completely symmetric**.  
Maximum of 2 series transistors in carry generation
- In layout → critical to minimize capacitance at node  $C_0$ .  
Reduction of junction capacitances is particularly important
- Capacitance at node  $C_0$  is composed of 4 junction capacitances, 2 internal gate capacitances, and 6 gate capacitances in connecting adder cell
- Transistors connected to  $C_i$  are closest to output
- Only optimize transistors in carry stage for speed  
Transistors in sum stage can be small


8

# Mirror Adder

Stick diagram of layout

 


9

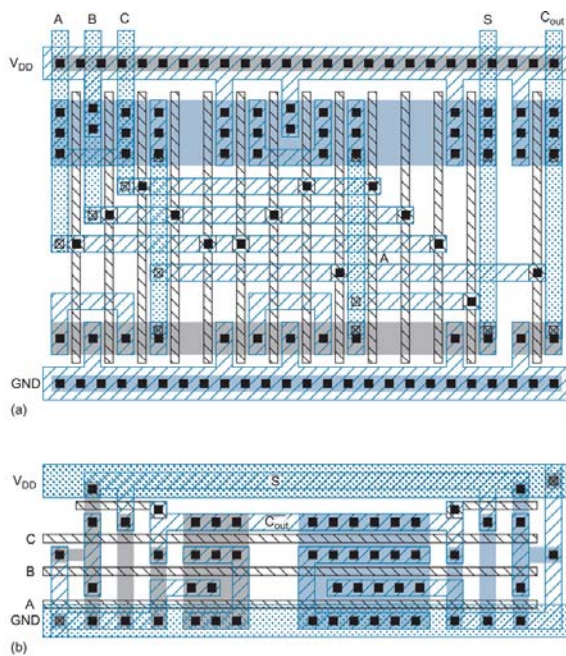

- 2 possible layouts of mirror adder
- (a) corresponds roughly to last slide's stick diagram
- Layout (b) is datapath-oriented (ex. M2 can easily run horizontally across cell)


10

## Sizing Mirror Adder

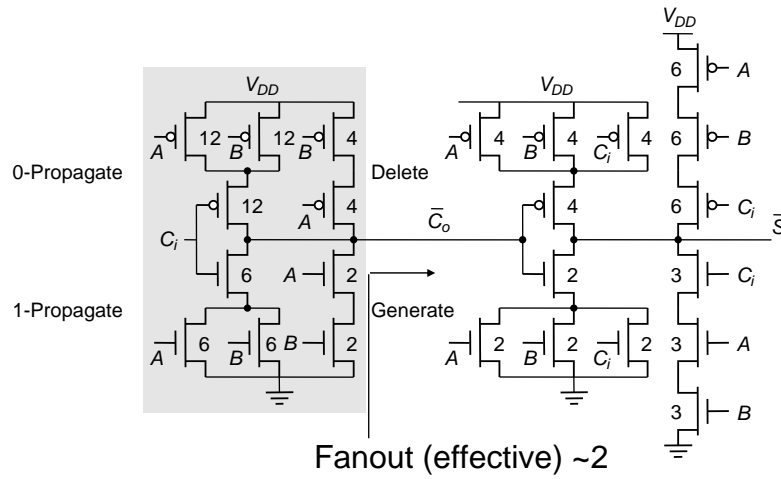


11

## Transmission Gate Full Adder

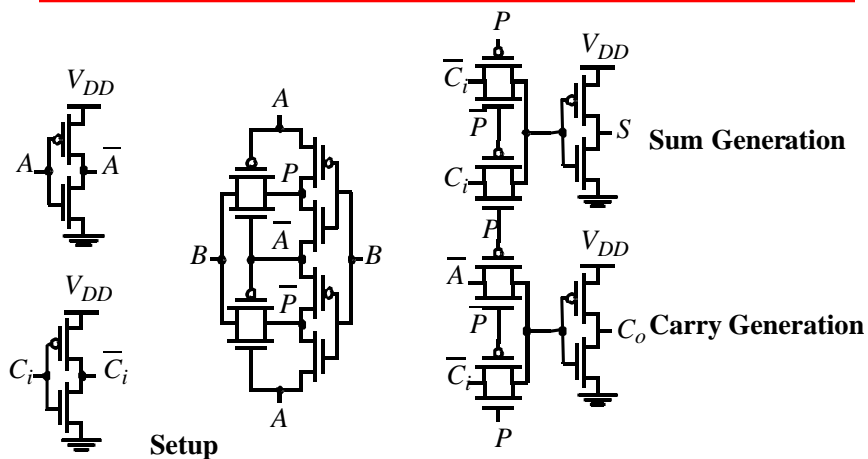

12


# Manchester Carry Chain

 

13

 
# Manchester Carry Chain

- Implement P with pass-transistors
- Implement G with pull-up OR delete with pull-down (note inversion)
- Use dynamic logic to reduce complexity and speed up



14


# Carry-Bypass Adder

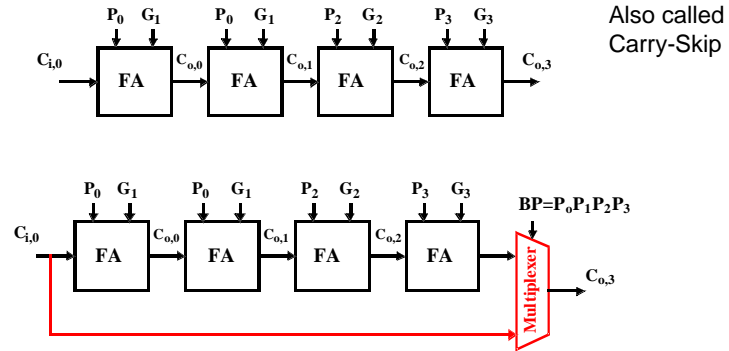

Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ )  
then  $C_{03} = C_0$ , else “delete” or “generate”

15

# Carry-Bypass Adder (cont.)

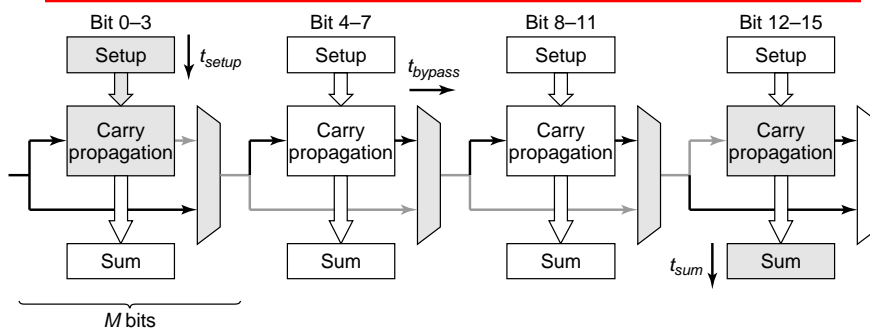


$$t_{adder} = t_{setup} + Mt_{carry} + (N/M-1)t_{bypass} + (M-1)t_{carry} + t_{sum}$$

Inner blocks do not contribute to worst-case delay since they have time to compute while bits 0-3 are propagating (assuming they have a generate or delete)

Block sizes can be made non-uniform (HOW?)

# Carry Ripple versus Carry Bypass


---

 

17


# Carry-Select Adder

---

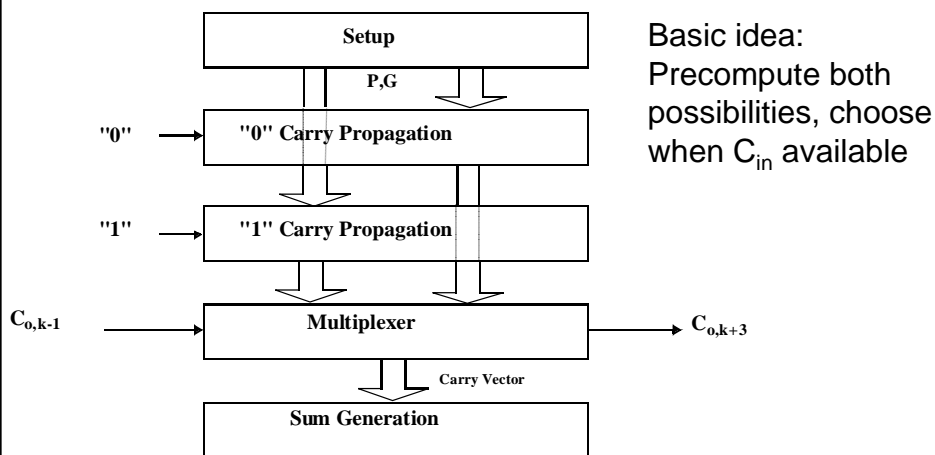


18

# Carry Select Adder: Critical Path

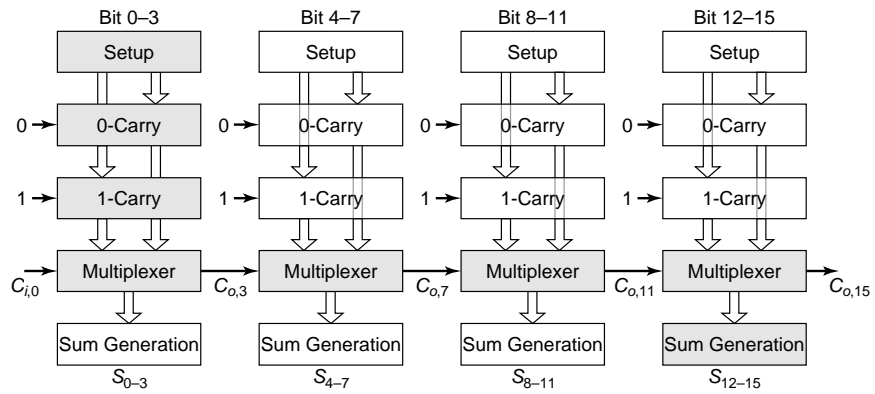

19


# Linear Carry Select

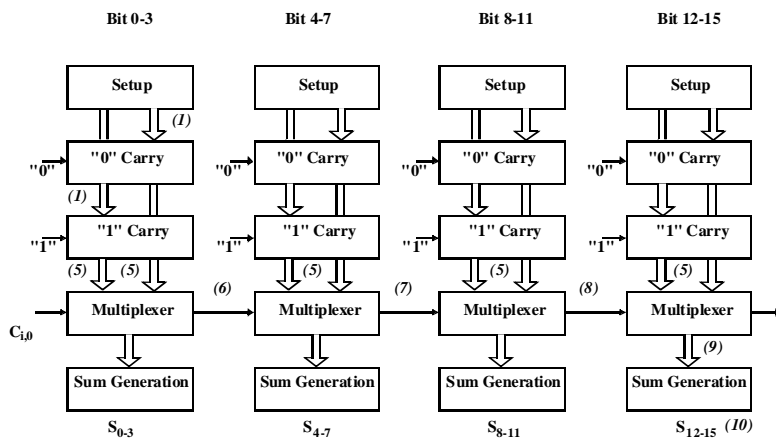


$$t_{\text{add}} = t_{\text{setup}} + M \cdot t_{\text{carry}} + (N/M) t_{\text{mux}} + t_{\text{sum}}$$

20

# Square Root Carry Select

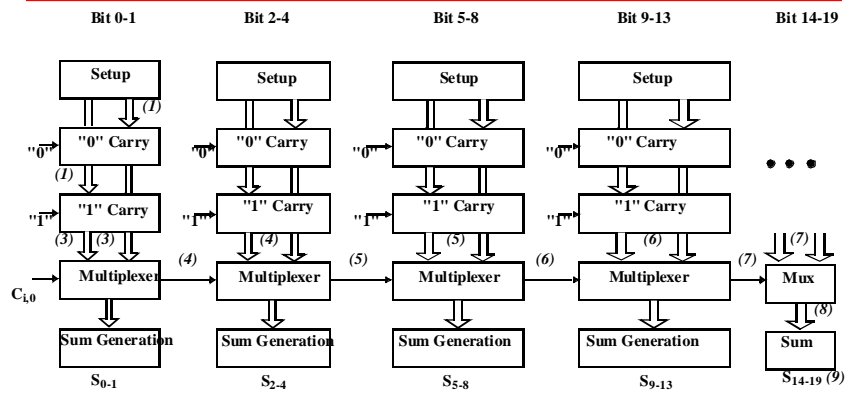


# Adder Delays - Comparison

 

# Carry Lookahead Adder

---

 

Weinberger, Smith, 1958.

23

# Lookahead Adder

---

Lookahead Equations

Position  $i$ :  $c_i = g_i + p_i c_{i-1}$

Position  $i + 1$ :  $c_{i+1} = g_{i+1} + p_{i+1} c_i$   
 $= g_{i+1} + p_{i+1} (g_i + p_i c_{i-1})$   
 $= g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_{i-1}$

Carry exists if:

- generated in stage  $i + 1$
- generated in stage  $i$  and propagated through  $i + 1$
- propagated through both  $i$  and  $i + 1$

24

# Lookahead Adder

---


- Unrolling of carry recurrence can be continued
- If unrolled to level  $k$ , resulting in two-level AND-OR structure
  - AND Fan-In =  $k + 1$ , OR Fan-In =  $k + 1$
  - $k + 1$  transistors in the MOS stack
  - Limits  $k$  to 3 -4

25

# Lookahead Adder

---

Mirror Implementation

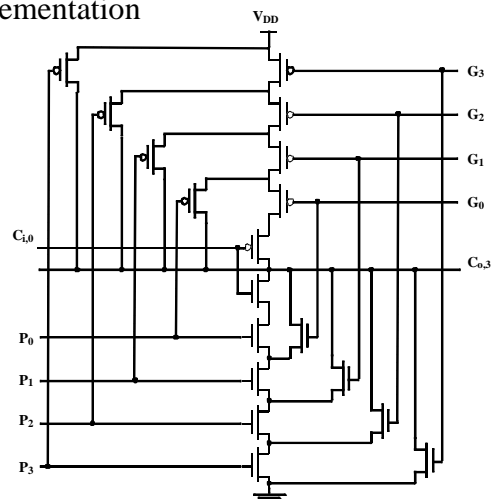

26

## Block Lookahead

---

4<sup>th</sup> bit carry:

$$c_{i+3} = g_{i+3} + p_{i+3}g_{i+2} + p_{i+3}p_{i+2}g_{i+1} \\ + p_{i+3}p_{i+2}p_{i+1}g_i + p_{i+3}p_{i+2}p_{i+1}p_i c_{i-1}$$

Block generate and block propagate:

$$G_{i,i+3} = g_{i+3} + p_{i+3}g_{i+2} + p_{i+3}p_{i+2}g_{i+1} + p_{i+3}p_{i+2}p_{i+1}g_i$$

$$P_{i,i+3} = p_{i+3}p_{i+2}p_{i+1}p_i$$

$$c_{i+3} = G_{i,i+3} + P_{i,i+3}c_{i-1}$$

## Block Lookahead

---

Can create groups of groups, or 'super-groups':

$$G_{j+3:j}^* = G_{j+3} + P_{j+3}G_{j+2} + P_{j+3}P_{j+2}G_{j+1} + P_{j+3}P_{j+2}P_{j+1}G_j$$

$$P_{j+3:j}^* = P_{j+3}P_{j+2}P_{j+1}P_j$$

$$t_d \propto \log N$$

An overview of hierarchical tree-style carry lookahead structures:

[http://fourier.eng.hmc.edu/e85/lectures/arithmetic\\_html/node7.html](http://fourier.eng.hmc.edu/e85/lectures/arithmetic_html/node7.html)

# Summary

---

- Many topologies for adders
  - Extensions of carry lookahead are dominant today
- For 16-bit addition, complex techniques such as carry lookahead do not offer much benefit
  - Carry select and carry bypass yield good performance in this case
  - Can string together 4-bit lookahead structures in a ripple fashion to achieve decent performance
- Adder cells may use mirror structure or transmission gates